

**GOVERNMENT OF TAMILNADU
DIRECTORATE OF TECHNICAL EDUCATION
CHENNAI – 600 025
STATE PROJECT COORDINATION UNIT**

Diploma in Electrical and Electronics Engineering

**Course Code: 1030
M – Scheme**

**e-TEXTBOOK
on
ELECTRICAL CIRCUIT THEORY
for
III Semester DEEE**

Convener for EEE Discipline:

Er.R. Anbukarasi ME.,
Principal,
Tamilnadu Polytechnic College,
Madurai, 625011.

Team Members for ELECTRICAL CIRCUIT THEORY

THIRU M.RAVI, M.E., M.I.S.T.E
LECTURER/ELECTRICAL
GOVERNMENT POLYTECHNIC COLLEGE, SRIRENGAM

THIRU DINAKARAN, M.E.,
LECTURER /EEE
CENTRAL POLYTECHNIC COLLEGE, CHENNAI

THIRU G.RAJAGOPAL, M.E.,
LECTURER/ELECTRICAL
P.A.C. RAMASAMY RAJA POLYTECHNIC COLLEGE, RAJAPALAYAM

Validated by:

Dr. R. RAJAN PRAKASH
ASSISTANT PROFESSOR/EEE
THIAGARAJAR COLLEGE OF ENGINEERING, MADURAI.

DIPLOMA IN ELECTRICAL AND ELECTRONICS ENGINEERING

M - SCHEME

Course Name: Diploma in Electrical and Electronics Engineering

Subject Code: 33031

Semester: III

Subject Title: ELECTRICAL CIRCUIT THEORY

Rationale:

1. Electric circuit analysis is the process of determining the voltages across a component in the circuit and the currents passing through it. There are different methods to determine the voltage and current.
2. This course covers, introduction to network elements and methods for finding voltage and current across desired network Component for DC, single phase AC and 3 phase ac sources.
3. It aims at making the student conversant with different techniques of solving the problems in the field of Electric circuits and analysis.

Objectives:

The objective is to enable students to:

1. Understand the concept of electrostatics and capacitance effect and analyze different Circuit Elements, Energy Sources and analysis of Network by Kirchhoff's Laws.
2. Apply the concept of Node and Mesh methods for circuit analysis; apply superposition theorem, Thevenin's Theorem , Norton's Theorem, Maximum Power Transfer theorem and Star-delta conversion for simplification and analyzing dc circuits.
3. Analyze single phase circuits using Resistor, Inductor & Capacitor elements.
4. Understand and analyze series and parallel resonant behavior of a circuit.
5. Analyse balanced three phase ac circuit and three phase power measurement.

DETAILED SYLLABUS

33031 - ELECTRICAL CIRCUIT THEORY (M - SCHEME)

Unit -I (a) ELECTROSTATICS (b) D C CIRCUITS

Page No: 5 - 51

(a) ELECTROSTATICS

Electric Flux-Electric Flux Density-electric Field Intensity-electric potential-Coulomb's laws of electrostaticsconcept of capacitance - Relationship between Voltage, Charge and capacitance – energy stored in a capacitor – capacitors in series and in parallel –Problems in above topics.

(b) D C CIRCUITS

Basic concepts of current, emf, potential difference, resistivity, temperature coefficient of resistance – Ohm's Law –application of Ohm's law – work, power energy – relationship between electrical, mechanical and thermal units – resistance – series circuits – parallel and Series parallel circuits – Kirchhoff's laws –Problems in the above topics.

Unit-II CIRCUIT THEOREMS

Page No: 52 - 126

Mesh equations – Nodal equations – star/delta transformations –Superposition theorem – Thevenin's theorem – Norton's theorem – Maximum power transfer theorem. (Problems in DC circuits only)

Unit-III SINGLE PHASE CIRCUITS

Page No: 127 - 193

'j' notations – rectangular and polar coordinates – Sinusoidal voltage and current – instantaneous, peak, average and effective values – form factor and peak factor(derivation for sine wave) – pure resistive, inductive and capacitive circuits – RL, RC, RLC series circuits –impedance –phase angle – phasor diagram – power and power factor – power triangle – apparent power, active and reactive power – parallel circuits (two branches only) - Conductance, susceptance and admittance –problems on all above topics.

Unit-IV RESONANT CIRCUITS

Page No: 194 - 219

Series resonance – parallel resonance (R,L &C; RL&C only) – quality factor – dynamic resistance – comparison of series and parallel resonance –Problems in the above topics - Applications of resonant circuits.

Unit-V THREE PHASE CIRCUITS

Page No: 220 - 263

Three phase systems-phase sequence –necessity of three phase system–concept of balanced and unbalanced load - balanced star &delta connected loads – relation between line and phase voltages and currents –phasor diagram –three phase power and power factor measurement by single wattmeter and two wattmeter methods –Problems in all above topics.

TEXT BOOK:

| Sl.No | Name of the Book | Author | Publisher |
|-------|-------------------------|--|--------------------------------|
| 1. | Electric Circuit Theory | Dr. M. Arumugam Dr. N. Premakumaran | Khanna Publishers New Delhi |

REFERENCE BOOKS:

| Sl.No | Name of the Book | Author | Publisher |
|-------|---|--------------------------------------|--|
| 1. | Circuits and Networks Analysis and Synthesis | A.SudhakarShyammohan S.Pali | Tata McGraw Hill Education Private Ltd., |
| 2. | Electric Circuits | Mohamood Nahvi Joseph A Edminster | Tata McGraw Hill Education Private Ltd., |

UNIT 1 – (A) ELECTROSTATICS (B) D.C CIRCUITS

Syllabus:

(a) ELECTROSTATICS

Electric Flux - Electric Flux Density - Electric Field Intensity - Electric potential - Coulomb's laws of electrostatics - Concept of capacitance - Relationship between Voltage, Charge and capacitance – Energy stored in a capacitor – Capacitors in series and in parallel – Problems in above topics.

(b) D.C CIRCUITS

Basic concepts of current, emf, potential difference, resistivity, temperature coefficient of resistance – Ohm's Law – application of Ohm's law – work, power energy – relationship between electrical, mechanical and thermal units – resistance – series circuits – parallel and Series parallel circuits – Kirchhoff's laws –Problems in the above topics.

1.0 Electrostatics:

Electrostatics is the study of charges at rest. Electric charges are fundamental in nature. There are two types of charges and can be produced by friction. When a glass rod is rubbed with a silk cloth, some electrons from glass rod are migrated into the silk cloth. This makes the glass rod positively charged due to loss of electrons in it and the silk cloth negatively charged due to excess of electrons in it. Similarly, when the plastic rod is rubbed with fur, electrons migrate from the fur into the plastic rod making the rod negative and the fur positive. Also there is a force of attraction between the glass rod and silk cloth. There is a force of repulsion between similarly charged bodies and a force of attraction between oppositely charged bodies.

1.1 Electrostatic force:

The forces between particles that are caused by their electric charges. It exists between moving charges as well as stationary ones. This force may be illustrated with lines as shown in Figure 1.1.

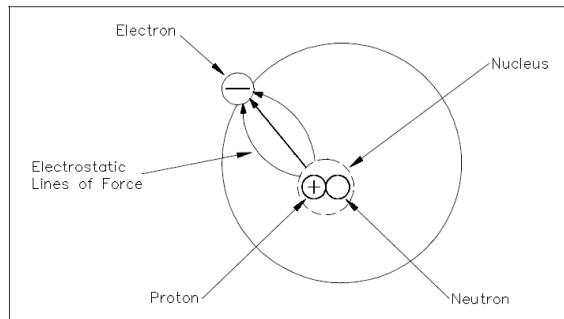



Figure 1.1 Electrostatic Force

1.2 Electric field:

An electric field is defined as the space in which an electric charge experiences a force. The electric field is represented by electric flux lines.

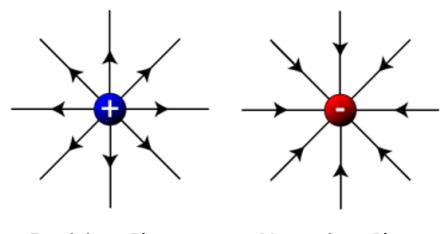1.2.1 Electric Field Line:

It is defined as the direction of electric field. It leaves the positive charged conductor and enters a negatively charged conductor. The field configuration for isolated charges is shown in figure 1.2.



Positive Charge Negative Charge
Figure 1.2 Electric Field Line

1.2.2 Properties of Electric field lines:

1. A line starts from a positive charge and ends on a negative charge.
2. The lines enter or leave a charged body at a right angle to the surface.
3. The lines go from more positive body towards the more negative body
4. The lines do not intersect.

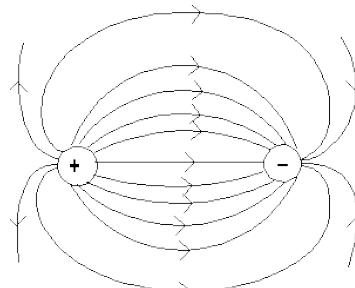


Figure 1.3 Electric field around two unlike charges

1.3 Electric Flux:

The total number of electric field lines is called electric flux. The unit of electric flux is the coulomb. The symbol for electric flux is ψ (psi)

One 'line' of flux is assumed to radiate from the surface of a positive charge of one coulomb and terminate at the surface of a negative charge of one coulomb. Hence the electric flux has the same numerical value as the charge that produces it. Therefore, the coulomb is used as the unit of electric flux.

1.4 Electric flux density:

The electric flux density is defined as the amount of flux per square metre of the electric field. This area (A) is measured at right angles to the lines of force. Electric flux density is denoted by D .

$$\text{Electric Flux Density: } D = \frac{\psi}{A} \text{ coulomb/metre}^2$$

1.5 Electric field intensity:

Electric field intensity at any point in an electric field is the force on unit positive charge placed at that point. It is expressed in Newton per coulomb (N/C). Electric flux intensity is denoted by E.

$$\text{Electric Field Intensity: } E = \frac{F}{Q} ; \text{Newton/coulomb}$$

1.6 Electric Potential:

The potential at any point in an electric field is the amount of work done in bringing a charge of 1 coulomb of positive charge to that point against the electric field.

1.7 Permittivity of Free Space (ϵ_0):

When an electric field exists in a vacuum then the ratio of the electric flux density to the electric field strength is a constant, known as the permittivity of free space.

$$\begin{aligned}\epsilon_0 &= 8.854 \times 10^{-12} \text{ farad/metre} \\ \frac{D}{E} &= \epsilon_0 \epsilon_r \\ \text{where, } \epsilon_r &= \text{relative permittivity of the insulating material}\end{aligned}$$

1.7.1 Absolute permittivity: (ϵ)

For a given system the ratio of the electric flux density to the electric field strength is a constant, known as the absolute permittivity of the dielectric being used.

$$\begin{aligned}\epsilon &= \frac{D}{E} ; \text{ farad/metre} \\ \epsilon &= \epsilon_0 \epsilon_r ; \text{ farad/metre}\end{aligned}$$

1.7.2 Relative permittivity: (ϵ_r)

The capacitance of two plates will be increased if, instead of a vacuum between the plates, some other dielectric is used. Thus relative permittivity is defined as the ratio of the capacitance with that dielectric to the capacitance with a vacuum dielectric.

$$\begin{aligned}\epsilon_r &= \frac{C_2}{C_1} \\ \text{where, } C_1 &= \text{Capacitance with a vacuum dielectric} \\ C_2 &= \text{Capacitance with other dielectric}\end{aligned}$$

1.8 Capacitor:

A capacitor is a passive electrical component that stores electrical charge in an electric field. The effect of a capacitor is known as capacitance.



Fixed capacitor



Variable capacitor

Figure 1.4 Symbol of Capacitor

1.8.1 Basic Construction:

A capacitor is an electrical device that stores electrical charge and is constructed of two parallel plates separated by an insulating material called the dielectric. Connecting leads are attached to the parallel plates as shown in figure 1.5.

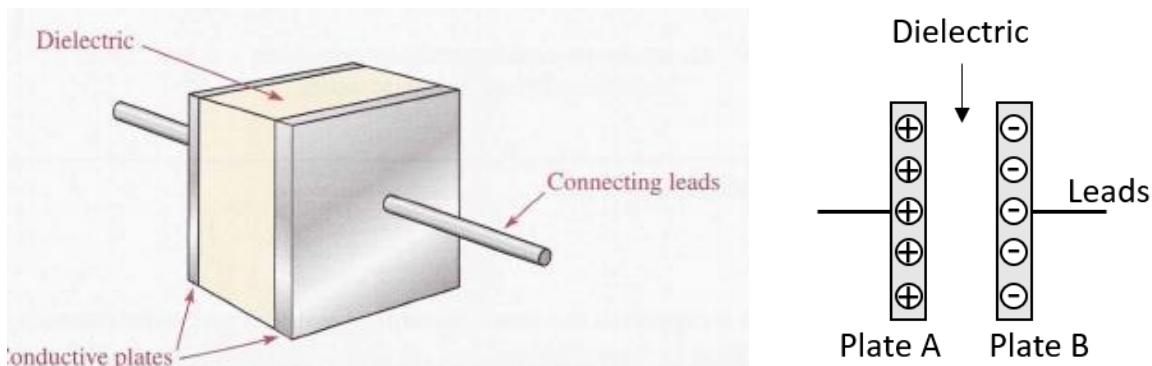


Figure 154 : Construction of Capacitor

1.8.2 Working of Capacitor:

In the natural state, both plates of a capacitor have an equal number of free electrons. When the capacitor is connected to a voltage source, electrons are removed from plate A, and an equal number are deposited on plate B. As plate A loses electrons and plate B gains electrons, plate A becomes positive with respect to plate B. During this charging process, electrons flow only through the connecting leads. No electrons flow through the dielectric of the capacitor because it is an insulator. The movement of electrons ceases when the voltage across the capacitor equals the source voltage. A charged capacitor can act as a temporary battery.


1.9 Coulomb's law of electrostatics:

First Law:

Like charges of electricity repel each other and unlike charges attract each other.

Second law:

The force (F) exists between two point-source charges (Q_1 and Q_2) is directly proportional to the product of the two charges and is inversely proportional to the square of the distance (d) between the charges.
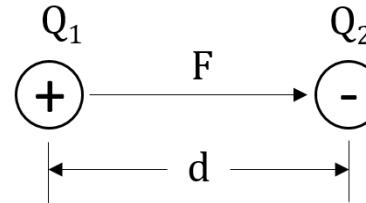
$$F \propto \frac{Q_1 Q_2}{d^2}$$
$$F = k \cdot \frac{Q_1 Q_2}{d^2}$$
$$\text{Constant, } k = \frac{1}{4\pi\epsilon_0\epsilon_r}$$


Where, F = Force between the charges (N)

Q_1 and Q_2 = Magnitude of two charges in coulomb

F = Force between the charges (N)

d = distance between the charges (m)

ϵ_0 = Permittivity of the free space

In S.I.: $\epsilon_0 = 8.854 \times 10^{-12}$ farad/metre

ϵ_r = relative permittivity of the medium

ϵ_r = 1 for vacuum or air

$$\text{Therefore, Force: } F = \frac{Q_1 Q_2}{4\pi\epsilon_0\epsilon_r d^2}$$
$$F = \frac{Q_1 Q_2}{4\pi \times 8.854 \times 10^{-12} \times \epsilon_r d^2}$$
$$F = \frac{9 \times 10^9 \times Q_1 Q_2}{\epsilon_r d^2} ; \text{ for a medium}$$
$$F = \frac{9 \times 10^9 \times Q_1 Q_2}{d^2} ; \text{ for air}$$

1.10 Capacitance:

The amount of charge that a capacitor can store per unit of voltage across its plates is its capacitance. It is represented by C . The capacitance is a measure of a capacitor's ability to store charge. Farad is the unit of capacitance.

One farad is the amount of capacitance when one coulomb of charge is stored with one volt across the plates.

1.11 Relationship between the voltage, capacitance and charge:

$$\text{Capacitance: } C = \frac{Q}{V} ; \text{ farad}$$

$$\text{Charge: } Q = C \cdot V ; \text{ Coulomb}$$

$$\text{Voltage: } V = \frac{Q}{C} ; \text{ Volts}$$

1.12 Capacitors connected in series:

Consider three capacitors, C_1 , C_2 and C_3 , are connected in series to a d.c supply of 'V' volts.


Let,

C = Equivalent capacitance of series combination

V_1 = p.d. across capacitor C_1

V_2 = p.d. across capacitor C_2

V_3 = p.d. across capacitor C_3

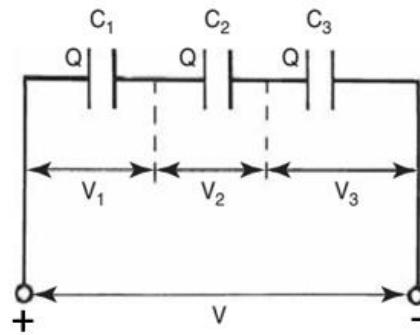

Since the charging current at every point of the circuit is same and the charge stored on each capacitor is 'Q' coulombs.

$$V_1 = \frac{Q}{C_1}; \quad V_2 = \frac{Q}{C_2}; \quad V_3 = \frac{Q}{C_3} \quad \dots \quad (1)$$

$$\text{In series circuit, } V = V_1 + V_2 + V_3 \quad \dots \quad (2)$$

Substitute the value of equation (1) in equation (2)

$$\frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} \quad \dots \quad (3)$$

Where C is the total equivalent circuit capacitance, then it stores the same charge (Q) when connected to the same voltage (V).

Divide equation (3) by Q :

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

If 'n' series-connected capacitors:

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

In case of two capacitors in series :

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C = \frac{C_1 \cdot C_2}{C_1 + C_2} \quad \text{i.e. } \frac{\text{Product}}{\text{Sum}}$$

1.13 Capacitors connected in parallel:

Consider three capacitors, C_1 , C_2 and C_3 , are connected in parallel to a d.c supply of 'V' volts.

Let,


C = Equivalent capacitance of series combination

V = Voltage across each capacitor

Q_1 = Charge stored by C_1

Q_2 = Charge stored by C_2

Q_3 = Charge stored by C_3

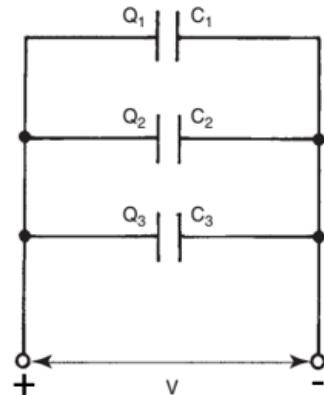

$$\text{In series circuit, } Q_T = Q_1 + Q_2 + Q_3 \quad \dots \quad (1)$$

$$\text{Where, } Q_1 = C_1 V$$

$$Q_2 = C_2 V \quad \dots \quad (2)$$

$$Q_3 = C_3 V$$

Where C is the total equivalent circuit capacitance, then it stores the same charge (Q) when connected to the same voltage (V).

$$\text{Then, } Q_T = C V \quad \dots \quad (3)$$

Substitute the value of equation (2) & (3) in equation (1)

$$C V = C_1 V + C_2 V + C_3 V \quad \dots \quad (4)$$

Divide equation (4) by V :

$$C = C_1 + C_2 + C_3$$


If 'n' number of capacitor in parallel:

$$C = C_1 + C_2 + \dots + C_n$$

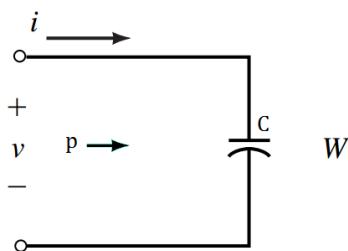1.14 Energy stored in a capacitor:

When a capacitor is charged, Energy is stored in it. In the charging process, the potential difference across the plates is proportional to the charge stored.

During this process, the capacitor draws some current from the source called charging current and energy is stored in it. When the capacitor is fully charged, no more current is drawn from the source.



Where,
 v – voltage applied to capacitor in volts
 I – Current flow in amps
 C – Capacitance of capacitor in farad
 P – power consumed by the capacitor

$$\text{Power to the capacitor, } p = vi$$

$$\text{Current: } i = \frac{CdV}{dt}$$

$$p = \frac{C \cdot v \cdot dv}{dt}$$

$$p = \frac{dW}{dt}$$

Integrating both sides,

$$\text{Energy stored in Capacitor, } W = \int_0^t p \cdot dt$$

$$W = \int_0^t \frac{C \cdot v \cdot dv}{dt} \cdot dt$$

$$W = C \int_0^t \frac{v \cdot dv}{dt} \cdot dt$$

$$W = C \int_0^v v \cdot dv$$

$$W = \frac{1}{2} Cv^2$$

Example: 1

A capacitor supplied from 250 Volts DC mains, takes 25 milli Coulombs. Find its capacitance.
 What will be its charge if the voltage is raised to 1000V.

Given Data:

| | |
|--------------------|---------------------------------|
| Supply Voltage (V) | = 250V |
| Charge (C) | = 25 mC = 25×10^{-3} C |
| Raised Voltage | = 1000V |

To Find:

- i) Capacitance
- ii) Charge at 1000V

Solution:

$$\text{Capacitance: } C = \frac{Q}{V} = \frac{25 \times 10^{-3}}{250} = 10^{-4} \text{ F}$$

For the supply voltage of 1000V:

$$\text{Charge: } Q = CV$$

$$Q = 10^{-4} \times 1000$$

$$Q = 0.1 \text{ Coulomb}$$

Example: 2

Three capacitors have capacitance of 4mfd, 6mfd and 8mfd respectively. Find the total capacitance when they are connected (a) in series (b) Parallel.

Given Data:

$$\begin{aligned}\text{Capacitance } (C_1) &= 4 \text{ mfd} \\ \text{Capacitance } (C_2) &= 6 \text{ mfd} \\ \text{Capacitance } (C_3) &= 8 \text{ mfd}\end{aligned}$$

To Find:

- i) Total Capacitance in series
- ii) Total Capacitance in parallel

Solution:

In Series Connection:

$$\begin{aligned}\text{Equivalent Capacitance: } \frac{1}{C_{\text{eq}}} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \\ \frac{1}{C_{\text{eq}}} &= \frac{1}{4} + \frac{1}{6} + \frac{1}{8} \\ \frac{1}{C_{\text{eq}}} &= \frac{6+4+3}{24} = \frac{13}{24} \\ C_{\text{eq}} &= \frac{24}{13} = 1.846 \text{ mfd}\end{aligned}$$

In parallel connection:

$$\begin{aligned}\text{Equivalent Capacitance: } C_{\text{eq}} &= C_1 + C_2 + C_3 \\ &= 4 + 6 + 8 = 18 \text{ mfd}\end{aligned}$$

Example: 3

Three capacitors have capacitance of 1mfd, 2mfd and 6mfd respectively. Find the total capacitance when they are connected (a) in parallel (b) series.

Given Data:

$$\begin{aligned}\text{Capacitance } (C_1) &= 1 \text{ mfd} \\ \text{Capacitance } (C_2) &= 2 \text{ mfd} \\ \text{Capacitance } (C_3) &= 6 \text{ mfd}\end{aligned}$$

To Find:

- i) Total Capacitance in parallel
- ii) Total Capacitance in series

Solution:

In parallel connection:

$$\begin{aligned}\text{Equivalent Capacitance: } C_{\text{eq}} &= C_1 + C_2 + C_3 \\ &= 1 + 2 + 6 = 9 \text{ mfd}\end{aligned}$$

In Series Connection:

$$\begin{aligned}\text{Equivalent Capacitance: } \frac{1}{C_{\text{eq}}} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \\ \frac{1}{C_{\text{eq}}} &= \frac{1}{1} + \frac{1}{2} + \frac{1}{6} \\ \frac{1}{C_{\text{eq}}} &= \frac{6+3+1}{6} = \frac{10}{6} \\ C_{\text{eq}} &= \frac{6}{10} = 0.6 \text{ mfd}\end{aligned}$$

Example: 4

If two capacitors having capacitance of 6mfd and 10mfd respectively are connected in series across a 320V supply. Find (a) the p.d across each capacitor (b) the charge on each capacitor.

Given Data:

$$\begin{aligned}\text{Capacitance } (C_1) &= 6 \text{ mfd} \\ \text{Capacitance } (C_2) &= 10 \text{ mfd} \\ \text{Supply Voltage } (V) &= 320 \text{ V}\end{aligned}$$

To Find:

- i) the p.d across each capacitor
- ii) the charge on each capacitor

Solution:

In Series Connection:

Equivalent Capacitance:

$$\begin{aligned}\frac{1}{C_{\text{eq}}} &= \frac{1}{C_1} + \frac{1}{C_2} \\ \frac{1}{C_{\text{eq}}} &= \frac{1}{6} + \frac{1}{10} \\ \frac{1}{C_{\text{eq}}} &= \frac{10+6}{60} = \frac{16}{60} \\ C_{\text{eq}} &= \frac{60}{16} = 3.75 \text{ mfd}\end{aligned}$$

$$\begin{aligned}\text{Charge : } Q &= C \cdot V \\ Q &= 3.75 \times 10^{-6} \times 320 = 0.0012 \text{ Coulomb}\end{aligned}$$

$$\begin{aligned}\text{Charge on capacitor } C_1 : Q_1 &= 0.0012 \text{ Coulomb} \\ \text{Charge on capacitor } C_2 : Q_2 &= 0.0012 \text{ Coulomb}\end{aligned}$$

$$\begin{aligned}\text{P.d across Capacitor } C_1 : V_1 &= \frac{Q_1}{C_1} \\ V_1 &= \frac{0.0012}{6 \times 10^{-6}} = 200 \text{ Volts}\end{aligned}$$

$$\begin{aligned}\text{P.d across Capacitor } C_2 : V_2 &= \frac{Q_2}{C_2} \\ V_2 &= \frac{0.0012}{10 \times 10^{-6}} = 120 \text{ Volts}\end{aligned}$$

Example: 5

Three capacitors 5mfd, 10mfd and 15mfd are connected in parallel across 250V supply. Find the energy stored.

Given Data:

$$\begin{aligned}\text{Capacitance } (C_1) &= 5 \text{ mfd} \\ \text{Capacitance } (C_2) &= 10 \text{ mfd} \\ \text{Capacitance } (C_3) &= 15 \text{ mfd}\end{aligned}$$

To Find:

- i) Energy stored

Solution:

In parallel connection:

$$\begin{aligned}\text{Equivalent Capacitance : } C_{\text{eq}} &= C_1 + C_2 + C_3 \\ C_{\text{eq}} &= 5 + 10 + 15 = 30 \text{ mfd}\end{aligned}$$

$$\begin{aligned}
 \text{Energy Stored: } E &= \frac{1}{2} C V^2 \\
 &= \frac{1}{2} \times 30 \times 10^{-6} \times 250^2 \\
 &= 0.9375 \text{ Joules}
 \end{aligned}$$

Example: 6

Two capacitors each of $3\mu\text{f}$ and $4\mu\text{f}$ are connected in series across 100V d.c supply. Calculate
(i) the voltage across each capacitor (ii) the energy stored across each capacitor and (iii)
the equivalent capacitance of the combination.

Given Data:

$$\begin{aligned}
 \text{Capacitance } (C_1) &= 3 \mu\text{f} \\
 \text{Capacitance } (C_2) &= 4\mu\text{f} \\
 \text{Supply Voltage } (V) &= 100\text{V}
 \end{aligned}$$

To Find:

- i) Voltage across each capacitor
- ii) Energy stored across each capacitor
- iii) equivalent capacitance

Solution:

In parallel connection:

$$\begin{aligned}
 \text{Equivalent Capacitance: } \frac{1}{C_{eq}} &= \frac{1}{C_1} + \frac{1}{C_2} \\
 \frac{1}{C_{eq}} &= \frac{1}{3} + \frac{1}{4} \\
 \frac{1}{C_{eq}} &= \frac{4+3}{12} = \frac{7}{12} \\
 C_{eq} &= \frac{12}{7} = 1.71 \text{ mfd}
 \end{aligned}$$

$$\begin{aligned}
 \text{Energy Stored: } E &= \frac{1}{2} C V^2 \\
 &= \frac{1}{2} \times 1.71 \times 10^{-6} \times 100^2 \\
 &= 0.00855 \text{ Joules}
 \end{aligned}$$

$$\text{Charge : } Q = C \cdot V$$

$$Q = 1.71 \times 10^{-6} \times 100 = 1.71 \times 10^{-4} \text{ Coulomb}$$

$$\text{Charge on capacitor } C_1 : Q_1 = 1.71 \times 10^{-4} \text{ Coulomb}$$

$$\text{Charge on capacitor } C_2 : Q_2 = 1.71 \times 10^{-4} \text{ Coulomb}$$

$$\text{Potential difference across Capacitor } C_1 : V_1 = \frac{Q_1}{C_1} = \frac{1.71 \times 10^{-4}}{3 \times 10^{-6}} = 57 \text{ Volts}$$

$$\text{Potential difference across Capacitor } C_2 : V_2 = \frac{Q_2}{C_2} = \frac{1.71 \times 10^{-4}}{4 \times 10^{-6}} = 42.8 \text{ Volts}$$

(B) D.C CIRCUITS

1.15 Introduction:

Matter is anything that has mass and occupies space; matter exists in three states normally solid, liquid and gaseous form. All matter in the universe are made up of fundamental building blocks called atoms. Figure shows the simplified structure of an atom. All atoms consist of **protons**, **neutrons** and **electrons**. The protons, which have positive electrical charges, and the neutrons, which have no electrical charge, are contained within the **nucleus**.

The mass of proton is approximately 1840 times that of an electron. A neutron has a mass equal to that of a proton but it has no charge. Electrons carry a negative charge of -1.602×10^{-19} Coulomb. The electrons move round the nucleus in different orbit or shells.

The maximum number of electrons allowed in each orbit is given by $2n^2$ where n is the number of orbit. Thus first orbit can accommodate $2 \times 1^2 = 2$ electrons; the second orbit has $2 \times 2^2 = 8$ electrons, the third electrons $2 \times 3^2 = 18$ electrons and so on.

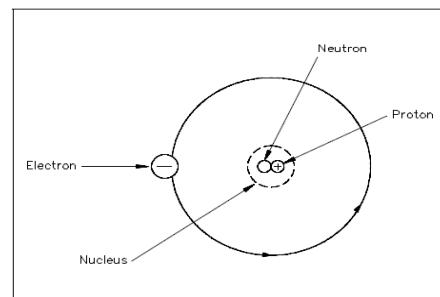


Figure 1.6 Atomic Structure

1.16 Electrical Circuit:

Electrical circuit is an interconnection of electrical devices which has atleast one closed path for current flow.

1.16.1 Conductors:

Conductors are materials that readily allow current. They have a large number of free electrons. Most metals are good conductors. Silver is the best conductor and copper is next. Copper is the most widely used conductive material because it is less expensive than silver. Copper wire is commonly used as a conductor in electric circuits.

Examples: Copper, Aluminium, Brass, Platinum, Silver, Gold and Carbon etc.,

1.16.2 Insulators:

Insulators, or nonconductors, are materials with electrons that are tightly bound to their atoms and require large amounts of energy to free them from the influence of the nucleus.

Examples: Plastic, Rubber, Glass, Porcelain, Air, Paper, Cork, Mica, Ceramics and Certain oils

1.16.3 Semiconductors:

These materials are neither good conductor nor insulators. Their electrical conductivity lies between good conductors and insulators.

Examples: Silicon and germanium

1.16.4 Super conductors:

Super conductors are a group of metals and alloys which have zero resistivity of infinite conductivity.

1.16.5 Newton:

The Newton is defined as the force required to accelerate a mass of one kg, by one metre per second squared (1m/s^2). The unit of force is the Newton (N) where one Newton is one kilogram metre per second squared.

$$\text{Force: } F = m \cdot a ; N$$

1.16.6 Joule:

The unit of work or energy is the **joule (J)** where one joule is one Newton Metre. One joule is defined as the work done by the application of constant 1 Newton through a 1 metre distance.

$$\begin{aligned}\text{Workdone} &= \text{Force} \times \text{Distance} \\ W &= F \times d ; N - \text{m or Joule}\end{aligned}$$

1.17 Electricity:

It can be defined in terms of its behavior. It classified as either static or dynamic depending on whether the charge carries either static or dynamic.

1.18 Electrical Charge:

Electrical charge, denoted by Q. Charge is the characteristics property of the elementary particles of the matter. The elementary particles are electrons, protons and neutron. Charge can be either positive or negative and is usually measured in coulombs. The charge of an electron is called negative charge and charge of a proton is called positive charge.

The charge of an electron is equal to 1.602×10^{-19} coulombs.

1.18.1 Coulomb:

The coulomb is the basic unit of electrical charge. It is denoted by C. One coulomb of charge consists of approximately 6.24×10^{18} electrons or protons.

1.19 Current:

The rate of flow of electric charges is called, “electric current”. The unit of current is ampere (A). It is denoted by the letter ‘I’

$$\begin{aligned}\text{Current} &= \frac{\text{Charges}}{\text{Time}} \\ I &= \frac{Q}{t}\end{aligned}$$

Where, Q = electric charge; coulomb (C)

T = time; second (S)

1.19.1 Ampere:

An ampere is defined as the flow of one coulomb of charge in one second.

$$1 \text{ ampere} = 1 \text{ coulomb per second}$$

Example : 7

A charge of 35 mC is transferred between two points in a circuit in a time of 20 ms. Calculate the value of current flowing.

Solution:

$$Q = 35 \times 10^{-3} \text{ C}; t = 20 \times 10^{-3} \text{ s}$$

$$I = \frac{Q}{t} \text{ amp}$$

$$= \frac{35 \times 10^{-3}}{20 \times 10^{-3}}$$

$$I = 1.75 \text{ A } \mathbf{Ans}$$

Example : 8

If a current of 120 μA flows for a time of 15s, determine the amount of charge transferred.

Solution:

$$I = 120 \times 10^{-6} \text{ A}; t = 15 \text{ s}$$

$$Q = It \text{ coulomb}$$

$$= 120 \times 10^{-6} \times 15$$

$$Q = 1.8 \text{ mC } \mathbf{Ans}$$

Example : 9

80 coulombs of charge were transferred by a current of 0.5 A. Calculate the time for which the current flowed.

Solution:

$$Q = 80 \text{ C}; I = 0.5 \text{ A}$$

$$t = \frac{Q}{I} \text{ seconds}$$

$$= \frac{80}{0.5}$$

$$t = 160 \text{ s } \mathbf{Ans}$$

1.20 Electro Motive Force (E.M.F):

It is the force which causes the flow of electrons in any closed circuit. The unit of electro motive force is volt. It is represented by letter E or V.

$$\begin{aligned} \text{EMF} &= \frac{\text{Workdone}}{\text{Charge}} \\ \text{E or V} &= \frac{\text{W}}{\text{Q}} \end{aligned}$$

1.21 Potential Difference (p.d):

Whenever current flows through a resistor there will be a potential difference (p.d) developed across it. Essentially, emf causes current to flow; whilst a p.d. is the result of current flowing through a resistor. The unit of potential difference is volt (V).

1.21.1 Difference between E.M.F and Potential difference (p.d):

| S.No | E.M.F | Potential difference |
|------|--|---|
| 1 | It refers to source of electrical energy | It exists between any points in a circuit |
| 2 | It is measured in open circuit | It is measured in closed circuit |
| 3 | It is a cause for current flow | It is the effect of current flow |
| 4 | It is greater than the potential difference in the same circuit. | It is less than the E.M.F in the same circuit |

1.22 Electrical power:

Power is defined as the rate of doing work. It is represented by 'P'.

$$P = \frac{dW}{dt} = \frac{dW}{dQ} \times \frac{dQ}{dt} = V \times I$$

$$\text{Power} = \text{Voltage} \times \text{current}$$

Hence, the electrical power is given by the product of voltage and current. The unit of power is the **watt (W)**.

Note:

- $1 \text{ KW} = 1000 \text{ Watts} = 10^3 \text{ W}$
- $1 \text{ MW} = 1000000 \text{ Watts} = 10^6 \text{ W}$
- Wattmeter is used to measure the power

1.23 Energy:

It is defined as the capacity to do work. It is the total electrical energy consumed over a period.

$$\text{Electrical Energy} = \text{Power} \times \text{Time}$$

$$E = P \times t$$


$$\text{Or } E = V \times I \times t ; \text{ watt-hour}$$

Note:

- $1 \text{ KWH} = 1 \text{ Unit}$
 $= 1000 \text{ Watt Hour}$
 $= 1000 \times 3600 \text{ Watt Second or Joules}$
 $= 3600000 \text{ Joules}$
- *Energy meter is used to measure the Energy*

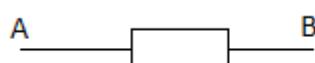1.24 Electrical Circuit Elements:

Electrical circuit elements are two terminal devices which are basic building blocks of the electrical circuit. Figure shows the general form of two terminal device, where A and B forms the terminals.



1.24.1 Classifications of Electrical Circuit Elements:

1. Passive Elements (Resistor, Inductor and Capacitor)
2. Active Elements

1.24.2 Passive Elements:

- ✓ Passive elements stores or dissipates the energy.
- ✓ Example: Resistor dissipates energy and capacitor stores energy.

1.24.3 Active Elements:

- ✓ An element capable of supplying energy is called as active elements.
- ✓ An active element can be considered as source of energy.

1.25 Resistance:

It is defined as the property of a substance which opposes the flow of current through it. It is represented by R. The unit of resistance is ohm (Ω). One ohm is one volt per ampere.

1.25.1 Laws of Resistance:

The resistance of an electrical conductor depends upon the following factors:

- (a) The length of the conductor,
- (b) The cross-sectional area of the conductor,
- (c) The type of material and
- (d) The temperature of the material.

Resistance (R) is directly proportional to length (l), and inversely proportional to the cross-sectional area (a).

$$\text{i.e., } R \propto \frac{l}{a}$$

$$\text{i.e., } R = \frac{\rho l}{a}$$

Where, 'ρ' is the **resistivity** of the material

1.25.2 Specific Resistance:

The specific resistance of the material is the resistance of a unit cube of the material measured between opposite faces of the cube. Resistivity varies with temperature. It is represented by the symbol 'ρ' (Greek rho) and the unit of 'ρ' is ohm metre ($\Omega\text{-m}$)

1.26 Conductance:

Conductance may be defined as the ability of the conductor to allow the current freely through it. Conductance is reciprocal of resistance. It is represented by the letter 'G'. The unit for the conductance is siemen.

$$\text{i.e., } G \propto \frac{1}{R}$$

Example: 10

A coil of copper wire 200 m long and of cross sectional area of 0.8 mm^2 has a resistivity of $0.02 \mu\Omega \text{ m}$ at normal working temperature. Calculate the resistance of the coil.

Solution:

$$\ell = 200 \text{ m}; \rho = 2 \times 10^{-8} \Omega \text{m}; A = 8 \times 10^{-7} \text{ m}^2$$

$$R = \frac{\rho \ell}{A} \text{ ohm}$$

$$= \frac{2 \times 10^{-8} \times 200}{8 \times 10^{-7}}$$

$$R = 5 \Omega \text{ Ans}$$

Example: 11

A wire-wound resistor is made from a 250 metre length of copper wire having a circular cross-section of diameter 0.5 mm. Given that the wire has a resistivity of $0.018 \mu\Omega \text{ m}$, calculate its resistance value.

Solution:

$$\ell = 250 \text{ m}; d = 5 \times 10^{-4} \text{ m}; \rho = 1.8 \times 10^{-8} \Omega \text{m}$$

$$R = \frac{\rho \ell}{A} \text{ ohm, where cross-sectional area, } A = \frac{\pi d^2}{4} \text{ metre}^2$$

$$\text{hence, } A = \frac{\pi \times (5 \times 10^{-4})^2}{4} = 1.9635 \times 10^{-7} \text{ m}^2$$

$$\text{hence, } R = \frac{1.8 \times 10^{-8} \times 250}{1.9635 \times 10^{-7}}$$

$$\text{so, } R = 22.92 \Omega \text{ Ans}$$

1.27 Temperature coefficient of resistance:

The resistance of almost all electricity conducting materials changes with the variation in temperature. This variation of resistance with change in temperature is governed by a property of a material called temperature coefficient of resistance (α).

The temperature coefficient of resistance can be defined as the change in resistance per degree change in temperature and expressed as a fraction of the resistance at the reference temperature considered.

Let,


R_0 = Resistance at 0°C

R_1 = Resistance at $t_1^\circ\text{C}$

R_2 = Resistance at $t_2^\circ\text{C}$

α_0 = temp. coefficient of resistance at 0°C

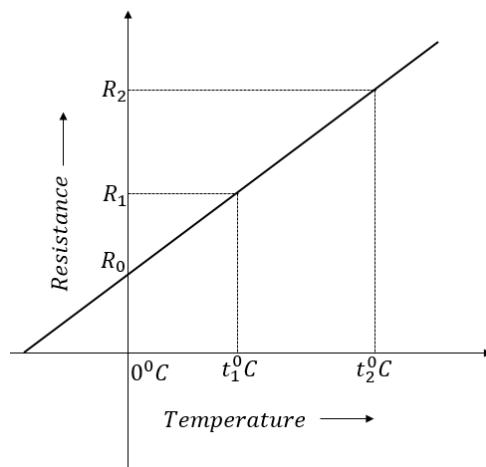α_1 = temp. coefficient of resistance at $t_1^\circ\text{C}$



Temperature coefficient of resistance at 0°C :

$$\alpha_0 = \frac{\text{Change in resistance}}{\text{Original resistance} \times \text{Change in temperature}}$$

$$\alpha_0 = \frac{R_1 - R_0}{R_0 \times t_1}$$

$$R_1 - R_0 = \alpha_0 (R_0 \times t_1) = \alpha_0 R_0 t_1$$

$$R_1 = \alpha_0 R_0 t_1 + R_0 = R_0 (\alpha_0 t_1 + 1)$$

$$R_1 = R_0 (1 + \alpha_0 t_1) \quad \dots \dots \dots (1)$$

$$\text{Similarly, } R_2 = R_0 (1 + \alpha_0 t_2) \quad \dots \dots \dots (2)$$

Equation $\frac{(2)}{(1)}$, we get :

$$\frac{R_2}{R_1} = \frac{R_0 (1 + \alpha_0 t_2)}{R_0 (1 + \alpha_0 t_1)}$$

$$\frac{R_2}{R_1} = \frac{(1 + \alpha_0 t_2)}{(1 + \alpha_0 t_1)} \quad \dots \dots \dots (3)$$

Temperature coefficient of resistance at $t_1^\circ\text{C}$:

$$\alpha_1 = \frac{R_2 - R_1}{(t_2 - t_1) R_1}$$

$$R_2 - R_1 = \alpha_1 (t_2 - t_1) R_1$$

$$R_2 = \alpha_1 (t_2 - t_1) R_1 + R_1$$

$$R_2 = R_1 [\alpha_1 (t_2 - t_1) + 1]$$

$$R_2 = R_1 [1 + \alpha_1 (t_2 - t_1)]$$

$$\frac{R_2}{R_1} = [1 + \alpha_1 (t_2 - t_1)] \quad \dots \dots \dots (4)$$

$$\begin{array}{lcl} \text{L.H.S of Equation (3)} & = & \text{L.H.S of Equation (4)} \\ \text{Hence, R.H.S of Equation (3)} & = & \text{R.H.S of Equation (4)} \end{array}$$

$$\frac{(1 + \alpha_0 t_2)}{(1 + \alpha_0 t_1)} = [1 + \alpha_1 (t_2 - t_1)]$$

Add - 1 on both sides:

$$\frac{(1 + \alpha_0 t_2)}{(1 + \alpha_0 t_1)} - 1 = [1 + \alpha_1 (t_2 - t_1)] - 1$$

$$\frac{(1 + \alpha_0 t_2)}{(1 + \alpha_0 t_1)} - 1 = \alpha_1 (t_2 - t_1)$$

$$\frac{(1 + \alpha_0 t_2) - (1 + \alpha_0 t_1)}{(1 + \alpha_0 t_1)} = \alpha_1 (t_2 - t_1)$$

$$\frac{\alpha_0 t_2 - \alpha_0 t_1}{(1 + \alpha_0 t_1)} = \alpha_1 (t_2 - t_1)$$

$$\frac{\alpha_0 (t_2 - t_1)}{(1 + \alpha_0 t_1)} = \alpha_1 (t_2 - t_1)$$

$$\frac{\alpha_0}{(1 + \alpha_0 t_1)} = \alpha_1$$

Temperature coefficient of resistance at $t_1^\circ\text{C}$:

$$\alpha_1 = \frac{\alpha_0}{(1 + \alpha_0 t_1)}$$

Example: 12

A copper coil has a resistance of $30\ \Omega$ at 0°C . Find the resistance of the coil at 40°C . Temp co-efficient of copper is 0.0043 at 0°C .

Given Data:

$$\begin{array}{lll} \text{Resistance at } 0^\circ\text{C } (R_0) & = & 30\Omega \\ \text{Temp co-efficient at } 0^\circ\text{C } (t_0) & = & 0.0043 \end{array}$$

To Find:

i) Resistance at 40°C

Solution:

$$\begin{aligned} \text{Resistance at } 40^\circ\text{C} : \quad R_t &= R_0 [1 + \alpha_0 \cdot t] \\ R_t &= 30 [1 + 0.0043 \times 40] \\ R_t &= 35.16\ \Omega \end{aligned}$$

Answer:

$$\text{Resistance at } 40^\circ\text{C} = 35.16\ \Omega$$

Example: 13

An aluminium wire has a resistance of $25\ \Omega$ at 20°C . What is the resistance at 50°C . Temp co-efficient of copper is 0.00403 at 20°C .

Given Data:

$$\begin{array}{lll} \text{Resistance at } 20^\circ\text{C } (R_1) & = & 25\Omega \\ \text{Temp co-efficient at } 20^\circ\text{C } (t_1) & = & 0.00403 \end{array}$$

To Find:

i) Resistance at 50°C

Solution:

$$\begin{aligned} \text{Resistance at } 50^\circ\text{C} : \quad R_2 &= R_1 [1 + \alpha_1 (t_2 - t_1)] \\ R_2 &= 25 [1 + 0.00403 (50 - 20)] \\ R_2 &= 25 [1 + 0.00403 (30)] \\ R_2 &= 25 [1 + 0.1209] = 25 \times 1.1209 = 28.02\ \Omega \end{aligned}$$

Answer:

$$\text{Resistance at } 50^\circ\text{C} = 28.02\ \Omega$$

Example: 14

The field coil of a motor has a resistance of $250\ \Omega$ at 15°C . Find the increase in resistance of the field at a temperature of 45°C . Take $\alpha = 0.00428$ at 0°C .

Given Data:

$$\begin{array}{lll} \text{Resistance at } 15^\circ\text{C } (R_1) & = & 250\Omega \\ \text{Temp co-efficient at } 0^\circ\text{C } (t_1) & = & 0.00428 \end{array}$$

To Find:

i) Resistance at 45°C

Solution:

$$\text{Resistance at } 45^\circ\text{C} : \quad R_2 = R_1 [1 + \alpha_1 (t_2 - t_1)]$$

$$\begin{aligned}
 \alpha_0 &= \frac{\alpha_0}{1 + \alpha_0 t_1} \\
 &= \frac{0.00428}{1 + 0.00428 \times 15} \\
 \alpha_0 &= \frac{0.00428}{1.0642} = 0.0040218 \\
 R_2 &= 250 [1 + 0.0040218 (45 - 15)] \\
 R_2 &= 250 [1 + 0.0040218 (30)] \\
 R_2 &= 250 [1 + 0.1206] = 25 \times 1.1206 = 280.15 \Omega
 \end{aligned}$$

Answer:

Resistance at 45°C = 280.15 Ω

Example: 15

If the temperature co-efficient of copper at 20°C is 0.00393 find its resistance at 80°C given that resistance at 20°C is 30Ω.

Given Data:

$$\begin{aligned}
 \text{Resistance at } 20^\circ\text{C} (R_1) &= 30\Omega \\
 \text{Temp co-efficient at } 20^\circ\text{C} (t_1) &= 0.00393
 \end{aligned}$$

To Find:

i) Resistance at 80°C

Solution:

$$\begin{aligned}
 \text{Resistance at } 80^\circ\text{C} : R_2 &= R_1 [1 + \alpha_1 (t_2 - t_1)] \\
 R_2 &= 30 [1 + 0.00393 (80 - 20)] \\
 R_2 &= 30 [1 + 0.00393 (60)] \\
 R_2 &= 30 [1 + 0.2358] = 25 \times 1.2358 = 37.07\Omega
 \end{aligned}$$

Answer:

Resistance at 80°C = 37.07 Ω

Example: 16

An aluminium wire has a resistance of 3.6 Ω at 20°C. What is its resistance at 50°C if the temperature co-efficient of resistance is 0.00403 at 20°C.

Given Data:

$$\begin{aligned}
 \text{Resistance at } 20^\circ\text{C} (R_1) &= 3.6\Omega \\
 \text{Temp co-efficient at } 20^\circ\text{C} (t_1) &= 0.00403
 \end{aligned}$$

To Find:

i) Resistance at 50°C

Solution:

$$\begin{aligned}
 \text{Resistance at } 50^\circ\text{C} : R_2 &= R_1 [1 + \alpha_1 (t_2 - t_1)] \\
 R_2 &= 3.6 [1 + 0.00403 (50 - 20)] \\
 R_2 &= 3.6 [1 + 0.00403 (30)] \\
 R_2 &= 3.6 [1 + 0.1209] = 3.6 \times 1.1209 = 4.035\Omega
 \end{aligned}$$


1.28 Ohms law:

The relationship between Voltage, Current and Resistance in any DC electrical circuit was explained by the German physicist Georg Ohm, (1787 - 1854). Georg Ohm found that, at a constant temperature, the electrical current flowing through a fixed linear resistance is directly proportional to the voltage applied across it, and also inversely proportional to the resistance.

Statement:

It states that the current 'I' flowing in a circuit is directly proportional to the applied voltage 'V' and inversely proportional to the resistance 'R', provided the temperature remains constant.
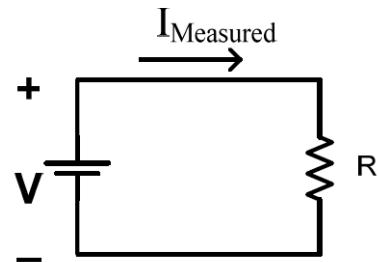
$$\begin{aligned} \text{Thus, } I &\propto V \\ \text{Current : } I &= \frac{V}{R} \\ \text{Voltage : } V &= I \cdot R \\ \text{Resistance : } R &= \frac{V}{I} \end{aligned}$$



According to Ohm's Law :

$$\begin{aligned} \text{Power : } P &= \text{Voltage} \times \text{Current} \\ P &= V \times I \quad \cdots \cdots (1) \\ \text{Substitute, } V &= I \cdot R \quad \text{in equation (1)} \\ P &= I \cdot R \times I \\ P &= I^2 R \\ \text{Substitute, } I &= \frac{V}{R} \quad \text{in equation (1)} \\ P &= V \cdot \frac{V}{R} \\ P &= \frac{V^2}{R} \end{aligned}$$

According to Ohm's Law :

$$\begin{aligned} \text{Energy : } E &= \text{Voltage} \times \text{Current} \times \text{Time} \\ E &= V \times I \times t \quad \cdots \cdots (1) \\ \text{Substitute, } V &= I \cdot R \quad \text{in equation (1)} \\ E &= I \cdot R \times I \times t \\ E &= I^2 R t \\ \text{Substitute, } I &= \frac{V}{R} \quad \text{in equation (1)} \\ E &= V \cdot \frac{V}{R} \cdot t \\ E &= \frac{V^2 t}{R} \end{aligned}$$

1.29 Relation between Mechanical, Electrical & Thermal Energy:

$$1 \text{ N-M} = 1 \text{ Joule} = 1 \text{ watt-sec}$$

$$1 \text{ calorie} = 4.186 \text{ joules}$$

1.29.1 Electrical to Thermal energy:

$$\begin{aligned} 1 \text{ KWH} &= 1000 \times 60 \times 60 \text{ watt-sec} && \{\text{KWH} = \text{Kilo Watt Hour}\} \\ &= 36 \times 10^5 \text{ watt-sec} && (1 \text{ watt sec} = 1 \text{ Joule}) \\ &= 36 \times 10^5 \text{ joules} && (\text{or}) \\ 1 \text{ KWH} &= 8.6 \times 10^2 \text{ Kilo calories} && (1 \text{ calorie} = 4.186 \text{ J}) \end{aligned}$$

1.29.2 Mechanical Power to Electrical Power:

$$\begin{aligned} 1 \text{ horse power} &= 75 \text{ kg. m/sec} && (1 \text{ kgm} = 9.81 \text{ m}) \\ &= 75 \times 9.81 \text{ Nm/sec} \\ &= 75 \times 9.81 \text{ joules/sec} \\ 1 \text{ h.p.} &= 735.5 \text{ watts or } 736 \text{ watts} && (1 \text{ joule/sec} = 1 \text{ watt}) \end{aligned}$$

1.29.3 Electrical Power to Mechanical Power:

$$\begin{aligned} 1 \text{ KW} &= 1000 \text{ watts} && \{\text{KW} = \text{Kilo Watts}\} \\ 1 \text{ h.p.} &= 735.5 \text{ watts} \\ 1 \text{ KW} &= 1.33 \text{ h.p.} \end{aligned}$$

Example: 18

An electric heater is rated 1KW, 250V. Find the current drawn and the resistance of the heating element.

Given Data:

$$\begin{aligned} \text{Power (P)} &= 1 \text{ KW} = 1000 \text{ W} \\ \text{Voltage} &= 250 \text{ V} \end{aligned}$$

To Find:

$$\begin{aligned} \text{Resistance (R)} &=? \\ \text{Current (I)} &=? \end{aligned}$$

Solution:

$$\begin{aligned} \text{Resistance: } R &= \frac{V^2}{P} \\ &= \frac{250^2}{1000} = 62.5 \Omega \\ \text{Current: } I &= \frac{V}{R} \\ I &= \frac{250}{62.5} = 4 \text{ A} \end{aligned}$$

Answer:

$$\begin{aligned} \text{Resistance of the heating element (R)} &= 62.5 \Omega \\ \text{Current drawn by the heater (I)} &= 4 \text{ Amps} \end{aligned}$$

1.30 Resistors in series:

The circuit in which dissimilar ends are connected together is called as series circuit. In series circuit the current through all the resistors are same.

Let,


$R_1, R_2 \text{ & } R_3$ – Three resistances connected in series.

E - Applied voltage across the circuit in volts

I – Circuit current in amps

R - The equivalent resistance in ohms

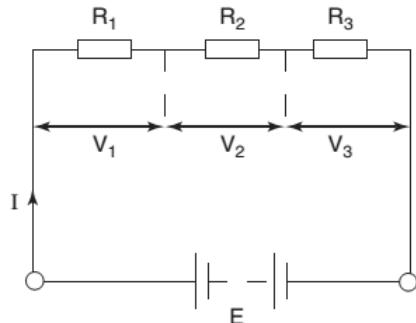$V_1, V_2 \text{ & } V_3$ – p.d across $R_1, R_2 \text{ & } R_3$ respectively.



By applying KVL to the circuit,

The sum of potential drops across each resistor is equal to the applied voltage.

$$E = V_1 + V_2 + V_3 \quad \dots \quad (1)$$

Apply ohm's law for individual resistors,

$$V_1 = I.R_1 \quad \dots \quad (2)$$

$$V_2 = I.R_2 \quad \dots \quad (3)$$

$$V_3 = I.R_3 \quad \dots \quad (4) \quad [\text{current is same}]$$

Substitute equation (2), (3) & (4) in equation (1)

$$\Rightarrow E = V_1 + V_2 + V_3$$

$$E = I.R_1 + I.R_2 + I.R_3$$

$$E = I(R_1 + R_2 + R_3) \quad \dots \quad (5)$$

$$\text{Where, } E = I.R_{\text{eq}} \quad \dots \quad (6)$$

Equating equations (5) & (6)

$$I.R_{\text{eq}} = I(R_1 + R_2 + R_3)$$

$$R_{\text{eq}} = R_1 + R_2 + R_3 \quad \Omega \quad [\text{Three resistance in series}]$$

If there are 'n' resistance connected in series,

$$\text{Then equivalent resistance, } R_{\text{eq}} = R_1 + R_2 + R_3 + \dots + R_n$$

1.31 Resistors in Parallel:

The circuit in which similar ends are connected together is called as parallel circuit. In the given circuit R_1, R_2 and R_3 are connected in parallel. There are many separate paths for current flow. The voltage across all parallel branches is the same. Current in each branch is different and depends on the value of resistance in the branch.

Equivalent resistance of parallel connected resistances:

Let,

$R_1, R_2 \text{ & } R_3$ – Three resistances connected in parallel


E - Applied voltage across the circuit in volts

I – Total current in amps

R - The equivalent resistance in ohms

$I_1, I_2 \text{ & } I_3$ – current through $R_1, R_2 \text{ & } R_3$ respectively

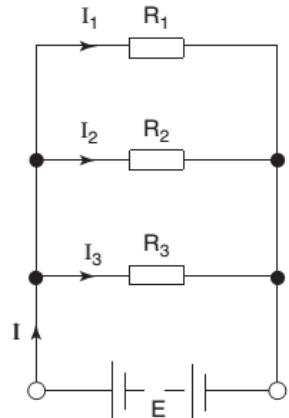Since all resistors are connected across battery, the p.d across all are same.



$$V \text{ or } E = V_1 + V_2 + V_3$$

By applying KCL in the circuit:

$$I = I_1 + I_2 + I_3 \quad \dots \dots \dots (1)$$

Apply Ohm's law for individual Resistor:

$$\text{Current: } I_1 = \frac{E}{R_1} \quad \dots \dots \dots (2)$$

$$I_2 = \frac{E}{R_2} \quad \dots \dots \dots (3)$$

$$I_3 = \frac{E}{R_3} \quad \dots \dots \dots (4)$$

Substitute equation (2), (3) & (4) in equation (1)

$$I = I_1 + I_2 + I_3$$

$$I = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

$$I = E \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\frac{I}{E} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{Equivalent Resistance: } \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

If 'n' number of Resistors are connected in parallel:

$$\text{Equivalent Resistance: } \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

1.31.1 Two resistances in parallel:

This equation must be used when finding the total resistance R of a parallel circuit. For the special case of two resistors in parallel.

In case of two Resistors in parallel:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad \text{i.e. } \frac{\text{Product}}{\text{Sum}}$$

1.32 Current Division in Parallel Connected Resistances:

Consider two resistances R_1 and R_2 in parallel and connected to a dc source of V Volts.


Let,

V - Supply Voltage

I - Circuit Current

I_1 – Current through R_1

I_2 – Current through R_2

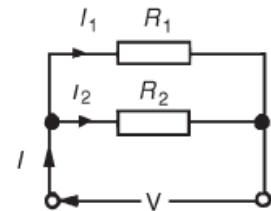

$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad \text{i.e. } \frac{\text{Product}}{\text{Sum}}$$

$$V = I \cdot R_{eq}$$

$$V = I \cdot \left[\frac{R_1 \cdot R_2}{R_1 + R_2} \right]$$

Current through R_1 ; $I_1 = \frac{V}{R_1}$

$$I_1 = \frac{I \cdot \left[\frac{R_1 \cdot R_2}{R_1 + R_2} \right]}{R_1}$$

$$I_1 = \frac{I \cdot R_2}{R_1 + R_2} \quad \text{----- (1)}$$

Similarly,

$$\text{Current through } R_2 ; \quad I_2 = \frac{I \cdot R_1}{R_1 + R_2} \quad \text{----- (2)}$$

The equation (1) and (2) are called as current divide rule.

1.33 Voltage Division in Series Connected Resistances:

Consider two resistances R_1 and R_2 in series and connected to a dc source of V Volts.


Let,

V - Supply Voltage

I - Circuit Current

V_1 – P.D across R_1

V_2 – P.D across R_2

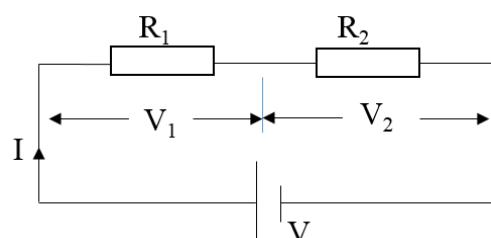

$$R_{eq} = R_1 + R_2$$

Circuit Current ; $I = \frac{V}{R_{eq}}$

Circuit Current ; $I = \frac{V}{R_1 + R_2}$

P. D across R_1 ; $V_1 = I \cdot R_1$ [In series circuit: $I=I_1=I_2$]

P. D across R_1 ; $V_1 = \frac{V}{R_1 + R_2} \cdot R_1$ ----- (1)

Similarly,

$$\text{P. D across } R_2 ; V_2 = \frac{V}{R_1 + R_2} \cdot R_2 \text{ ----- (2)}$$

The equation (1) and (2) are called as voltage divide rule.

Example: 19

A 100Watt, 250 Volts lamp is connected in series with a 100W, 200Volts lamp across a 250 Volts supply. Find the value of current flows through the lamp and voltage across each lamp.

Given Data:

| | | |
|-------------------|---|-------|
| Power (P_1) | = | 100W |
| Voltage (V_1) | = | 250 V |
| Power (P_2) | = | 100W |
| Voltage (V_2) | = | 200 V |

To Find:

| |
|------------------------------|
| Current (I) = ? |
| Voltage drop across Lamp1 =? |
| Voltage drop across Lamp2=? |

Solution:

$$\text{Resistance: } R_1 = \frac{V^2}{P_1} = \frac{250^2}{100} = 625\Omega$$

$$\text{Resistance : } R_2 = \frac{V^2}{P} = \frac{200^2}{100} = 400 \Omega$$

$$\text{Current: } I = \frac{V}{R_1 + R_2} = \frac{250}{625 + 400} = 0.243A$$

$$\text{Current flow through Lamp 1} = \text{Current flow through Lamp 2}$$

$$\text{Voltage across lamp L}_1 = I \times R_1 = 0.243 \times 625 = 152.4V$$

$$\text{Voltage across lamp L}_2 = I \times R_2 = 0.243 \times 400 = 97.2V$$

Answer:

| | | |
|-------------------------------|---|--------|
| Current flow through Lamp | = | 0.243A |
| Voltage across lamp (L_1) | = | 152.4V |
| Voltage across lamp (L_2) | = | 97.2V |

1.34 Comparison between series circuit and parallel circuit:

| S.NO | Series circuit | Parallel circuit |
|------|--|---|
| 1 | There are only one path for the current to flow | There are as many paths as the resistors are connected in parallel |
| 2 | Same current through all the resistor | Potential is same across all the resistor |
| 3 | The voltage drop across each resistor is different | The current in each resistor is different |
| 4 | The sum of voltage drop is equal to the applied voltage. | The sum of branch current is equal to the total current applied |
| 5 | The total resistance is equal to the sum of all resistors $R = R_1 + R_2 + R_3 + \dots + R_n$ | The reciprocal of the total resistance is equal to the sum of the reciprocals of all resistors $1/R = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_n$ |
| 6 | The total resistance is always greater than the greatest resistance in the circuit | The total resistance is always less than the smallest resistance in the circuit. |
| 7. | Dissimilar ends of resistors are connected together to form a closed circuit | similar ends of resistors are connected together to form a closed circuit |
| 8 | Uses: To operate low voltage devices with high voltage source Ex. Decorative lamps(serial set) | All lamps, fans, motors etc., are connected in parallel across the supply in house wiring |

Example: 20

Three resistances of values 8Ω , 12Ω and 24Ω are connected in series. Find the equivalent resistance. Also find the equivalent resistances when they are connected in parallel.

Given Data:

$$\begin{aligned} \text{Resistance } (R_1) &= 8\Omega \\ \text{Resistance } (R_2) &= 12\Omega \\ \text{Resistance } (R_3) &= 24\Omega \end{aligned}$$

To Find:

- i) Equivalent resistance at series
- ii) Equivalent resistance at parallel

Solution:

In Series Connection:

$$\text{Equivalent Resistance } (R_{eq}) = R_1 + R_2 + R_3$$

$$R_{eq} = 8 + 12 + 24$$

$$R_{eq} = 44\Omega$$

In Parallel Connection:

$$\begin{aligned}\text{Equivalent Resistance: } \frac{1}{R_{eq}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ \frac{1}{R_{eq}} &= \frac{1}{8} + \frac{1}{12} + \frac{1}{24} \\ &= \frac{3+2+1}{24} = \frac{6}{24} \\ R_{eq} &= \frac{24}{6} = 4\Omega\end{aligned}$$

Answer:

Equivalent Resistance in series connection = 44Ω

Equivalent Resistance in parallel connection = 4Ω

Example: 21

Two resistors are connected in parallel and a voltage of 200 volts is applied to the combination. The total current is 25 amps and the power dissipated in one of the resistors is 500 watts. What is the value of each resistance?

Given Data:

Two Resistors in parallel
Supply Voltage (V) = 200 Volts
Total Current (I) = 25 Amps
Power Dissipated in R_1 (P_1) = 500 Watts

To Find:

- i) Value of R_1
- ii) Value of R_2

Solution:

$$\text{Equivalent Resistance: } R_{eq} = \frac{V}{I} = \frac{200}{25} = 8\Omega$$

$$\text{Power dissipated in } R_1: P_1 = \frac{V^2}{R_1}$$

$$\text{Resistance: } R_1 = \frac{V^2}{P_1} = \frac{200^2}{500} = 80\Omega$$

$$\text{Current through } R_1: I_1 = \frac{V}{R_1} = \frac{200}{80} = 2.5\text{Amps}$$

$$\text{Current through } R_2: I_2 = I - I_1 = 25 - 2.5 = 22.5\text{Amps}$$

$$\text{Resistance : } R_2 = \frac{V}{I_2} = \frac{200}{22.5} = 8.89\Omega$$

Answer:

Resistance $R_1 = 80\Omega$

Resistance $R_2 = 8.89\Omega$

Example: 22

A circuit consists of two resistors $20\ \Omega$ and $30\ \Omega$ connected in parallel. They are connected in series with a resistor of $15\ \Omega$. If the current through $15\ \Omega$ resistor is 3 amps find the current in the other resistors, total voltage and total power.

Given Data:

| | | |
|-----------------------|---|--------------|
| Resistance (R_1) | = | $20\ \Omega$ |
| Resistance (R_2) | = | $30\ \Omega$ |
| Resistance (R_3) | = | $15\ \Omega$ |
| Current through R_3 | = | 3 Amps |

To Find:

- i) Current through R_1
- ii) Current through R_2
- iii) Total Voltage
- iv) Total Power

Solution:

R_1 & R_2 in Parallel Connection:

$$\text{Resistance: } R_{12} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{20 \times 30}{20 + 30} = 12\ \Omega$$

$$\text{Equivalent Resistance : } R_{eq} = R_{12} + R_3 = 12 + 15 = 27\ \Omega$$

$$\text{Current through } R_1: I_1 = \frac{I \times R_2}{R_1 + R_2} = \frac{3 \times 30}{20 + 30} = 1.8 \text{ Amps}$$

$$\text{Current through } R_2: I_2 = \frac{I \times R_1}{R_1 + R_2} = \frac{3 \times 20}{20 + 30} = 1.2 \text{ Amps}$$

$$\text{Total Voltage : } V = I \times R_{eq} = 3 \times 27 = 81 \text{ Volts}$$

$$\text{Total Power : } P = V \times I = 81 \times 3 = 243 \text{ Watts}$$

Example: 23

A resistor of $3.6\ \Omega$ is connected in series with another of $4.56\ \Omega$. What resistance should be connected across $3.6\ \Omega$ resistor so that the total resistance of the circuit shall be $6\ \Omega$?

Given Data:

| | | |
|------------------------------------|---|----------------|
| Resistance (R_1) | = | $3.6\ \Omega$ |
| Resistance (R_3) | = | $4.56\ \Omega$ |
| Equivalent Resistance (R_{eq}) | = | $6\ \Omega$ |

To Find:

- i) Resistance R_2

Solution:

R_1 & R_2 in Parallel Connection:

$$\text{Resistance: } R_{12+R_3} = \frac{R_1 \times R_2}{R_1 + R_2} + R_3 = \frac{3.6 \times R_2}{3.6 + R_2} + 4.56$$

$$6 = \frac{3.6 \times R_2}{3.6 + R_2} + 4.56$$

$$6 = \frac{3.6 \times R_2 + 4.56(3.6 + R_2)}{3.6 + R_2}$$

$$6(3.6 + R_2) = 3.6 \times R_2 + 4.56(3.6 + R_2)$$

$$\begin{aligned}
 21.6 + 6R_2 &= 3.6R_2 + 16.41 + 4.56R_2 \\
 21.6 - 16.41 &= 3.6R_2 + 4.56R_2 - 6R_2 \\
 5.19 &= 2.16R_2 \\
 2.16 R_2 &= 5.19 \\
 R_2 &= \frac{5.19}{2.16} = 2.4\Omega
 \end{aligned}$$

Example: 24

A resistor of $R\Omega$ is connected in series with a parallel circuit consisting of 12Ω and 8Ω . The total power in the circuit is 80Watts when the applied voltage is 20V. Calculate the value of R .

Given Data:

| | | |
|----------------------|---|------------|
| Resistance (R_2) | = | 12Ω |
| Resistance (R_3) | = | 8Ω |
| Total Power | = | 80 Watts |
| Supply Voltage | = | 20 Volts |

To Find:

i) Resistance R_1

Solution:

R_2 & R_3 in Parallel Connection:

$$\begin{aligned}
 \text{Resistance: } R_{23} &= \frac{R_2 \times R_3}{R_2 + R_3} = \frac{12 \times 8}{12 + 8} = 4.8\Omega \\
 \text{Current : } I &= \frac{P}{V} = \frac{80}{20} = 4 \text{ Amps} \\
 \text{Equivalent Resistance : } R_{eq} &= \frac{V}{I} = \frac{20}{4} = 5\Omega \\
 R_{eq} &= R_1 + R_{23} \\
 5 &= R_1 + 4.8 \\
 R_1 &= 5 - 4.8 = 0.2\Omega
 \end{aligned}$$

Answer:

Resistance $R_1 = 0.2\Omega$

Example: 25

A circuit consist of two resistances 10Ω and 5Ω connected in series across a supply of 60V.Calculate the voltage across each resistance.

Given Data:

| | | |
|----------------------|---|------------|
| Resistance (R_1) | = | 10Ω |
| Resistance (R_2) | = | 5Ω |
| Supply Voltage | = | 60 Volts |

To Find:

i) Voltage across Resistance R_1
ii) Voltage across Resistance R_2

Solution:*In Series Connection:*

$$\text{Equivalent Resistance } (R_{eq}) = R_1 + R_2$$

$$R_{eq} = 10 + 5$$

$$R_{eq} = 15\Omega$$

$$\text{Current : } I = \frac{V}{R_{eq}} = \frac{60}{15} = 4 \text{ Amps}$$

$$\text{Voltage across Resistance } R_1: V_1 = I \cdot R_1 = 4 \times 10 = 40 \text{ Volts}$$

$$\text{Voltage across Resistance } R_2: V_2 = I \cdot R_2 = 4 \times 5 = 20 \text{ Volts}$$

Answer:

$$\text{Voltage across Resistance } R_1 = 40 \text{ Volts}$$

$$\text{Voltage across Resistance } R_2 = 20 \text{ Volts}$$

Example: 26

A circuit consist of two resistances 6Ω and 3Ω connected in parallel and takes a total circuit of $12A$ from the supply. Calculate the current through each resistance.

Given Data:

$$\text{Resistance } (R_1) = 6\Omega$$

$$\text{Resistance } (R_2) = 3\Omega$$

$$\text{Total Current} = 12 \text{ Amps}$$

To Find:

$$\text{i) Current through Resistance } R_1$$

$$\text{ii) Current through Resistance } R_2$$

Solution:

$$\text{Current through } R_1: I_1 = \frac{I \times R_2}{R_1 + R_2} = \frac{12 \times 3}{6 + 3} = \frac{36}{9} = 4 \text{ Amps}$$

$$\text{Current through } R_2: I_2 = \frac{I \times R_1}{R_1 + R_2} = \frac{12 \times 6}{6 + 3} = \frac{72}{9} = 8 \text{ Amps}$$

Answer:

$$\text{Current through Resistance } R_1 = 4 \text{ Amps}$$

$$\text{Current through Resistance } R_2 = 8 \text{ Amps}$$

Example: 27

Two resistors 4Ω and 6Ω are connected in parallel. The total current flowing through the resistors is $5A$. Find the current flowing through each resistor.

Given Data:

$$\text{Resistance } (R_1) = 4\Omega$$

$$\text{Resistance } (R_2) = 6 \Omega$$

$$\text{Total Current} = 5 \text{ Amps}$$

To Find:

$$\text{i) Current through Resistance } R_1$$

$$\text{ii) Current through Resistance } R_2$$

Solution:

$$\text{Current through } R_1 : I_1 = \frac{I \times R_2}{R_1 + R_2} = \frac{5 \times 6}{4 + 6} = \frac{30}{10} = 3 \text{ Amps}$$

$$\text{Current through } R_2 : I_2 = \frac{I \times R_1}{R_1 + R_2} = \frac{5 \times 4}{4 + 6} = \frac{20}{10} = 2 \text{ Amps}$$

Answer:

Current through Resistance R_1 = 3 Amps

Current through Resistance R_2 = 2 Amps

Example: 28

The resistors of 1Ω , 2Ω and 4Ω are connected in parallel. A 5Ω resistor is connected in series with this parallel combination and a $24V$ battery is connected to the circuit. Find the total current and power in each resistor.

Given Data:

$$\text{Resistance } (R_1) = 1\Omega$$

$$\text{Resistance } (R_2) = 2\Omega$$

$$\text{Resistance } (R_3) = 4\Omega$$

$$\text{Resistance } (R_4) = 5\Omega$$

To Find:

i) Total Current

ii) Power in each resistor

Solution:

In Parallel Connection:

$$\begin{aligned}\text{Equivalent Resistance: } \frac{1}{R_{eq}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ \frac{1}{R_{eq}} &= \frac{1}{1} + \frac{1}{2} + \frac{1}{4} \\ \frac{1}{R_{eq}} &= \frac{4 + 2 + 1}{4} = \frac{7}{4} \\ R_{eq} &= \frac{4}{7} = 0.57\Omega\end{aligned}$$

$$\text{Equivalent Resistance: } R_{eq} = R_{13} + R_4 = 0.57 + 5 = 5.57\Omega$$

$$\text{Total Current : } I = \frac{V}{R_{eq}} = \frac{24}{5.57} = 4.3 \text{ Amps}$$

$$\text{Voltage drop across } R_4 (V_4) = I \times R_4 = 4.3 \times 5 = 21.5 \text{ Volts}$$

$$\text{Voltage drop across } R_1 (V_1) = \text{Supply Voltage (V)} - \text{Voltage drop across } R_4$$

$$\text{Voltage drop across } R_1 (V_1) = 24 - 21.5 = 2.5 \text{ Volts}$$

$$\text{Voltage drop: } V_1 = V_2 = V_3 = 2.5 \text{ Volts}$$

$$\text{Power dissipated in } R_1 = \frac{V^2}{R_1} = \frac{2.5^2}{1} = 1.25 \text{ Watts}$$

$$\text{Power dissipated in } R_2 = \frac{V^2}{R_2} = \frac{2.5^2}{2} = 3.125 \text{ Watts}$$

$$\text{Power dissipated in } R_3 = \frac{V^2}{R_3} = \frac{2.5^2}{4} = 1.5625 \text{ Watts}$$

$$\text{Power dissipated in } R_4 = \frac{V^2}{R_4} = \frac{2.5^2}{5} = 1.25 \text{ Watts}$$

Example: 29

The resistors of 2Ω , 4Ω and 12Ω are connected in parallel across a 24 Volts battery. Find the current through each resistor and the battery. Also find power dissipated in each resistors.

Given Data:

$$\text{Resistance (R}_1\text{)} = 2\Omega$$

$$\text{Resistance (R}_2\text{)} = 4\Omega$$

$$\text{Resistance (R}_3\text{)} = 12\Omega$$

$$\text{Supply Voltage (V)} = 24V$$

To Find:

i) Current through each resistor

ii) Power in each resistor

Solution:

$$\begin{aligned}\text{Current through Resistor R}_1 : I_1 &= \frac{V}{R_1} \\ &= \frac{24}{2} = 12 \text{ Amps}\end{aligned}$$

$$\begin{aligned}\text{Current through Resistor R}_2 : I_2 &= \frac{V}{R_2} \\ &= \frac{24}{4} = 6 \text{ Am}\end{aligned}$$

$$\begin{aligned}\text{Current through Resistor R}_3 : I_3 &= \frac{V}{R_3} \\ &= \frac{24}{12} = 2 \text{ Amps}\end{aligned}$$

$$\text{Power dissipated in } R_1 = \frac{V^2}{R_1} = \frac{24^2}{2} = 288 \text{ Watts}$$

$$\text{Power dissipated in } R_2 = \frac{V^2}{R_2} = \frac{24^2}{4} = 144 \text{ Watts}$$

$$\text{Power dissipated in } R_3 = \frac{V^2}{R_3} = \frac{24^2}{12} = 48 \text{ Watts}$$

Kirchhoff's laws:

Kirchhoff's laws are more comprehensive than ohm's law and are used for solving electrical networks.

The two Kirchhoff's laws are:

1. Kirchhoff's Current Law (KCL)
2. Kirchhoff's Voltage Law (KVL)

Kirchhoff's Current Law (KCL)

It states that “the algebraic sum of the currents in a junction of a circuit is zero.

(or)

The sum of current entering the junction is equal to the sum of the current leaving the junction.

Explanation:

Consider 5 conductors carrying currents. Assume positive sign for the current flowing towards the junction and negative sign for the current flowing away from the junction.

Let P is a junction

$I_1, I_3, \& I_4$ = incoming current towards the junction P


$I_2, \& I_5$ = outgoing current away from the junction P

By applying Kirchhoff's current law at junction P,

$$I_1 - I_2 + I_3 + I_4 - I_5 = 0$$

$$I_1 + I_3 + I_4 = I_2 + I_5$$

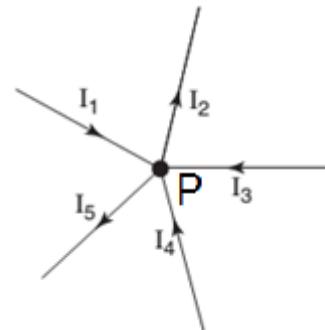Sum of incoming current = sum of outgoing current



Kirchhoff's Voltage Law (KVL):

It states that in any closed electrical circuit, “the algebraic sum of voltage is zero”.

(OR)

That is the sum of voltage rises (EMF) in a closed network is equal to the sum of voltages drops (P.D)

Explanation:

Consider a simple closed electrical circuit,

Let,

E - Supply voltage


R_1, R_2 & R_3 - Resistors in the circuit.

I - Current flow through the circuit

V_1 - p.d across R_1

V_2 - p.d across R_2

V_3 - p.d across R_3

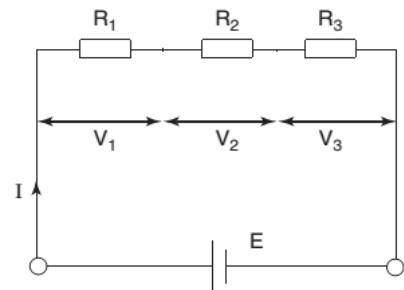

Applying Kirchhoff's voltage law to the closed circuit,

$$E - V_1 - V_2 - V_3 = 0$$

$$E = V_1 + V_2 + V_3 \quad \dots \quad (1)$$


Substitute, $V_1 = I.R_1$, $V_2 = I.R_2$ & $V_3 = I.R_3$ in equation (1)

$$E = IR_1 + IR_2 + IR_3$$


$E - IR_1 - IR_2 - IR_3 = 0$ [Algebraic sum of voltages is zero]

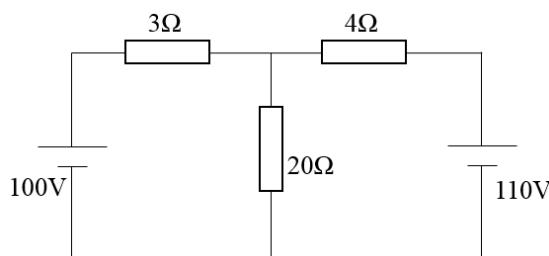Example: 30

Determine the currents in different branches of the circuit shown in figure by applying Kirchhoff's law.



Solution:

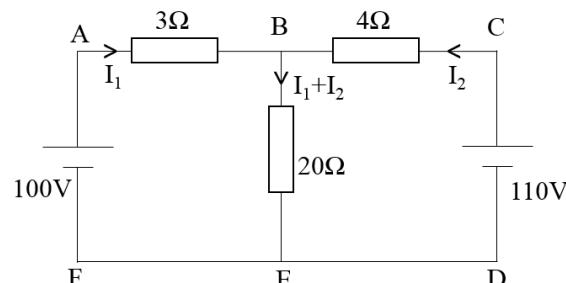

Apply KVL in Loop ABEFA

| Branch | Potential Drop | Potential Rise |
|--------|------------------------|----------------|
| AB | $3I_1$ | - |
| BE | $20(I_1 + I_2)$ | - |
| EF | - | - |
| FA | - | 100 |
| | $3I_1 + 20(I_1 + I_2)$ | 100 |

According to KVL:

$$\begin{aligned}
 \text{Sum of Potential Drop} &= \text{Sum of Potential Rise} \\
 3I_1 + 20(I_1 + I_2) &= 100 \\
 3I_1 + 20I_1 + 20I_2 &= 100 \\
 23I_1 + 20I_2 &= 100 \quad \cdots\cdots\cdots (1)
 \end{aligned}$$

Apply KVL in Loop CBEDC:

| Branch | Potential Drop | Potential Rise |
|--------|------------------------|----------------|
| CB | $4I_2$ | - |
| BE | $20(I_1 + I_2)$ | - |
| ED | - | - |
| DC | - | 110 |
| | $4I_2 + 20(I_1 + I_2)$ | 110 |

According to KVL:

$$\begin{aligned}
 \text{Sum of Potential Drop} &= \text{Sum of Potential Rise} \\
 4I_2 + 20(I_1 + I_2) &= 110 \\
 4I_2 + 20I_1 + 20I_2 &= 110 \\
 20I_1 + 24I_2 &= 110 \quad \cdots\cdots\cdots (2)
 \end{aligned}$$

$$23I_1 + 20I_2 = 100 \quad \cdots\cdots\cdots (1)$$

$$20I_1 + 24I_2 = 110 \quad \cdots\cdots\cdots (2)$$

$$\begin{aligned}
 \begin{vmatrix} 23 & 20 \\ 20 & 24 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} &= \begin{vmatrix} 100 \\ 110 \end{vmatrix} \\
 \Delta &= \begin{vmatrix} 23 & 20 \\ 20 & 24 \end{vmatrix} \\
 \Delta &= (23 \times 24) - (20 \times 20) = 152 \\
 \Delta I_1 &= \begin{vmatrix} 100 & 20 \\ 110 & 24 \end{vmatrix} \\
 &= (100 \times 24) - (20 \times 110) = 200 \\
 I_1 &= \frac{\Delta I_1}{\Delta} = \frac{200}{152} = 1.315 \text{ Amps} \\
 \Delta I_2 &= \begin{vmatrix} 23 & 100 \\ 20 & 110 \end{vmatrix} \\
 &= (23 \times 110) - (100 \times 20) = 530 \\
 I_2 &= \frac{\Delta I_2}{\Delta} = \frac{530}{152} = 3.486 \text{ Amps}
 \end{aligned}$$

Answer:


$$\text{Current through } 3\Omega \text{ resistor : } I_1 = 1.315 \text{ Amps}$$

$$\text{Current through } 4\Omega \text{ resistor : } I_2 = 3.486 \text{ Amps}$$


$$\text{Current through } 20\Omega \text{ resistor : } I_1 + I_2 = 1.315 + 3.486 = 4.801 \text{ Amps}$$

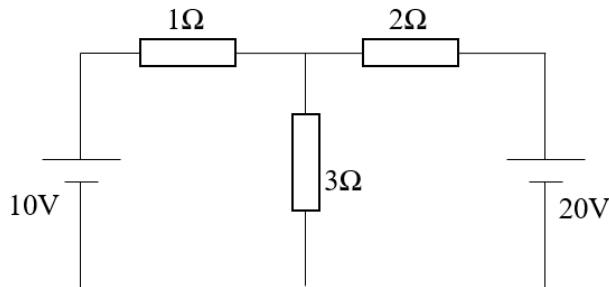Example: 31

Find the current in the 3 ohm resistor in the circuit shown in figure.



Solution:

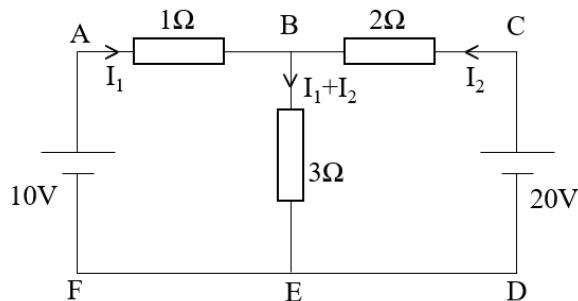

Apply KVL in Loop ABEFA:

| Branch | Potential Drop | Potential Rise |
|--------|-----------------------|----------------|
| AB | $1I_1$ | - |
| BE | $3(I_1 + I_2)$ | - |
| EF | - | - |
| FA | - | 10 |
| | $1I_1 + 3(I_1 + I_2)$ | 10 |

According to KVL:

$$\begin{aligned} \text{Sum of Potential Drop} &= \text{Sum of Potential Rise} \\ 1I_1 + 3(I_1 + I_2) &= 10 \\ 1I_1 + 3I_1 + 3I_2 &= 10 \\ 4I_1 + 3I_2 &= 10 \quad \text{----- (1)} \end{aligned}$$

Apply KVL in Loop CBEDC:

| Branch | Potential Drop | Potential Rise |
|--------|-----------------------|----------------|
| CB | $2I_2$ | - |
| BE | $3(I_1 + I_2)$ | - |
| ED | - | - |
| DC | - | 20 |
| | $2I_2 + 3(I_1 + I_2)$ | 20 |

According to KVL:

$$\begin{aligned} \text{Sum of Potential Drop} &= \text{Sum of Potential Rise} \\ 2I_2 + 3(I_1 + I_2) &= 20 \\ 2I_2 + 3I_1 + 3I_2 &= 20 \end{aligned}$$

$$3I_1 + 5I_2 = 20 \quad \dots \dots \dots (2)$$

$$4I_1 + 3I_2 = 10 \quad \dots \dots \dots (1)$$

$$3I_1 + 5I_2 = 20 \quad \dots \dots \dots (2)$$

$$\begin{vmatrix} 4 & 3 \\ 3 & 5 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 10 \\ 20 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 4 & 3 \\ 3 & 5 \end{vmatrix}$$

$$\Delta = (4 \times 5) - (3 \times 3) = 11$$

$$\Delta I_1 = \begin{vmatrix} 10 & 3 \\ 20 & 5 \end{vmatrix}$$

$$= (10 \times 5) - (20 \times 3) = -10$$

$$I_1 = \frac{\Delta I_1}{\Delta} = \frac{-10}{11} = -0.909 \text{ Amps}$$

$$\Delta I_2 = \begin{vmatrix} 4 & 10 \\ 3 & 20 \end{vmatrix}$$

$$= (4 \times 20) - (3 \times 10) = 50$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{50}{11} = 4.54 \text{ Amps}$$

Answer:

Current through 1Ω resistor : $I_1 = -0.909$ Amps


Current through 2Ω resistor : $I_2 = 4.54$ Amps

Current through 30Ω resistor : $I_1 + I_2 = -0.909 + 4.54 = 3.631$ Amps

Example: 32

A wheat stone bridge ABCD is arranged as follows $AB=1\Omega$, $BC=2\Omega$, $CD=3\Omega$, $DA=4\Omega$. A galvanometer of resistance 5Ω is connected between B and D. A battery of 4 volt with internal resistance 1Ω is connected between A and C. Calculate current flow through 5Ω .

Solution:

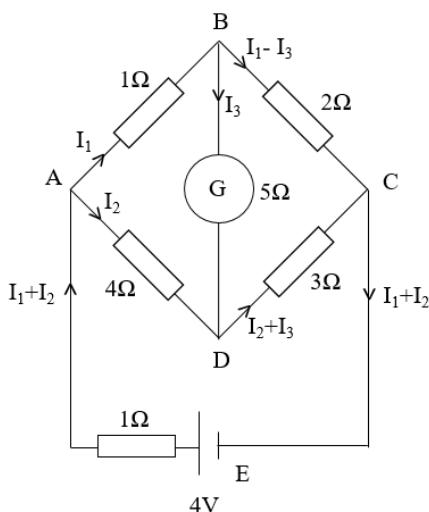

Apply KVL in Loop ABDA:

| Branch | Potential Drop | Potential Rise |
|--------|----------------|----------------|
| AB | $1I_1$ | - |
| BD | $5I_3$ | - |
| DA | - | $4I_2$ |
| | $1I_1 + 5I_3$ | $4I_2$ |

According to KVL:

$$\begin{aligned}
 \text{Sum of Potential Drop} &= \text{Sum of Potential Rise} \\
 1I_1 + 5I_3 &= 4I_2 \\
 1I_1 + 5I_3 - 4I_2 &= 0 \\
 1I_1 - 4I_2 + 5I_3 &= 0 \quad \text{----- (1)}
 \end{aligned}$$

Apply KVL in Loop BCDB:

| Branch | Potential Drop | Potential Rise |
|--------|----------------|-----------------------|
| BC | $2(I_1 - I_3)$ | - |
| CD | - | $3(I_2 + I_3)$ |
| DB | - | $5I_3$ |
| | $2(I_1 - I_3)$ | $3(I_2 + I_3) + 5I_3$ |

According to KVL:

$$\begin{aligned}
 \text{Sum of Potential Drop} &= \text{Sum of Potential Rise} \\
 2(I_1 - I_3) &= 3(I_2 + I_3) + 5I_3 \\
 2(I_1 - I_3) - 3(I_2 + I_3) - 5I_3 &= 0 \\
 2(I_1 - I_3) - 3(I_2 + I_3) - 5I_3 &= 0 \\
 2I_1 - 2I_3 - 3I_2 - 3I_3 - 5I_3 &= 0 \\
 2I_1 - 3I_2 - 10I_3 &= 0 \quad \text{----- (2)}
 \end{aligned}$$

Apply KVL in Loop ADCA:

| Branch | Potential Drop | Potential Rise |
|--------|--------------------------------------|----------------|
| AD | $4I_2$ | - |
| DC | $3(I_2 + I_3)$ | - |
| CA | $1(I_1 + I_2)$ | 4 |
| | $4I_2 + 3(I_2 + I_3) + 1(I_1 + I_2)$ | 4 |

According to KVL:

$$\begin{aligned}
 \text{Sum of Potential Drop} &= \text{Sum of Potential Rise} \\
 4I_2 + 3(I_2 + I_3) + 1(I_1 + I_2) &= 0 \\
 4I_2 + 3I_2 + 3I_3 + 1I_1 + 1I_2 &= 0 \\
 1I_1 + 8I_2 + 3I_3 &= 4 \quad \text{----- (3)}
 \end{aligned}$$

$$\begin{aligned} I_1 - 4I_2 + 5I_3 &= 0 & \dots (1) \\ 2I_1 - 3I_2 - 10I_3 &= 0 & \dots (2) \\ I_1 + 8I_2 + 3I_3 &= 4 & \dots (3) \end{aligned}$$

$$\left| \begin{array}{ccc} 1 & -4 & 5 \\ 2 & -3 & -10 \\ 1 & 8 & 3 \end{array} \right| \left| \begin{array}{c} I_1 \\ I_2 \\ I_3 \end{array} \right| = \left| \begin{array}{c} 0 \\ 0 \\ 4 \end{array} \right|$$

$$\Delta = \left| \begin{array}{ccc} 1 & -4 & 5 \\ 2 & -3 & -10 \\ 1 & 8 & 3 \end{array} \right|$$

$$\Delta = 1[(-3 \times 3) - (-10 \times 8)] - (-4)[(2 \times 3) - (-10 \times 1)] + 5[(2 \times 8) - (-3)]$$

$$\Delta = 1[(-9) - (-80)] - (-4)[(6) - (-10)] + 5[(16) - (-3)]$$

$$\Delta = 1[-9 + 80] + 4[6 + 10] + 5[16 + 3]$$

$$\Delta = 1[71] + 4[16] + 5[19]$$

$$\Delta = 71 + 64 + 95$$

$$\Delta = 230$$

$$\Delta I_3 = \left| \begin{array}{ccc} 1 & -4 & 0 \\ 2 & -3 & 0 \\ 1 & 8 & 4 \end{array} \right|$$

$$\Delta I_3 = 1[(-3 \times 4) - (0 \times 8)] - (-4)[(2 \times 4) - (0 \times 1)] + 0$$

$$\Delta I_3 = 1[-12 - 0] + 4[8 - 0] + 0$$

$$\Delta I_3 = 1[-12] + 4[8]$$

$$\Delta I_3 = -12 + 32$$

$$\Delta I_3 = 20$$

$$I_3 = \frac{\Delta I_3}{\Delta} = \frac{20}{230}$$

$$I_3 = 0.087 \text{ Amps}$$


Answer:

Current through 5Ω resistor : $I_3 = 0.087$ Amps

Example: 33

A wheat stone bridge consists of $AB=10\Omega$, $BC=10\Omega$, $CD=4\Omega$, $DA=5\Omega$. A galvanometer of resistance 20Ω is connected across BD . Calculate the current through the galvanometer when a p.d of $10V$ is maintained across AC .

Solution:

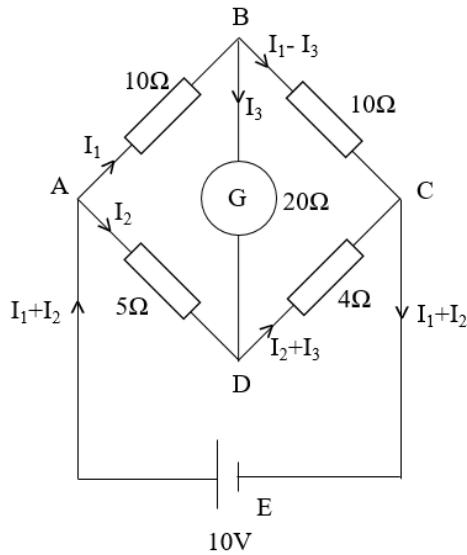

Apply KVL in Loop ABDA

| Branch | Potential Drop | Potential Rise |
|--------|-----------------|----------------|
| AB | $10I_1$ | - |
| BD | $20I_3$ | - |
| DA | - | $5I_2$ |
| | $10I_1 + 20I_3$ | $5I_2$ |

According to KVL:

$$\text{Sum of Potential Drop} = \text{Sum of Potential Rise}$$

$$10I_1 + 20I_3 = 5I_2$$

$$10I_1 + 20I_3 - 5I_2 = 0$$

$$10I_1 - 5I_2 + 20I_3 = 0 \quad \text{----- (1)}$$

Apply KVL in Loop BCDB

| Branch | Potential Drop | Potential Rise |
|--------|-----------------|------------------------|
| BC | $10(I_1 - I_3)$ | - |
| CD | - | $4(I_2 + I_3)$ |
| DB | - | $20I_3$ |
| | $10(I_1 - I_3)$ | $4(I_2 + I_3) + 20I_3$ |

According to KVL:

$$\text{Sum of Potential Drop} = \text{Sum of Potential Rise}$$

$$10(I_1 - I_3) = 4(I_2 + I_3) + 20I_3$$

$$10(I_1 - I_3) - 4(I_2 + I_3) - 20I_3 = 0$$

$$10I_1 - 10I_3 - 4I_2 - 4I_3 - 20I_3 = 0$$

$$10I_1 - 4I_2 - 34I_3 = 0$$

$$10I_1 - 4I_2 - 34I_3 = 0 \quad \text{----- (2)}$$

Apply KVL in Loop ADCA:

| Branch | Potential Drop | Potential Rise |
|--------|-----------------------|----------------|
| AD | $5I_2$ | - |
| DC | $4(I_2 + I_3)$ | - |
| CA | - | 10 |
| | $5I_2 + 4(I_2 + I_3)$ | 10 |

According to KVL:

$$\text{Sum of Potential Drop} = \text{Sum of Potential Rise}$$

$$5I_2 + 4(I_2 + I_3) = 10$$

$$5I_2 + 4I_2 + 4I_3 = 10$$

$$9I_2 + 4I_3 = 10 \quad \dots \dots \dots (3)$$

$$10I_1 - 5I_2 + 20I_3 = 0 \quad \dots \dots \dots (1)$$

$$10I_1 - 4I_2 - 34I_3 = 0 \quad \dots \dots \dots (2)$$

$$9I_2 + 4I_3 = 10 \quad \dots \dots \dots (3)$$

$$\begin{vmatrix} 10 & -5 & 20 \\ 10 & -4 & -34 \\ 0 & 9 & 4 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 0 \\ 0 \\ 10 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 10 & -5 & 20 \\ 10 & -4 & -34 \\ 0 & 9 & 4 \end{vmatrix}$$

$$\Delta = 10[(-4 \times 4) - (-34 \times 9)] - (-5)[(10 \times 4) - (-34 \times 0)] + 20[(10 \times 9) - (0)]$$

$$\Delta = 10[(-16) - (-306)] + 5[40 - 0] + 20[90 - 0]$$

$$\Delta = 10[-16 + 306] + 5[40] + 20[90]$$

$$\Delta = 10[290] + 5[40] + 20[90]$$

$$\Delta = 2900 + 200 + 1800$$

$$\Delta = 4900$$

$$\Delta I_3 = \begin{vmatrix} 10 & -5 & 0 \\ 10 & -4 & 0 \\ 0 & 9 & 10 \end{vmatrix}$$

$$\Delta I_3 = 10[(-4 \times 10) - (0 \times 9)] - (-5)[(10 \times 10) - (0 \times 0)] + 0$$

$$\Delta I_3 = 10[-40 - 0] + 5[100 - 0] + 0$$

$$\Delta I_3 = 10[-40] + 5[100] = -400 + 500$$

$$\Delta I_3 = 100$$

$$I_3 = \frac{\Delta I_3}{\Delta} = \frac{100}{4900}$$

$$I_3 = 0.0204 \text{ Amps}$$


Answer:

Current through 20Ω resistor : $I_3 = 0.0204 \text{ Amps}$

Example: 34

A wheat stone bridge consist of AB=10Ω, BC=30Ω, CD=15Ω, DA=20Ω. A galvanometer of resistance 40Ω is connected across BD. Calculate the current through the galvanometer when a p.d of 2V is maintained across A.C.

Solution:

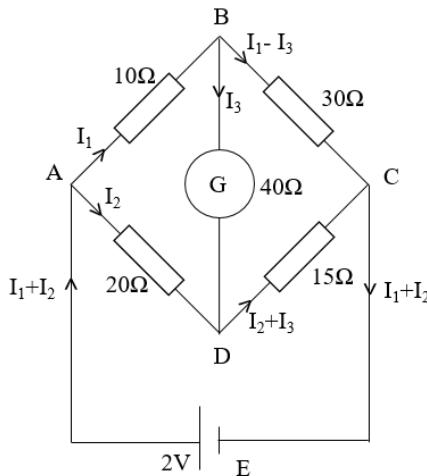

Apply KVL in Loop ABDA

| Branch | Potential Drop | Potential Rise |
|--------|-----------------|----------------|
| AB | $10I_1$ | - |
| BD | $40I_3$ | - |
| DA | - | $20I_2$ |
| | $10I_1 + 40I_3$ | $20I_2$ |

According to KVL:

$$\text{Sum of Potential Drop} = \text{Sum of Potential Rise}$$

$$10I_1 + 40I_3 = 20I_2$$

$$10I_1 + 40I_3 - 20I_2 = 0$$

$$10I_1 - 20I_2 + 40I_3 = 0 \quad \dots\dots\dots (1)$$

Apply KVL in Loop BCDB:

| Branch | Potential Drop | Potential Rise |
|--------|-----------------|-------------------------|
| BC | $30(I_1 - I_3)$ | - |
| CD | - | $15(I_2 + I_3)$ |
| DB | - | $40I_3$ |
| | $30(I_1 - I_3)$ | $15(I_2 + I_3) + 40I_3$ |

According to KVL:

$$\text{Sum of Potential Drop} = \text{Sum of Potential Rise}$$

$$30(I_1 - I_3) = 15(I_2 + I_3) + 40I_3$$

$$30(I_1 - I_3) - 15(I_2 + I_3) - 40I_3 = 0$$

$$30I_1 - 30I_3 - 15I_2 - 15I_3 - 40I_3 = 0$$

$$30I_1 - 15I_2 - 85I_3 = 0 \quad \dots\dots\dots (2)$$

Apply KVL in Loop ADCA:

| Branch | Potential Drop | Potential Rise |
|--------|-------------------------|----------------|
| AD | $20I_2$ | - |
| DC | $15(I_2 + I_3)$ | - |
| CA | - | 2 |
| | $20I_2 + 15(I_2 + I_3)$ | 2 |

According to KVL:

$$\text{Sum of Potential Drop} = \text{Sum of Potential Rise}$$

$$20I_2 + 15(I_2 + I_3) = 2$$

$$20I_2 + 15I_2 + 15I_3 = 2$$

$$35I_2 + 15I_3 = 2 \quad \dots \dots \dots (3)$$

$$10I_1 - 20I_2 + 40I_3 = 0 \quad \dots \dots \dots (1)$$

$$30I_1 - 15I_2 - 85I_3 = 0 \quad \dots \dots \dots (2)$$

$$35I_2 + 15I_3 = 2 \quad \dots \dots \dots (3)$$

$$\begin{vmatrix} 10 & -20 & 40 \\ 30 & -15 & -85 \\ 0 & 35 & 15 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 0 \\ 0 \\ 2 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 10 & -20 & 40 \\ 30 & -15 & -85 \\ 0 & 35 & 15 \end{vmatrix}$$

$$\Delta = 10[(-15 \times 15) - (-85 \times 35)] - (-20)[(30 \times 15) - (0)] + 40[(30 \times 35) - (0)]$$

$$\Delta = 10[-225 + 2975] - (-20)[450 - 0] + 40[1050 - 0]$$

$$\Delta = 10[2750] + 20[450] + 40[1050]$$

$$\Delta = 27500 + 9000 + 42000$$

$$\Delta = 78500$$

$$\Delta I_3 = \begin{vmatrix} 10 & -20 & 0 \\ 30 & -15 & 0 \\ 0 & 35 & 2 \end{vmatrix}$$

$$\Delta I_3 = 10[(-15 \times 2) - (0 \times 35)] - (-20)[(30 \times 2) - (0 \times 0)] + 0$$

$$\Delta I_3 = 10[-30 - 0] + 20[60 - 0] + 0$$

$$\Delta I_3 = 10[-30] + 20[60]$$

$$\Delta I_3 = 900$$

$$I_3 = \frac{\Delta I_3}{\Delta} = \frac{900}{78500}$$

$$I_3 = 0.0114 \text{ Amps}$$

Answer:

Current through 40Ω resistor : $I_3 = 0.0114 \text{ Amps}$

REVIEW QUESTIONS
UNIT : I ELECTROSTATICS & D.C CIRCUITS

PART - A : 2 Mark Questions.

1. Define Electric flux.
2. Define flux density.
3. Define electric field intensity.
4. Define electric potential.
5. Define a capacitance.
6. Write the expression for energy stored in a capacitor.
7. State expression for the equivalent capacitance of two capacitors in series.
8. State expression for the equivalent capacitance of two capacitors in parallel.
9. If a $2\mu F$ capacitor and $4 \mu F$ capacitor are connected in parallel. What is its equivalent capacitance?
10. Define permittivity?
11. Define relative permittivity?
12. State the relation between electric flux density and field intensity?
13. Define electric current.
14. Define electromotive force.
15. Define potential difference.
16. Define Resistance.
17. Define electric power.
18. Define electrical energy.
19. State the unit of electric current and Resistance.
20. State the unit of electrical power and Electrical Energy.
21. Define Specific resistance or resistivity.
22. State ohm's law.
23. Define temperature coefficient of resistance.
24. State Kirchhoff's Current Law.
25. State Kirchhoff's Voltage Law.


PART – B : 3 Mark Questions

1. Define: (i) Electric Flux (ii) Electric Flux Density
2. Define: (i) Electric field Intensity (ii) Electric Potential
3. State Coulomb's law of electrostatics.
4. Define Capacitance and state its fundamental practical unit.
5. Derive an expression for energy stored in a capacitor.
6. Derive an equation for the equivalent capacitance of two capacitors connected in series.
7. Derive an equation for the equivalent capacitance of two capacitors connected in parallel.


8. Define: (i) Current (ii) E.M.F (iii) Resistance
9. Define power. What is the relationship between power, voltage and current?
10. Define resistance and conductance.
11. Define resistivity or specific resistance and state its unit.
12. What are the factors on which resistance of a material depend?
13. Define temperature co-efficient of resistance. Give its unit of measurements.
14. State ohm's law and write its expression in 3 different forms
15. Prove that Power $P = V \cdot I$ Watts.
16. Define Electric power and energy. Mention the unit of measurement
17. State Kirchhoff's laws.
18. A $100\mu F$ capacitance is charged to a steady voltage of 500V. What is the energy stored in the capacitance?
19. Two resistors are connected in series and connected across a battery. The p.d across first resistor is 10V and p.d across second resistor is 25V. The current through the resistors is 2 Amps. Find the value of each resistor.
20. A battery of 20V is connected across a resistor so that the current is limited to 0.2Amps. Calculate the value of resistance and its power rating.
21. A resistor has a resistance of 150Ω at $20^\circ C$ and 166Ω at $55^\circ C$. Find the temperature coefficient of the resistance at $0^\circ C$.
22. Find the resistances in ohm of incandescent lamps of (a) 100W at 120V and (b) 60W at 12V.

PART – C : 10 Mark Questions

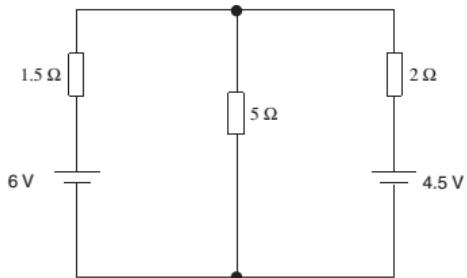1. Define the following terms and state their units :
 - (i) Electric flux (ii) Electric flux density (iii) Field intensity (iv) Electric Potential
2. Show that $R_t = R_0 + (1+\alpha_0 t)$
3. State and explain coulomb's laws of electrostatics.
4. Derive equivalent capacitance of 3 capacitors in series.
5. Derive equivalent capacitance of 3 capacitors in parallel.
6. Define the following terms and state their units :
 - (i) Electric Current (ii) E.M.F (iii) Resistance (iv) Electrical Power
7. Derive equivalent resistance of 3 resistors in series.
8. Derive equivalent resistance of 3 resistors in parallel.
9. State and explain kirchhoff's Laws.
10. For the given circuit, use Kirchhoff ' s Laws to calculate (a) the current flowing in each branch of the circuit, and (b) the p.d. across the 5Ω resistor.



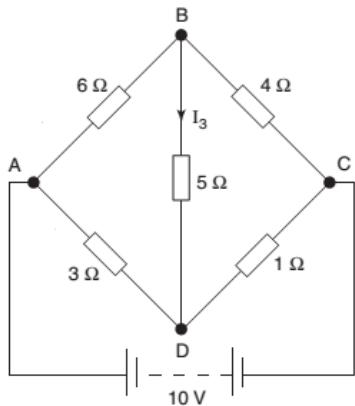11. For the given bridge, calculate the current through $5\ \Omega$ resistor, and the current drawn from the supply.



12. Capacitors of $3\ \mu F$, $6\ \mu F$ and $12\ \mu F$ are connected in series across a $400\ V$ supply. Determine the p.d. across each capacitor.
13. Three resistors of resistance 10Ω , 15Ω and 20Ω are connected once in series and then parallel. Find the equivalent resistance for each case. Also calculate the power dissipated in each case, if the supply voltage is $15V$.
14. Two incandescent lamps of $100W$ and $60W$ and rated voltage of $110V$ are supplied by a source of $110V$ d.c. Determine the current drawn from the source (a) when the lamps are connected in parallel, (b) when the lamps are connected in series.

UNIT 2 - CIRCUIT THEOREMS

Syllabus:

Mesh equations – Nodal equations – star/delta transformations – Superposition theorem – Thevenin’s theorem – Norton’s theorem – Maximum power transfer theorem. (Problems in DC circuits only).

2.0 Introductions:

In unit 1, we analysed the various types of circuits using ohm's law and Kirchhoff's laws. Some circuits are difficult to solve using only basics laws and require additional methods in order to simplify the analysis. In this unit, we shall understand a variety of techniques such as Mesh Current Analysis, Nodal analysis, the Superposition theorem, Thévenin's theorem and Norton's theorem, which will speed up the analysis of the more complicated networks.

The theorems and conversions make analysis easier for certain types of circuit. These methods do not replace Ohm's law and Kirchhoff's laws, but they are normally used in conjunction with laws in certain situation.

Electric circuit theorems are always beneficial to find voltage and currents in multi loop circuits. These theorems use fundamental rules or formulae and basic equations of mathematics to analyze basic components of electrical or electronics parameters such as voltages, currents, resistance, and so on. These fundamental theorems include the basic theorems like Superposition theorem, Thevenin's theorems, Norton's theorem and Maximum power transfer theorem.

Not all loads are connected in series or in parallel. There are two other arrangements known as star and delta. They are not so common but, because they are interchangeable, we can readily find a solution to any network in which they appear – so long as we can transform the one into the other.

Because all electric circuits are driven by either voltage sources or current sources, it is important to understand how to work with these elements. Source conversion technique also useful to get the solution easily. The superposition theorem will help you to deal with circuits that have multiple sources. Super position theorem is used only in linear networks. This theorem is used in both AC and DC circuits wherein it helps to construct Thevenin and Norton equivalent circuit

Thevenin's and Norton's theorems provide methods for reducing a circuit to a simple equivalent form for ease of analysis. This theorem can be applied to both linear and bilateral networks. The maximum power transfer theorem is used in applications where it is important for a given circuit to provide maximum power to a load.

2.1 Terms and Definition:

| Sl.No | Term | Definition |
|-------|-------------------------------|---|
| 1 | Network Element | Any individual element which can be connected to some other element is called network element. |
| 2 | Active Element | These are elements which can deliver electrical energy. <i>Example: Voltage source and Current source</i> |
| 3 | Passive Element | These are elements which consumes electrical energy either by absorbing or storing in it. <i>Example: R, L and C</i> |
| 4 | Electric Network | Interconnection of elements like resistor or inductor or capacitor or electrical energy sources are known as networks. |
| 5 | Electric circuit | A closed energized network is known as circuit. |
| 6 | Node or Junction in a network | A point at which two or more elements are joined together is called node. |
| 7 | Simple Node | A node where only two elements are joined is called simple node. |
| 8 | Principal Node | A node where three or more elements are joined is called Principal Node. |
| 9 | Branch of a network | A branch is a path that connects two nodes. |
| 10 | Loop in a network | A closed path obtained by starting at a node and returning back to the same node through a set of connected circuit elements. |
| 11 | Mesh in a circuit | A loop that does not contain any other loops within it. |

2.2 Active Network Vs Passive Network:

| Sl.No | Active network | Passive network |
|-------|---|--|
| 1 | A network which contains a source of energy is called active network. | A network which contains no energy source of energy is called passive network. |
| 2 | Example: Voltage source and current source | Example: It contains R, L and C |

2.3 Unilateral Circuit Vs Bilateral Circuit:

| Unilateral circuit | Bilateral circuit |
|---|---|
| It is that circuit whose properties or characteristics change with the direction of its operation. A diode rectifier is a unilateral circuit, because it cannot perform rectification in both directions. | A bilateral circuit is one whose properties or characteristics are the same in either direction. The usual transmission line is bilateral, because it can be made to perform its function equally well in either direction. |

2.4 Linear Circuit Vs Non-Linear Circuit:

| Sl.No | Linear circuit | Non-Linear circuit |
|-------|---|--|
| 1 | A circuit or network whose parameters i.e., elements like resistances, inductances and capacitances are always constant irrespective of the change in time, voltage, temperature etc. is known as linear network. | A circuit whose parameters change their values with change in time, temperature, voltage etc. is known as nonlinear network. |
| 2 | The ohm's law can be applied to such network. Such network follow the law of superposition. | The ohm's law may not be applied to such network. Such network does not follow the law of superposition. |

2.5 Ideal voltage source:

A voltage source which maintains a constant potential difference at a given magnitude and a prescribed waveform across its terminals independent of the current supplied by it.

2.5.1 Characteristics of Ideal voltage source:

- i) It is the energy source whose output voltage remains constant whatever be the value of the output current.
- ii) It has zero internal resistance so that voltage drop in the source is zero.

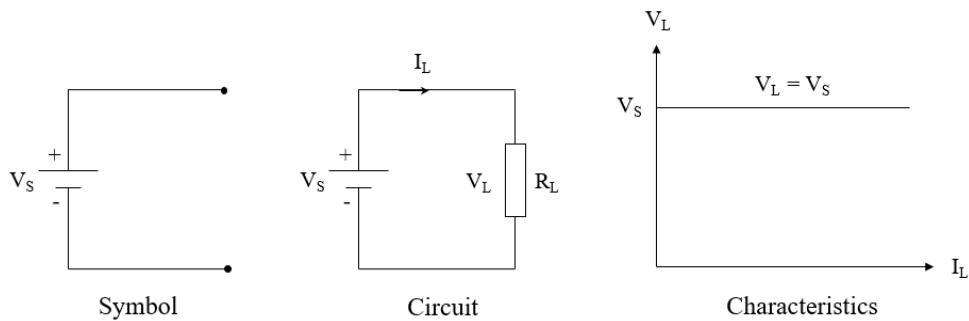


Figure 2.1: Ideal Voltage Source

2.5.2 Characteristics of Practical voltage source:

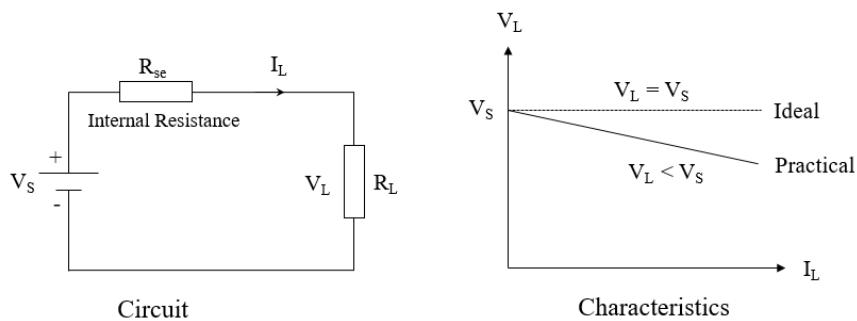


Figure 2.2: Practical Voltage Source

Practically, every voltage source has small internal resistance in series with voltage source and is represented by R_{se} as shown in figure 2.2. In this source, the voltage does not remain constant, but falls slightly with addition of load.

2.6 Ideal Current source:

A current source is one which maintains a current of a given magnitude and a prescribed waveform across its terminals independent of the potential difference appearing across its terminals. Symbolically, we represent a general current source as a two terminal device as shown in figure.

2.6.1 Characteristics of Ideal current source:

- i) It produces a constant current irrespective of the value of the voltage across it.
- ii) It has infinity resistance.
- iii) It is capable of supplying infinity power.

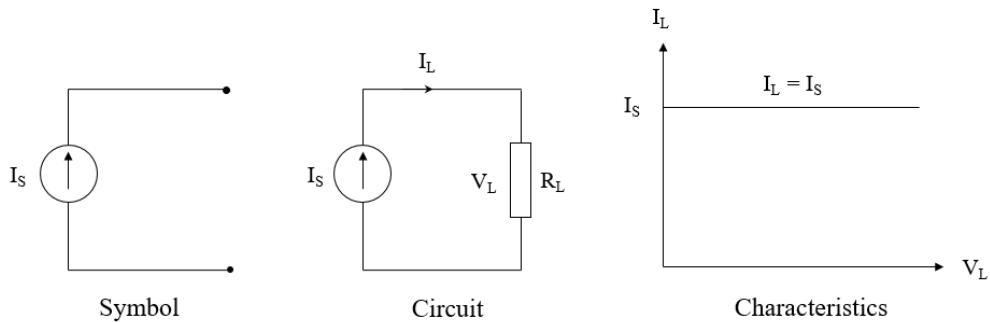


Figure 2.3: Ideal Current Source

2.6.2 Characteristics of Practical current source:

Practically, every current source has high internal resistance in parallel with current source and it is represented by R_{sh} . This is shown in figure 2.4. In practical current source, the current does not remain constant, but falls slightly.

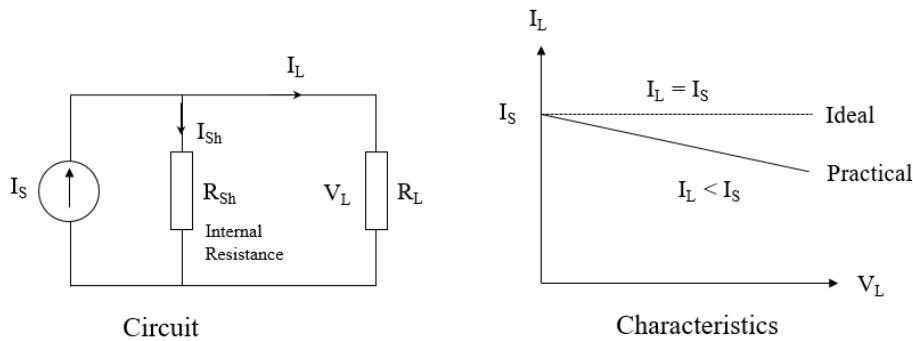


Figure 2.4: Practical Current Source

2.6.3 Loading of sources:


The output voltage of a voltage source decreases as the load current increases. If the source is loaded in such a way that the output voltage falls below a specified full load value, then the source is said to be loaded and the situation is known as loading of source.

2.7 Source Transformation:

Transformation of several voltage (or current) sources into a single voltage (or current) source and a voltage source into a current source or vice-versa is known as source transformation. This makes circuit analysis easier.

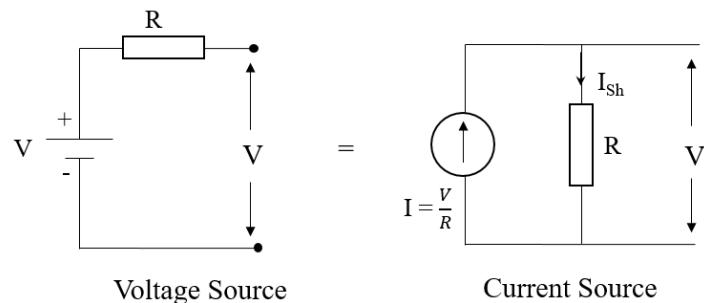
2.7.1 Ideal voltage sources be converted into ideal current sources:

A voltage source V with an internal resistance R can be converted into a current source I in parallel with the same resistance R where, $I = V/R$.



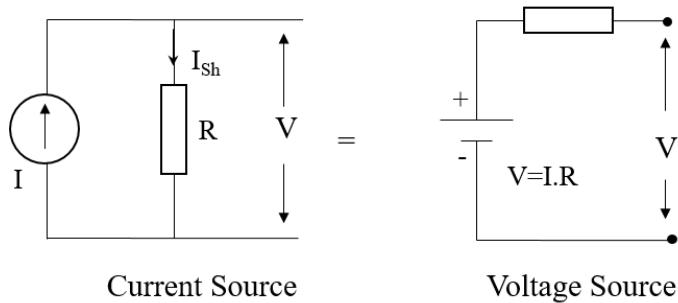2.7.2 Ideal current sources be converted into ideal voltage sources:


A current source I with an internal resistance R can be converted into a voltage source V in series with the same resistance R where, $V = I.R$.



Example: 1

Convert the given voltage source into an equivalent current source.

Given:

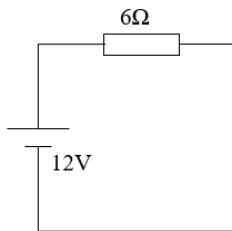


Solution:

$$V = 12V$$

$$R = 6\Omega$$
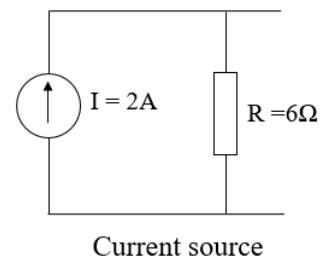
$$I = \frac{V}{R} = \frac{12}{6} = 2 \text{ Amps}$$




2.8 Mech Equation:

This method is also called as mesh current analysis. In this method, we consider loop or mesh current instead of branch current. For each loop, an equation is written based on Kirchhoff's Voltage Law KVL and there are many equations as the number of loops. The current directions are chosen arbitrarily.

Procedure:

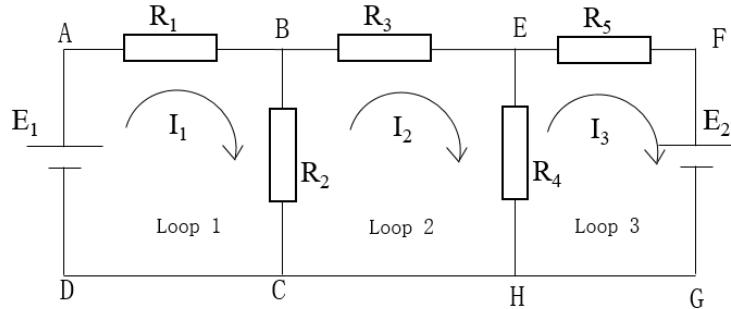- i) Circulating currents are allocated to closed loops or meshes in the circuit.
- ii) An equation for each loop of the circuit is then obtained by Kirchhoff's voltage law.
- iii) Branch currents are found thereafter by taking the algebraic sum of the loop currents common to individual branches.



By applying KVL in Loop 1 (ABCD):

$$\begin{aligned}
 \text{Potential Rise} &= \text{Potential Drop} \\
 E_1 &= I_1 R_1 + (I_1 - I_2) R_2 \\
 E_1 &= I_1 R_1 + I_1 R_2 - I_2 R_2 \\
 E_1 &= I_1 (R_1 + R_2) - I_2 R_2 \\
 I_1 (R_1 + R_2) - I_2 R_2 &= 0 \quad \text{----- (1)}
 \end{aligned}$$

By applying KVL in Loop 2 (BEHC):

$$\begin{aligned}
 \text{Potential Rise} &= \text{Potential Drop} \\
 0 &= I_2 R_3 + (I_2 - I_3) R_4 + (I_2 - I_1) R_2 \\
 0 &= I_2 R_3 + I_2 R_4 - I_3 R_4 + I_2 R_2 - I_1 R_2 \\
 0 &= -I_1 R_2 + I_2 (R_2 + R_3 + R_4) - I_3 R_4 \\
 -I_1 R_2 + I_2 (R_2 + R_3 + R_4) - I_3 R_4 &= 0 \quad \text{----- (2)}
 \end{aligned}$$

By applying KVL in Loop 3 (EFGH):

$$\begin{aligned}
 \text{Potential Rise} &= \text{Potential Drop} \\
 -E_2 &= I_3 R_5 + (I_3 - I_2) R_4 \\
 -E_2 &= I_3 R_5 + I_3 R_4 - I_2 R_4 \\
 -E_2 &= -I_2 R_4 + I_3 (R_4 + R_5) \\
 -I_2 R_4 + I_3 (R_4 + R_5) &= -E_2 \quad \text{----- (3)}
 \end{aligned}$$

The equation (1), (2) and (3) can be arranged in matrix form:

$$[R] [I] = [V]$$

$$\begin{vmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ 0 & -R_4 & R_4 + R_5 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} E_1 \\ 0 \\ -E_2 \end{vmatrix}$$

The resistance matrix and its formation is shown below:

$$[R] = \begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix}$$

Where,

R_{11} = Self-Resistance of Loop 1

R_{22} = Self-Resistance of Loop 2

R_{33} = Self-Resistance of Loop 3


$R_{12} = R_{21}$ = Common Resistance between Loop 1 & 2

$R_{13} = R_{31}$ = Common Resistance between Loop 1 & 3

$R_{23} = R_{32}$ = Common Resistance between Loop 2 & 3

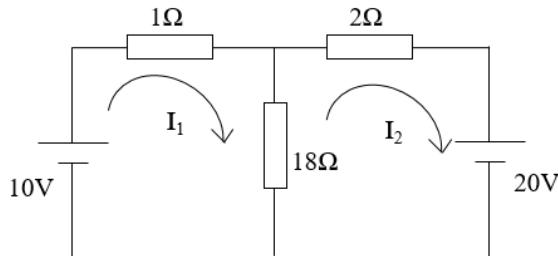Example: 2

Find the current through 18Ω resistor in the given circuit using mesh current analysis.



Given Data:

Number of loops = 2

To Find:

Current through 18Ω Resistor = ?

Solution:

By inspection Method:

$$\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix} \begin{vmatrix} I_1 \\ -I_2 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \end{vmatrix}$$

$$\begin{vmatrix} 1 + 18 & -18 \\ -18 & 2 + 18 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 10 \\ -20 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 19 & -18 \\ -18 & 20 \end{vmatrix} = 56$$

$$\Delta I_1 = \begin{vmatrix} 10 & -18 \\ -20 & 20 \end{vmatrix} = -160$$

$$I_1 = \frac{\Delta I_1}{\Delta} = \frac{-160}{56} = -2.86 \text{ Amps}$$

$$\Delta I_2 = \begin{vmatrix} 19 & 10 \\ -18 & -20 \end{vmatrix} = -200$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{-200}{56} = -3.57 \text{ Amps}$$


$$\text{Current through } 18\Omega \text{ Resistor} = I_1 - I_2 = -2.86 - (-3.57) = 0.71 \text{ Amps}$$

Answer:

$$\text{Current through } 18\Omega \text{ Resistor} = 0.71 \text{ Amps}$$

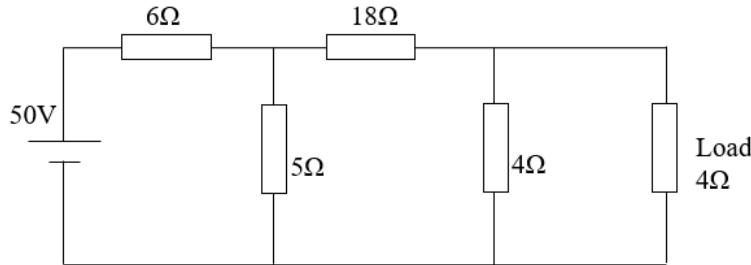Example: 3

Find the current through 4Ω load resistor using mesh current analysis.




Given Data:

$$\text{Number of loops} = 3$$

To Find:

i) Current through 4Ω Resistance =?

Solution:

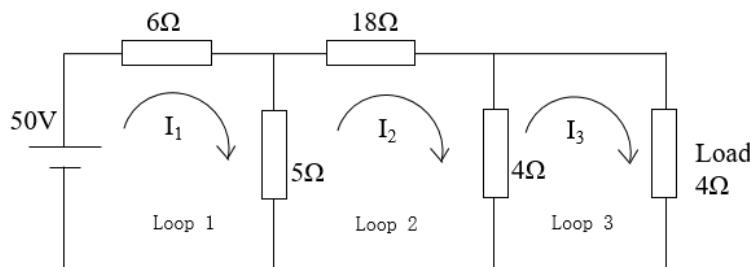

By inspection Method:

$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \\ V_3 \end{vmatrix}$$

Where, $R_{11} = 6 + 5 = 11\Omega$
 $R_{22} = 5 + 18 + 4 = 27\Omega$
 $R_{33} = 4 + 4 = 8\Omega$

$$\begin{vmatrix} 11 & -5 & 0 \\ -5 & 27 & -4 \\ 0 & -4 & 8 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 50 \\ 0 \\ 0 \end{vmatrix}$$

$R_{12} = R_{21} = 5\Omega$
 $R_{23} = R_{32} = 4\Omega$
 $R_{13} = R_{31} = 0$

$$\Delta = \begin{vmatrix} 11 & -5 & 0 \\ -5 & 27 & -4 \\ 0 & -4 & 8 \end{vmatrix}$$

$$\Delta = 11[27 \times 8 - (-4 \times -4)] - (-5)[(-5 \times 8) - (0 \times -4)] + 0$$

$$\Delta = 11[216 - 16] + 5[-40] + 0 = 11[200] - 200$$

$$\Delta = 2000$$

$$\Delta I_3 = \begin{vmatrix} 11 & -5 & 50 \\ -5 & 27 & 0 \\ 0 & -4 & 0 \end{vmatrix}$$

$$\Delta I_3 = 11[27 \times 0 - (0)] - (-5)[0 - 0] + 50[(-5 \times -4) - (0 \times 27)]$$

$$\Delta I_3 = 50[(-5 \times -4) - (0 \times 27)] = 50[20]$$

$$\Delta I_3 = 1000$$

$$I_3 = \frac{\Delta I_3}{\Delta} = \frac{1000}{2000} = 0.5 \text{ Amps}$$


$$I_3 = 0.5 \text{ Amps}$$

Answer:


$$\text{Current through } 4\Omega \text{ Resistor} = 0.5 \text{ Amps}$$

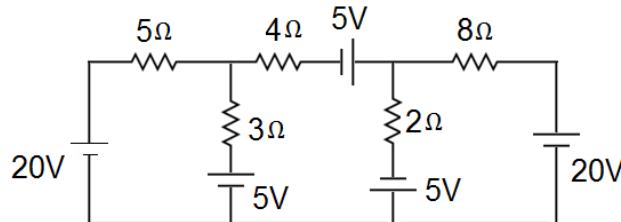Example: 4

By mesh current method determine the current through 5Ω , 4Ω and 8Ω Resistor.



Solution:

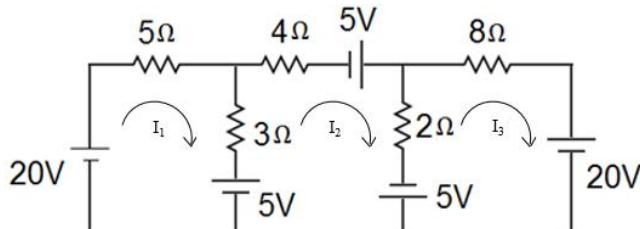

By inspection Method:

$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \\ V_3 \end{vmatrix}$$

Where, $R_{11} = 5 + 3 = 8\Omega$
 $R_{22} = 3 + 4 + 2 = 9\Omega$
 $R_{33} = 2 + 8 = 10\Omega$

$$\begin{vmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 15 \\ 15 \\ -25 \end{vmatrix}$$

$R_{12} = R_{21} = 3\Omega$
 $R_{23} = R_{32} = 2\Omega$
 $R_{13} = R_{31} = 0$

$$\Delta = \begin{vmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{vmatrix}$$

$$\Delta = 8[9 \times 10 - (-2 \times -2)] - (-3)[(-3 \times 10) - (0 \times -2)] + 0$$

$$\Delta = 8[90 - 4] + 3[-30] + 0$$

$$\Delta = 688 - 90$$

$$\Delta = 598$$

$$\Delta I_1 = \begin{vmatrix} 15 & -3 & 0 \\ 15 & 9 & -2 \\ -25 & -2 & 10 \end{vmatrix}$$

$$\Delta I_1 = 15[(9 \times 10) - (-2 \times -2)] + 3[(15 \times 10) - (-2 \times -25)] +$$

$$\Delta I_1 = 15[90 - 4] + 3[150 - 50] + 0$$

$$\Delta I_1 = 15[86] + 300 + 0$$

$$\Delta I_1 = 1290 + 300$$

$$\Delta I_1 = 1590$$

$$I_1 = \frac{\Delta I_1}{\Delta}$$

$$I_1 = \frac{1590}{598}$$

$$I_1 = 2.65 \text{Amps}$$

$$\Delta I_2 = \begin{vmatrix} 8 & 15 & 0 \\ -3 & 15 & -2 \\ 0 & -25 & 10 \end{vmatrix}$$

$$\Delta I_2 = 8[(15 \times 10) - (-2 \times -25)] - 15[(-3 \times 10) - 0] + 0$$

$$\Delta I_2 = 8[150 - 50] - 15[-30] + 0$$

$$\Delta I_2 = 8[100] + 450 = 800 + 450$$

$$\Delta I_2 = 1250$$

$$I_2 = \frac{\Delta I_2}{\Delta}$$

$$I_2 = \frac{1250}{598} = 2.09 \text{ Amps}$$

$$\Delta I_3 = \begin{vmatrix} 8 & -3 & 15 \\ -3 & 9 & 15 \\ 0 & -2 & -25 \end{vmatrix}$$

$$\Delta I_3 = 8[(9 \times -25) - (-2 \times 15)] + 3[(-3 \times -25) - 0] + 15[-3 \times -$$

$$\Delta I_3 = 8[-225 + 30] + 3[75] + 15[6]$$

$$\Delta I_3 = 8[-195] + 225 + 90 = -1560 + 225 + 90$$

$$\Delta I_3 = -1245$$

$$I_3 = \frac{\Delta I_3}{\Delta}$$

$$I_3 = \frac{-1245}{598} = -2.08 \text{ Amps}$$

Answer:



$$\text{Current through } 5\Omega \text{ Resistor} = 2.65 \text{ Amps}$$

$$\text{Current through } 4\Omega \text{ Resistor} = 2.09 \text{ Amps}$$

$$\text{Current through } 8\Omega \text{ Resistor} = -2.08 \text{ Amps}$$

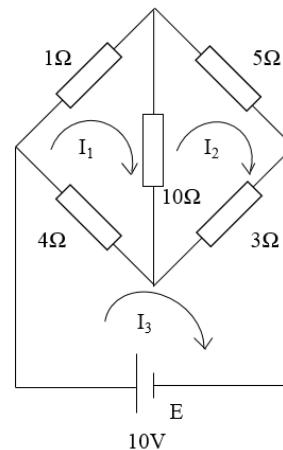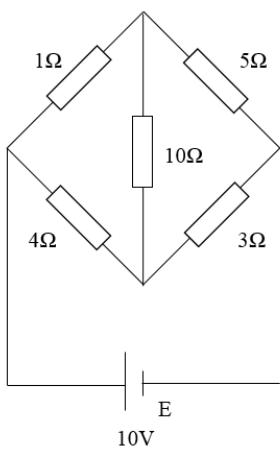Example: 5

Find the current through 10Ω load resistor using mesh current analysis.



Given Data:

$$\text{Number of loops} = 3$$

To Find:

$$\text{i) Current through } 10\Omega = ?$$

Solution:

By inspection Method:

$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \\ V_3 \end{vmatrix}$$

$$\begin{vmatrix} 15 & -10 & -4 \\ -10 & 18 & -3 \\ -4 & -3 & 7 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 0 \\ 0 \\ 10 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 15 & -10 & -4 \\ -10 & 18 & -3 \\ -4 & -3 & 7 \end{vmatrix}$$

$$\Delta = 15(126 - 9) + 10(-70 - 12) - 4(30 + 72)$$

$$\Delta = 15(117) + 10(-82) - 4(102)$$

$$\Delta = 1755 - 820 - 408$$

$$\Delta = 527$$

$$\Delta I_1 = \begin{vmatrix} 0 & -10 & -4 \\ 0 & 18 & -3 \\ 10 & -3 & 7 \end{vmatrix}$$

$$\Delta I_1 = 0 + 10(0 + 30) - 4(0 - 180)$$

$$\Delta I_1 = 10(30) - 4(-180) = 300 + 720$$

$$\Delta I_1 = 1020$$

$$I_1 = \frac{\Delta I_1}{\Delta}$$

$$I_1 = \frac{1020}{527}$$

$$I_1 = 1.94 \text{Amps}$$

$$\Delta I_2 = \begin{vmatrix} 15 & 0 & -4 \\ -10 & 0 & -3 \\ -4 & 10 & 7 \end{vmatrix}$$

$$\Delta I_2 = 15(0 + 30) - 0 - 4(-100 + 0)$$

$$\Delta I_2 = 15(30) - 4(-100)$$

$$\Delta I_2 = 450 + 400 = 850$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{850}{527}$$

$$I_2 = 1.61 \text{Amps}$$

$$\begin{aligned} \text{Current through } 10\Omega \text{ Resistor} &= I_1 - I_2 \\ &= 1.94 - 1.61 \\ &= 0.33 \text{ Amps} \end{aligned}$$

Answer:


$$\text{Current through } 10\Omega \text{ Resistor} = 0.33 \text{ Amps}$$

2.9 Nodal Equations :

This method of circuit solution, also known as the Node Voltage method, is based on the application of Kirchhoff's Current Law at each junction (node) of the circuit, to find the node voltages.

Procedure:

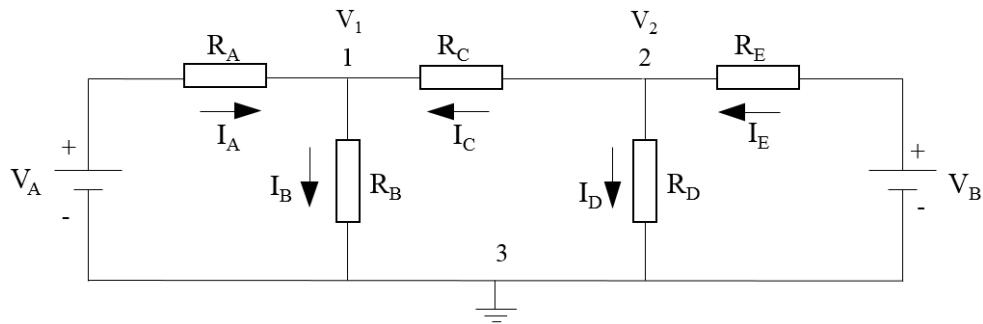- i) Select a node as the reference node.
- ii) Assign voltages $V_1, V_2 \dots, V_{n-1}$ to the remaining $n-1$ nodes. The voltages are referenced with respect to the reference node.
- iii) Apply KCL to each of the $n-1$ non-reference nodes. Use ohm's law to express the branch currents in terms of node voltages.
- iv) Solve the resulting simultaneous equations to obtain the unknown node voltage.



Let, V_1 and V_2 – Voltage of Node 1 and 2 with respect to Reference Node 3

$$\text{Number of Node} = 3$$

$$\text{Independent Node} = \text{Node 1 and 2}$$

By applying KCL at Node 1 (Junction of R_A, R_B & R_C):

$$\text{Sum of Incoming Current} = \text{Sum of Outgoing Current}$$

$$\begin{aligned}
 I_A + I_C &= I_B \\
 \frac{V_A - V_1}{R_A} + \frac{V_2 - V_1}{R_C} &= \frac{V_1}{R_B} \\
 \frac{V_A}{R_A} - \frac{V_1}{R_A} + \frac{V_2}{R_C} - \frac{V_1}{R_C} &= \frac{V_1}{R_B} \\
 -\frac{V_1}{R_A} + \frac{V_2}{R_C} - \frac{V_1}{R_C} - \frac{V_1}{R_B} &= -\frac{V_A}{R_A} \\
 \frac{V_1}{R_A} - \frac{V_2}{R_C} + \frac{V_1}{R_C} + \frac{V_1}{R_B} &= \frac{V_A}{R_A} \\
 V_1 \left[\frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} \right] - V_2 \left[\frac{1}{R_C} \right] &= \frac{V_A}{R_A}
 \end{aligned} \quad (1)$$

By applying KCL at Node 2:(Junction of R_C, R_D & R_E):

$$\text{Sum of Incoming Current} = \text{Sum of Outgoing Current}$$

$$I_E = I_C + I_D$$

$$\begin{aligned}
 \frac{V_B - V_2}{R_E} &= \frac{V_2 - V_1}{R_C} + \frac{V_2}{R_D} \\
 \frac{V_B}{R_E} - \frac{V_2}{R_E} &= \frac{V_2}{R_C} - \frac{V_1}{R_C} + \frac{V_2}{R_D} \\
 -\frac{V_2}{R_E} - \frac{V_2}{R_C} + \frac{V_1}{R_C} - \frac{V_2}{R_D} &= -\frac{V_B}{R_E} \\
 \frac{V_2}{R_E} + \frac{V_2}{R_C} - \frac{V_1}{R_C} + \frac{V_2}{R_D} &= \frac{V_B}{R_E} \\
 -V_1 \left[\frac{1}{R_C} \right] + V_2 \left[\frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \right] &= \frac{V_B}{R_E} \quad \dots\dots\dots (2)
 \end{aligned}$$

Equation (1) & (2) can be put in matrix form as follows:

$$\begin{vmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} \frac{V_A}{R_A} \\ \frac{V_B}{R_E} \end{vmatrix}$$

The resistance matrix and its formation is shown below:

$$[G] = \begin{vmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{vmatrix}$$


Where,

$$\begin{aligned}
 \text{Diagonal elements (Top to bottom)} &= \text{Conductance of resistors of Node 1 \& 2} \\
 \text{Other diagonal} &= \text{Conductance of resistor common to Nodes} \\
 (\text{Bottom left to top right}) &= 1 \& 2
 \end{aligned}$$

Note: For nodal analysis, the number of equations required to solve a network is less than what we require in other methods.

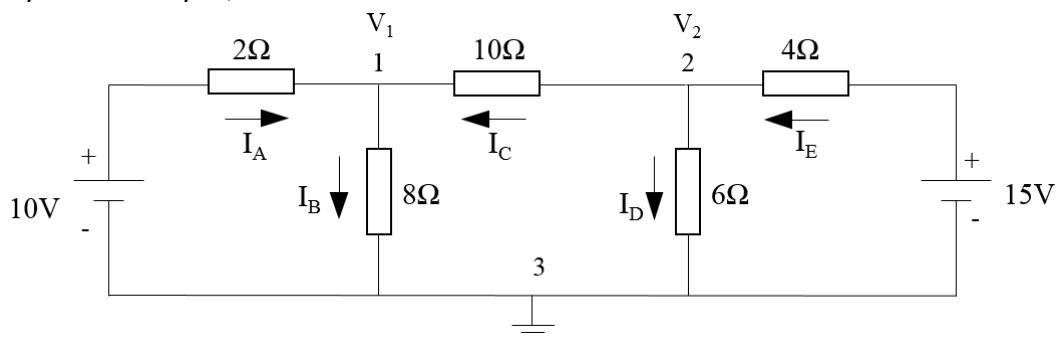Example: 6

Find by nodal analysis, the current I_A and I_C in the circuit shown.



Given Data:

$$\begin{aligned}
 \text{Number of Node} &= 3 \\
 \text{Number of equation} &= 3-1 = 2
 \end{aligned}$$

To Find:

$$\begin{aligned}
 \text{i) Current } I_A &=? \\
 \text{i) Current } I_C &=?
 \end{aligned}$$

Solution:

$$\begin{vmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} \frac{V_A}{R_A} \\ \frac{V_B}{R_E} \end{vmatrix}$$

$$\begin{vmatrix} \frac{1}{2} + \frac{1}{8} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{6} + \frac{1}{4} \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} \frac{10}{2} \\ \frac{15}{4} \end{vmatrix}$$

$$\begin{vmatrix} 0.5 + 0.125 + 0.1 & -0.1 \\ -0.1 & 0.1 + 0.167 + 0.25 \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} 5 \\ 3.75 \end{vmatrix}$$

$$\begin{vmatrix} 0.725 & -0.1 \\ -0.1 & 0.517 \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} 5 \\ 3.75 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 0.725 & -0.1 \\ -0.1 & 0.517 \end{vmatrix}$$

$$\Delta = (0.725 \times 0.517) - (-0.1 \times 0.1)$$

$$\Delta = 0.375 - 0.01$$

$$\Delta = 0.365$$

$$\Delta V_1 = \begin{vmatrix} 5 & -0.1 \\ 3.75 & 0.517 \end{vmatrix}$$

$$\Delta V_1 = (5 \times 0.517) - (-0.1 \times 3.75)$$

$$\Delta V_1 = 2.585 + 0.375$$

$$\Delta V_1 = 2.96$$

$$V_1 = \frac{\Delta V_1}{\Delta} = \frac{2.96}{0.365} = 8.1V$$

$$\Delta V_2 = \begin{vmatrix} 0.725 & 5 \\ -0.1 & 3.75 \end{vmatrix}$$

$$\Delta V_2 = (0.725 \times 3.75) - (-0.1 \times 5)$$

$$\Delta V_2 = 2.719 + 0.5$$

$$\Delta V_2 = 3.219$$

$$V_2 = \frac{\Delta V_2}{\Delta} = \frac{3.219}{0.365} = 8.8V$$

$$I_A = \frac{V_A - V_1}{R_A} = \frac{10 - 8.1}{2} = 0.95 \text{ Amps}$$

$$I_B = \frac{V_1}{R_B} = \frac{8.1}{8} = 1.01 \text{ Amps}$$

$$I_C = \frac{V_2 - V_1}{R_C} = \frac{8.8 - 8.1}{10} = 0.07 \text{ Amps}$$


Answer:

$$\text{Current through } 8\Omega \text{ Resistor} = I_A = 0.95 \text{ Amps}$$

$$\text{Current through } 6\Omega \text{ Resistor} = I_C = 0.07 \text{ Amps}$$

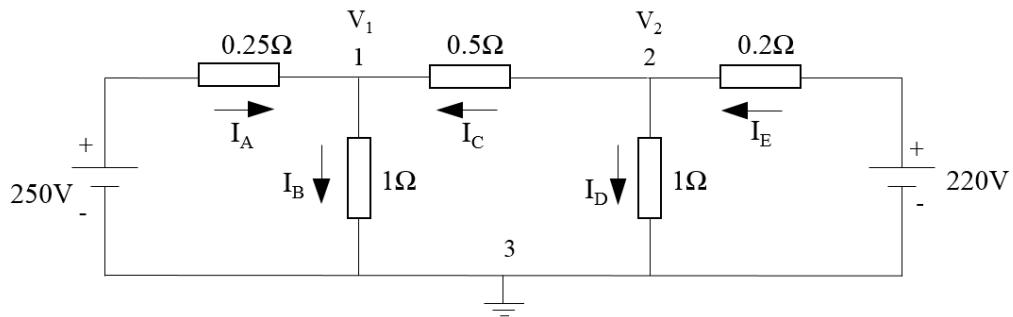Example: 7

Find by nodal analysis, the current I_A and I_C in the circuit shown.



Given Data:

$$\begin{array}{ll} \text{Number of Node} & = 3 \\ \text{Number of equation} & = 3-1=2 \end{array}$$

To Find:

$$\begin{array}{l} \text{i) Current } I_A = ? \\ \text{ii) Current } I_C = ? \end{array}$$

Solution:

$$\begin{vmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} \frac{V_A}{R_A} \\ \frac{V_B}{R_E} \end{vmatrix}$$

$$\begin{vmatrix} \frac{1}{0.25} + \frac{1}{1} + \frac{1}{0.5} & -\frac{1}{0.5} \\ -\frac{1}{0.5} & \frac{1}{0.5} + \frac{1}{1} + \frac{1}{0.2} \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} \frac{250}{0.25} \\ \frac{220}{0.2} \end{vmatrix}$$

$$\begin{vmatrix} 4+1+2 & -2 \\ -2 & 2+1+5 \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} 1000 \\ 1100 \end{vmatrix}$$

$$\begin{vmatrix} 7 & -2 \\ -2 & 8 \end{vmatrix} \begin{vmatrix} V_1 \\ V_2 \end{vmatrix} = \begin{vmatrix} 1000 \\ 1100 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 7 & -2 \\ -2 & 8 \end{vmatrix}$$

$$\Delta = 56 - 4$$

$$\Delta = 52$$

$$\Delta V_1 = \begin{vmatrix} 1000 & -2 \\ 1100 & 8 \end{vmatrix}$$

$$\Delta V_1 = 8000 + 2200$$

$$\Delta V_1 = 10200$$

$$V_1 = \frac{\Delta V_1}{\Delta}$$

$$V_1 = \frac{10200}{52}$$

$$V_1 = 196.15V$$

$$\Delta V_2 = \begin{vmatrix} 7 & 1000 \\ -2 & 1100 \end{vmatrix}$$

$$\begin{aligned}
 \Delta V_2 &= 7700 + 2000 \\
 \Delta V_2 &= 9700 \\
 V_2 &= \frac{\Delta V_2}{\Delta} \\
 V_2 &= \frac{9700}{52} \\
 V_2 &= 186.5V
 \end{aligned}$$

$$\begin{aligned}
 I_A &= \frac{V_A - V_1}{R_A} \\
 I_A &= \frac{250 - 196.15}{0.25} = 215.4 \text{ Amps} \\
 I_B &= \frac{V_1}{R_B} \\
 I_B &= \frac{196.15}{1} = 196.15 \text{ Amps} \\
 I_C &= \frac{V_2 - V_1}{R_C} \\
 I_C &= \frac{186.5 - 196.15}{0.5} = -19.3 \text{ Amps}
 \end{aligned}$$

Answer:

Current through 1Ω Resistor = $I_A = 215.4$ Amps

Current through 0.5Ω Resistor = $I_C = -19.3$ Amps

2.10 Superposition Theorem:


Some circuits require more than one voltage or current source. For example, most amplifiers operate with two voltage sources. When multiple sources are used in a circuit, the superposition theorem provides a methods for analysis. Hence the superposition theorem is a way to determine currents in a circuit with multiple sources, by considering one source at a time and replacing the other sources by their internal resistances.

Statement:


In a linear, bilateral network having more than one source, the current and voltage in any part of the network can be found by adding algebraically the effect of each source separately.

Procedure:

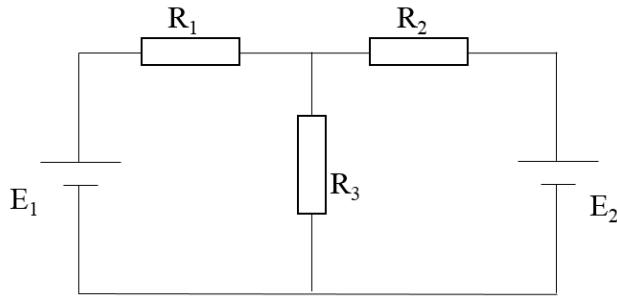- i) Consider only one source E_1 and replace the other source E_2 by its internal resistance.
(If it is voltage source open circuit it and Current source short circuit it.)
- ii) Determine the current (I_L) through load resistance.
- iii) Then consider the other source E_2 and replace the source E_1 by its internal resistance.
- iv) Determine the current (I'_L) through load resistance.
- v) Final load current is the algebraic sum of current supplied by E_1 and E_2 i.e I_L and I'_L .



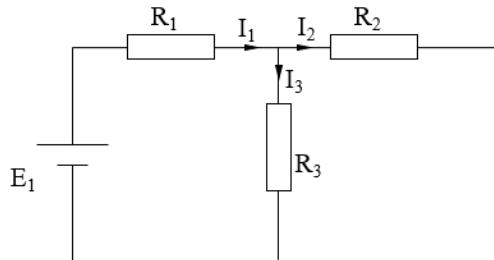Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R_{eq} = R_1 + \left(\frac{R_2 \times R_3}{R_2 + R_3} \right)$$

$$\text{Current } I_1 = \frac{E_1}{R_{eq}}$$


$$I_1 = \frac{E_1}{R_1 + \left(\frac{R_2 \times R_3}{R_2 + R_3} \right)}$$

When E_1 is Working:

$$\text{Current through Load}(R_3) = I_3$$

$$\text{So, } I_3 = \frac{I_1 \times R_2}{R_2 + R_3}$$

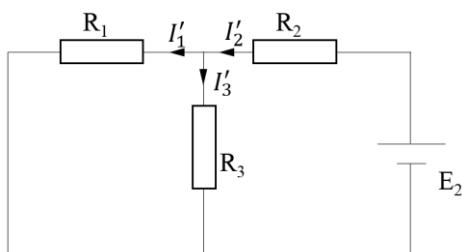Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R'_{eq} = R_2 + \left(\frac{R_1 \times R_3}{R_1 + R_3} \right)$$

$$\text{Current } I'_2 = \frac{E_2}{R'_{eq}}$$

$$I'_2 = \frac{E_1}{R_2 + \left(\frac{R_1 \times R_3}{R_1 + R_3} \right)}$$

When E_2 is Working:

$$\text{Current through Load}(R_3) = I'_3$$

$$\text{So, } I'_3 = \frac{I'_2 \times R_1}{R_1 + R_3}$$

When E_1 and E_2 are working:

$$\text{Current through Load } R_3 = \text{Current supplied by } E_1 + \text{Current supplied by } E_2$$


$$= I_3 + I'_3$$

When E_1 and E_2 are working:

$$\text{Current through Load } R_3 = \frac{I_1 \times R_2}{R_2 + R_3} + \frac{I'_2 \times R_1}{R_1 + R_3}$$

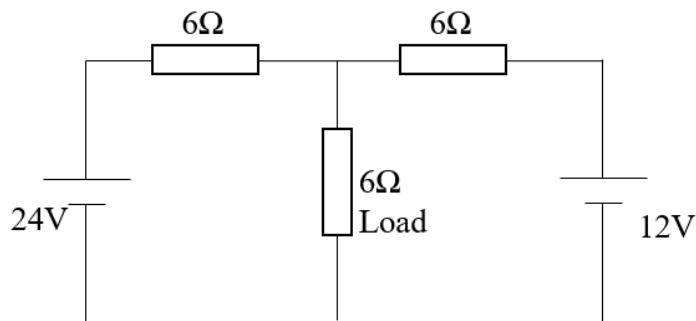Example: 8

Find the current through Load Resistor (6Ω) resistor in the following circuit by the principle of superposition theorem



Given Data:

$$\text{Voltage source } E_1 = 24V$$


$$\text{Voltage source } E_2 = 12V$$

To Find:

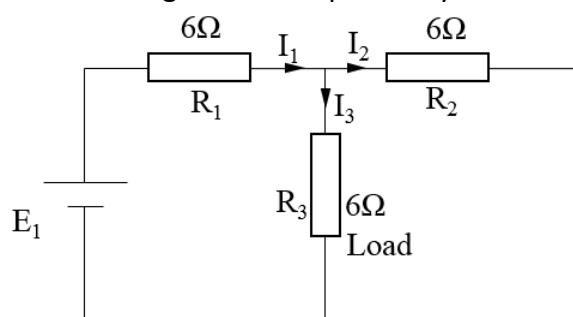i) Current through 6Ω Resistor=?

Solution:

Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R_{eq} = R_1 + \left(\frac{R_2 \times R_3}{R_2 + R_3} \right)$$

$$\text{Equivalent Resistance } R_{eq} = 6 + \left(\frac{6 \times 6}{6 + 6} \right) = 6 + 3 = 9\Omega$$

$$\text{Current } I_1 = \frac{E_1}{R_{eq}}$$

$$\text{Current } I_1 = \frac{24}{9} = 2.67 \text{ Amps}$$


When E_1 is Working:

$$\text{Current through Load } R_3 = I_3$$

$$\text{So, } I_3 = \frac{I_1 \times R_2}{R_2 + R_3}$$

$$\text{So, } I_3 = \frac{2.67 \times 6}{6 + 6} = 1.335 \text{ Amps}$$

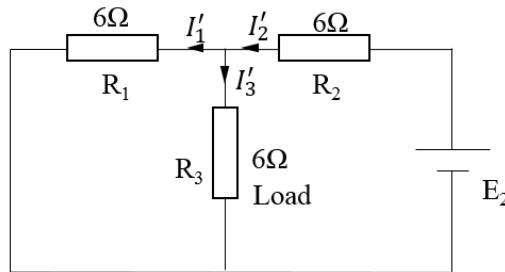Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R'_{\text{eq}} = R_2 + \left(\frac{R_1 \times R_3}{R_1 + R_3} \right)$$

$$\text{Equivalent Resistance } R'_{\text{eq}} = 6 + \left(\frac{6 \times 6}{6 + 6} \right) = 9\Omega$$

$$\text{Current } I'_2 = \frac{E_2}{R'_{\text{eq}}}$$

$$\text{Current } I'_2 = \frac{12}{9} = 1.33 \text{ Amps}$$

When E_2 is Working:

$$\text{Current through Load } R_3 = I'_3$$

$$\text{So, } I'_3 = \frac{I'_2 \times R_1}{R_1 + R_3}$$

$$\text{So, } I'_3 = \frac{1.33 \times 6}{6 + 6} = 0.665 \text{ Amps}$$

When E_1 and E_2 are working:

$$\text{Current through Load } R_3 = \text{Current supplied by } E_1 + \text{Current supplied by } E_2$$

$$= I_3 + I'_3$$

$$= 1.335 + 0.665$$

When E_1 and E_2 are working:


$$\text{Current through Load } R_3 = 2 \text{ Amps}$$

Answer:

$$\text{Current through } 6\Omega \text{ Load Resistor} = 2 \text{ Amps}$$

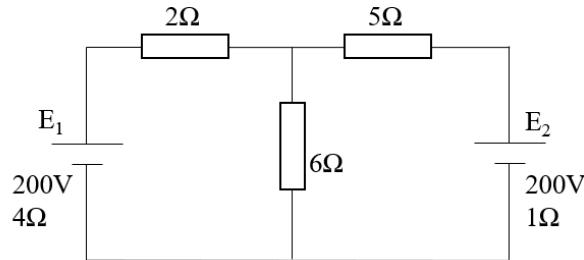Example: 9

Find the current through 6Ω resistor in the following circuit by the principle of superposition theorem.



Given Data:

$$\begin{aligned} \text{Voltage source } E_1 &= 200V \\ \text{Voltage source } E_2 &= 200V \end{aligned}$$


To Find:

i) Current through 6Ω Resistor=?

Solution:

[Method -1]

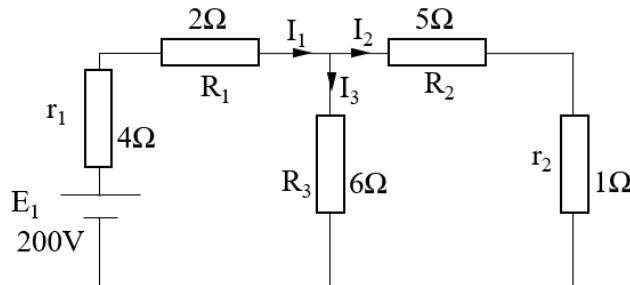Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R_{eq} = (r_1 + R_1) + \left(\frac{(R_2 + r_2) \times R_3}{(R_2 + r_2) + R_3} \right)$$

$$\text{Equivalent Resistance } R_{eq} = (4 + 2) + \left(\frac{(5 + 1) \times 6}{(5 + 1) + 6} \right) = 6 + 3 = 9\Omega$$

$$\text{Equivalent Resistance } R_{eq} = 6 + \left(\frac{6 \times 6}{6 + 6} \right) = 6 + 3 = 9\Omega$$

$$\text{Current } I_1 = \frac{E_1}{R_{eq}}$$

$$\text{Current } I_1 = \frac{200}{9} = 22.22 \text{ Amps}$$


When E_1 is Working:

$$\text{Current through Load}(R_3) = I_3$$

$$\text{So, } I_3 = \frac{I_1 \times (R_2 + r_2)}{(R_2 + r_2) + R_3}$$

$$\text{So, } I_3 = \frac{22.22 \times 6}{6 + 6} = 11.11 \text{ Amps}$$

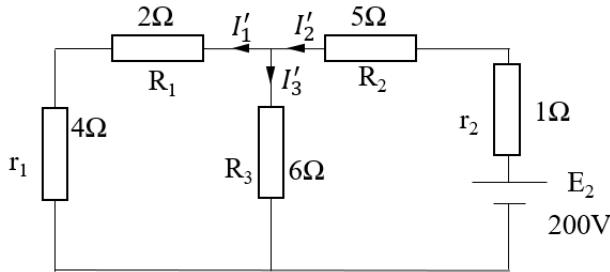Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R'_{\text{eq}} = (r_2 + R_2) + \left(\frac{(R_1 + r_1) \times R_3}{(R_1 + r_1) + R_3} \right)$$

$$\begin{aligned} \text{Equivalent Resistance } R'_{\text{eq}} &= (1 + 5) + \left(\frac{(2 + 4) \times 6}{(2 + 4) + 6} \right) \\ &= 6 + \left(\frac{6 \times 6}{6 + 6} \right) = 6 + 3 = 9\Omega \end{aligned}$$

$$\text{Current } I'_2 = \frac{E_2}{R'_{\text{eq}}}$$

$$\text{Current } I'_2 = \frac{200}{9} = 22.22 \text{Amps}$$

When E_2 is Working:

$$\text{Current through Load}(R_3) = I'_3$$

$$\text{So, } I'_3 = \frac{I'_2 \times (R_1 + r_1)}{(R_1 + r_1) + R_3}$$

$$\text{So, } I'_3 = \frac{22.22 \times 6}{6 + 6} = 11.11 \text{ Amps}$$

When E_1 and E_2 are working:

$$\text{Current through Load } R_3 = \text{Current supplied by } E_1 + \text{Current supplied by } E_2$$

$$= I_3 + I'_3$$

$$= 11.11 + 11.11$$


$$= 22.22 \text{ Amps}$$

Answer:

$$\text{Current through } 6\Omega \text{ Resistor} = 22.22 \text{ Amps}$$

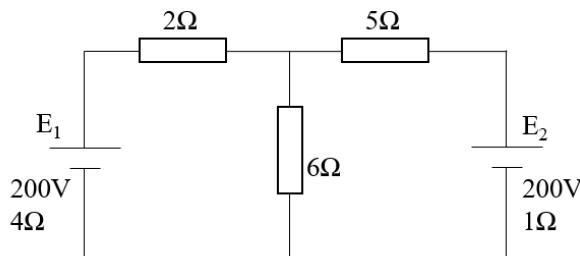Example: 10

Find the current through 6Ω resistor in the following circuit by the principle of superposition theorem.



Given Data:

$$\text{Voltage source } E_1 = 200V$$


$$\text{Voltage source } E_2 = 200V$$

To Find:

$$\text{i) Current through } 6\Omega \text{ Resistor} = ?$$

Solution:**[Method -2]**

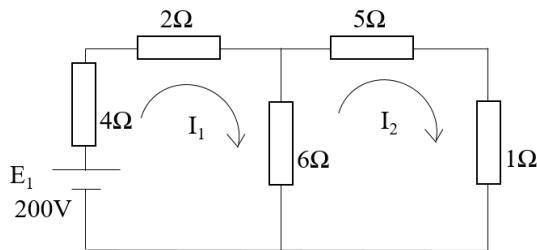Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\begin{vmatrix} 4+2+6 & -6 \\ -6 & 6+5+1 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} E_1 \\ E_2 \end{vmatrix}$$

$$\begin{vmatrix} 12 & -6 \\ -6 & 12 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 200 \\ 0 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 12 & -6 \\ -6 & 12 \end{vmatrix}$$

$$\Delta = 144 - 36$$

$$\Delta = 108$$

$$\Delta I_1 = \begin{vmatrix} 200 & -6 \\ 0 & 12 \end{vmatrix}$$

$$\Delta I_1 = 200 \times 12 = 2400$$

$$\Delta I_1 = 2400$$

$$I_1 = \frac{\Delta I_1}{\Delta} = \frac{2400}{108} = 22.22 \text{ Amps}$$

$$\Delta I_2 = \begin{vmatrix} 12 & 200 \\ -6 & 0 \end{vmatrix}$$

$$\Delta I_2 = 200 \times 6 = 1200$$


$$\Delta I_2 = 1200$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{1200}{108} = 11.11 \text{ Amps}$$

When E_1 is working:

$$\begin{aligned} \text{Current through } 6\Omega \text{ Resistor} &= I_1 - I_2 \\ &= 22.22 - 11.11 \\ &= 11.11 \text{ Amps (downwards)} \end{aligned}$$

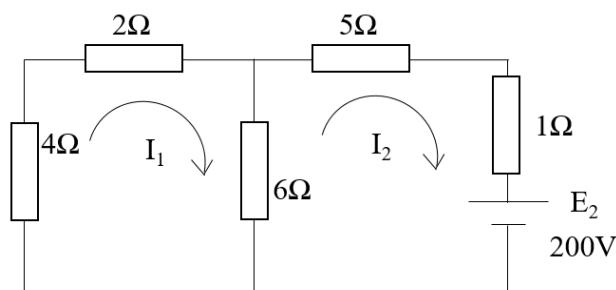Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\begin{vmatrix} 4+2+6 & -6 \\ -6 & 6+5+1 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} E_1 \\ E_2 \end{vmatrix}$$

$$\begin{vmatrix} 12 & -6 \\ -6 & 12 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 0 \\ -200 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 12 & -6 \\ -6 & 12 \end{vmatrix}$$

$$\Delta = 144 - 36$$

$$\Delta = 108$$

$$\Delta I_1 = \begin{vmatrix} 0 & -6 \\ -200 & 12 \end{vmatrix}$$

$$\Delta I_1 = -200 \times 6 = -1200$$

$$\Delta I_1 = -1200$$

$$I_1 = \frac{\Delta I_1}{\Delta} = \frac{-1200}{108} = -11.11 \text{ Amps}$$

$$\Delta I_2 = \begin{vmatrix} 12 & 0 \\ -6 & -200 \end{vmatrix}$$

$$\Delta I_2 = 12 \times -200 = -2400$$

$$\Delta I_2 = -2400$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{-2400}{108} = -22.22 \text{ Amps}$$

When E_2 is working:

$$\begin{aligned} \text{Current through } 6\Omega \text{ Resistor} &= I_1 - I_2 \\ &= -11.11 - (-22.22) = -11.11 + 22.22 \\ &= 11.11 \text{ Amps (downwards)} \end{aligned}$$

When E_1 and E_2 are working:


$$\begin{aligned} \text{Current through } 6\Omega \text{ Resistor} &= I_1 + I_2 \\ &= 11.11 + 11.11 \\ &= 22.22 \text{ Amps} \end{aligned}$$

Answer:

$$\text{Current through } 6\Omega \text{ Resistor} = 22.22 \text{ Amps}$$

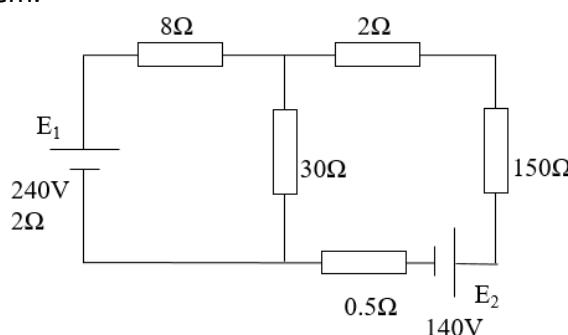Example: 11

Find the current in the 150Ω resistor and the power consumed in it by the principle of superposition theorem.



Given Data:


$$\begin{aligned} \text{Voltage source } E_1 &= 240V \\ \text{Voltage source } E_2 &= 140V \end{aligned}$$

To Find:

$$\text{i) Current through } 150\Omega \text{ Resistor} = ?$$

Solution:**[Method -1]**

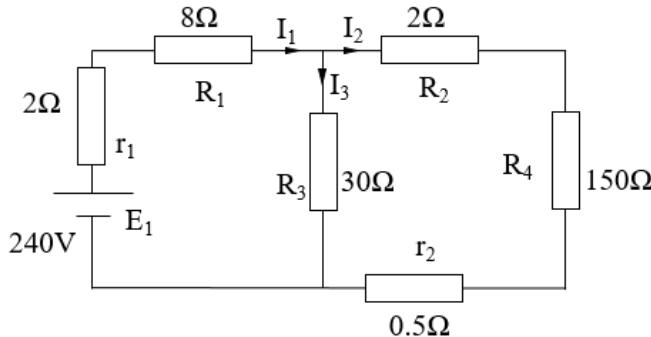Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R_{eq} = (r_1 + R_1) + \left(\frac{(R_2 + R_4 + r_2) \times R_3}{(R_2 + R_4 + r_2) + R_3} \right)$$

$$\text{Equivalent Resistance } R_{eq} = (2 + 8) + \left(\frac{(2 + 150 + 0.5) \times 30}{(2 + 150 + 0.5) + 30} \right)$$

$$\text{Equivalent Resistance } R_{eq} = 10 + \left(\frac{152.5 \times 30}{152.5 + 30} \right)$$

$$\text{Equivalent Resistance } R_{eq} = 35.07\Omega$$

$$\text{Current } I_1 = \frac{E_1}{R_{eq}}$$

$$\text{Current } I_1 = \frac{240}{35.07} = 6.84 \text{ Amps}$$


When E_1 is Working:

$$\text{Current through } 150\Omega \text{ Resistor} = I_2$$

$$\text{So, } I_2 = \frac{I_1 \times R_3}{R_3 + (R_2 + R_4 + r_2)}$$

$$\text{So, } I_2 = \frac{6.84 \times 30}{30 + 152.5} = 1.125 \text{ Amps}$$

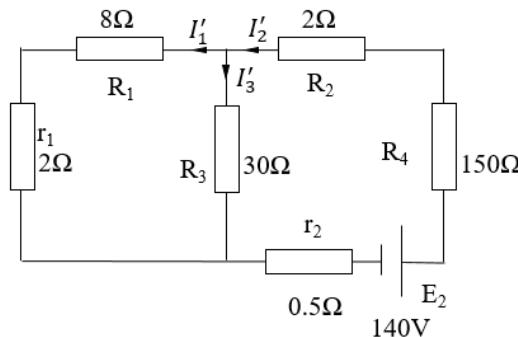Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R'_{eq} = (r_2 + R_4 + R_2) + \left(\frac{(R_1 + r_1) \times R_3}{(R_1 + r_1) + R_3} \right)$$

$$\text{Equivalent Resistance } R'_{eq} = (0.5 + 150 + 2) + \left(\frac{(8 + 2) \times 30}{(8 + 2) + 30} \right)$$

$$\text{Equivalent Resistance } R'_{eq} = 152.5 + \left(\frac{10 \times 30}{10 + 30} \right)$$

$$\text{Equivalent Resistance } R'_{\text{eq}} = 152.5 + 7.5 = 160\Omega$$

$$\text{Current } I'_2 = \frac{E_2}{R'_{\text{eq}}}$$

$$\text{Current } I'_2 = \frac{140}{160} = 0.875 \text{ Amps}$$

When E_2 is Working:

$$\text{Current through } 150\Omega \text{ Resistor} = I'_2$$

$$\text{So, } I'_2 = 0.875 \text{ Amps}$$

When E_1 and E_2 are working:

$$\text{Current through } 150\Omega = \text{Current supplied by } E_1 + \text{Current supplied by } E_2$$

$$= I_2 - I'_2$$

$$= 1.125 - 0.875 = 0.25 \text{ Amps}$$

$$\text{Power consumed by } 150\Omega \text{ Resistor} = I^2 R$$

$$P = 0.25^2 \times 150 = 9.375 \text{ Watts}$$


Answer:

$$\text{Current through } 150\Omega \text{ Resistor} = 0.25 \text{ Amps}$$

$$\text{Power consumed by } 150\Omega \text{ Resistor} = 9.375 \text{ Watts}$$

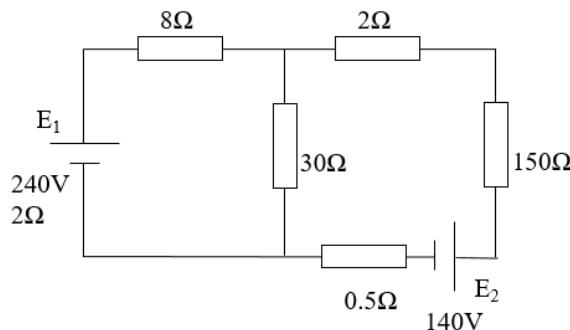Example: 12

Find the current in the 150Ω resistor and the power consumed in it by the principle of superposition theorem.



Given Data:

$$\text{Voltage source } E_1 = 240V$$

$$\text{Voltage source } E_2 = 140V$$


To Find:

i) Current through 150Ω Resistor =?

Solution:

[Method -2]

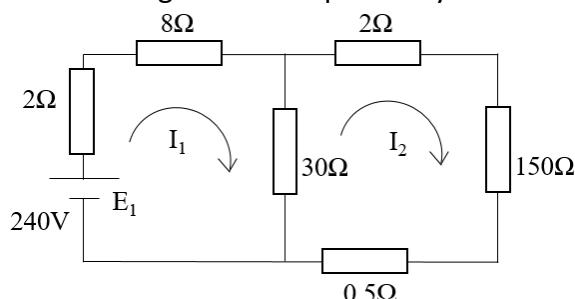Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\begin{vmatrix} 2 + 8 + 30 & -30 \\ -30 & 30 + 2 + 150 + 0.5 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} E_1 \\ E_2 \end{vmatrix}$$

$$\begin{vmatrix} 40 & -30 \\ -30 & 182.5 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 240 \\ 0 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 40 & -30 \\ -30 & 182.5 \end{vmatrix}$$

$$\Delta = (40 \times 182.5) - (-30 \times -30)$$

$$\Delta = 7300 - 900$$

$$\Delta = 6400$$

$$\Delta I_2 = \begin{vmatrix} 40 & 240 \\ -30 & 0 \end{vmatrix}$$

$$\Delta I_2 = 240 \times 30 = 7200$$


$$\Delta I_2 = 7200$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{7200}{6400} = 1.125 \text{ Amps}$$

When E_1 is working:

Current through 150Ω Resistor = $I_2 = 1.125 \text{ Amps}$ (downwards)

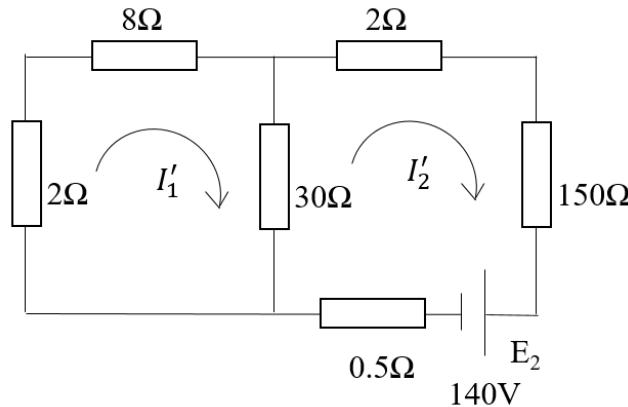Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\begin{vmatrix} 40 & -30 \\ -30 & 182.5 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} E_1 \\ E_2 \end{vmatrix}$$

$$\begin{vmatrix} 40 & -30 \\ -30 & 182.5 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 0 \\ -140 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 40 & -30 \\ -30 & 182.5 \end{vmatrix}$$

$$\Delta = (40 \times 182.5) - (-30 \times -30)$$

$$\Delta = 7300 - 900$$

$$\Delta = 6400$$

$$\Delta I_2' = \begin{vmatrix} 40 & 0 \\ -30 & -140 \end{vmatrix}$$

$$\Delta I_2' = 40 \times -140 = -5600$$

$$\Delta I_2' = -5600$$

$$I'_2 = \frac{\Delta I'_2}{\Delta}$$

$$I'_2 = \frac{-5600}{6400} = -0.875 \text{ Amps}$$

When E_2 is working:

$$\begin{aligned}\text{Current through } 150\Omega \text{ Resistor} &= I'_2 = -0.875 \text{ Amps} \\ &= I_2 + I'_2 \\ &= 1.125 - 0.875 \\ &= 0.25 \text{ Amps}\end{aligned}$$


$$\begin{aligned}\text{Power consumed by } 150\Omega \text{ Resistor} &= I^2 R \\ P &= 0.25^2 \times 150 = 9.375 \text{ Watts}\end{aligned}$$

Answer:

$$\begin{aligned}\text{Current through } 150\Omega \text{ Resistor} &= 0.25 \text{ Amps} \\ \text{Power consumed by } 150\Omega \text{ Resistor} &= 9.375 \text{ Watts}\end{aligned}$$

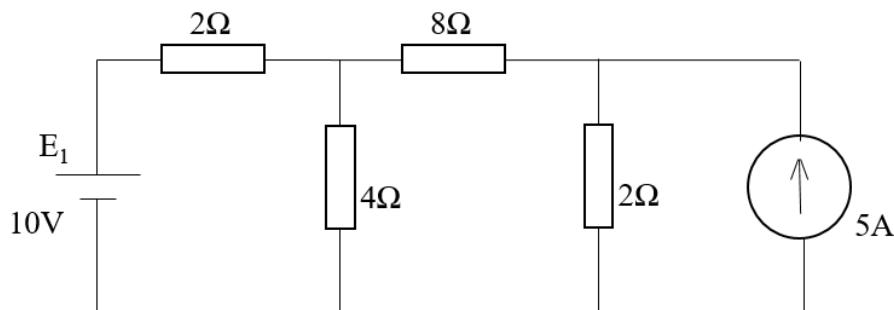Example: 13

Find the current through 8Ω resistor and its direction for the network shown below.



Given Data:

$$\begin{aligned}\text{Voltage source } E_1 &= 10V \\ \text{Current source } I &= 5A\end{aligned}$$


To Find:

$$\text{i) Current through } 8\Omega \text{ Resistor} = ?$$


Solution:

[Method -1]

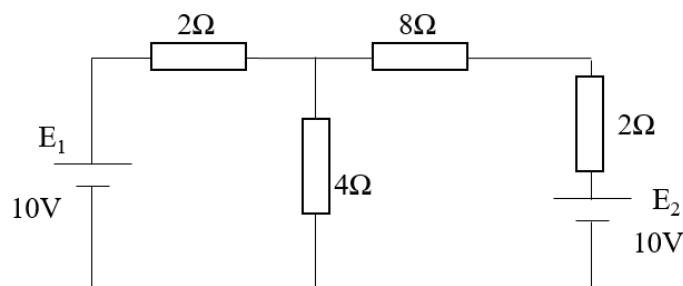Current source is converted into voltage source as follows.



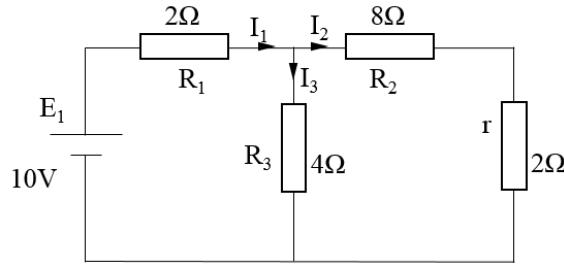Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R_{eq} = R_1 + \left(\frac{(R_2 + r) \times R_3}{(R_2 + r) + R_3} \right)$$

$$\text{Equivalent Resistance } R_{eq} = 2 + \left(\frac{(8 + 2) \times 4}{(8 + 2) + 4} \right)$$

$$\text{Equivalent Resistance } R_{eq} = 2 + \left(\frac{10 \times 4}{10 + 4} \right) = 2 + 2.86 = 4.86\Omega$$

$$\text{Current } I_1 = \frac{E_1}{R_{eq}}$$

$$\text{Current } I_1 = \frac{10}{4.86} = 2.06 \text{ Amps}$$


When E_1 is Working:

$$\text{Current through } 8\Omega \text{ Resistor} = I_2$$

$$\text{So, } I_2 = \frac{I_1 \times R_3}{R_3 + (R_2 + r)}$$

$$\text{So, } I_2 = \frac{2.06 \times 4}{4 + 10} = 0.59 \text{ Amps}$$

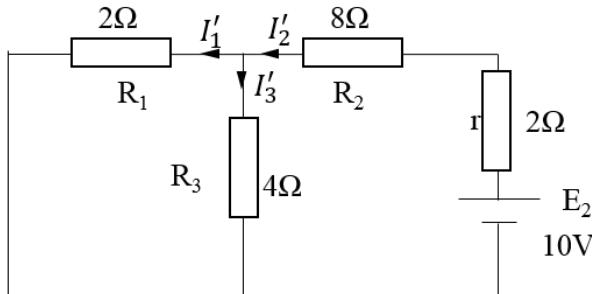Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\text{Equivalent Resistance } R'_{eq} = (r + R_2) + \left(\frac{R_1 \times R_3}{R_1 + R_3} \right)$$

$$\begin{aligned} \text{Equivalent Resistance } R'_{eq} &= (2 + 8) + \left(\frac{2 \times 4}{2 + 4} \right) \\ &= 10 + \left(\frac{8}{6} \right) = 10 + 1.33 = 11.33\Omega \end{aligned}$$

$$\text{Current } I'_2 = \frac{E_2}{R'_{eq}}$$

$$\text{Current } I'_2 = \frac{10}{11.33} = 0.88 \text{ Amps}$$

When E_2 is Working:

$$\text{Current through Load}(R_2) = I'_2$$

$$\text{So, } I'_2 = 0.88 \text{ Amps}$$

When E_1 and E_2 are working:


$$\begin{aligned}\text{Current through } 8\Omega \text{ Resistor} &= \text{Current supplied by } E_1 + E_2 \\ &= I_2 - I'_2 \\ &= 0.59 - 0.88 \\ &= -0.29 \text{ Amps}\end{aligned}$$

Answer:

$$\begin{aligned}\text{Current through } 8\Omega \text{ Resistor} &= -0.29 \text{ Amps} \\ \text{Direction of current through } 8\Omega &= \text{Right to Left}\end{aligned}$$

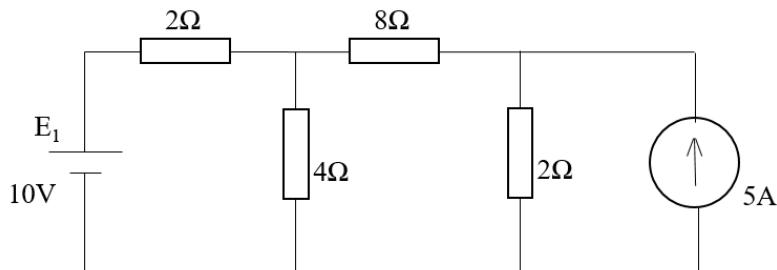Example: 14

Find the current through 8Ω resistor and its direction for the network shown below.



Given Data:


$$\begin{aligned}\text{Voltage source } E_1 &= 10V \\ \text{Voltage source } E_2 &= 10V\end{aligned}$$

To Find:


$$\text{i) Current through } 8\Omega \text{ Resistor} = ?$$

Solution:

[Method -2]

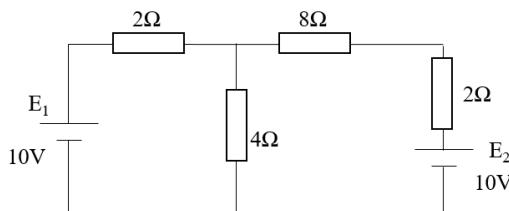

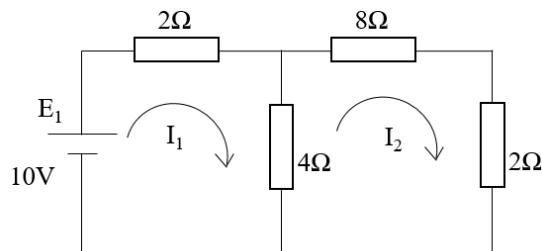Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\begin{vmatrix} 2+4 & -4 \\ -4 & 4+8+2 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} E_1 \\ E_2 \end{vmatrix}$$

$$\begin{vmatrix} 6 & -4 \\ -4 & 14 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 10 \\ 0 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 6 & -4 \\ -4 & 14 \end{vmatrix}$$


$$\Delta = 84 - 16 = 68$$

$$\begin{aligned}\Delta I_2 &= \begin{vmatrix} 6 & 10 \\ -4 & 0 \end{vmatrix} \\ \Delta I_2 &= 40 \\ I_2 &= \frac{\Delta I_2}{\Delta} = \frac{40}{68} = 0.59 \text{ Amps}\end{aligned}$$

When E_1 is working:

$$\begin{aligned}\text{Current through } 8\Omega \text{ Resistor} &= I_2 \\ &= 0.59 \text{ Amps}\end{aligned}$$

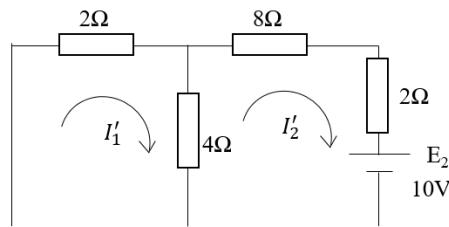Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\begin{aligned}\begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} &= \begin{vmatrix} E_1 \\ E_2 \end{vmatrix} \\ \begin{vmatrix} 6 & -4 \\ -4 & 14 \end{vmatrix} \begin{vmatrix} I'_1 \\ I'_2 \end{vmatrix} &= \begin{vmatrix} 0 \\ -10 \end{vmatrix} \\ \Delta &= \begin{vmatrix} 6 & -4 \\ -4 & 14 \end{vmatrix} \\ \Delta &= 84 - 16 \\ \Delta &= 68 \\ \Delta I'_2 &= \begin{vmatrix} 6 & 0 \\ -4 & -10 \end{vmatrix} \\ \Delta I'_2 &= -60 \\ I'_2 &= \frac{\Delta I'_2}{\Delta} = \frac{-60}{68} = -0.88 \text{ Amps}\end{aligned}$$

When E_2 is working:


$$\begin{aligned}\text{Current through } 8\Omega \text{ Resistor} &= I'_2 = -0.88 \text{ Amps} \\ &= I_1 + I_2 \\ &= 0.59 + (-0.88) \\ &= 0.59 - 0.88 \\ &= -0.29 \text{ Amps}\end{aligned}$$

Answer:

$$\text{Current through } 8\Omega \text{ Resistor} = -0.29 \text{ Amps (Direction: Right to Left)}$$

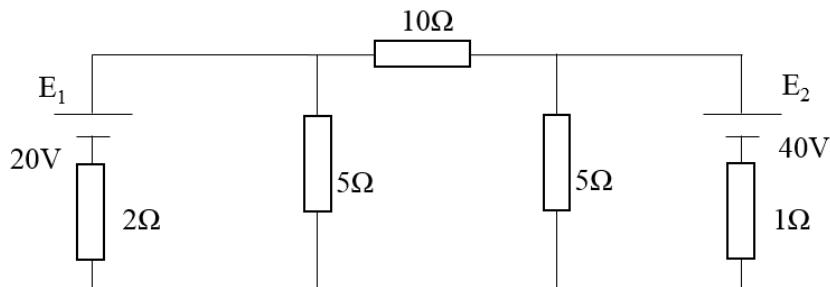Example: 15

Find the current through 10Ω resistor using superposition theorem.



Given Data:


$$\begin{array}{ll} \text{Voltage source } E_1 & = 20V \\ \text{Voltage source } E_2 & = 40V \end{array}$$

To Find:

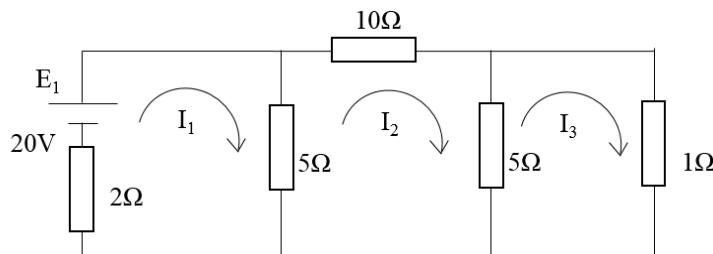i) Current through 10Ω Resistor =?

Solution:

Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} E_1 \\ E_2 \\ E_3 \end{vmatrix}$$

$$\begin{vmatrix} 7 & -5 & 0 \\ -5 & 20 & -5 \\ 0 & -5 & 6 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 20 \\ 0 \\ 0 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 7 & -5 & 0 \\ -5 & 20 & -5 \\ 0 & -5 & 6 \end{vmatrix}$$

$$\Delta = 7 [20 \times 6 - (-5 \times 5)] - (-5) [(-5 \times 6) - 0] + 0$$

$$\Delta = 7[120 - 25] + 5[-30]$$

$$\Delta = 7[95] - 150 = 665 - 150$$

$$\Delta = 515$$

$$\Delta I_2 = \begin{vmatrix} 7 & 20 & 0 \\ -5 & 0 & -5 \\ 0 & 0 & 6 \end{vmatrix}$$


$$\Delta I_2 = -20(-30) = 600$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{600}{515} = 1.16 \text{ Amps}$$

When E_1 is working:

$$\begin{array}{ll} \text{Current through } 10\Omega \text{ Resistor} & = I_2 \\ & = 1.16 \text{ Amps} \end{array}$$

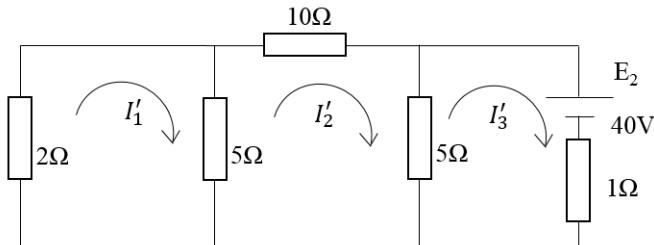Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\begin{vmatrix} 7 & -5 & 0 \\ -5 & 20 & -5 \\ 0 & -5 & 6 \end{vmatrix} \begin{vmatrix} I'_1 \\ I'_2 \\ I'_3 \end{vmatrix} = \begin{vmatrix} 0 \\ 0 \\ -40 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 7 & -5 & 0 \\ -5 & 20 & -5 \\ 0 & -5 & 6 \end{vmatrix}$$

$$\Delta = 895$$

$$\Delta I'_2 = \begin{vmatrix} 7 & 0 & 0 \\ -5 & 0 & -5 \\ 0 & -40 & 6 \end{vmatrix}$$

$$\Delta I'_2 = 7(0 - 200) = 7(-200)$$

$$\Delta I'_2 = -1400$$

$$I'_2 = \frac{\Delta I'_2}{\Delta} = \frac{-1400}{515} = -2.72 \text{ Amps}$$

When E_2 is working:

$$\begin{aligned} \text{Current through } 10\Omega \text{ Resistor} &= I'_2 \\ &= -2.72 \text{ Amps} \end{aligned}$$

When E_1 and E_2 are working:


$$\begin{aligned} \text{Current through } 10\Omega \text{ Resistor} &= I_1 + I_2 \\ &= 1.16 + (-2.72) \\ &= 0.67 - 2.72 \\ &= -1.55 \text{ Amps} \end{aligned}$$

Answer:

$$\text{Current through } 10\Omega \text{ Resistor} = -1.55 \text{ Amps}$$

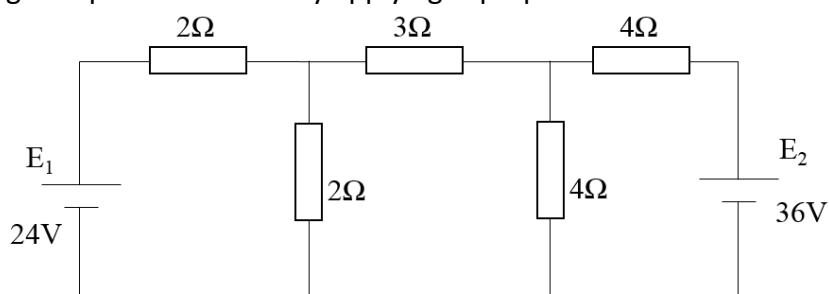Example: 16

Find the voltage drop in 3Ω resistor by applying superposition theorem.



Given Data:


$$\begin{aligned} \text{Voltage source } E_1 &= 24V \\ \text{Voltage source } E_2 &= 36V \end{aligned}$$

To Find:

$$\text{i) Current through } 3\Omega \text{ Resistor} = ?$$

Solution:

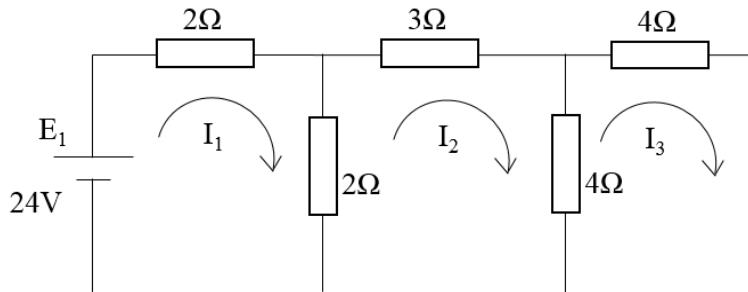Step 1: Voltage Source E_1 is Working and E_2 is replaced by its internal resistance.



$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} E_1 \\ E_2 \\ E_3 \end{vmatrix}$$

$$\begin{vmatrix} 4 & -2 & 0 \\ -2 & 9 & -4 \\ 0 & -4 & 8 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 24 \\ 0 \\ 0 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 4 & -2 & 0 \\ -2 & 9 & -4 \\ 0 & -4 & 8 \end{vmatrix}$$

$$\Delta = 4 [9 \times 8 - (-4 \times 4)] - (-2) [(-2 \times 8) - 0] + 0$$

$$\Delta = 4[72 - 16] + 2[-16]$$

$$\Delta = 4[56] - 32 = 224 - 32$$

$$\Delta = 192$$

$$\Delta I_2 = \begin{vmatrix} 4 & 24 & 0 \\ -2 & 0 & -4 \\ 0 & 0 & 8 \end{vmatrix}$$


$$\Delta I_2 = -24(-16) = 384$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{384}{192} = 2 \text{ Amps}$$

When E_1 is working:

$$\text{Current through } 3\Omega \text{ Resistor} = I_2 = 2 \text{ Amps}$$

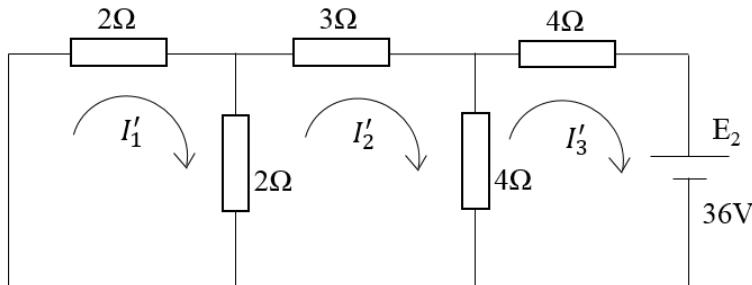Step 2: Voltage Source E_2 is Working and E_1 is replaced by its internal resistance.



$$\begin{vmatrix} 4 & -2 & 0 \\ -2 & 9 & -4 \\ 0 & -4 & 8 \end{vmatrix} \begin{vmatrix} I'_1 \\ I'_2 \\ I'_3 \end{vmatrix} = \begin{vmatrix} 0 \\ 0 \\ -36 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 4 & -2 & 0 \\ -2 & 9 & -4 \\ 0 & -4 & 8 \end{vmatrix}$$

$$\Delta = 192$$

$$\Delta I'_2 = \begin{vmatrix} 4 & 0 & 0 \\ -2 & 0 & -4 \\ 0 & -36 & 8 \end{vmatrix}$$

$$\Delta I'_2 = 4(0 - 144) = 4(-144)$$

$$\Delta I'_2 = -576$$

$$I'_2 = \frac{\Delta I'_2}{\Delta} = \frac{-576}{192} = -3 \text{Amps}$$

When E_2 is working:

$$\begin{aligned} \text{Current through } 10\Omega \text{ Resistor} &= I'_2 \\ &= -3 \text{ Amps} \end{aligned}$$

When E_1 and E_2 are working:

$$\begin{aligned} \text{Current through } 10\Omega \text{ Resistor} &= I_1 + I_2 \\ &= 2 + (-3) \\ &= 2 - 3 \\ &= -1 \text{ Amps} \end{aligned}$$

$$\begin{aligned} \text{Voltage drop across } 3\Omega \text{ Resistor} &= \text{Current through } 3\Omega \text{ resistor} \times 3 \\ &= -1 \times 3 = -3 \text{ Volts} \end{aligned}$$

Answer:

$$\begin{aligned} \text{Current through } 3\Omega \text{ Resistor} &= -1 \text{ Amps} \\ \text{Voltage drop across } 3\Omega \text{ Resistor} &= -3 \text{ Volts} \end{aligned}$$

2.11 Thevenin's theorem:

Thevenin's theorem provides a method for simplifying a circuit to a standard equivalent form. This theorem can be used to simplify the analysis of complex circuits.

Statement:

Any linear bilateral network may be reduced to a simplified two-terminal circuit consisting of a single voltage source (V_{th}) in series with a single resistor (R_{th})


Procedure:

- i) Remove the load resistance R_L and put an open circuit across terminals.
- ii) Find the voltage across open circuited terminals (V_{th} or V_{oc})
- iii) Find the equivalent resistance R_{th} as seen from open circuited terminals by replacing the voltage source by its internal resistance.
- iv) Draw the thevenin's equivalent circuit by a voltage V_{th} in series with the equivalent resistance R_{th}


v) Find the current through R_L by applying ohms law.

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

Explanation:

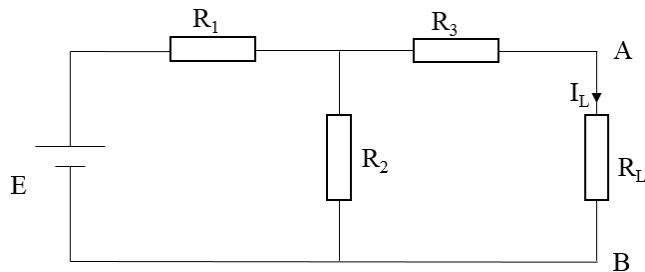

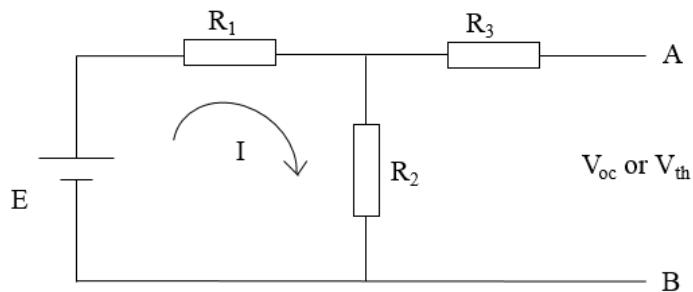
Step 1: Open Circuit the Load Resistor (R_L)




Step 2: Find Open Circuit Voltage (V_{th})

$$\begin{aligned} V_{th} &= \text{P.D across terminals A} \\ \text{P.D across terminals A and B} &= \text{P.D across } R_2 \text{ Resistor} \\ V_{th} &= I \times R_2 \\ I &= \frac{E}{(R_1 + R_2)} \\ V_{th} &= \frac{E \cdot R_2}{(R_1 + R_2)} \end{aligned}$$

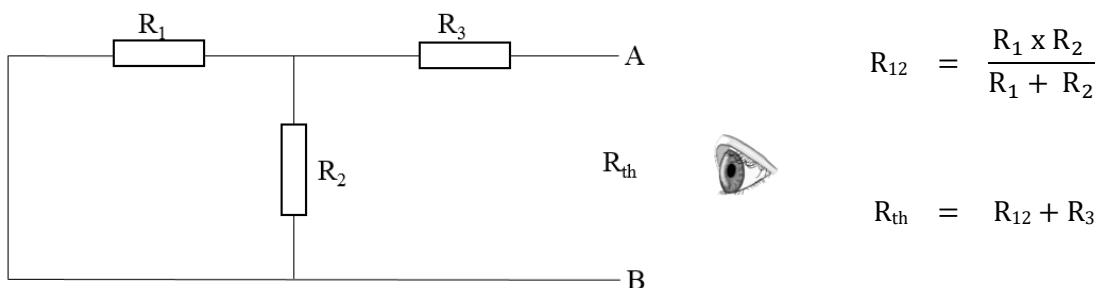Step 3: Find Thevenin's equivalent Resistance: R_{th}



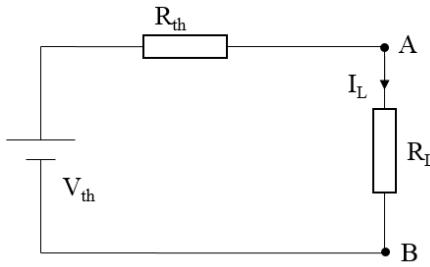Step 4: Draw Thevenin's equivalent circuit




Step 5: Find the Load Current (I_L):

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

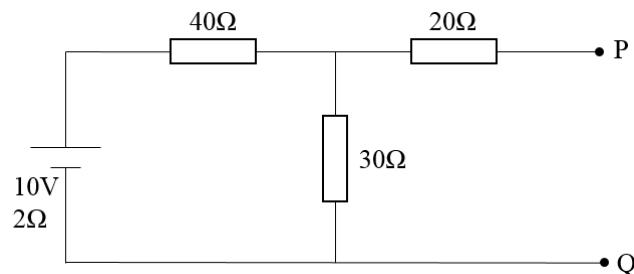Example: 17

Obtain the Thevenin's equivalent circuit at terminals PQ of the following active network.



Given Data:


Supply Voltage = 10V

To Find:

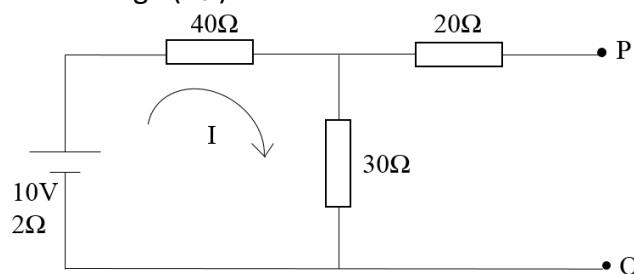i) Draw thevenin's equivalent circuit

Solution:

Step 1: Find Open Circuit Voltage (V_{th})



V_{th} = P.D across terminals P and Q (or)

P.D across terminals P and Q = P.D across 30Ω Resistor


V_{th} = $I \times 30$

$$I = \frac{10}{(40 + 30 + 2)} = \frac{10}{72} = 0.14 \text{ Amps}$$

$$V_{th} = 0.14 \times 30$$


$$V_{th} = 4.2 \text{ Volts}$$

Step 2: Find R_{th}

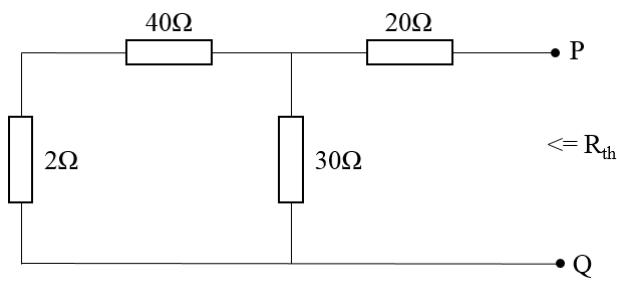


$$\begin{aligned}
 R_{12} &= R_1 + R_2 \\
 R_{12} &= 2 + 40 = 42 \Omega \\
 R_{123} &= \frac{R_{12} \times R_3}{R_{12} + R_3} = \frac{42 \times 30}{42 + 30} = \frac{1260}{72} \\
 R_{123} &= 17.5 \Omega \\
 R_{th} &= R_{123} + R_4 \\
 R_{th} &= 17.5 + 20 \\
 R_{th} &= 37.5 \Omega
 \end{aligned}$$

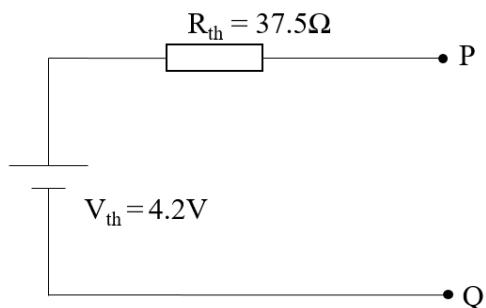Step 3: Draw thevenin's equivalent circuit



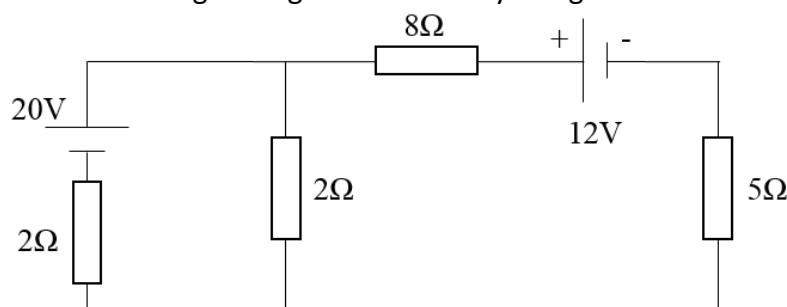Example: 18

Determine the current flowing through 5Ω resistor by using Thevenin's theorem.



Given Data:


Load Resistance $= 5 \Omega$

To Find:

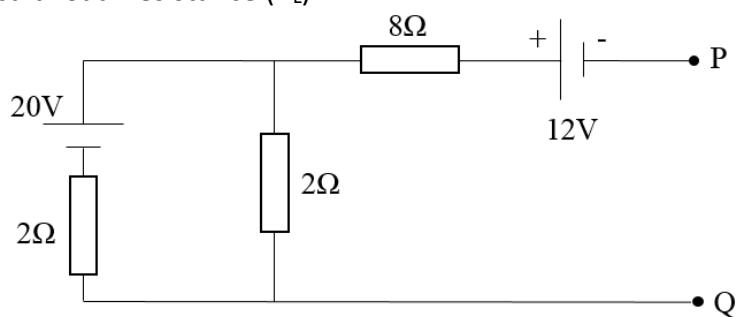
i) Current through 5Ω Resistor = ?

Solution:

Step 1: Open Circuit Load Resistance (R_L)



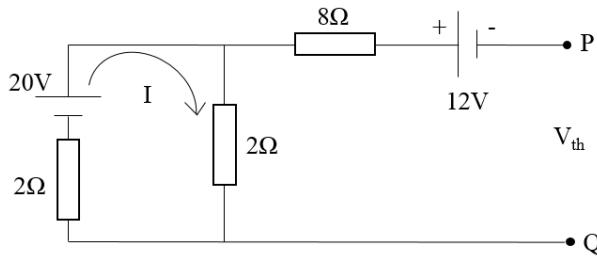Step 1: Find Open Circuit Voltage (V_{th})



$V_{th} = \text{P.D across terminals P and Q}$ (or)

P.D across terminals P and Q = P.D across 2Ω Resistor - 12V

$$V_{th} = I \times 30$$


$$I = \frac{20}{(2+2)} = \frac{20}{4} = 5 \text{Amps}$$

$$V_{th} = (5 \times 2) - 12$$

$$V_{th} = 10 - 12$$

$$V_{th} = -2 \text{V}$$

Step 2: Find R_{th}

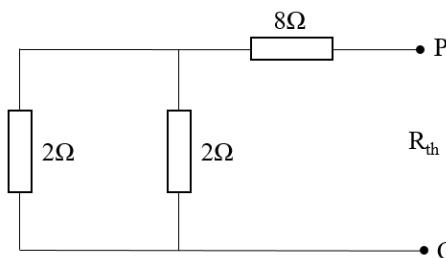


$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{2 \times 2}{2 + 2} = \frac{4}{4} = 1 \Omega$$

$$R_{th} = R_{12} + R_3 = 1 + 8 = 9 \Omega$$

$$R_{th} = 9 \Omega$$

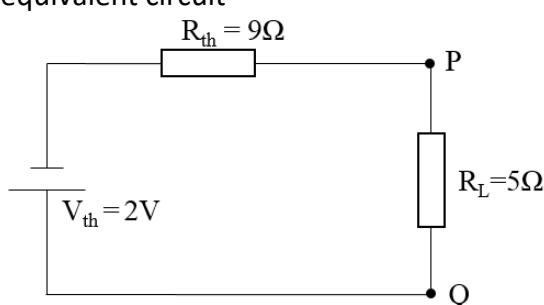Step 3: Draw thevenin's equivalent circuit



Step 3: Find the Load Current (I_L):

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{-2}{9 + 5} = \frac{-2}{14}$$


$$I_L = -0.143 \text{ Amps}$$

Answer:

Current through 5Ω Resistor = -0.143 Amps

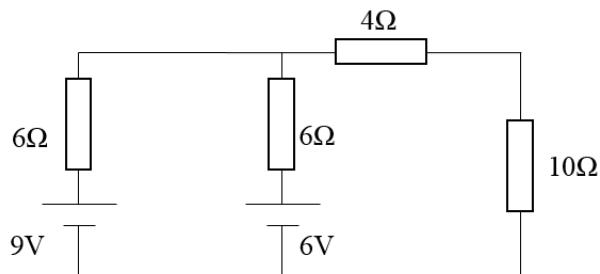Example: 19

Determine the current flowing through 10Ω resistor by using Thevenin's theorem.



Given Data:


$$\text{Load Resistance} = 10\Omega$$

To Find:


$$\text{i) Current through } 10\Omega \text{ Resistor} = ?$$

Solution:

Step 1: Open Circuit Load

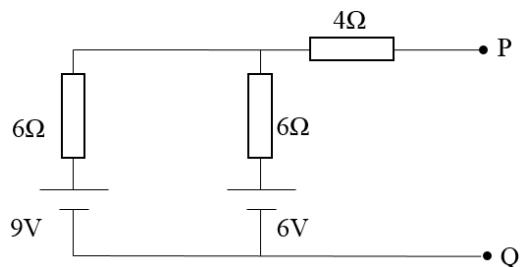

Step 1: Find Open Circuit

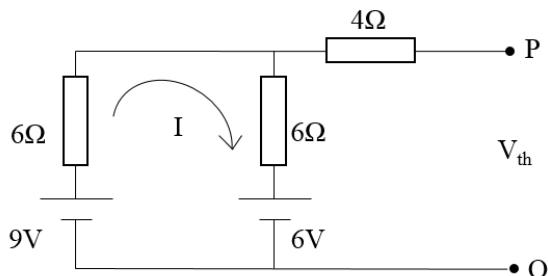

$$V_{th} = 9V - \text{P.D across } 6\Omega \text{ (or)} 6V + \text{P.D across } 6\Omega$$

$$\text{P.D across } 6\Omega \text{ Resistor} = I \times 6$$

$$I = \frac{9 - 6}{(6 + 6)} = \frac{3}{12} = 0.25 \text{ Amps}$$


$$\text{P.D across } 6\Omega \text{ Resistor} = 0.25 \times 6 = 1.5V$$

$$V_{th} = 9 - 1.5 = 7.5V \text{ (or)}$$

$$V_{th} = 6 + 1.5 = 7.5V$$

$$V_{th} = 7.5V$$

Step 2: Find R_{th}

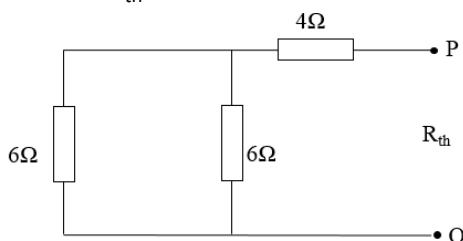


$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{6 \times 6}{6 + 6} = \frac{36}{12}$$

$$R_{12} = 3 \Omega$$

$$R_{th} = R_{12} + R_3 = 3 + 4 = 7 \Omega$$

$$R_{th} = 7 \Omega$$

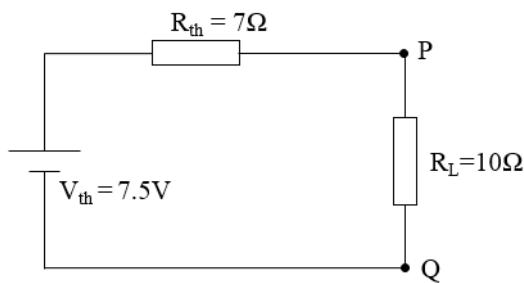Step 3: Draw thevenin's equivalent circuit



Step 3: Find the Load Current (I_L):

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{7.5}{7 + 10} = \frac{7.5}{17}$$


$$I_L = 0.44 \text{ Amps}$$

Answer:

$$\text{Current through } 10\Omega \text{ Resistor} = 0.44 \text{ Amps}$$

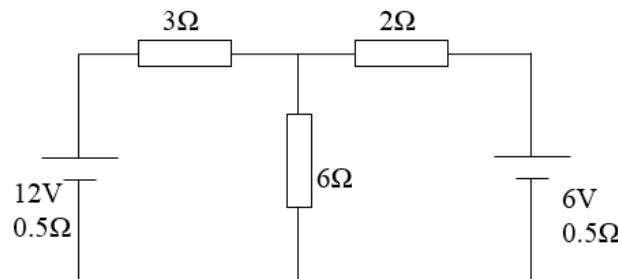Example: 20

Determine the current flowing through 6Ω resistor by using Thevenin's theorem.




Given Data:

To Find:

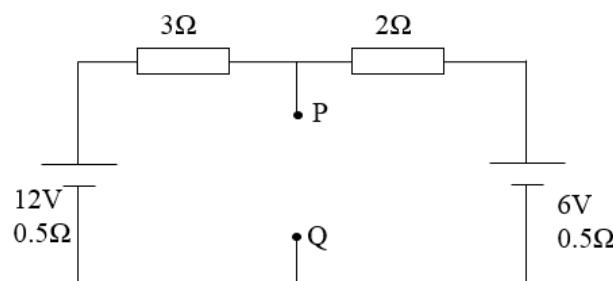
i) Current through 6Ω Resistor = ?

Solution:

Step 1: Open Circuit Load Resistance (R_L)



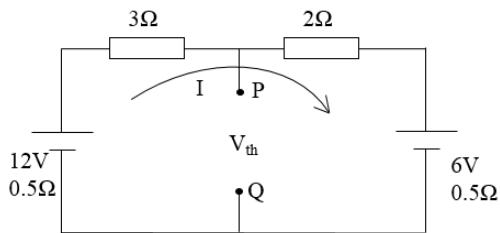Step 1: Find Open Circuit Voltage (V_{th})



$$V_{th} = 12V - \text{P.D across } 3.5\Omega \text{ Resistor} \quad (\text{or})$$

$$= 6V + \text{P.D across } 2.5\Omega \text{ Resistor}$$

$$\text{P.D across } 3\Omega \text{ Resistor} = I \times 3.5$$

$$I = \frac{12 - 6}{(3 + 2 + 0.5 + 0.5)} = \frac{6}{6} = 1 \text{ Amps}$$


$$\text{P.D across } 3\Omega \text{ Resistor} = 1 \times 3.5 = 3.5V$$

$$V_{th} = 12 - 3.5 = 8.5V \quad (\text{or})$$

$$V_{th} = 6 + 2.5 = 8.5V$$

$$V_{th} = 8.5V$$


Step 2: Find R_{th}

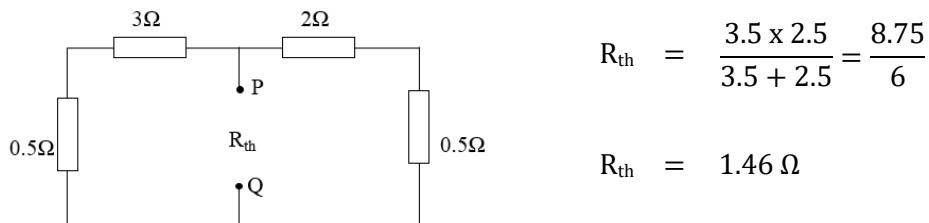

$$R_{th} = \frac{3.5 \times 2.5}{3.5 + 2.5} = \frac{8.75}{6}$$

$$R_{th} = 1.46 \Omega$$

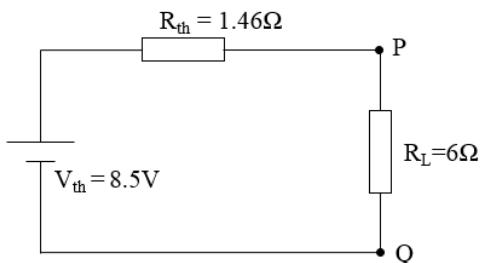Step 3: Draw thevenin's equivalent circuit



Step 3: Find the Load Current (I_L):

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{8.5}{1.46 + 6} = \frac{8.5}{7.46}$$


$$I_L = 1.14 \text{ Amps}$$

Answer:

$$\text{Current through } 6\Omega \text{ Resistor} = 1.14 \text{ Amps}$$

Example: 21

Find the current through 10Ω load resistor using Thevenin's Theorem.

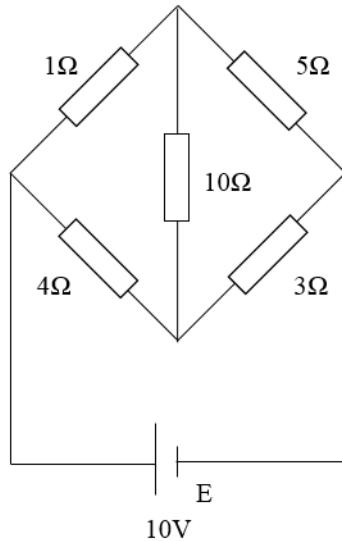**Given Data:**


$$\text{Supply Voltage} = 10V$$

To Find:

$$\text{i) Current through } 10\Omega \text{ Resistor} = ?$$

Solution:

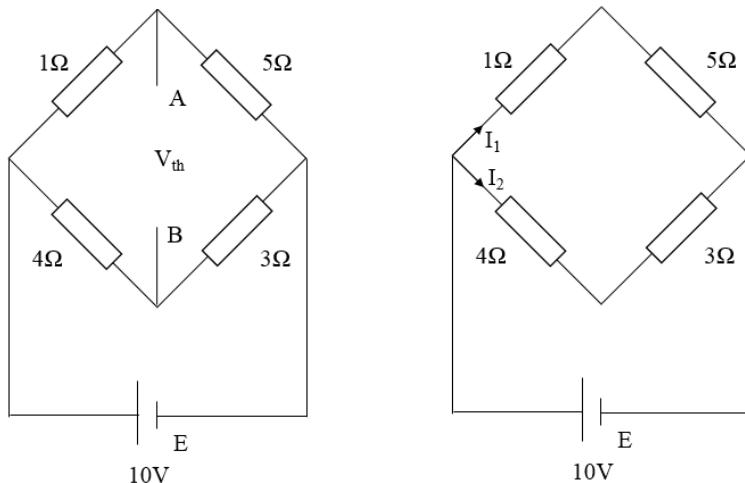Step 1: Open Circuit Load Resistance (R_L)



Step 1: Find Open Circuit Voltage (V_{th})

$$V_{th} = \text{Voltage at point A} - \text{Voltage at point B}$$

$$V_{th} = V_A - V_B$$

$$V_A = \text{Supply Voltage} - \text{P.D across } 1\Omega \text{ Resistor}$$

$$\text{P.D across } 1\Omega \text{ Resistor} = I_1 \times 1$$

$$I_1 = \frac{10}{1 + 5} = \frac{10}{6} = 1.67 \text{ Amps}$$

$$\text{P.D across } 1\Omega \text{ Resistor} = 1.67 \times 1 = 1.67V$$

$$V_B = \text{Supply Voltage} - \text{P.D across } 1\Omega \text{ Resistor}$$

$$\text{P.D across } 4\Omega \text{ Resistor} = I_2 \times 4$$

$$I_2 = \frac{10}{4+3} = \frac{10}{7} = 1.43 \text{ Amps}$$


$$\text{P.D across } 4\Omega \text{ Resistor} = 1.43 \times 4 = 5.72\text{V}$$

$$V_{th} = V_A - V_B$$

$$V_{th} = 1.67 - 5.72 = -4.05\text{V}$$

$$V_{th} = -4.05\text{V}$$

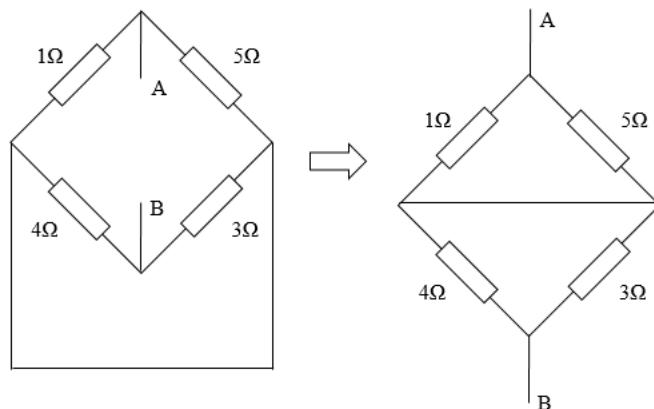Step 3: Find Thevenin's equivalent Resistance R_{th}



Step 2: Find R_{th}


$$R_{th} = \left(\frac{1 \times 5}{1+5} \right) + \left(\frac{4 \times 3}{4+3} \right)$$

$$R_{th} = \left(\frac{5}{6} \right) + \left(\frac{12}{7} \right)$$

$$R_{th} = 0.833 + 1.71$$

$$R_{th} = 2.54 \Omega$$

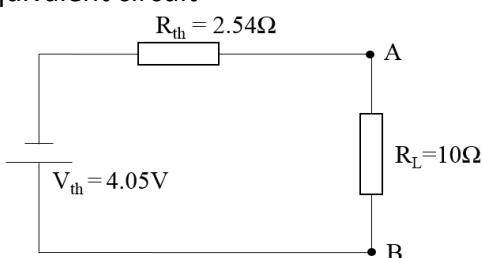Step 4: Draw Thevenin's equivalent circuit



Step 3: Find the Load Current (I_L):

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{4.05}{2.54 + 10} = \frac{4.05}{12.54}$$

$$I_L = 0.32 \text{ Amps}$$

Answer:

$$\text{Current through } 10\Omega \text{ Resistor} = 0.32 \text{ Amps}$$

2.12 Norton's Theorem:

Norton's theorem is a method for simplifying a two terminal linear circuit to an equivalent circuit with only a current source in parallel with a resistor. This basic difference between Thevenin's Theorem and Norton's theorem is that, Norton's theorem results in an equivalent source in parallel with an equivalent resistance. The equivalent current source is designated I_N , and the equivalent resistance is designated R_N . To apply Norton's theorem, you must know how to find the two quantities I_N and R_N .

Statement:

Norton's theorem states that any two terminal network can be replaced by a single current source I_N in parallel with a single resistance R_N .


Procedure:

- i) Remove the load resistance R_L and put a short circuit across terminals.
- ii) Find the short circuit current (I_N or I_{SC})
- iii) Find the equivalent resistance R_N as seen from open circuited terminals by replacing the voltage source by its internal resistance.
- iv) Draw the Norton's equivalent circuit by a current I_{SC} in series with the equivalent resistance R_{th} or R_N
- v) Find the current through R_L by applying current divider rule.


$$I_L = \frac{I_N \times R_N}{R_N + R_L}$$

Explanation:

Unit: 2

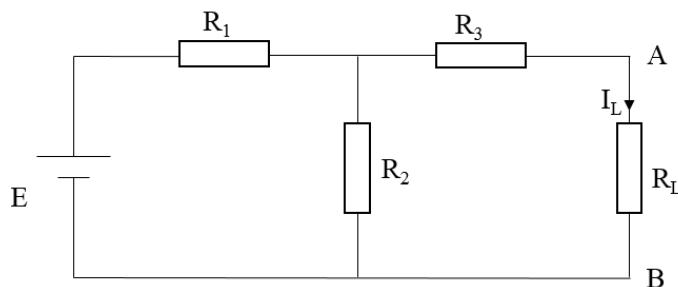

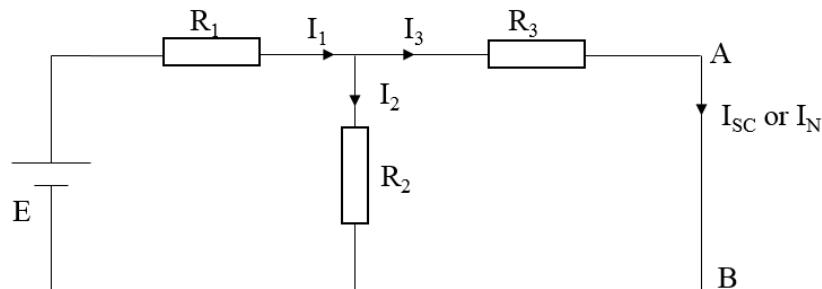Step 1: Remove the Load Resistor (R_L) and Short circuit its terminals.



Step 2: Find Short Circuit Current or Norton's Current (I_{SC} or I_N)

I_{SC} or I_N = Current through branch A and B

$$I_{SC} \text{ or } I_N = I_3$$


$$\text{Equivalent Resistance } R_{eq} = R_1 + \left(\frac{R_2 \times R_3}{R_2 + R_3} \right)$$

$$\text{Current } I_1 = \frac{E}{R_{eq}}$$

$$\text{Current through Shorted path}(I_{SC} \text{ or } I_N) = I_3$$

$$\text{So, } I_{SC} \text{ or } I_N = \frac{I_1 \times R_2}{R_2 + R_3}$$

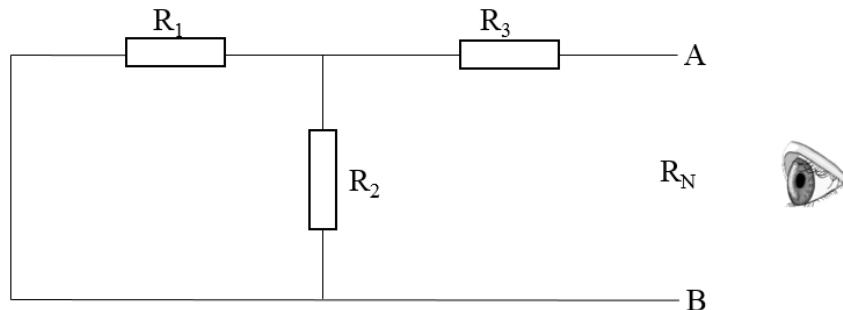
Step 3: Find R_N (Equivalent Resistance between Terminal A and B)



$$R_{12} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_N = R_{12} + R_3$$

Step 4: Draw Norton's equivalent circuit

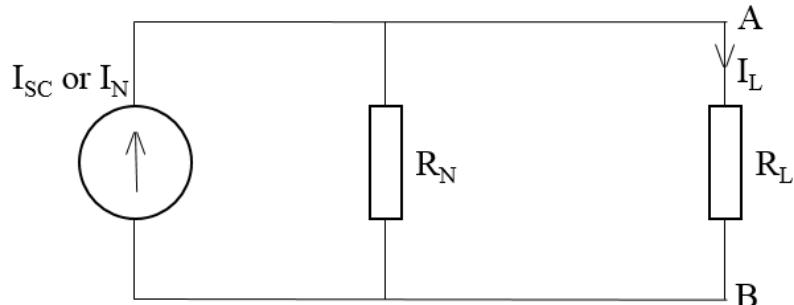


Step 5: Find the Load Current (I_L):

$$I_L = \frac{I_N \times R_N}{R_N + R_L}$$

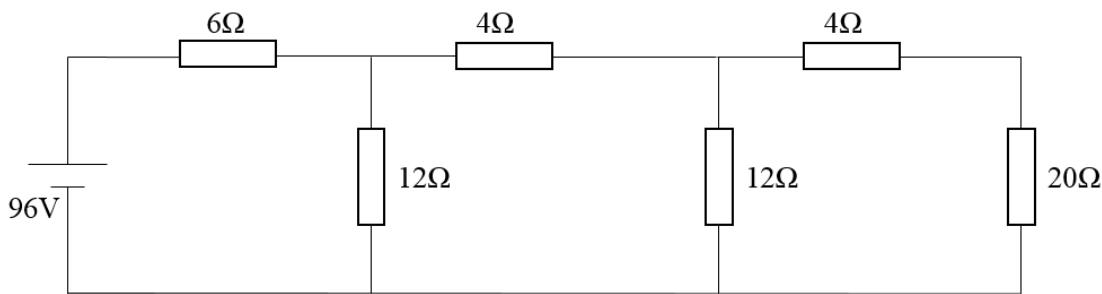Example: 22

Find the current through 20Ω load resistor using Norton's Theorem.



Given Data:


$$\text{Supply Voltage} = 96V$$

To Find:

$$\text{i) Current through } 20\Omega \text{ Resistor} = ?$$

Solution:

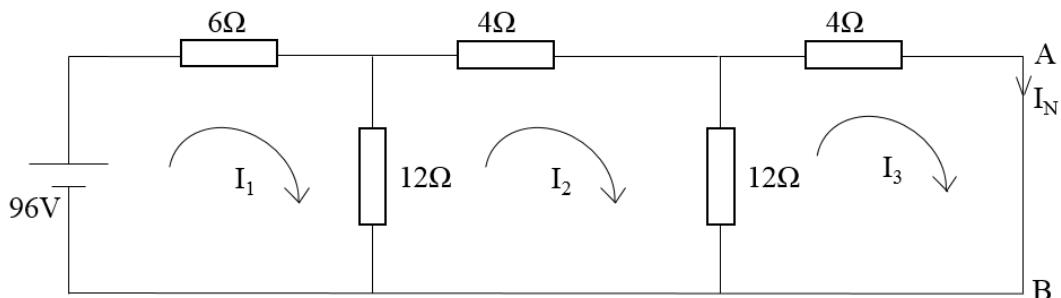Step 1: Remove the Load Resistance and Short Circuit its terminal.



Step 2: Find Current through short circuited Terminals I_N

$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \\ V_3 \end{vmatrix}$$

$$\begin{vmatrix} 18 & -12 & 0 \\ -12 & 28 & -12 \\ 0 & -12 & 16 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 96 \\ 0 \\ 0 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 18 & -12 & 0 \\ -12 & 28 & -12 \\ 0 & -12 & 16 \end{vmatrix}$$

$$\Delta = 18[28 \times 16 - (-12 \times -12)] + 12[(-12 \times 16) - 0] + 0$$

$$\Delta = 18[448 - 144] + 12[-192]$$

$$\Delta = 5472 - 2304$$

$$\Delta = 3168$$

$$\Delta I_3 = \begin{vmatrix} 18 & -12 & 96 \\ -12 & 28 & 0 \\ 0 & -12 & 0 \end{vmatrix}$$


$$\Delta I_3 = 18(0) - 12(0) + 96[(-12 \times -12) - (0 \times 28)]$$

$$\Delta I_3 = 96 \times 144$$

$$\Delta I_3 = 13824$$


$$\begin{aligned}
 I_3 &= \frac{\Delta I_3}{\Delta} \\
 I_3 &= \frac{13824}{3168} \\
 I_3 &= 4.36 \text{Amps} \\
 I_3 = I_N &= 4.36 \text{Amps}
 \end{aligned}$$

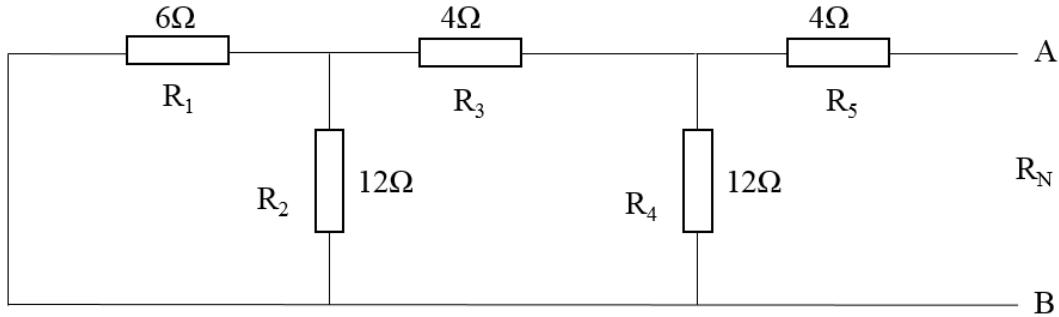Step 3: Find Norton equivalent Resistance R_N



$$\begin{aligned}
 R_{12} &= \frac{R_1 \times R_2}{R_1 + R_2} = \frac{6 \times 12}{6 + 12} = \frac{72}{18} = 4\Omega \\
 R_{123} &= R_{12} + R_3 \\
 &\quad 4 + 4 = 8\Omega \\
 R_{1234} &= \frac{R_{123} \times R_4}{R_{123} + R_4} = \frac{8 \times 12}{8 + 12} = \frac{96}{20} = 4.8\Omega \\
 R_N &= R_{1234} + R_5 \\
 R_{th} &= 4.8 + 4 \\
 R_N &= 8.8 \Omega
 \end{aligned}$$

Step 4: Draw Norton's equivalent circuit

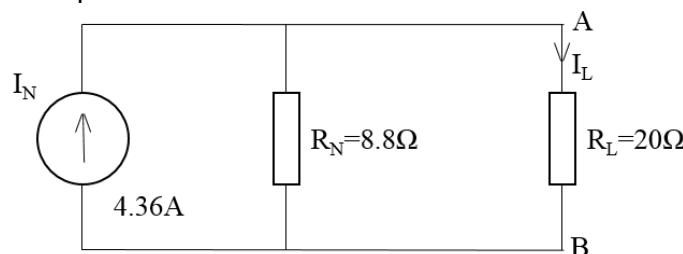

Step 5: Find Load Current (I_L)


$$\begin{aligned}
 I_L &= \frac{I_N \times R_N}{R_N + R_L} \\
 I_L &= \frac{4.36 \times 8.8}{8.8 + 20} = \frac{38.37}{28.8} = 1.33 \text{ Amps} \\
 I_L &= 1.33 \text{ Amps}
 \end{aligned}$$

Answer:

Current through 10Ω Resistor = 1.33 Amps

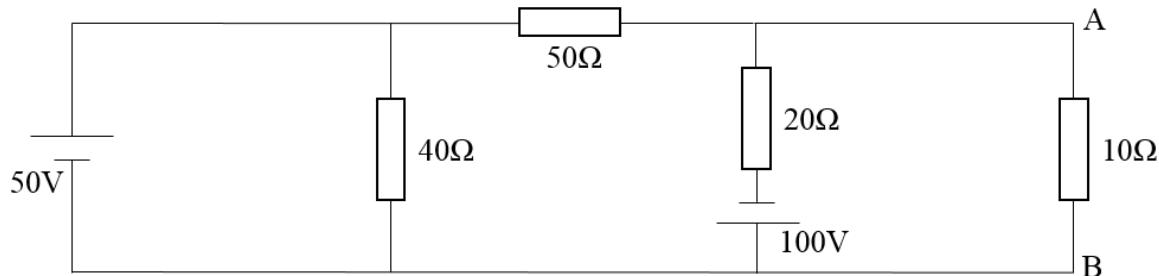Example: 23

Calculate the current flow through 10Ω resistor by using Norton's theorem.



Given Data:


$$\begin{aligned} \text{Voltage source } E_1 &= 50V \\ \text{Voltage source } E_2 &= 100V \end{aligned}$$

To Find:

$$\text{i) Current through } 10\Omega \text{ Resistor} = ?$$

Solution:

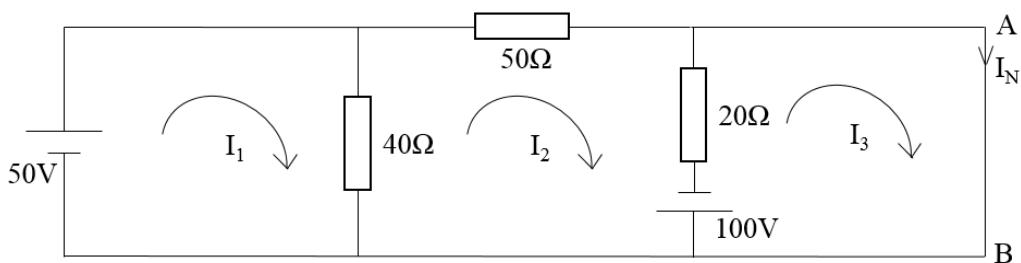Step 1: Remove the Load Resistance and Short Circuit its terminal.



Step 2: Find Current through short circuited Terminals I_N

$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \\ V_3 \end{vmatrix}$$

$$\begin{vmatrix} 40 & -40 & 0 \\ -40 & 110 & -20 \\ 0 & -20 & 20 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 50 \\ 100 \\ -100 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 40 & -40 & 0 \\ -40 & 110 & -20 \\ 0 & -20 & 20 \end{vmatrix}$$

$$\Delta = 40[110 \times 20 - (-20 \times -20)] + 40 [(-40 \times 20) - 0] + 0$$

$$\Delta = 40[2200 - 400] + 40(-800)$$

$$\Delta = 72000 - 32000$$

$$\Delta = 40000$$

$$\Delta I_3 = \begin{vmatrix} 40 & -40 & 50 \\ -40 & 110 & 100 \\ 0 & -20 & -100 \end{vmatrix}$$


$$\Delta I_3 = 40(-1100 + 2000) + 40(4000) + 50(800)$$

$$\Delta I_3 = -360000 + 160000 + 40000$$

$$\Delta I_3 = -160000$$


$$\begin{aligned}
 I_3 &= \frac{\Delta I_3}{\Delta} \\
 I_3 &= \frac{-160000}{40000} \\
 I_3 &= -4 \text{ Amps} \\
 I_3 = I_N &= -4 \text{ Amps}
 \end{aligned}$$

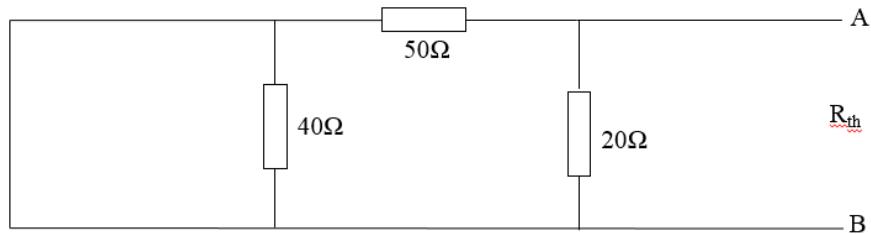Step 3: Find Norton equivalent Resistance R_N



$$\begin{aligned}
 R_N &= \frac{50 \times 20}{50 + 20} = \frac{1000}{70} = 14.29\Omega \\
 R_N &= 14.29 \Omega
 \end{aligned}$$

Step 4: Draw Norton's equivalent circuit

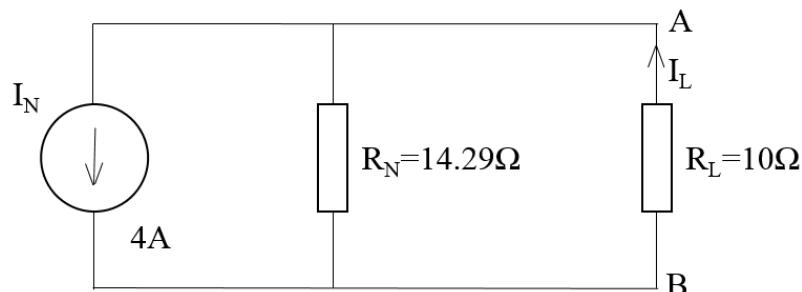

Step 5: Find Load Current (I_L)

$$\begin{aligned}
 I_L &= \frac{I_N \times R_N}{R_N + R_L} \\
 I_L &= \frac{-4 \times 14.29}{14.29 + 10} = \frac{-57.16}{24.29} = -2.35 \text{ Amps} \\
 I_L &= -2.35 \text{ Amps}
 \end{aligned}$$


$$\begin{aligned}
 \text{Voltage across } 10\Omega \text{ Resistor} \quad V_L &= I_L \times R_L \\
 V_L &= -2.35 \times 10 \\
 V_L &= -23.5 \text{ Volts}
 \end{aligned}$$

Answer:

$$\begin{aligned}
 \text{Current through } 10\Omega \text{ Resistor} &= -2.35 \text{ Amps} \\
 \text{Voltage drop across } 10\Omega \text{ Resistor} &= -23.5 \text{ Volts}
 \end{aligned}$$

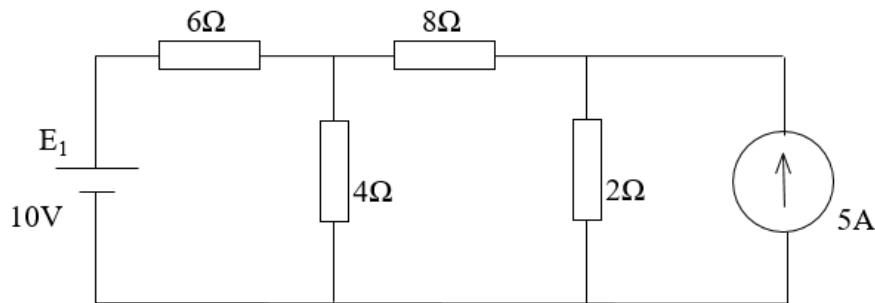Example: 24

Find the current through 4Ω resistance by using Norton's theorem.



Given Data:


$$\begin{aligned} \text{Voltage source } E_1 &= 50\text{V} \\ \text{Voltage source } E_2 &= 100\text{V} \end{aligned}$$

To Find:


$$\text{i) Current through } 10\Omega \text{ Resistor} = ?$$

Solution:

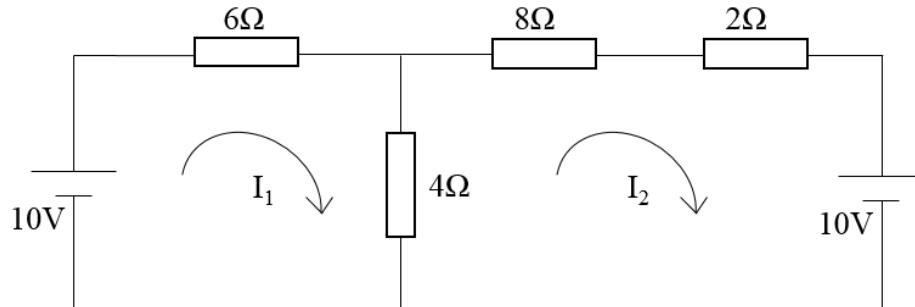Convert the given current source into equivalent voltage source.



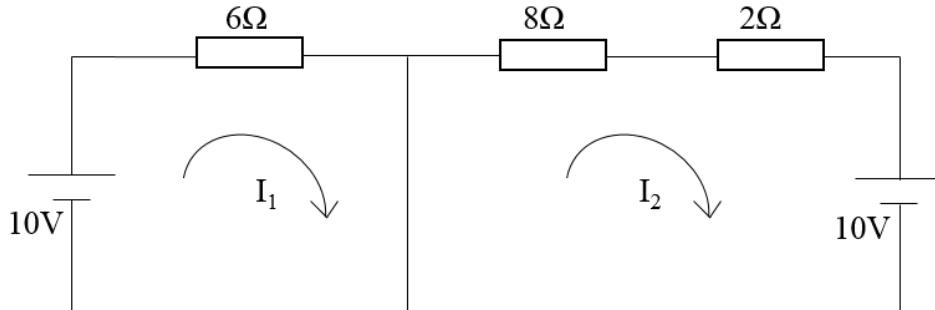Step 1: Remove the Load Resistance and Short Circuit its terminal.



Step 2: Find Current through short circuited Terminals I_N

$$\begin{vmatrix} R_{11} & -R_{12} \\ -R_{21} & R_{22} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \end{vmatrix}$$

$$\begin{vmatrix} 6 & 0 \\ 0 & 10 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 10 \\ -10 \end{vmatrix}$$


$$\Delta = \begin{vmatrix} 6 & 0 \\ 0 & 10 \end{vmatrix}$$

$$\Delta = 60$$

$$\Delta I_1 = \begin{vmatrix} 10 & 0 \\ -10 & 10 \end{vmatrix}$$


$$\begin{aligned}\Delta I_1 &= 100 \\ I_1 &= \frac{\Delta I_1}{\Delta} = \frac{100}{60} = 1.67 \text{ Amps} \\ \Delta I_2 &= \begin{vmatrix} 6 & 10 \\ 0 & -10 \end{vmatrix} \\ \Delta I_2 &= -60 \\ I_2 &= \frac{\Delta I_2}{\Delta} = \frac{-60}{60} = -1 \text{ Amps} \\ I_2 &= 0.67 \text{ Amps} \\ I_N &= I_1 - I_2 \\ I_N &= 1.67 - (-1) = 2.67 \text{ Amps}\end{aligned}$$

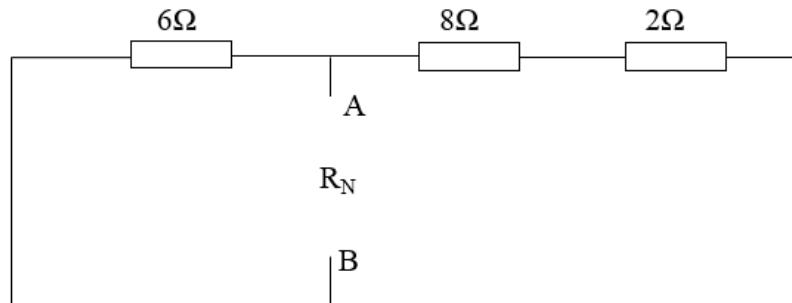Step 3: Find Norton equivalent Resistance R_N



$$\begin{aligned}R_N &= \frac{6 \times 10}{6 + 10} = \frac{60}{16} = 3.75 \Omega \\ R_N &= 3.75 \Omega\end{aligned}$$

Step 4: Draw Norton's equivalent circuit

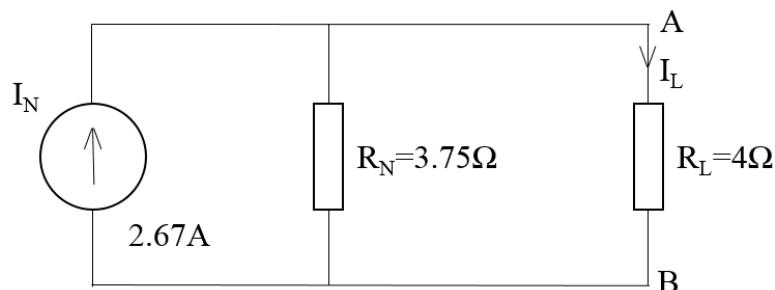

Step 5: Find Load Current (I_L)

$$\begin{aligned}I_L &= \frac{I_N \times R_N}{R_N + R_L} \\ I_L &= \frac{2.67 \times 3.75}{3.75 + 4} = \frac{2.51}{7.75} = 1.29 \text{ Amps}\end{aligned}$$


Current through 4Ω Resistance $I_L = 1.29 \text{ Amps}$

Answer:

Current through 4Ω Resistor = 1.29 Amps

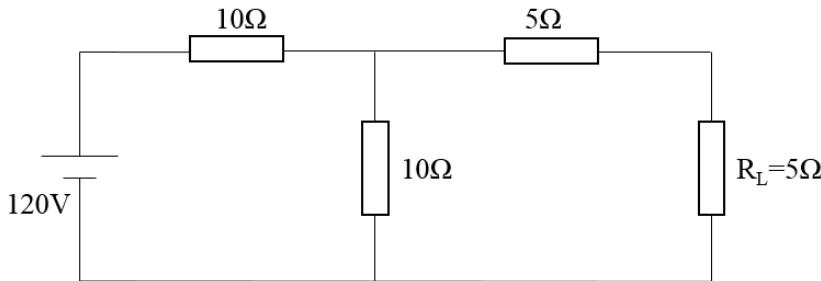Example: 25

Using Norton's theorem find the current in the load resistance R_L of the circuit given below.



Given Data:


$$\begin{aligned} \text{Voltage source } E_1 &= 120\text{V} \\ \text{Load Resistance } R_L &= 5\Omega \end{aligned}$$

To Find:

$$\text{i) Current through } 10\Omega \text{ Resistor} = ?$$

Solution:

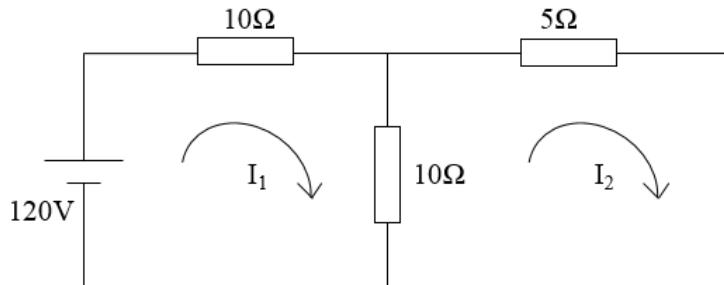Step 1: Remove the Load Resistance and Short Circuit its terminal.



Step 2: Find Current through short circuited Terminals I_N

$$\begin{vmatrix} R_{11} & -R_{12} \\ -R_{21} & R_{22} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \end{vmatrix}$$

$$\begin{vmatrix} 20 & -10 \\ -10 & 15 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} 120 \\ 0 \end{vmatrix}$$


$$\Delta = \begin{vmatrix} 20 & -10 \\ -10 & 15 \end{vmatrix} = 300 - 100 = 200$$

$$\Delta I_2 = \begin{vmatrix} 20 & 120 \\ -10 & 0 \end{vmatrix} = 1200$$


$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{1200}{200} = 6 \text{ Amps}$$

$$I_2 = I_N = 6 \text{ Amps}$$

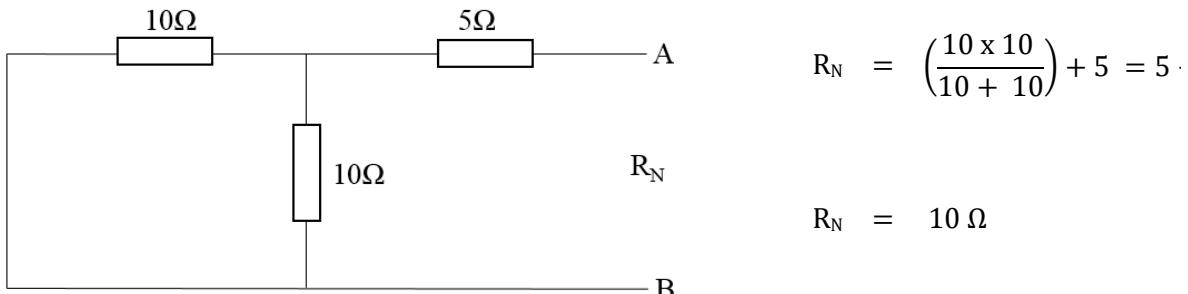Step 3: Find Norton equivalent Resistance R_N



Step 4: Draw Norton's equivalent circuit

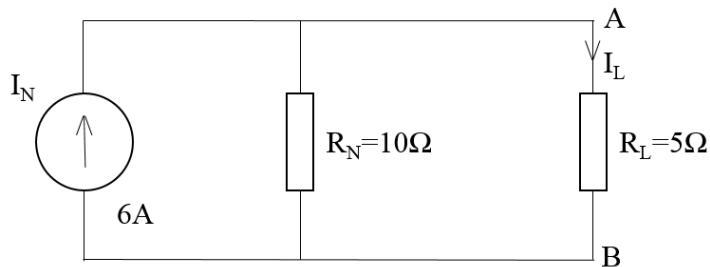

Step 5: Find Load Current (I_L)

$$I_L = \frac{I_N \times R_N}{R_N + R_L}$$

$$I_L = \frac{6 \times 10}{10 + 5} = \frac{60}{15} = 4 \text{ Amps}$$


Current through 5Ω Resistor $I_L = 4 \text{ Amps}$

Answer:

Current through 5Ω Resistor = 4 Amps

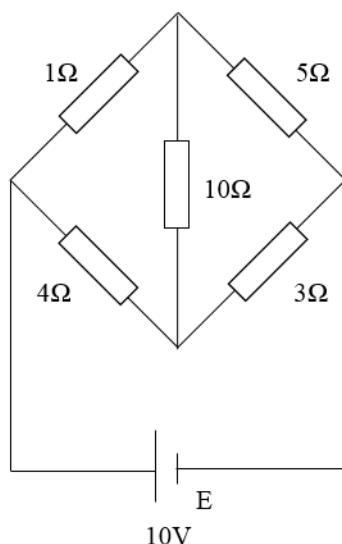Example: 26

Find the current through 10Ω load resistor using Norton's Theorem.



Given Data:


| | |
|-----------------------|-------|
| Voltage source E | = 10V |
| Load Resistance R_L | = 10Ω |

To Find:

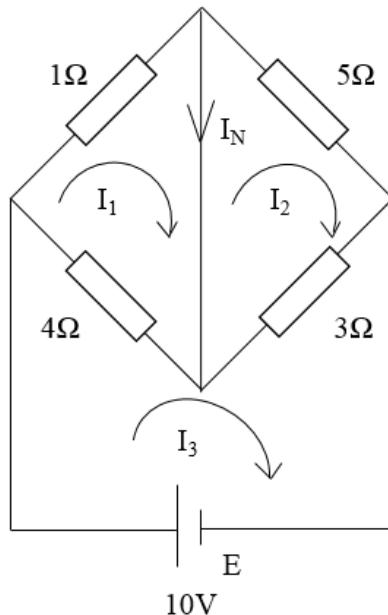i) Current through 10Ω Resistor = ?

Solution:

Step 1: Remove the Load Resistance and Short Circuit its terminal.



Step 2: Find Current through short circuited Terminals I_N

$$\begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} V_1 \\ V_2 \\ V_3 \end{vmatrix}$$

$$\begin{vmatrix} 5 & -0 & -4 \\ -0 & 8 & -3 \\ -4 & -3 & 7 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 0 \\ 0 \\ 10 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 5 & -0 & -4 \\ -0 & 8 & -3 \\ -4 & -3 & 7 \end{vmatrix}$$

$$\Delta = 5(56 - 9) + 0 - 4(0 + 32)$$

$$\Delta = 5(47) - 4(32)$$

$$\Delta = 235 - 128$$

$$\Delta = 107$$

$$\Delta I_1 = \begin{vmatrix} 0 & -0 & -4 \\ 0 & 8 & -3 \\ 10 & -3 & 7 \end{vmatrix}$$

$$\Delta I_1 = -4(0 - 80)$$

$$\Delta I_1 = -4(-80)$$

$$\Delta I_1 = 320$$


$$I_1 = \frac{\Delta I_1}{\Delta}$$

$$I_1 = \frac{320}{107}$$

$$I_1 = 2.99 \text{Amps}$$


$$\begin{aligned}
 \Delta I_2 &= \begin{vmatrix} 5 & 0 & -4 \\ -0 & 0 & -3 \\ -4 & 10 & 7 \end{vmatrix} \\
 \Delta I_2 &= 5(0 + 30) - 0 - 4(0) \\
 \Delta I_2 &= 150 \\
 I_2 &= \frac{\Delta I_1}{\Delta} \\
 I_2 &= \frac{150}{107} \\
 I_2 &= 1.4 \text{ Amps} \\
 \text{Short circuit current } I_N &= I_1 - I_2 \\
 I_N &= 2.99 - 1.4 \\
 I_N &= 1.59 \text{ Amps}
 \end{aligned}$$

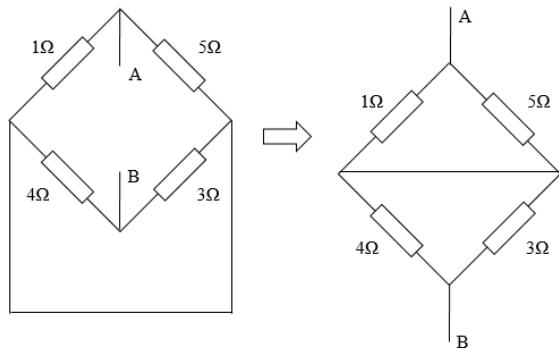Step 3: Find Norton equivalent Resistance R_N



$$\begin{aligned}
 R_N &= \left(\frac{1 \times 5}{1 + 5}\right) + \left(\frac{4 \times 3}{4 + 3}\right) \\
 R_N &= \left(\frac{5}{6}\right) + \left(\frac{12}{7}\right) \\
 R_N &= 0.833 + 1.71 \\
 R_N &= 2.54 \Omega
 \end{aligned}$$

Step 4: Draw Norton's equivalent circuit

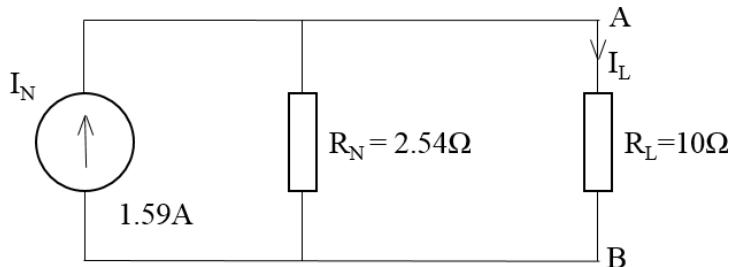

Step 5: Find Load Current (I_L)

$$\begin{aligned}
 I_L &= \frac{I_N \times R_N}{R_N + R_L} \\
 I_L &= \frac{1.59 \times 2.54}{2.54 + 10} = \frac{4.04}{12.54} = 0.32 \text{ Amps} \\
 I_L &= 0.32 \text{ Amps}
 \end{aligned}$$

Answer:

$$\text{Current through } 10\Omega \text{ Resistor} = 0.32 \text{ Amps}$$

2.13 Maximum Power Transfer Theorem:

Statement:

It states that maximum power will be transferred from source to load when load resistance is equal to source resistance.

Procedure:

- i) Remove the load resistance and find the Thevenin's resistance R_{th} of the source network looking through the open circuited load terminals.
- ii) Calculate thevenin's voltage V_{th} or Norton's current I_N
- iii) Draw thevenin's equivalent circuit.
- iv) As per maximum power transfer theorem this R_{th} is the load resistance of the network, i.e., $R_L = R_{th}$
- v) Maximum power is given by,

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

Proof:

Consider the given circuit, which supplies power directly to the load.

Let,


E – Supply Voltage

R_S – Internal Resistance of the Source

R_L – Load Resistance

P_L – Power delivered to the load

I – Circuit Current

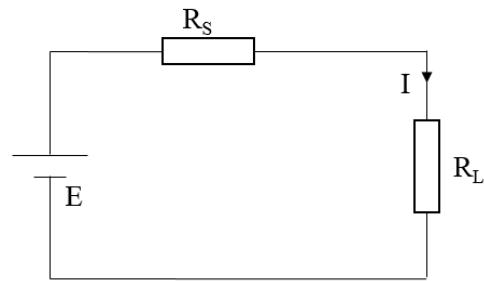

$$\text{Current through Load } (I) = \frac{E}{R_S + R_L} \quad \dots \quad (1)$$

$$\text{Load Power } (P) = I^2 R_L$$

$$\begin{aligned} \text{Load Power } (P) &= \left(\frac{E}{R_S + R_L} \right)^2 R_L \\ P &= \frac{E^2 R_L}{(R_S + R_L)^2} \end{aligned} \quad \dots \quad (2)$$

The power delivery will be maximum when:

$$\frac{dP}{dR_L} = 0 \quad \dots \quad (3)$$

Differentiating the equation (2) w.r.t R_L and equating to zero

$$\frac{d}{dR_L} \left[\frac{E^2 R_L}{(R_S + R_L)^2} \right] = 0$$

$$\frac{E^2 [(R_S + R_L)^2 \cdot 1 - R_L \cdot 2(R_S + R_L)]}{(R_S + R_L)^4} = 0$$

$$\begin{aligned}
 (R_S + R_L)(R_S + R_L) - 2R_L(R_S + R_L) &= 0 \\
 (R_S + R_L)(R_S + R_L) - 2R_L R_S - 2R_L^2 &= 0 \\
 R_S^2 + R_S R_L + R_L R_S + R_L^2 - 2R_L R_S - 2R_L^2 &= 0 \\
 R_S^2 - R_L^2 &= 0 \\
 R_S &= R_L
 \end{aligned} \quad \text{----- (4)}$$

Source Resistance = Load Resistance

Hence from the equation (4), the maximum power is transferred from the source to load when the load resistance equals the source resistance.

Substitute, $R_S = R_L$ in equation (1)

$$I_{\max} = \frac{E}{2R_L}$$

Substitute, $R_S = R_L$ in equation (2)

$$\begin{aligned}
 \text{Maximum Power } (P_{\max}) &= \frac{E^2 R_L}{(R_L + R_L)^2} \\
 P_{\max} &= \frac{E^2 R_L}{(2R_L)^2} \\
 P_{\max} &= \frac{E^2}{4R_L}
 \end{aligned}$$

The total power supplied is, thus


$$P = 2 \frac{V_{th}^2}{4R_{th}} = \frac{V_{th}^2}{2R_{th}}$$

During maximum power transfer, the efficiency becomes

$$\eta = \frac{P_{\max}}{P} \times 100 = 50\%$$

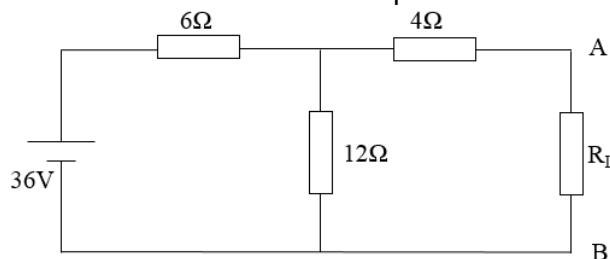Example: 27

For the circuit shown below, find the value of R_L for which the maximum power is transferred from the source. Find the value of that power.



Given Data:


Supply Voltage = 36 V

To Find:

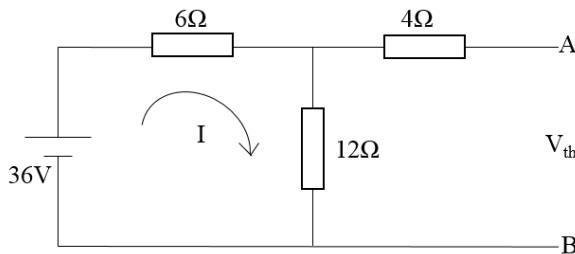- i) Load Resistance (R_L) = ?
- ii) Load Power (P) = ?

Solution:

Step 1: Find Open Circuit Voltage (V_{th})



V_{th} = P.D across 12Ω Resistor


$$V_{th} = I \times 12$$

$$I = \frac{36}{(6 + 12)} = \frac{36}{18} = 2 \text{ Amps}$$

$$V_{th} = 2 \times 12$$

$$V_{th} = 24 \text{ Volts}$$

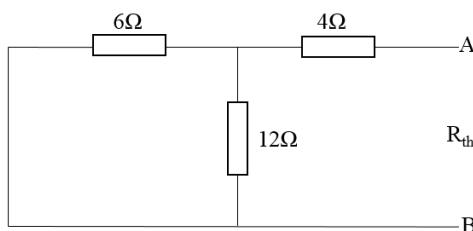Step 2: Find Thevenin Equivalent Resistance (R_{th}):



$$R_{123} = \frac{6 \times 12}{6 + 12} = \frac{72}{18}$$

$$R_{123} = 4 \Omega$$


$$R_{th} = 4 + 4 = 8$$

$$R_{th} = 8 \Omega$$

According to Max. Power Transfer Theorem:

$$R_L = R_{th} = 8 \Omega$$

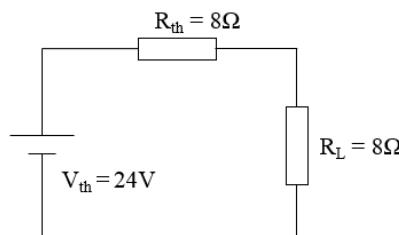Step 3: Draw thevenin's equivalent circuit




Step 4: Calculate Maximum Power:

$$\begin{aligned} \text{Maximum Power } (P_{max}) &= \frac{V_{th}^2}{4R_L} = \frac{24^2}{4 \times 8} = \frac{576}{32} \\ P_{max} &= 18 \text{ Watts} \end{aligned}$$

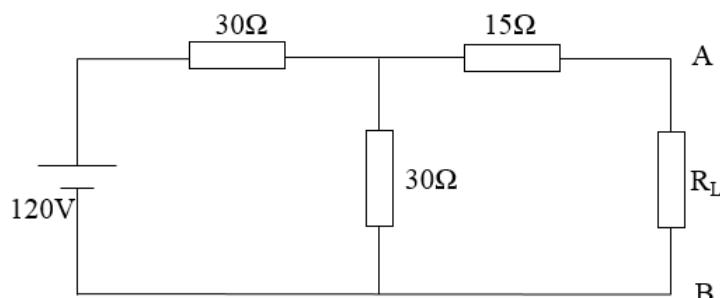Example: 28

Calculate the value of load resistance for maximum power transferred from the circuit shown below. Also find the value of that maximum power.



Given Data:


Supply Voltage = 120 V

To Find:

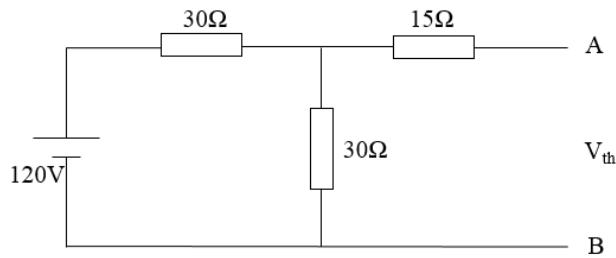- i) Load Resistance (R_L) =?
- ii) Load Power (P) =?

Solution:

Step 1: Find Open Circuit Voltage (V_{th})



V_{th} = P.D across 30Ω Resistor


$$V_{th} = I \times 30$$

$$I = \frac{120}{(30 + 30)} = \frac{120}{60} = 2 \text{ Amps}$$

$$V_{th} = 2 \times 30$$

$$V_{th} = 60 \text{ Volts}$$

Step 2: Find R_{th}

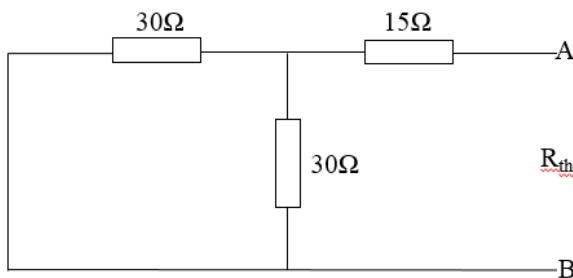

$$R_{123} = \frac{30 \times 30}{30 + 30} = \frac{900}{60}$$

$$R_{123} = 15 \Omega$$


$$R_{th} = 15 + 15$$

$$R_{th} = 30 \Omega$$

According to Maximum Power Transfer theorem:

$$R_L = R_{th} = 30 \Omega$$

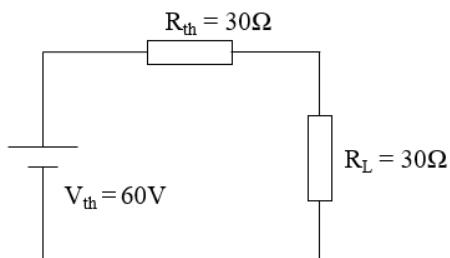Step 3: Draw thevenin's equivalent circuit




Step 4: Calculate Maximum Power:

$$\begin{aligned} \text{Maximum Power } (P_{max}) &= \frac{V_{th}^2}{4R_L} = \frac{60^2}{4 \times 30} = \frac{3600}{120} \\ P_{max} &= 30 \text{ Watts} \end{aligned}$$

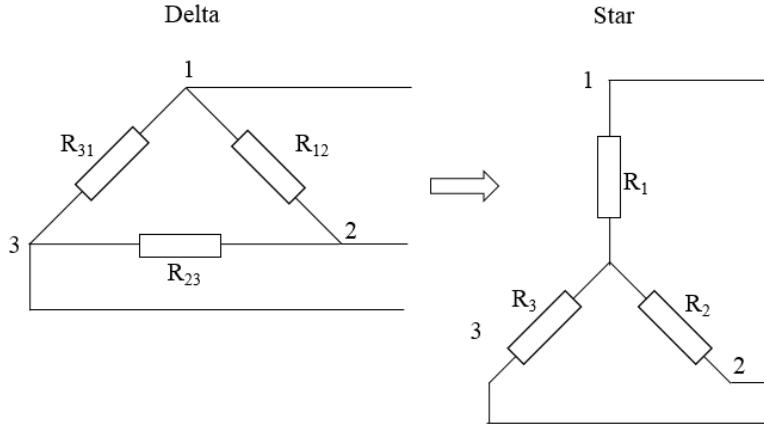2.14 Delta to Star Conversion:

Consider a three terminal network in which the resistors are connected in the form Δ . Such a network is known as delta network. Let the resistor values are R_{12} , R_{23} and R_{31} . Now we find its equivalent Y-network such that both the circuits are identical as far as the terminals 1, 2 and 3 are concerned. Let the resistor values are R_1 , R_2 and R_3 .



In Delta (Δ) Connection:

$$\text{Equivalent Resistance between 1 \& 2} = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

In Star (Y) Connection:

$$\text{Equivalent Resistance between 1 \& 2} = R_1 + R_2$$

$$\text{Resistance between terminal 1 \& 2 in Y} = \text{Resistance between terminal 1 \& 2 in } \Delta$$

$$R_1 + R_2 = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (1)$$

$$\text{Similarly, } R_2 + R_3 = \frac{R_{23}(R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (2)$$

$$R_3 + R_1 = \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (3)$$

Subtract Equation (2) from Equation (3):

$$R_1 - R_2 = \frac{(R_{12}R_{31} + R_{23}R_{31} - R_{23}R_{31} - R_{12}R_{23})}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_2 = \frac{R_{12}(R_{31} - R_{23})}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (4)$$

Add Equation (1) and Equation (4):


$$2R_1 = \frac{2R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\text{Similarly, } R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}}$$

2.15 Star to Delta Conversion:

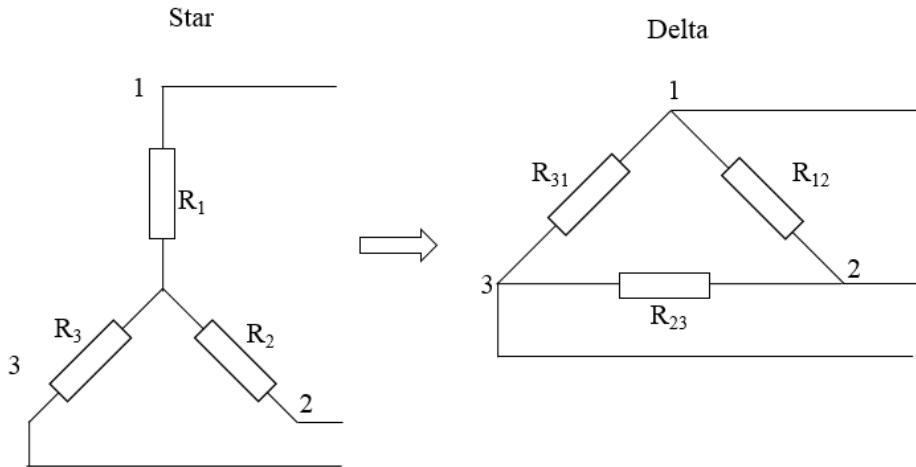

$$\text{We know, } R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (1)$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (2)$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (3)$$

From the above relations:

$$(1) \quad X(2) \Rightarrow R_1 R_2 = \frac{R_{12}^2 R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (4)$$

$$(2) \quad X(3) \Rightarrow R_2 R_3 = \frac{R_{12} R_{23}^2 R_{31}}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (5)$$


$$(3) \quad X(1) \Rightarrow R_3 R_1 = \frac{R_{12} R_{23} R_{31}^2}{R_{12} + R_{23} + R_{31}} \quad \dots \dots \dots (6)$$

By adding Equation: (4) + (5) + (6)

$$\begin{aligned}
 R_1 R_2 + R_2 R_3 + R_3 R_1 &= \frac{R_{12} R_{23} R_{31} (R_{12} + R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})^2} \\
 &= \frac{R_{12} R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \\
 R_{12} &= \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \times (R_1 R_2 + R_2 R_3 + R_3 R_1) \\
 R_{12} &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \\
 R_{23} &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \\
 R_{31} &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}
 \end{aligned}$$

Example: 29

Find the DELTA Resistance for given STAR.

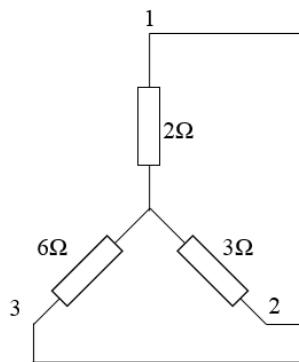**Given Data:**

| | | |
|------------------|---|-----------|
| Resistance R_1 | = | 2Ω |
| Resistance R_2 | = | 3Ω |
| Resistance R_3 | = | 6Ω |

To Find:

- i) $R_{12} = ?$
- ii) $R_{23} = ?$
- iii) $R_{31} = ?$

Solution:

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{(2 \times 3) + (3 \times 6) + (6 \times 2)}{6}$$


$$R_{12} = \frac{6 + 18 + 12}{6} = \frac{36}{6} = 6\Omega$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{(2 \times 3) + (3 \times 6) + (6 \times 2)}{2} = \frac{36}{2} = 18\Omega$$


$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{(2 \times 3) + (3 \times 6) + (6 \times 2)}{3} = \frac{36}{3} = 12\Omega$$

Answer:

$R_{12} = 6\Omega$, $R_{23} = 18\Omega$ and $R_{31} = 12\Omega$

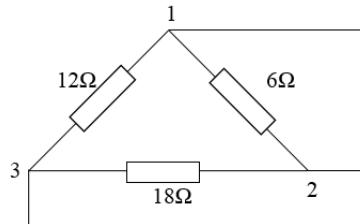**Example: 30**

Find the STAR Resistance for given DELTA.

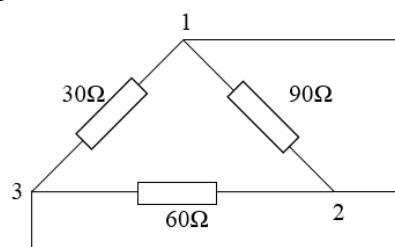**Given Data:**

| | | |
|---------------------|---|------------|
| Resistance R_{12} | = | 90Ω |
| Resistance R_{23} | = | 60Ω |
| Resistance R_{31} | = | 30Ω |

To Find:

- i) $R_1 = ?$
- ii) $R_2 = ?$
- iii) $R_3 = ?$

Solution:


$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{90 \times 30}{90 + 60 + 30} = \frac{2700}{180} = 15\Omega$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{60 \times 90}{90 + 60 + 30} = \frac{5400}{180} = 30\Omega$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{30 \times 60}{90 + 60 + 30} = \frac{1800}{180} = 10\Omega$$


Answer:

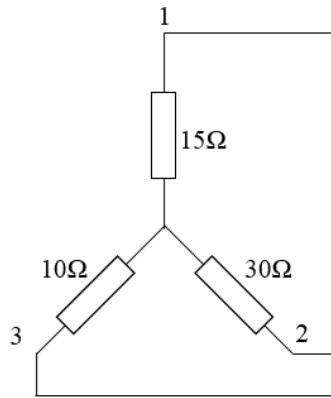$R_1 = 15\Omega$, $R_2 = 30\Omega$ and $R_3 =$



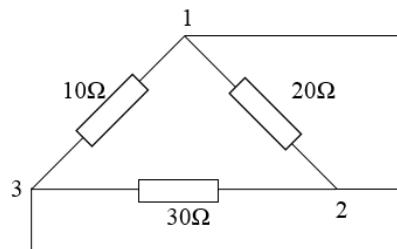Example: 31

Find the STAR Resistance for given DELTA.



Given Data:

$$\text{Resistance } R_{12} = 90\Omega$$

$$\text{Resistance } R_{23} = 60\Omega$$

$$\text{Resistance } R_{31} = 30\Omega$$

To Find:

$$\text{i) } R_1 = ?$$

$$\text{ii) } R_2 = ?$$

$$\text{iii) } R_3 = ?$$

Solution:

Step 1: Convert the Delta 123 into equivalent Star :

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{20 \times 10}{20 + 30 + 10} = \frac{200}{60} = 3.33\Omega$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{20 \times 30}{20 + 30 + 10} = \frac{600}{60} = 10\Omega$$



$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{10 \times 30}{20 + 30 + 10} = \frac{300}{60} = 5\Omega$$

Answer:

$R_1 = 3.33\Omega$, $R_2 = 10\Omega$ and $R_3 = 5\Omega$

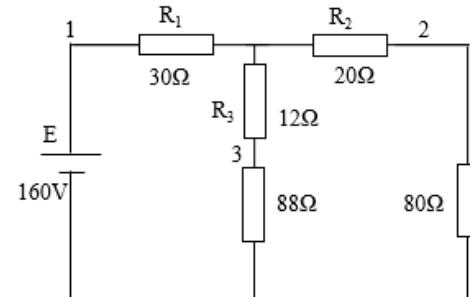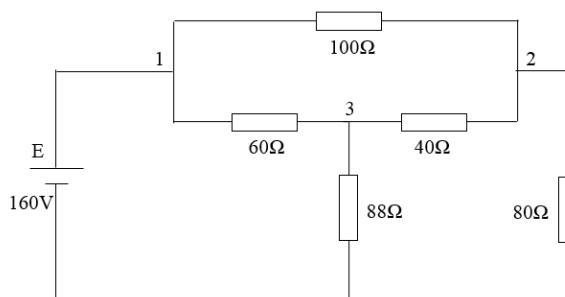Example: 32

Determine the total resistance and circuit current of the given circuit.



Given Data:

$$\text{Resistance } R_{12} = 100\Omega$$

$$\text{Resistance } R_{23} = 40\Omega$$

$$\text{Resistance } R_{31} = 60\Omega$$

To Find:

$$\text{i) } R_1 = ?$$

$$\text{ii) } R_2 = ?$$

$$\text{iii) } R_3 = ?$$

Solution:

Step 1: Convert the Delta 123 into equivalent Star :

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{100 \times 60}{100 + 40 + 60} = \frac{6000}{200} = 30\Omega$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{40 \times 100}{100 + 40 + 60} = \frac{4000}{200} = 20\Omega$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{60 \times 40}{100 + 40 + 60} = \frac{2400}{200} = 12\Omega$$

$$\text{Total Resistance } R = 30\Omega + [(12\Omega + 88\Omega) \parallel (20\Omega + 80\Omega)]$$

$$\text{Total Resistance } R = 30\Omega + [100\Omega \parallel 100\Omega] = 30\Omega + 50\Omega$$


$$\text{Total Resistance } R = 80\Omega$$

$$\text{Circuit Current } I = \frac{V}{R} = \frac{240}{80} = 3 \text{ Amps}$$

SIMULATED RESULT OF EXAMPLE PROBLEMS IN UNIT 2


Example: 3

Mesh Current Analysis

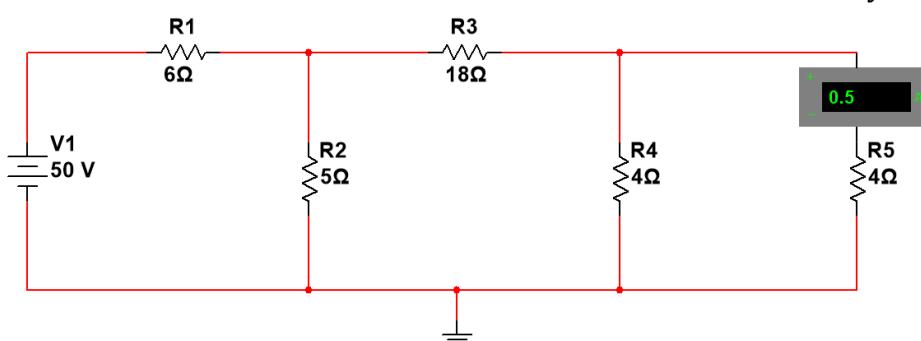


Example: 4

Mesh Current Analysis

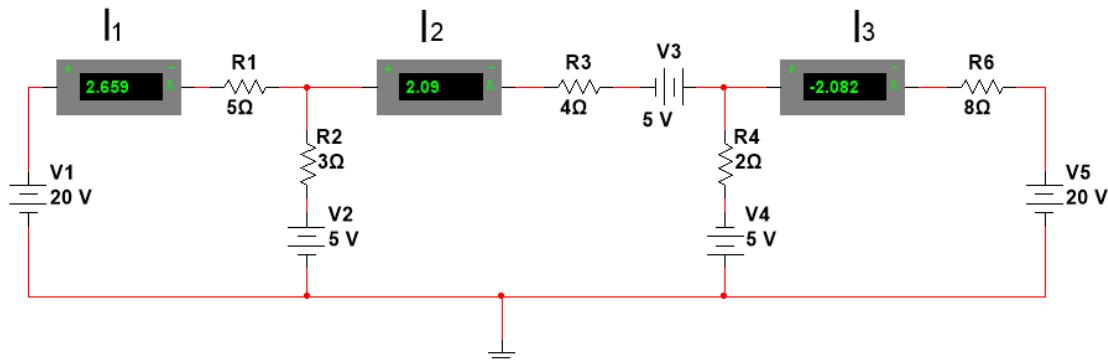


Example: 5

Mesh Current Analysis

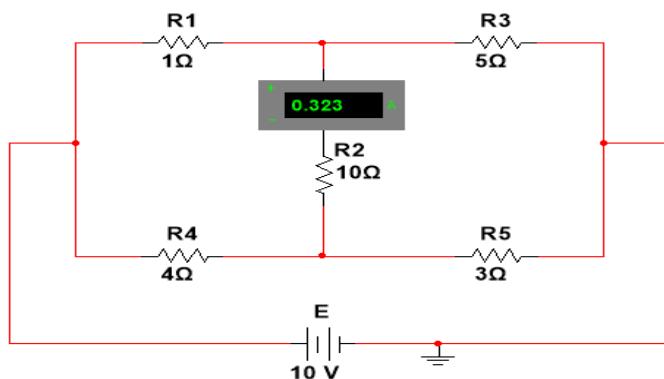


Example: 6

Nodal Voltage Analysis

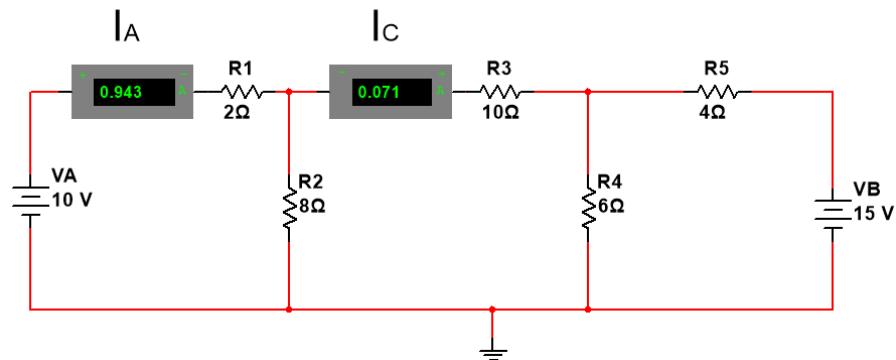


Example: 7

Nodal Voltage Analysis

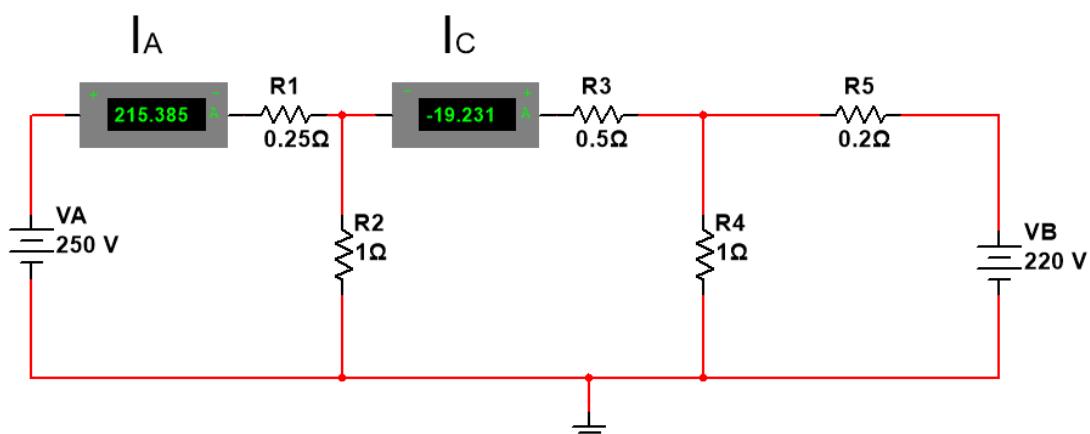


Example: 8

Superposition Theorem

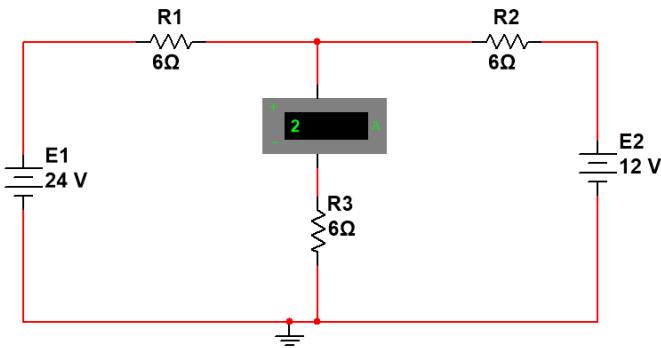


Example: 9 & 10

Superposition Theorem

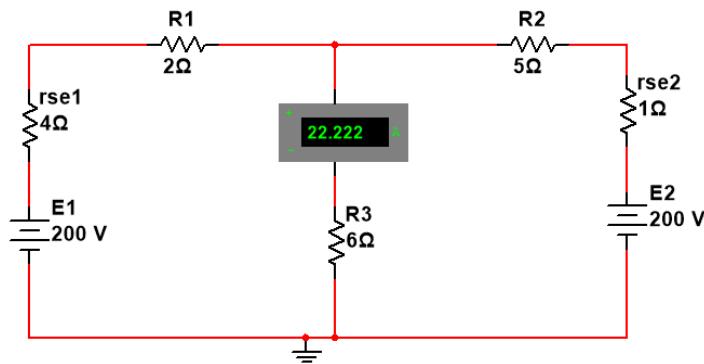


Example: 11 & 12

Superposition Theorem

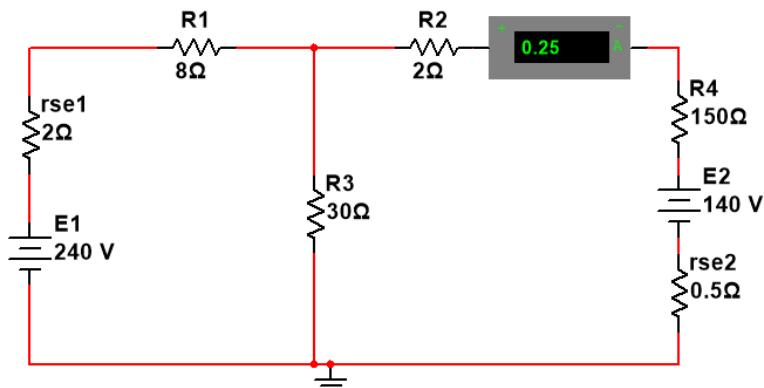


Example: 13 & 14

Superposition Theorem

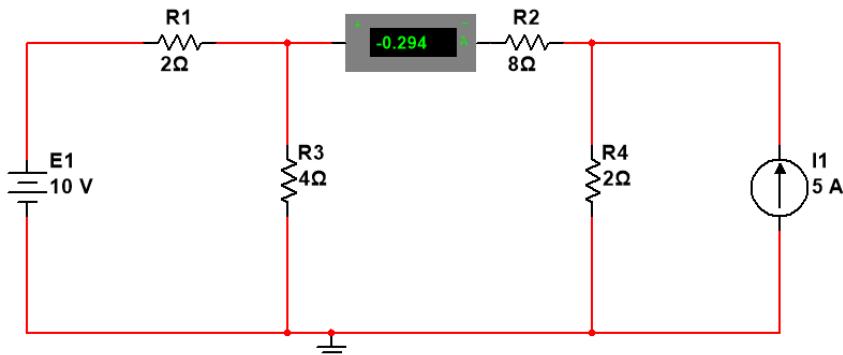


Example: 15

Superposition Theorem

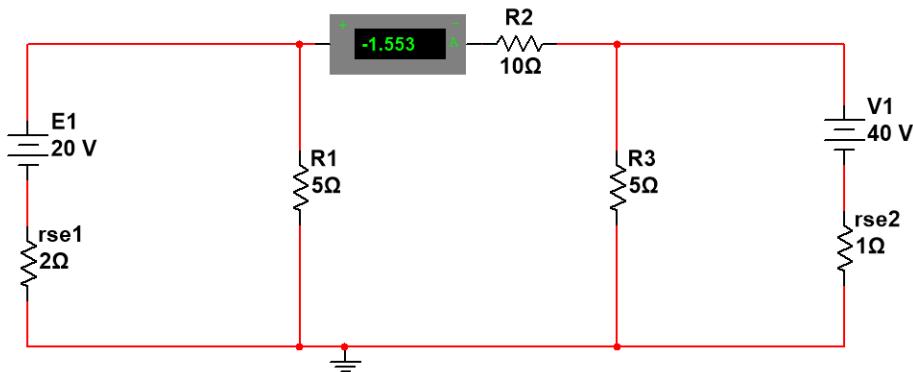


Example: 16

Superposition Theorem

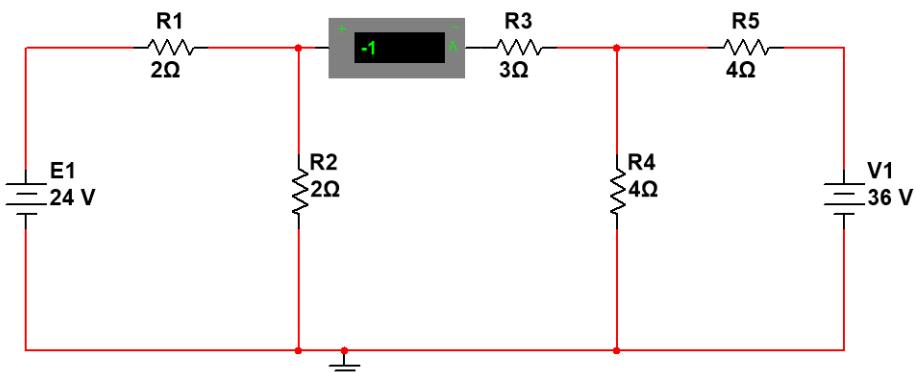


Example: 17

Thevenin's Theorem

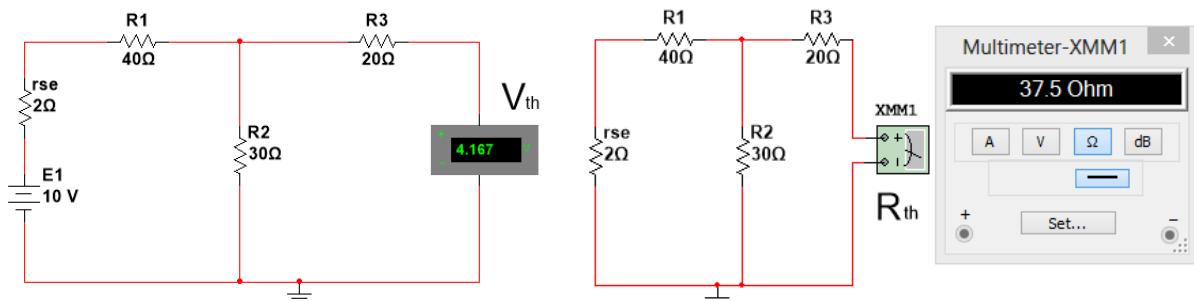


Example: 18


Thevenin's Theorem

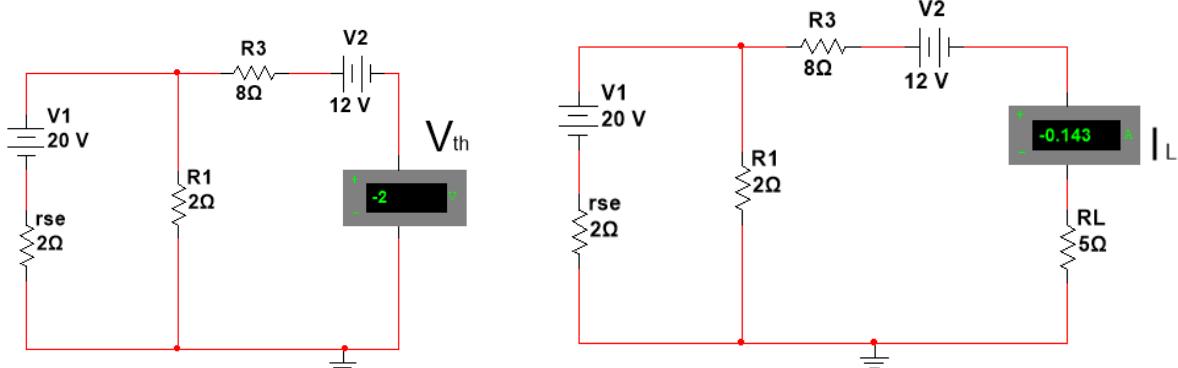


Example: 19

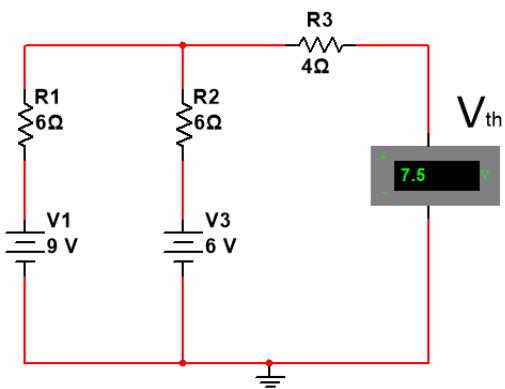


Thevenin's Theorem

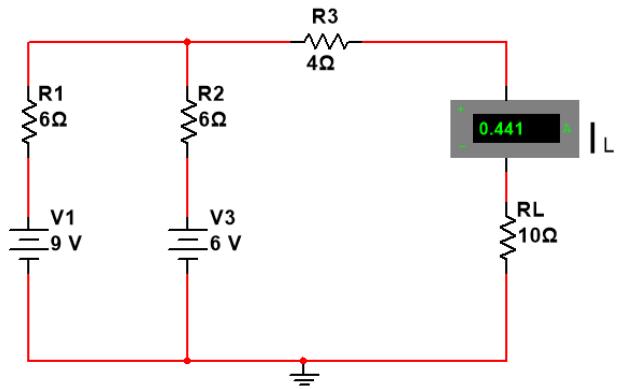


Example: 20

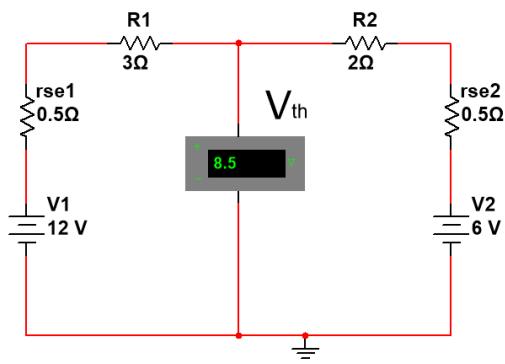


Thevenin's Theorem

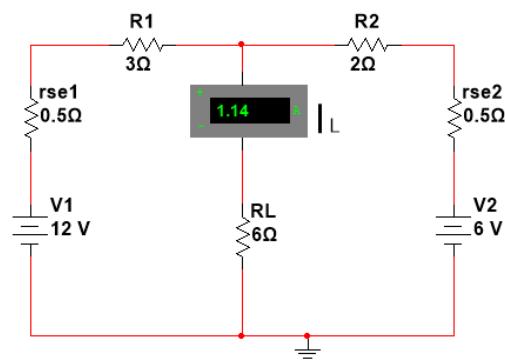


Example: 21

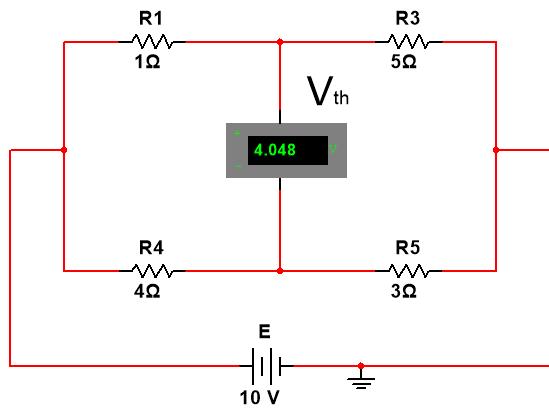


Thevenin's Theorem

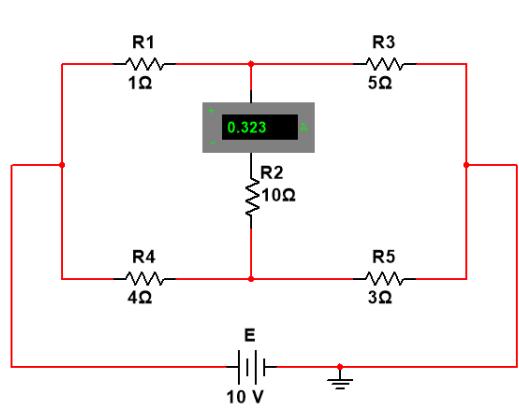


Example: 22

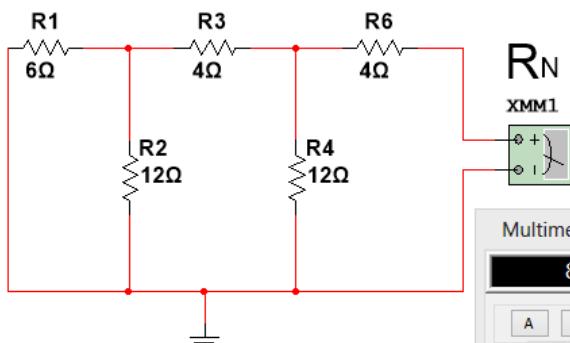



Norton's Theorem

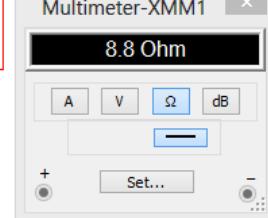

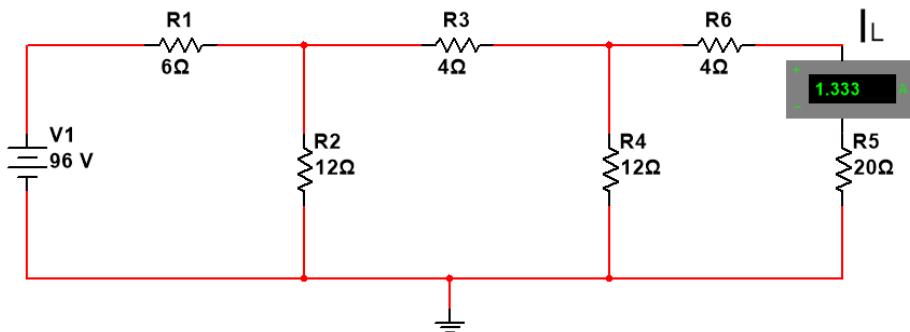



Example: 23

Norton's Theorem

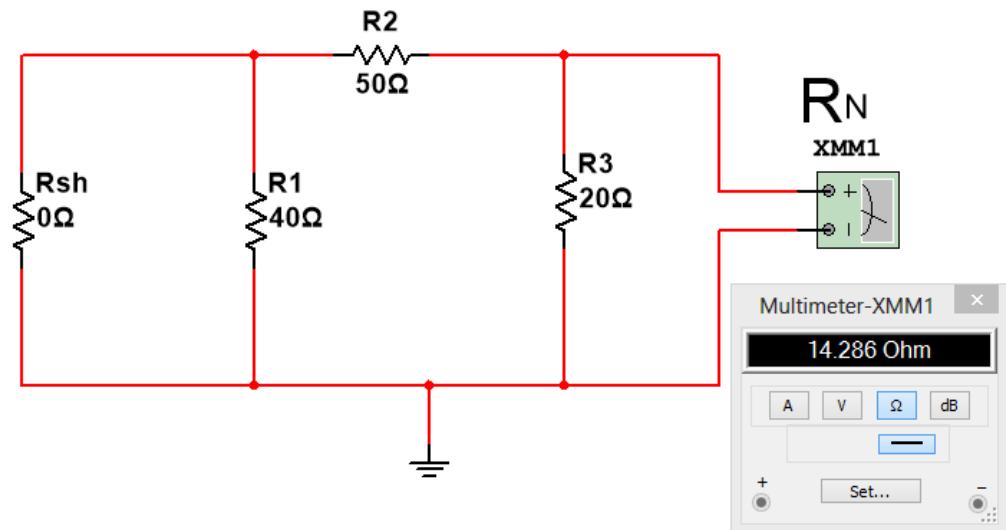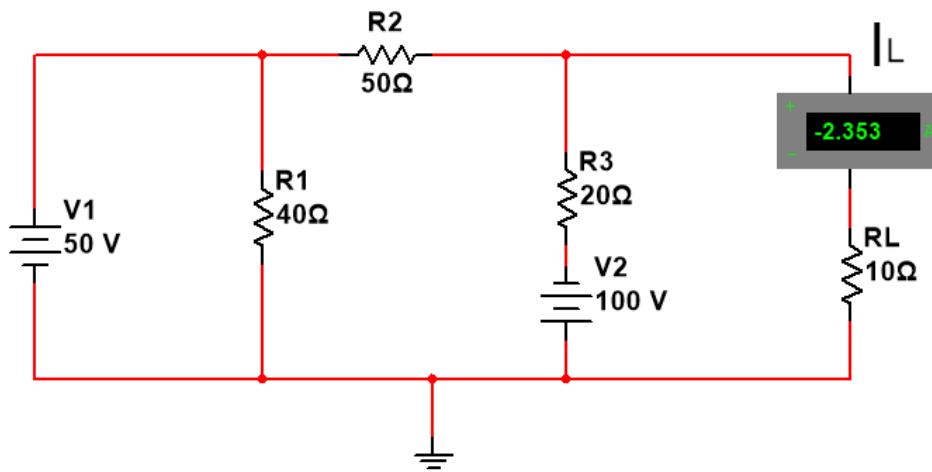


Example: 24


Norton's Theorem

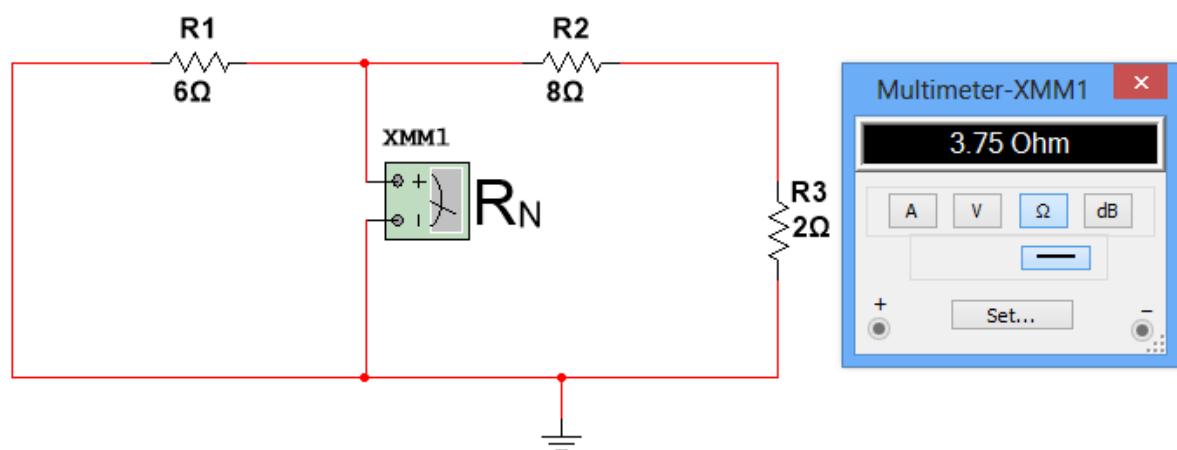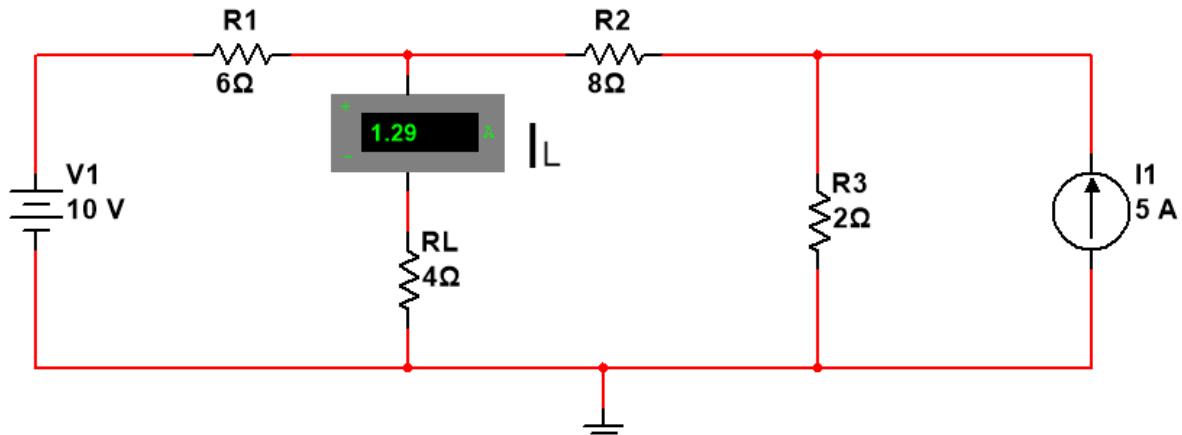

Example: 25


Norton's Theorem

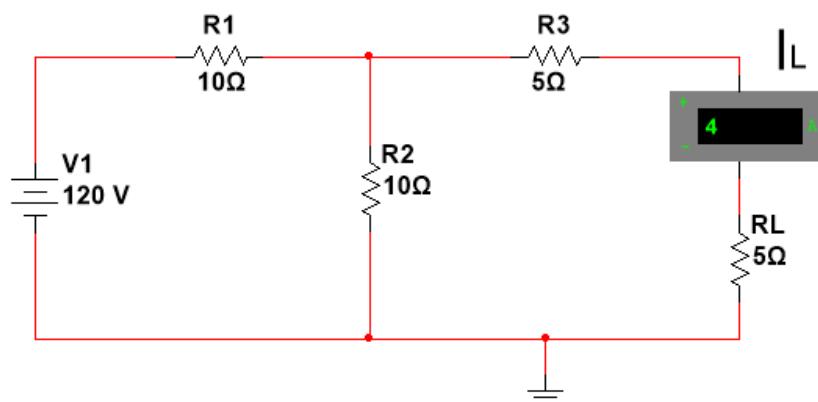

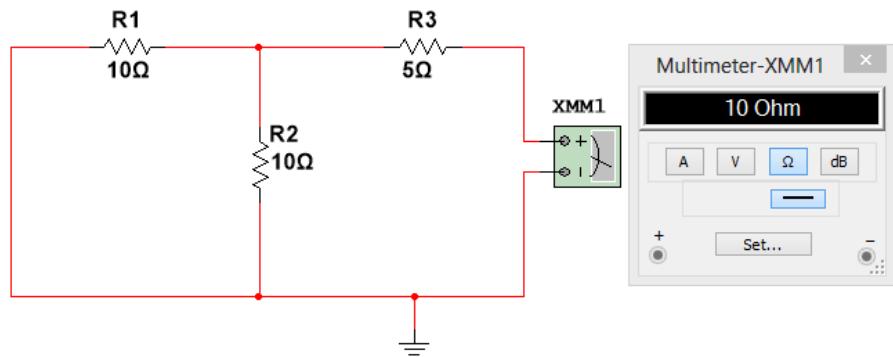


Example: 26

Norton's Theorem

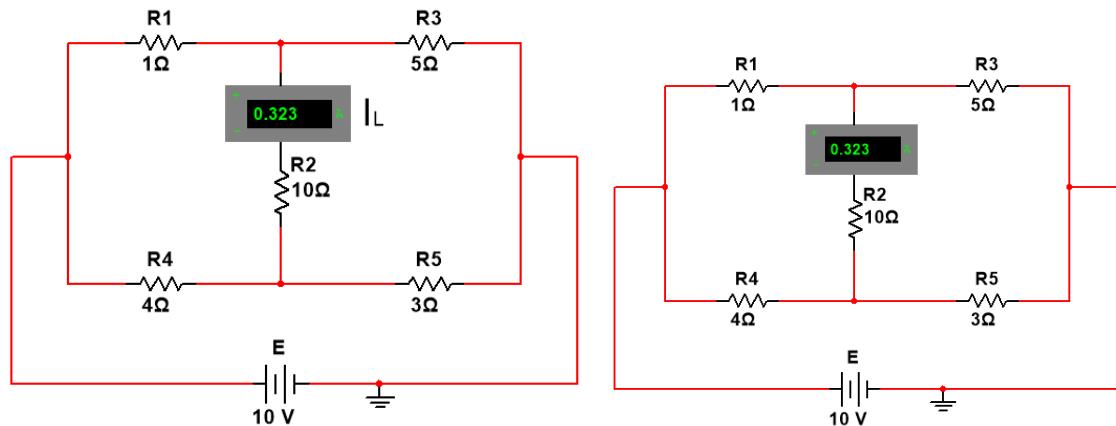


Example: 27

Maximum Power Transfer Theorem

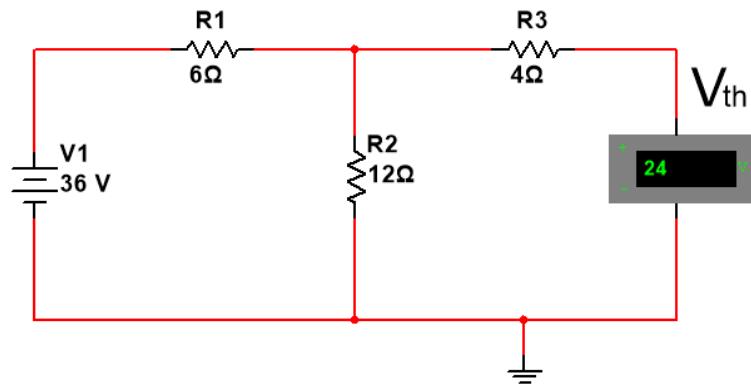

Example: 28

Maximum Power Transfer Theorem

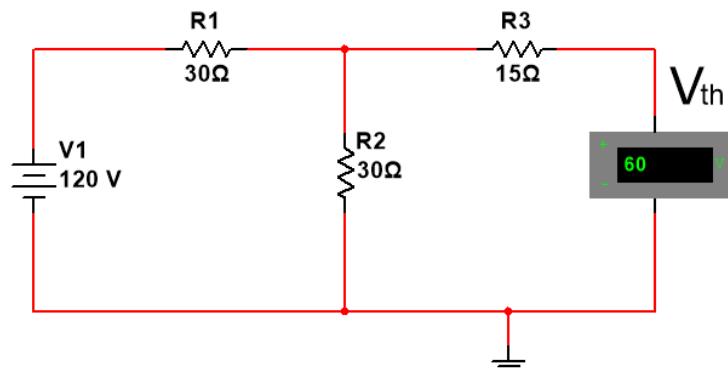


REVIEW QUESTIONS
UNIT : II NETWORK THEOREMS

PART – A : 2 Mark Questions


1. Define circuit element and state the elements.
2. Define electric circuit and network.
3. Define node or junction in a network.
4. Define simple node and principal node.
5. Define branch of a network.
6. Define mesh in a circuit.
7. Define loop in a network.
8. Define active network.
9. What is meant by a bilateral circuit?
10. What is meant by linear circuit?
11. State the name of the law applied in mesh current analysis.
12. State the name of the law applied in node voltage analysis.
13. What is the potential of reference node in node voltage analysis?
14. How many equations are required for mesh analysis?
15. How many equations are required for node voltage analysis?
16. A 10A current source has an internal resistance of 100Ω . Draw the equivalent voltage source.
17. A Voltage Source has a terminal voltage of 12V with an internal resistance of 0.1 Ohms. What is its equivalent current source?
18. Convert a current source of 100A with an internal resistance of 0.2 ohm into an equivalent voltage source.
19. State the condition for maximum power transfer theorem.
20. A source has an internal resistance of 8Ω . What must be the value of load resistance to transfer maximum power in it?
21. 3 identical resistors of 12Ω each are in delta. Find the equivalent value of resistors in star.
22. Three identical resistors of 8Ω each are in star. Find the equivalent value of resistor in delta.

PART – B : 3 Mark Questions

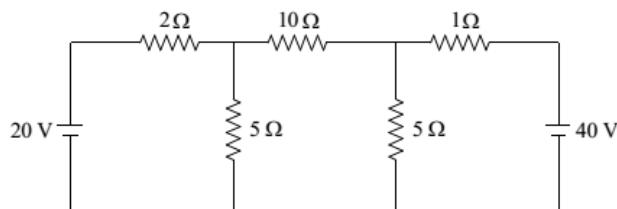1. Draw a network and show atleast two principal nodes.
2. Write the mesh equation in matrix form for the network shown below.



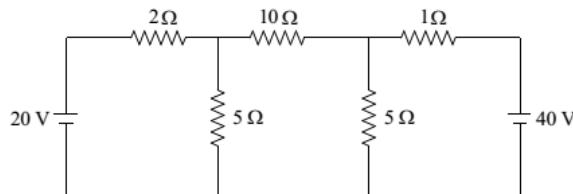
3. Write the node equation in matrix form for the network shown below.




4. Write the equations to transfer Y to Δ .
5. Write the equation to transfer Δ to Y.
6. State Superposition Theorem.
7. State Thevenin's Theorem.
8. State Norton's Theorem.
9. Show how a Thevenin's circuit can be obtained from Norton's form.
10. Show how a Norton's circuit can be obtained from Thevenin's form.
11. State maximum power transfer theorem.

PART – C : 10 Mark Questions

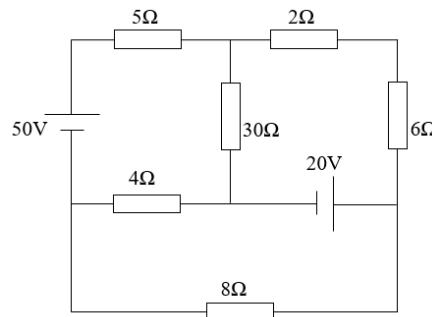
1. Discuss mesh current analysis with an example.
2. Discuss node voltage analysis with an example.
3. Derive the equations needed for star to delta and delta to star transformations.
4. State and explain Thevenin's theorem.
5. State and explain Norton's Theorem.
6. State and explain Superposition theorem with an example.
7. State Maximum power transfer theorem and derive the conditions for maximum power transfer in a single source circuit.
8. Determine the current through 30Ω resistor in the given circuit by using mesh analysis.



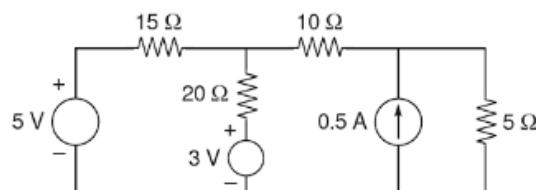
9. Use the mesh analysis method to find the current through the 20Ω resistance. Also find the voltage drop it.



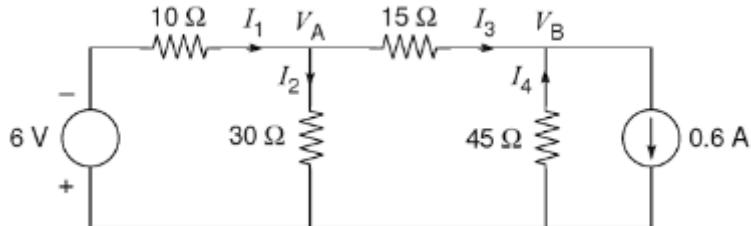
10. Use nodal analysis method to find current through 30 ohm resistor in the circuit given below.



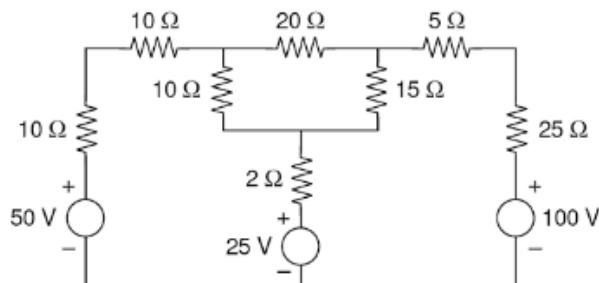
11. Determine the current through the 5Ω resistance using Nodal analysis.



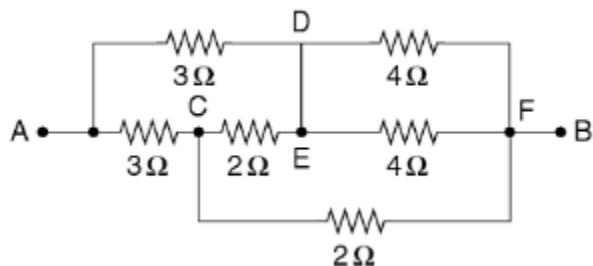
12. Calculate the equivalent resistance of the network shown in figure across terminals A and B using star delta transformation where necessary.



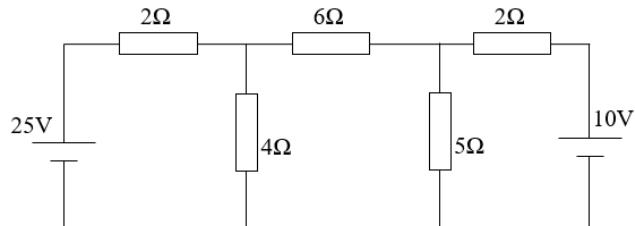
13. Determine the current through 6Ω resistor in the given circuit by using superposition theorem.



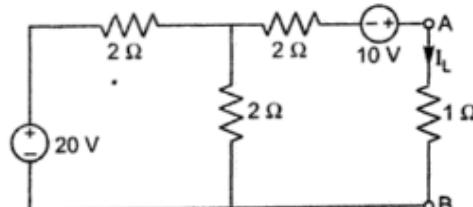
14. Determine current through load by using Thevenin's Theorem.



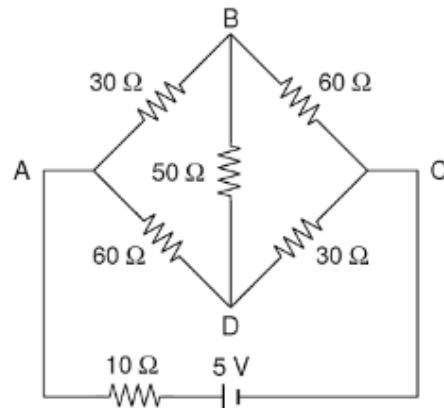
15. Determine the current through 50Ω Resistor by using Thevenin's Theorem.



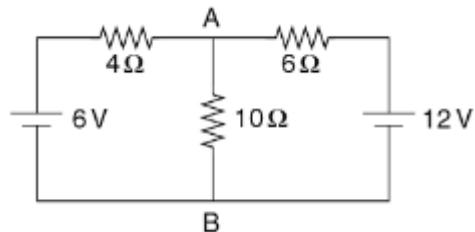
16. Using Norton's theorem, calculate the current through 10Ω resistor in the given circuit.



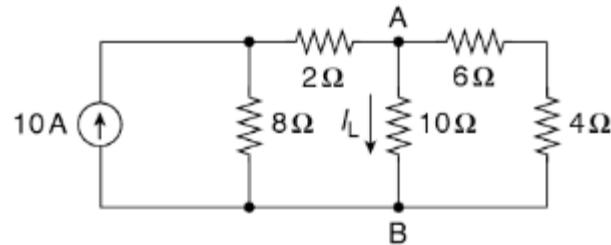17. Using Norton's theorem, calculate the current through 10Ω resistor in the given circuit.



18. Calculate the value of Load Resistance, at which the power transfer will be maximum in the given circuit.

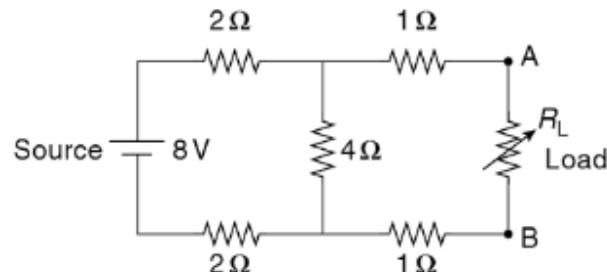

UNIT III – SINGLE PHASE CIRCUITS

Syllabus:

'j' notations – rectangular and polar coordinates – Sinusoidal voltage and current – instantaneous, peak, average and effective values – form factor and peak factor(derivation for sine wave) – pure resistive, inductive and capacitive circuits – RL, RC, RLC series circuits – impedance – phase angle – phasor diagram – power and power factor – power triangle – apparent power, active and reactive power – parallel circuits (two branches only) - Conductance, susceptance and admittance – problems on all above topics.

3.0 Introduction:

A.C means Alternating Current. The current or voltage which alternates its direction and magnitude every time. In dc circuits, Power = Voltage x Current. Everything was constant, so there was no problem between instantaneous power and average power. Resistance dissipates power, converting it to heat, light, sound or motion. It was simple and straight forward.

However in a,c circuits the voltage and current vary continuously. So taking the product $V \times I$ involves multiplying two sine waves at different angles and results in a sinusoid at twice the frequency and shifted in dc level.

3.1 'j' notation:

A complex number represents a point in a two-dimensional plane located with reference to two distinct axes. The horizontal axis is called the real axis, while the vertical axis is called the imaginary axis. In the complex plane, the horizontal or real axis represents all positive numbers to the right of the imaginary axis and all negative numbers to the left of the imaginary axis. All positive imaginary numbers are represented above the real axis, and all negative imaginary numbers, below the real axis.

In electrical circuit, a $\pm j$ prefix is used to designate numbers that lie on the imaginary axis in order to distinguish them from numbers lying on the real axis. The prefix is known as j operator.


$$j = \sqrt{-1}$$

$$j^2 = -1$$

$$j^3 = j^2 j = -1j = -j$$

$$j^4 = j^2 j^2 = (-1)(-1) = +1$$

$$j^5 = j$$

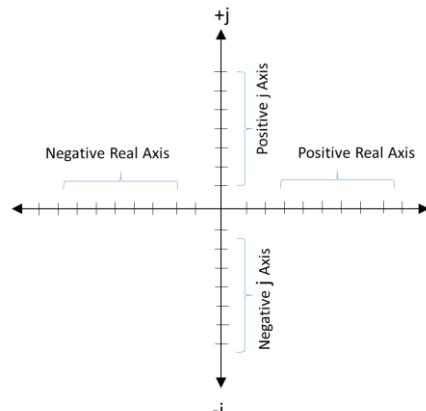

3.2 Rectangular and Polar Coordinates:

Rectangular and polar are two forms of complex numbers that are to represent phasor quantities. A phasor quantities contains both magnitude and angular position or phase.

3.2.1 Rectangular Form:

A phasor quantity is represented in rectangular form by the algebraic sum of the real value (A) of the coordinate and j value (B) of the coordinate, expressed in the following general form:

$$C = A + jB$$

3.2.2 Polar Form:

Phasor quantities can also be expressed in polar form, which consists of the phasor magnitude (A) and the angular relative to the positive real axis (θ), expressed in the following general form:

$$C = A \angle \pm \theta^\circ$$


3.2.3 Rectangular to Polar Conversion:

A phasor can be visualized as forming a right triangle in the complex plane as shown in figure below. The horizontal side of the triangle is the real value A and the vertical side is the j value B. The hypotenuse of the triangle is the length of the phasor C, representing the magnitude and can be expressed as follows:

$$C = A + jB$$

$$\text{Magnitude: } C = \sqrt{A^2 + B^2}$$
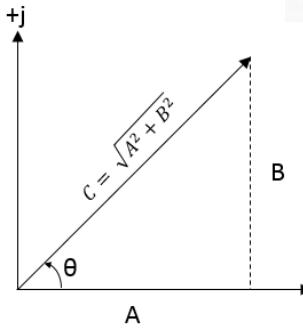
$$\text{Phase angle } \theta = \tan^{-1} \left(\frac{\pm B}{A} \right)$$



3.2.4 Polar to Rectangular Conversion:


The polar form gives the magnitude and angle of a phasor quantity as shown in figure.

$$A = C \cos \theta$$

$$B = C \sin \theta$$

$$C \angle \pm \theta^\circ = A + jB$$
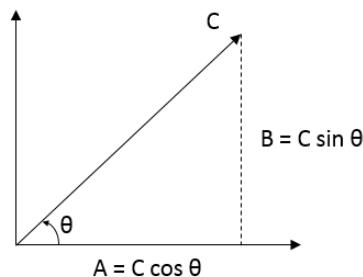
$$C \angle \pm \theta^\circ = C \cos \theta + jC \sin \theta$$



Example: 1

Express the following in j form.

- a) $15\angle 30^\circ$ b) $15\angle -30^\circ$ c) $20\angle 225^\circ$ d) $5\angle -200^\circ$

Solution:a) $15\angle 30^\circ$:

$$\begin{aligned} \text{Where, } C &= 15 \\ \theta &= 30^\circ \\ 15\angle 30^\circ &= C \cos \theta + jC \sin \theta \\ &= 15 \cos 30 + j15 \sin 30 \\ &= 15(0.86) + j15(0.5) \\ 15\angle 30^\circ &= 12.9 + j7.5 \quad (\text{'j' form}) \end{aligned}$$

b) $15\angle -30^\circ$:

$$\begin{aligned} \text{Where, } C &= 15 \\ \theta &= -30^\circ \\ 15\angle -30^\circ &= C \cos \theta + jC \sin \theta \\ &= 15 \cos(-30) + j15 \sin(-30) \\ &= 15(0.86) + j15(-0.5) \\ 15\angle -30^\circ &= 12.9 - j7.5 \quad (\text{'j' form}) \end{aligned}$$

c) $20\angle 225^\circ$:

$$\begin{aligned} \text{Where, } C &= 20 \\ \theta &= 225^\circ \\ 20\angle 225^\circ &= C \cos \theta + jC \sin \theta \\ &= 20 \cos 225 + j20 \sin 225 \\ &= 20(-0.707) + j15(-0.707) \\ 20\angle 225^\circ &= -14.14 - j10.6 \quad (\text{'j' form}) \end{aligned}$$

d) $5\angle -200^\circ$:

$$\begin{aligned} \text{Where, } C &= 5 \\ \theta &= -200^\circ \\ 5\angle -200^\circ &= C \cos \theta + jC \sin \theta \\ &= 5 \cos(-200) + j5 \sin(-200) \\ &= 5(-0.93) + j5(0.34) \\ 5\angle -200^\circ &= -4.65 + j1.7 \quad (\text{'j' form}) \end{aligned}$$

Example: 2

Express the following in polar form.

- a) $3 + j4$ b) $8 - j6$ c) $8 + j6$ d) $-6 + j10$

Solution:a) $3 + j4$:

$$\begin{aligned} \text{Where, } A &= 3 \\ B &= j4 \\ \text{Magnitude} &= \sqrt{3^2 + 4^2} \\ \text{Magnitude} &= 5 \\ \text{Phase angle } \theta &= \tan^{-1}\left(\frac{\pm B}{A}\right) \\ &= \tan^{-1}\left(\frac{4}{3}\right) \\ \theta &= 53.13^\circ \\ \text{In polar form} &= 5\angle 53.13^\circ \end{aligned}$$

b) $8 - j6$:

$$\begin{aligned} \text{Where, } A &= 8 \\ B &= -j6 \\ \text{Magnitude} &= \sqrt{8^2 + (-6)^2} \\ \text{Magnitude} &= 10 \\ \text{Phase angle } \theta &= \tan^{-1}\left(\frac{\pm B}{A}\right) \\ &= \tan^{-1}\left(\frac{-6}{8}\right) \\ \theta &= -36.86^\circ \\ \text{In polar form} &= 10\angle -36.86^\circ \end{aligned}$$

c) $8 + j6$:

$$\begin{aligned} \text{Where, } A &= 8 \\ B &= j6 \\ \text{Magnitude} &= \sqrt{8^2 + 6^2} \\ \text{Magnitude} &= 10 \\ \text{Phase angle } \theta &= \tan^{-1}\left(\frac{\pm B}{A}\right) \\ &= \tan^{-1}\left(\frac{6}{8}\right) \\ \theta &= 36.86^\circ \\ \text{In polar form} &= 10\angle 36.86^\circ \end{aligned}$$

d) $-6 + j10$:

$$\begin{aligned} \text{Where, } A &= -6 \\ B &= j10 \\ \text{Magnitude} &= \sqrt{(-6)^2 + 10^2} \\ \text{Magnitude} &= 11.66 \\ \text{Phase angle } \theta &= \tan^{-1}\left(\frac{\pm B}{A}\right) \\ &= \tan^{-1}\left(\frac{-10}{6}\right) \end{aligned}$$

$$\begin{aligned}\theta &= -59.03^\circ \\ \text{In polar form} &= 11.66\angle -59.03^\circ\end{aligned}$$

Example: 3

Add the vectors A and B and give result in polar form.

$$A = 16 + j12 \text{ and } B = -6 + j10$$

Solution:

$$\begin{aligned}A+B &= (16 + j12) + (-6 + j10) \\ &= 10 + j22 \\ &= 10 + j22 \quad (\text{Vector form}) \\ \text{Magnitude} &= \sqrt{10^2 + 22^2} \\ \text{Magnitude} &= 24.16 \\ \text{Phase angle } \theta &= \tan^{-1}\left(\frac{\pm B}{A}\right) \\ &= \tan^{-1}\left(\frac{22}{10}\right) \\ \theta &= 65.55^\circ \\ \text{In polar form } A+B &= 24.16\angle 65.55^\circ\end{aligned}$$

Example: 4

Multiply the two phasor A and B.

$$A = 40 + j30 \text{ and } B = 4 - j3$$

Solution:

$$\begin{aligned}A.B &= (40 + j30). (4 - j3) \\ &= (40 \times 4) - (40 \times j3) + j(30 \times 4) - (j30 \times j3) \\ &= 160 - j120 + j120 + 90 \\ A.B &= 250 + j0\end{aligned}$$

Example: 5

Find the ratio of the two phasor A and B. (A/B)

$$A = 100 + j60 \text{ and } B = 8 - j6$$

Solution:

$$\begin{aligned}\text{Ratio } \frac{A}{B} &= \frac{100 + j60}{8 - j6} \\ &= \frac{100 + j60}{8 - j6} \times \frac{8 + j6}{8 + j6} \\ &= \frac{(100 \times 8) + j(100 \times 6) + j(60 \times 8) + (j60 \times j6)}{(8 \times 8) + j(8 \times 6) - j(6 \times 8) - (j6 \times j6)} \\ &= \frac{800 + j600 + j480 - 360}{64 + j48 - j48 + 36}\end{aligned}$$

$$\begin{aligned}
 &= \frac{440 + j1080}{100} \\
 &= \frac{440}{100} + j\frac{1080}{100} \\
 \frac{A}{B} &= 4.4 + j10.8
 \end{aligned}$$

Example: 6

Two phasors are given by $A = 5 + j8$ and $B = 7 - j6.5$. Find: i) $A \cdot B$ ii) A/B

Solution:

$$\begin{aligned}
 A &= 5 + j8 \\
 \text{Magnitude} &= \sqrt{5^2 + 8^2} \\
 &= 9.43 \\
 \text{Phase angle } \theta &= \tan^{-1}\left(\frac{\pm B}{A}\right) \\
 &= \tan^{-1}\left(\frac{8}{5}\right) \\
 &= 57.99^\circ \\
 \text{In polar form: } A &= 9.43 \angle 57.99^\circ
 \end{aligned}$$

$$\begin{aligned}
 B &= 7 - j6.5 \\
 \text{Magnitude} &= \sqrt{7^2 + 6.5^2} \\
 &= 9.55 \\
 \text{Phase angle } \theta &= \tan^{-1}\left(\frac{\pm B}{A}\right) \\
 &= \tan^{-1}\left(\frac{-6.5}{7}\right) \\
 &= -42.88^\circ \\
 \text{In polar form: } B &= 9.55 \angle -42.88^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{i) Product } A \cdot B &= (9.43 \angle 57.06^\circ) \times (9.55 \angle -42.88^\circ) \\
 &= (9.43 \times 9.55) \angle 57.06^\circ + (-42.88^\circ) \\
 A \cdot B &= 90.05 \angle 14.18^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{ii) Ratio } \frac{A}{B} &= \frac{9.43 \angle 57.06^\circ}{9.55 \angle -42.88^\circ} \\
 &= \frac{9.43}{9.55} \angle 57.06^\circ - (-42.88^\circ) \\
 &= 0.987 \angle 99.94^\circ \\
 \frac{A}{B} &= 0.987 \angle 99.94^\circ
 \end{aligned}$$

3.4 A.C Voltage: (Sinusoidal Voltage)

A.C voltage or alternating voltage changes its polarity periodically and also changes its magnitude at every instant.

3.5 A.C Current: (Sinusoidal current)

An alternating current is a current which reverses its direction periodically and changes its magnitude at every instant.

3.6 Alternator:


An alternating current generator is called alternator. It works on the principle of electromagnetic induction. An alternator is also called as AC Generator or synchronous generator.

Working principle of alternator:

An alternator works on the principle of Faraday's law of electromagnetic induction. It states that when there is a relative motion between magnetic field and a conductor an e.m.f is induced in the conductor.

Alternating voltages / current may be generated by two ways:

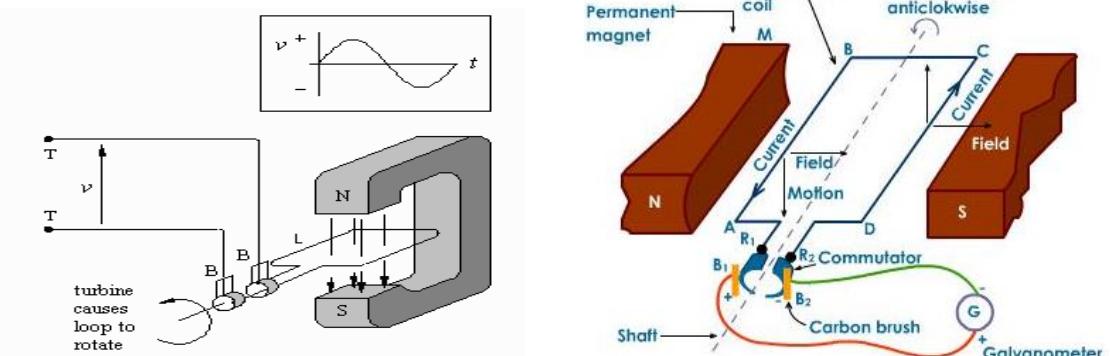- ❖ By rotating a coil in a magnetic field.
- ❖ By rotating a magnetic field within a stationary coil.



The quantity of voltages / current generated depends upon:

- ❖ The number of turns in the coil.
- ❖ Strength of the magnetic field
- ❖ The speed at which the coil rotates.

It is seen that the induced E.M.F. varies as a sine function of the time angle ωt . This curve is known as sine wave and the E.M.F which varies in this manner is known as sinusoidal E.M.F.

$$e = E_m \sin \omega t$$

Where, e = Instantaneous voltage

E_m = Maximum voltage

ωt = Angular velocity of the coil

The induced sinusoidal voltages produce sinusoidal current. These values are $I_m \sin \omega t$.

$$i = I_m \sin \omega t \quad \text{Where, } I_m = \text{Maximum value of alternating current.}$$

3.7 A.C Waveform:

The shape obtained by plotting the instantaneous ordinate values of either voltage or current against time is called an AC Waveform. An AC waveform is constantly changing its polarity every half cycle and alternating between a positive maximum value and a negative maximum value respectively with respect to time.

The sinusoidal waveform or sine wave is the fundamental type of alternating current and alternating voltage. It is also referred to as a sinusoidal wave or simply sinusoid. The electrical service provided by the power company (Electricity Board) is in the form of sinusoidal voltage or current.

AC waveforms can also take the shape of either *Complex Waves*, *Square Waves* or *Triangular Waves* and these are shown below.

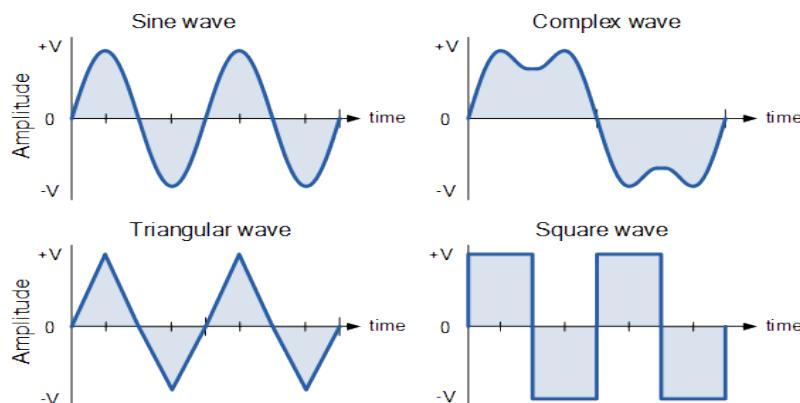


Fig. Types of periodic waveform

3.8 Instantaneous value:

The value of an alternating quantity at any instant is called instantaneous value. They are represented by small letters, i , v , e etc.,

Expression for instantaneous value of current:

$$i = I_m \sin \theta$$

$$i = I_m \sin \omega t$$

$$i = I_m \sin 2\pi ft$$

Expression for instantaneous value of voltage:

$$v = V_m \sin \theta$$

$$v = V_m \sin \omega t$$

$$v = V_m \sin 2\pi ft$$

3.9 Amplitude:

It is the highest value attained by the current or voltages in a half cycle either positive or negative half cycle of an alternating quantity.

3.10 Cycle:


One complete set of positive and negative value of an alternating quantity is called a cycle.

3.11 Time period (T):

The time required for a sine wave to complete one full cycle is called Time period.

$$T = 1/F \text{ sec (or) } m \text{ sec.} \quad F = \text{Frequency.}$$

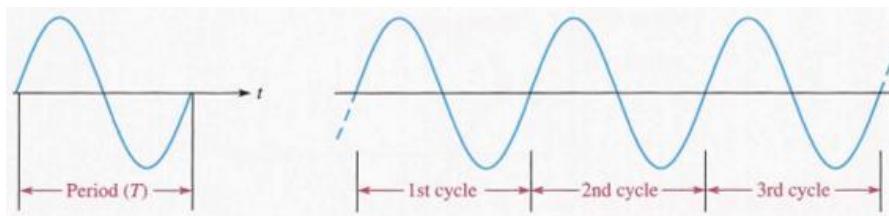The period of a sine wave can be measured from a zero crossing to the next corresponding zero crossing as shown in figure. The period can be also being measured from any peak in a given cycle to the corresponding peak in next cycle.



3.12 Frequency (F):

Frequency is the number of cycles that a wave completes per second. It is represented by F. Its unit is Hertz.

$$\text{One hertz} = 1 \text{ cycles per second}$$

3.12.1 Relationship between frequency and Time:

$$\text{Frequency} = \frac{1}{\text{Time Period}}$$


$$\text{Time Period} = \frac{1}{\text{Frequency}}$$

$$F = \frac{1}{T}$$

$$T = \frac{1}{F}$$

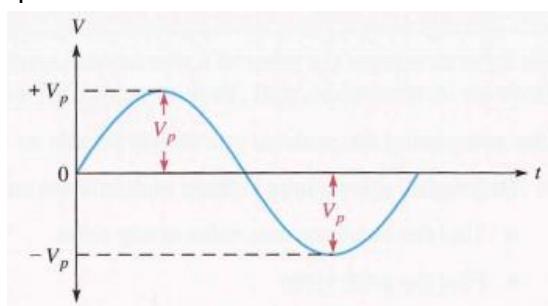3.13 Peak value or Maximum value:


The peak value of a sine wave is the value of voltage (or current) at the positive or the negative maximum with respect to zero.



Since the positive and negative peak values are equal in magnitude, a sine wave is characterized by a single peak value. It is represented by V_p or I_p .

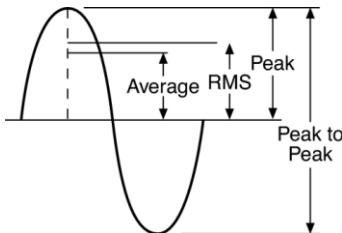3.14 Peak to Peak value:

The peak to peak value of a sine wave is the voltage or current from the positive peak to negative peak. It is always twice the peak value. It is represented by V_{pp} or I_{pp} .



3.15 Average value or Mean value:

This is the average of the instantaneous values of an alternating quantity over one complete cycle of the a.c waveform. It is also known as Mean value.

To obtain the average, divide the period into 'n' equal intervals. At these individual intervals let the current are $i_1, i_2, i_3 \dots, i_n$.

Thus the average value of the current and voltage are as follows:

$$I_{av} = \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$

Where, $i_1, i_2 \dots$ - instantaneous values

$$V_{av} = \frac{v_1 + v_2 + v_3 + \dots + v_n}{n}$$

Where, $v_1, v_2 \dots$ - instantaneous values

Average value can also be defined as the ratio of the total area under one half cycle to the base period.

$$\text{Average Value} = \frac{\text{Area Under the curve of half cycle}}{\text{Base of half cycle}}$$

3.15.1 Expression for Average Value of Sine wave:

$$\text{Instantaneous value of current } i = I_m \sin \theta \quad \text{Where, } \theta = \omega t$$

Consider an elementary strip of width $d\theta$ in the first half cycle of current wave. Let i be the mid-ordinate of this strip. Then,

$$\text{Area of strip} = i d\theta$$

$$\begin{aligned} \text{Area under the curve for half cycle} &= \int_0^{\pi} I_m \sin \theta d\theta \\ &= I_m \int_0^{\pi} \sin \theta d\theta \end{aligned}$$

$$\begin{aligned}
 &= I_m [-\cos \theta]_0^\pi \\
 &= I_m [-\cos \pi - (-\cos 0)] \\
 &= I_m [-(-1) + 1] \\
 &= I_m [1 + 1]
 \end{aligned}$$

$$\text{Area under the curve for half cycle} = 2I_m$$

$$\begin{aligned}
 \text{Average Value } I_{av} &= \frac{\text{Area of Half Cycle}}{\text{Base length of half cycle}} \\
 I_{av} &= \frac{2 I_m}{\pi} \\
 I_{av} &= 0.637 I_m \\
 I_{av} &= 63.7\% I_m
 \end{aligned}$$

Similarly,

$$\begin{aligned}
 \text{Average Voltage, } V_{av} &= \frac{2 V_m}{\pi} \\
 V_{av} &= 0.637 V_m \\
 V_{av} &= 63.7\% V_m
 \end{aligned}$$

3.16 RMS Value:

Root Mean Square value of an alternating current is given by the steady D.C current, which produce the same heat as that produced by the alternating current in a given time and given resistance.

To obtain the average, divide the period into 'n' equal intervals. At these individual intervals let the current are $i_1, i_2, i_3 \dots, i_n$.

Thus the r.m.s value of the current and voltage are as follows:

$$I_{rms} = \frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}$$

Where, $i_1, i_2 \dots$ - instantaneous values

$$V_{rms} = \frac{v_1^2 + v_2^2 + v_3^2 + \dots + v_n^2}{n}$$

Where, $v_1, v_2 \dots$ - instantaneous values

R.M.S value is also defined as follows:

$$\text{RMS Value} = \sqrt{\frac{\text{Area under the squared curve}}{\text{Base length or period}}}$$

3.16.1 Expression for RMS Value:

$$\text{Instantaneous value of current } i = I_m \sin \theta \quad \text{Where, } \theta = \omega t$$

Consider an elementary strip of width $d\theta$ in the first half cycle of current wave. Let i^2 be the mid-ordinate of this strip.

$$\text{Area of strip} = i^2 d\theta$$

$$\begin{aligned}
 \text{Area under squared curve for full cycle} &= \int_0^{2\pi} (I_m \sin \theta)^2 d\theta \\
 &= \int_0^{2\pi} I_m^2 \sin^2 \theta d\theta \\
 &= I_m^2 \int_0^{2\pi} \sin^2 \theta d\theta \\
 &= I_m^2 \int_0^{2\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta \\
 &= I_m^2 \int_0^{2\pi} \left(\frac{1}{2} - \frac{\cos 2\theta}{2} \right) d\theta \\
 &= I_m^2 \left[\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right]_0^{2\pi} \\
 &= I_m^2 \left[\frac{2\pi}{2} - \frac{\sin 2.2\pi}{4} - \frac{0}{2} + \frac{\sin 0}{4} \right] \\
 &= I_m^2 [\pi - 0 - 0 + 0]
 \end{aligned}$$

$$\begin{aligned}
 \text{Area under squared curve for full cycle} &= I_m^2 \pi \\
 \text{RMS Value of current} \quad I_{rms} &= \sqrt{\frac{\text{Area under the squared curve}}{\text{Base length or period}}} \\
 I_{rms} &= \sqrt{\frac{I_m^2 \pi}{2 \pi}} \\
 &= \sqrt{\frac{I_m^2}{2}} \\
 &= \frac{I_m}{\sqrt{2}} \\
 I_{rms} &= 0.707 I_m \\
 I_{rms} &= 70.7\% I_m
 \end{aligned}$$

Similarly,

$$\begin{aligned}
 \text{RMS Value of voltage} \quad V_{rms} &= \frac{V_m}{\sqrt{2}} \\
 V_{rms} &= 0.707 V_m \\
 V_{rms} &= 70.7\% V_m
 \end{aligned}$$

3.17 Form factor:

It is defined as the ratio of RMS value to the average value of alternating current or voltage.

$$\begin{aligned}\text{Form Factor} &= \frac{\text{RMS Value}}{\text{Average Value}} \\ &= \frac{\frac{I_m}{\sqrt{2}}}{\frac{2I_m}{\pi}} = \frac{I_m}{\sqrt{2}} * \frac{\pi}{2I_m} = \frac{\pi}{2\sqrt{2}} = 1.11\end{aligned}$$

3.18 Peak factor: (Crest factor)

It is defined as the ratio of maximum value to the RMS value of alternating current or voltage.

$$\begin{aligned}\text{Peak Factor} &= \frac{\text{Maximum Value}}{\text{RMS Value}} \\ &= \frac{I_m}{\frac{I_m}{\sqrt{2}}} = I_m * \frac{\sqrt{2}}{I_m} = \sqrt{2} = 1.414\end{aligned}$$

Example: 7

The alternating current passing through a circuit is being by $i = 141.4 \sin 314.2t$. Calculate (a) maximum value of current (b) r.m.s value of current (c) the frequency and (d) the instantaneous value of the current when $t=0.02$ sec.

Given Data:

instantaneous value (i) $= 141.4 \sin 314.2t$

To Find:

- i. maximum value of current (I_m)
- ii. RMS Current (I_{rms})
- iii. Frequency (F)
- iv. 'I' when $t=0.02$ sec

Solution:

$$\begin{aligned}\text{Maximum value: } I_m &= 141.4 \text{ A} \\ \text{RMS Value: } I_{rms} &= \frac{I_m}{\sqrt{2}} \\ &= \frac{141.4}{\sqrt{2}} \\ I_{rms} &= 100 \text{ A} \\ \text{Angular velocity: } \omega &= 2\pi f \\ &= 314.2 \\ \text{Frequency: } F &= \frac{314.2}{2\pi} \\ F &= 50 \text{ Hz}\end{aligned}$$

When $t = 0.02$ sec

$$\begin{aligned}\text{Instantaneous value of current: } i &= 141.4 \sin 314 \times 0.02 \\ &= 141.4 \sin \left(\frac{180}{\pi} \right) \times 314.2 \times 0.02\end{aligned}$$

$$= 141.4 \sin 360 \\ i = 0$$

Answer:

- | | |
|--|--|
| i) Maximum value $I_m = 141.4 \text{ A}$ | ii) RMS Value $I_{rms} = 100 \text{ A}$ |
| iii) Frequency (f) = 50 Hz | iv) Instantaneous value of current $i = 0$ |

Example: 8

What is the equation for a sinusoidal current of 25 Hz frequency having an RMS value of 40 Ampere?

Given Data:

| | | |
|------------------------------------|---------|---------------------------------|
| RMS value of current (I_{rms}) | = 40 A | Equation of sinusoidal current. |
| Frequency (F) | = 25 Hz | |

Solution:

$$\text{Instantaneous value of current: } i = I_m \sin 2\pi ft$$

$$I_m = I_{rms} \times \sqrt{2}$$

$$= 40 \times \sqrt{2}$$

$$I_m = 56.57 \text{ A}$$


$$i = 56.57 \sin 157t$$

3.19 Phase:

The phase of an alternating quantity at any time 't' is defined by the angle by which the phasor makes with reference value.

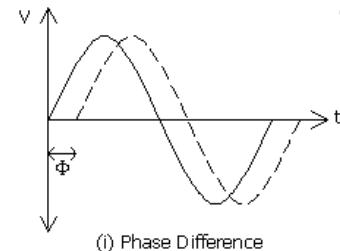
3.19.1 Phase Difference:

The difference in angle (ϕ) between two voltages or currents is known as *phase difference*.



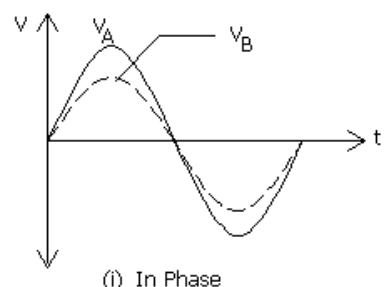
3.19.2 In-phase:

If the phase difference between the two voltages is zero, then they are said to be in-phase. In fig, V_A and V_B start at the same point and reach the maximum value at the same time. The angle between V_A and V_B is equal to zero.



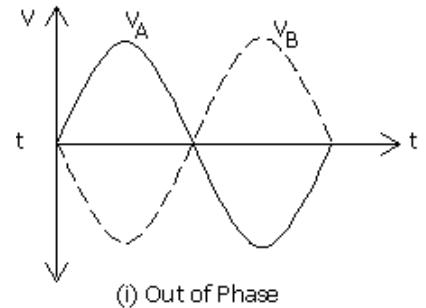3.19.3 Out of phase:

If the phase difference between two voltages is 180° then they are said to be out of phase. From the figure V_A and V_B are out of phase. Their starting points are same, but when voltage V_A reaches its positive maximum value, V_B reaches its negative maximum value.



3.20 Phase angle (θ):

It is defined as the angle between the voltage and current. It is represented by ' θ '.



3.20.1 Phase lag:

A lagging alternating quantity is one, which reaches its maximum (or zero) value later as compared to another alternating quantity. From the figure the alternating voltage V_B reaches its maximum value (or zero value) later by ϕ degrees when compared to V_A .

$$V_A = V_m \sin \omega t$$

and

$$V_B = V_m \sin (\omega t - \phi)$$

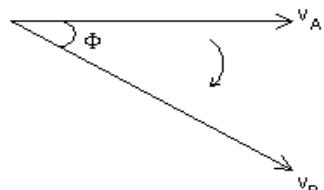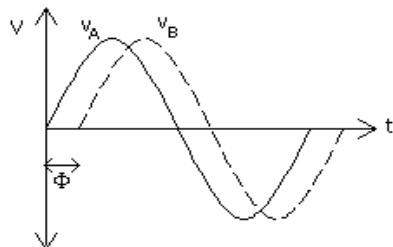



(i) Phase lag

The phasor diagram clearly shows that V_B lags V_A by an angle ϕ . A negative sign is used to denote the lagging angle.

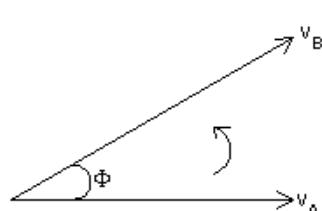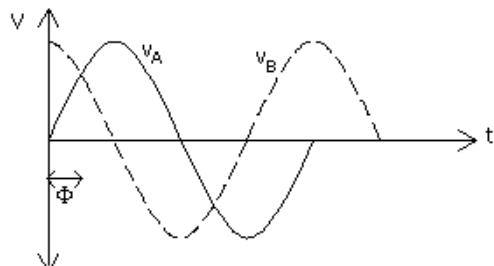3.20.2 Phase lead:

A leading quantity is one which reaches its maximum (or zero) value earlier than the other alternating quantity. From the figure, the alternating voltage V_B reaches its maximum or zero value earlier by ϕ degrees when compared to V_A . (V_B is leading than V_A)

$$V_A = V_m \sin \omega t, \text{ and } V_B = V_m \sin(\omega t + \phi) \quad \text{Where, '+ sign indicates leading}$$



(ii) Phase Lead

3.20.3 Phasor diagram:

So, far we have used phasor diagrams to solve problems on a.c circuits. A phasor diagram is a graphical representation of the phasors (i.e voltages and currents) of an a.c circuits and may not yield quick results in case of complex circuits. Engineers have developed techniques to represent a phasor in an algebraic (i.e mathematical) form. Such a technique is known as *phasor algebra or complex algebra*. Phasor algebra has provided a relatively simple but powerful tool for obtaining quick solution of a.c circuits. It simplifies the mathematical manipulation of phasors to a great extent.

In this chapter, we shall discuss the various methods of representing phasors in a mathematical form and their applications to a.c circuits.

Consider a phasor V lying along OX axis. If we multiply this phasor by -1 , the phasor is reversed i.e, it is rotated through 180° in the counter clockwise (CCW) direction.

Suppose this factor is j multiplying the phasor by j^2 rotates the phasor through 180° in CCW direction. This means that multiplying the phasor by j is the same as multiply by -1 .

$$j^2 = -1$$

We arrive at a very important conclusion that when a phasor is multiplied by j , the phasor is rotated through 90° in the CCW direction. Each successive multiplication by j rotates the phasor through an additional 90° in the CCW direction. It is easy to see that multiplying a phasor by,

$$j = \sqrt{-1} \quad \dots\dots\dots 90^\circ \text{ CCW direction from OX axis}$$

$$j^2 = -1 \quad \dots\dots\dots 180^\circ \text{ CCW direction from OX axis}$$

$$j^3 = j^2 \cdot j = -j \quad \dots\dots\dots 270^\circ \text{ CCW direction from OX axis}$$

$$j^4 = j^2 \cdot j^2 = 1 \quad \dots\dots\dots 360^\circ \text{ CCW direction from OX axis}$$

3.20.4 Reference Phasor:

The reference phasor is normally drawn horizontally along x-axis.

3.20.5 Angular velocity (ω):

The angle of one full cycle is 2π radians. When one second is covered in ' f ' cycles, the angle covered per second is $2\pi f$ radians.

Angular velocity, $\omega = 2\pi f$ radians / second.

3.21 Impedance (Z):

It is the opposition offered by an AC circuit to the flow of AC current. It is denoted by the letter 'Z'. Its unit is Ohm (Ω).

$$\text{Impedance (Z)} = \frac{V}{I}$$

Impedance in complex quantity: $Z = R + jX$

Where, Real part : R - Resistance

Imaginary part: X - Reactance.

3.22 Inductive Reactance (X_L):

The opposition offered by an inductance to current flow is called inductive reactance. It is denoted by the letter X_L and its unit is Ohm (Ω).

$$\text{Inductive Reactance } X_L = 2\pi fL$$

3.23 Capacitive Reactance (X_C):

The opposition offered by a capacitance to current flow is called capacitive reactance. It is denoted by the letter X_C and its unit is ohm (Ω).

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

3.24 Admittance (Y):

It is defined as the reciprocal of impedance. It is represented by the letter 'Y' and its unit is mho (Ω) or siemen.

$$Y = \frac{1}{Z}$$

Admittance (Y) in complex quantity $Y = G + jB$

Where, Real part : G - Conductance

Imaginary part : B - Susceptance

3.25 Conductance (G):

It is defined as the reciprocal of resistance. It is represented by the letter G and its unit is mho (Ω) or siemen.

$$G = \frac{1}{R}$$

3.26 Susceptance (B):

Susceptance is defined as the reciprocal of reactance. Its unit is also mho. It is denoted by the letter 'B' and its unit is mho (Ω) or siemen.

$$B = \frac{1}{X}$$

3.27 Power (P):

Power is generally defined as the rate at which the work is done.

3.27.1 Real power (P):

It is a resistive power that is dissipated as heat. Its unit is Watts. It is always positive.

$$P = VI \cos \theta$$

3.27.2 Reactive Power (Q):

It is the product of the power developed in reactance of the circuit. Its unit is Volt-Ampere Reactive (VAR).

$$Q = VI \sin \theta$$

3.27.3 Apparent Power (S):

It is defined as the product of magnitude of voltage and magnitude of current. It is measured in Volt-Ampere (VA).

$$S = VI$$

3.28 Power Factor ($\cos \theta$):

Power factor is defined as the cosine value of phase angle between the voltage and current.

Or

Power factor is defined as the ratio of real power to apparent power. It has no unit. It is always less than unity.

$$\text{Power Factor} = \frac{\text{Real Power}}{\text{Apparent Power}} = \frac{VI \cos \theta}{VI}$$

or

It is the ratio of resistance to the impedance of the a.c circuit.

$$\text{Power Factor} = \frac{R}{Z}$$

3.29 Voltage and Current Relationship in Pure Resistance:

Consider a circuit having a resistor of resistance R ohm and connected across a.c source.

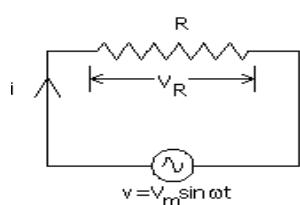


Fig. (i) Circuit Arrangement

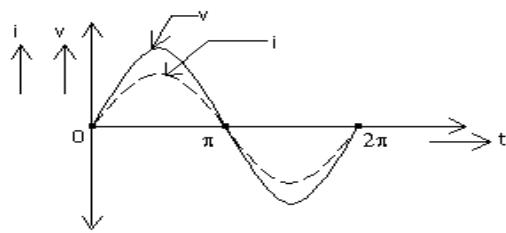


Fig. (ii) Wave form representation

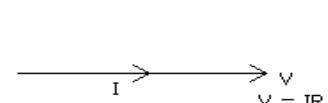


Fig. (iii) Phasor representation

Let 'v' be the AC voltage applied across the pure resistance 'R' and 'i' be the current flowing through the resistor.

According to ohm's law :

$$v = I \cdot R$$

$$i = \frac{v}{R}$$

$$v = V_m \sin \omega t \quad \dots \dots \dots (1)$$

$$i = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \cdot \sin \omega t \quad \dots \dots \dots (2)$$

$$\text{where, } i_m = \frac{V_m}{R}$$

$$\text{Hence, } i = i_m \cdot \sin \omega t \quad \dots \dots \dots (3)$$

$$\text{From equation (1): Instantaneous voltage (v)} = V_m \sin \omega t$$

$$\text{From equation (3): Instantaneous current (i)} = I_m \sin \omega t$$

$$I = 0 \text{ when } v = 0, \text{ so } i \propto v$$

$$\text{From equation (1) & (3): Phase angle between v & i} = 0$$

$$\text{Power factor } (\cos \theta) = \cos \theta = \cos 0 = 1 \text{ (unity)}$$

$$\text{Relationship between v & i} = \text{in phase}$$

$$\text{Instantaneous power: } p = v \times i$$

$$\text{Instantaneous power: } p = V_m \sin \omega t \times I_m \sin(\omega t \pm \theta)$$

$$\text{The average power over one complete cycle} = P_{av}$$

$$\text{Average power: } P_{av} = \frac{1}{\pi} \int_0^{\pi} p d(\omega t)$$

$$P_{av} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \times I_m \sin \omega t d(\omega t)$$

$$P_{av} = \frac{1}{\pi} \int_0^{\pi} V_m I_m \sin^2 \omega t d(\omega t)$$

$$P_{av} = \frac{V_m I_m}{\pi} \left[\frac{1 - \cos 2\omega t}{2} \right]_0^{\pi} d(\omega t)$$

$$P_{av} = \frac{V_m I_m}{2\pi} [1 - \cos 2\omega t]_0^{\pi} d(\omega t)$$

$$P_{av} = \frac{V_m I_m}{2\pi} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi}$$

$$P_{av} = \frac{V_m I_m}{2\pi} \left[\pi - \frac{\sin 2\pi}{2} - 0 + \frac{\sin 0}{2} \right]$$

$$P_{av} = \frac{V_m I_m}{2\pi} [\pi]$$

$$P_{av} = \frac{V_m I_m}{2}$$

$$P_{av} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$Average Power P_{av} = V I$$

Where, V and I are rms values

3.30 Voltage and Current Relationship in Pure Inductance:

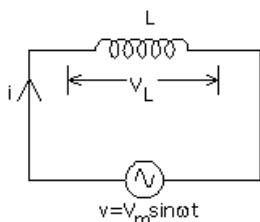


Fig. (i) Circuit Arrangement

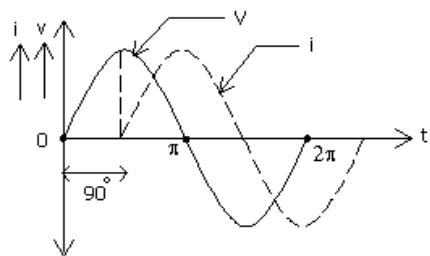


Fig. (ii) Wave form representation

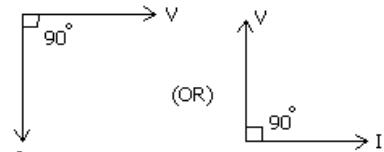


Fig. (iii) Phasor representation

When an alternating voltage is applied to an inductive coil, the back emf produced due to self-inductance opposes the rise or fall of current through it. Since there is no ohmic drop, the applied voltage has to overcome this induced e.m.f only.

$$\text{Let, } v = V_m \sin \omega t \quad \dots \dots \dots (1)$$

$$\text{The voltage across the coil, } v = L \frac{di}{dt}$$

$$v dt = L di \quad \dots \dots \dots (2)$$

Where, L = Self inductance of the coil

$\frac{di}{dt}$ = rate of change of current

By integrating the equation (2),

$$\int v dt = \int L di$$

$$\frac{1}{L} \int v dt = \int di$$

$$\frac{1}{L} \int v dt = i$$

$i = \frac{1}{L} \int v dt$

we know that $v = V_m \sin \omega t$

$$\therefore i = \frac{V_m}{L} \int \sin \omega t dt$$

$$i = \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right]$$

$$i = \frac{V_m}{\omega L} [-\cos \omega t]$$

Let $\omega L = X_L$ = Inductive Reactance

$$\therefore i = \frac{V_m}{X_L} [-\cos \omega t]$$

Since $\sin(\theta - 90^\circ) = -\cos \theta$, we can write,

$$i = \frac{V_m}{X_L} \sin(\omega t - 90^\circ)$$

Let, $\frac{V_m}{\sqrt{2}} = I_m$ = Maximum value of current

$$\therefore i = I_m \sin(\omega t - 90^\circ) \quad \dots \dots \dots (3)$$

From the equations (1)and (3)it is very clear that the current lags the voltage by 90° , in a pure inductance.

From equation (1): Instantaneous voltage (v) = $V_m \sin \omega t$

$$\text{From equation (3):} \quad \text{Instantaneous current } (i) = I_m \sin(\omega t - 90^\circ)$$

From equation (1) & (3): Phase angle between v & i = 90°

$$\text{Power factor} (\cos \theta) = \cos \theta = \cos 90^\circ = 0 \text{ (lagging)}$$

Relationship between v & i = Current lags the voltage by 90°

$$\text{Average power (P)} = \text{v} \times \text{i}$$

$$= V_m \sin \omega t \times I_m \sin(\omega t - 90^\circ)$$

$$\text{Average Power, } P = \frac{1}{\pi} \int_0^{\pi} pd(\omega t)$$

$$P = -\frac{V_m I_m}{2\pi} \int_0^{\pi} \sin 2\omega t d(\omega t) = -\frac{V_m I_m}{2\pi} \int_0^{\pi} \sin 2\omega t d(\omega t)$$




$$P = -\frac{V_m I_m}{2\pi} \left[\frac{-\cos 2\omega t}{2} \right]_0^\pi = -\frac{V_m I_m}{2\pi} \left[\frac{-\cos 2\pi + \cos 0}{2} \right]$$

$$P = -\frac{V_m I_m}{2\pi} \left[\frac{-1}{2} + \frac{1}{2} \right] = -\frac{V_m I_m}{2\pi} [0] = 0$$

Average Power, $P = 0$

Thus the average power in a pure inductive circuit is zero.

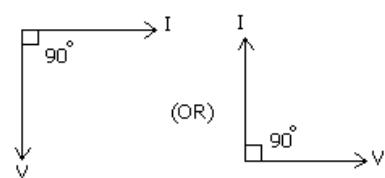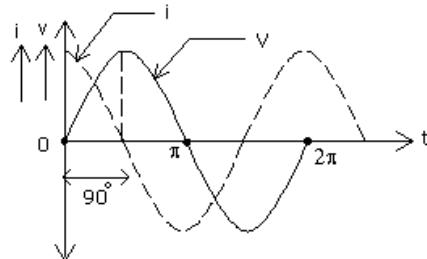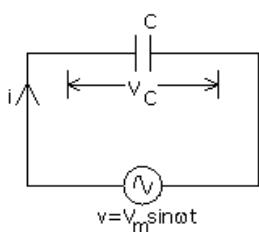3.31 Voltage and current relationship in capacitance:



Let 'v' is the instantaneous voltage applied across the capacitance 'C' and 'i' is the AC current flowing through it.

$$\text{Let, } v = V_m \sin \omega t \quad \dots \dots \dots (1)$$

$$\text{The current through capacitor, } i = C \frac{dv}{dt} \quad \dots \dots \dots (2)$$

Where, C = Capacitance

$\frac{dv}{dt}$ = rate of change of voltage

Substitute the value of v in equation (2),

$$i = C \frac{dv}{dt}$$

$$i = C \frac{dV_m \sin \omega t}{dt}$$

$$i = CV_m \frac{d \sin \omega t}{dt}$$

$$i = CV_m \cos \omega t \cdot \omega$$

$$i = C \omega V_m \cos \omega t$$

$$i = \frac{V_m}{\frac{1}{\omega C}} \cos \omega t$$

$$\text{Let, } \frac{1}{\omega C} = X_C = \text{Capacitive Reactance}$$

$$i = \frac{V_m}{X_C} \cos \omega t$$

$$\text{Since, } \sin(\theta + 90^\circ) = \cos \theta$$

$$\text{or } \sin(\omega t + 90^\circ) = \cos \omega t$$

$$i = \frac{V_m}{X_C} \sin(\omega t + 90^\circ)$$

$$\text{Let, } I_m = \frac{V_m}{X_C}$$

$$i = I_m \sin(\omega t + 90^\circ) \quad \dots \dots \dots (3)$$

From the equations (1) and (3) it is very clear that the current leads the voltage by 90° , in a pure capacitive circuit.

| | | |
|--------------------------|--------------------------------|--|
| From equation (1): | Instantaneous voltage (v) | $= V_m \sin \omega t$ |
| From equation (3): | Instantaneous current (i) | $= I_m \sin(\omega t + 90^\circ)$ |
| From equation (1) & (3): | Phase angle between v & i | $= 90^\circ$ |
| | Power factor ($\cos \theta$) | $= \cos \theta = \cos 90 = 0$ (leading) |
| | Relationship between v & i | $=$ Current leads the voltage by 90° |
| | Average power (P) | $= v \times i$ |
| | | $P = V_m \sin \omega t \times I_m \sin(\omega t + 90^\circ)$ |

$$\text{Average Power, } P = \frac{1}{\pi} \int_0^{\pi} pd(\omega t)$$

$$P = \frac{1}{\pi} \int_0^{\pi} \frac{V_m I_m}{2} \sin 2\omega t d(\omega t) = \frac{V_m I_m}{2\pi} \int_0^{\pi} \sin 2\omega t d(\omega t)$$

$$P = \frac{V_m I_m}{2\pi} \left[\frac{-\cos 2\omega t}{2} \right]_0^{\pi} = \frac{V_m I_m}{2\pi} \left[\frac{-\cos 2\pi}{2} + \frac{\cos 0}{2} \right]$$

$$P = \frac{V_m I_m}{2\pi} \left[\frac{-1}{2} + \frac{1}{2} \right] = \frac{V_m I_m}{2\pi} [0] = 0$$

$\boxed{\text{Average Power, } P = 0}$

Thus the average power in a pure capacitive circuit is zero.

3.32 SERIES RL CIRCUITS:

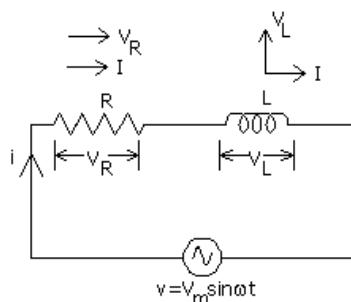


Fig. (i) RL Series Circuit

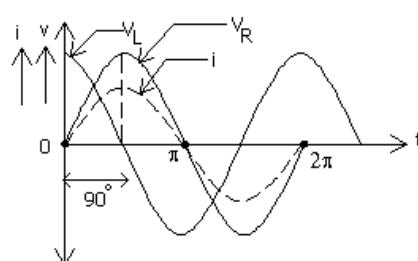


Fig. (ii) Wave form representation

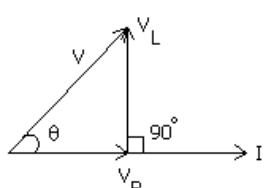


Fig. (iii) Phasor Diagram

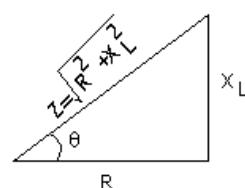


Fig. (iv) Impedance Triangle

Consider RL series circuit is shown in the figure (i), a pure resistance R and a pure inductive coil of inductance L are connected in series.

$$\begin{aligned}
 \text{r. m. s value of applied voltage} &= V \\
 \text{Current through R and L} &= I && (\text{Same current}) \\
 \text{Reference phasor} &= I && (\text{Same current}) \\
 \text{Voltage drop across the resistance} &= V_R = IR && (\text{in - phase with current}) \\
 \text{Voltage drop across the inductive coil} &= V_L = IX_L && (I \text{ lags the } V \text{ by } 90^\circ) \\
 \text{Voltage } V &= \text{Vector sum of } V_R \text{ and } V_L \\
 \text{Phase angle difference between } V \& I = \theta \\
 \text{From phasor diagram, } V^2 &= V_R^2 + V_L^2 \\
 V &= \sqrt{V_R^2 + V_L^2} = \sqrt{(IR)^2 + (IX_L)^2} \\
 &= I\sqrt{R^2 + X_L^2} \\
 \frac{V}{I} &= \sqrt{R^2 + X_L^2} \\
 Z &= \sqrt{R^2 + X_L^2} \\
 \tan \theta &= \frac{X_L}{R} \\
 \theta &= \tan^{-1}\left(\frac{X_L}{R}\right) \\
 \tan \theta &= \frac{X_L}{R}
 \end{aligned}$$

Average Power:

$$\begin{aligned}
 \text{Instantaneous voltage (v)} &= V_m \sin \omega t \\
 \text{Instantaneous current (i)} &= I_m \sin(\omega t - \theta) \\
 \text{Phase angle between } v \& i = \theta \\
 \text{Power factor } (\cos \theta) &= \cos \left[\tan^{-1}\left(\frac{X_L}{R}\right) \right] \\
 \text{Relationship between } v \& i &= \text{Current lags the voltage by } \theta \\
 \text{Instantaneous power: } p &= v \times i \\
 \text{Instantaneous power: } p &= V_m \sin \omega t \times I_m \sin(\omega t - \theta) \\
 &= V_m I_m [\sin \omega t \times \sin(\omega t - \theta)] \\
 p &= V_m I_m \left[\frac{\cos \theta - \cos(2\omega t - \theta)}{2} \right] \\
 p &= \frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos(2\omega t - \theta)
 \end{aligned}$$

The average power over one complete cycle = P_{av}

$$\begin{aligned}
 \text{Average power:} \quad P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} p d\theta \\
 P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos(2\omega t - \theta) d\theta \\
 P_{av} &= \frac{1}{2\pi} \cdot \frac{V_m I_m}{2} \int_0^{2\pi} \cos \theta - \cos(2\omega t - \theta) d\theta \\
 P_{av} &= \frac{1}{2\pi} \cdot \frac{V_m I_m}{2} \left[\int_0^{2\pi} \cos \theta d\theta - \int_0^{2\pi} \cos(2\omega t - \theta) d\theta \right] \\
 P_{av} &= \frac{V_m I_m}{2} \cos \theta \\
 P_{av} &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \theta \\
 P_{av} &= V I \cos \theta
 \end{aligned}$$

Where, V and I are rms values

3.33 SERIES RC CIRCUITS:

Consider RC series circuit is shown in the figure (i), a pure resistance R and a pure capacitance C are connected in series.

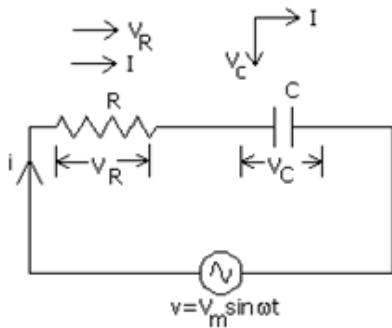


Fig. (i) RC Series Circuit

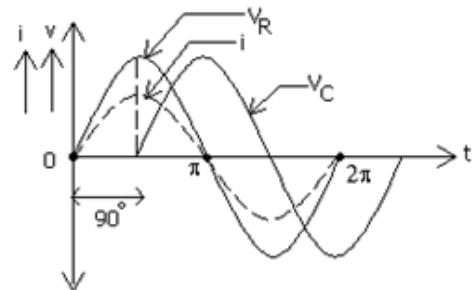


Fig. (ii) Wave form representation

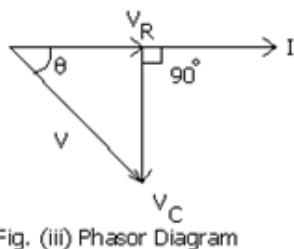


Fig. (iii) Phasor Diagram

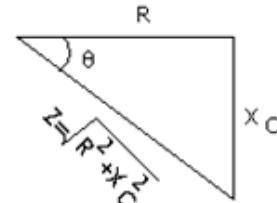


Fig. (iv) Impedance Triangle

Consider RC series circuit is shown in the figure (i), a pure resistance R and a pure capacitor of capacitance C are connected in series.

| | | | |
|--------------------------------------|---------------|---|--------------------------------|
| r. m. s value of applied voltage | = | V | |
| Current through R and L | = | I | (Same current) |
| Reference phasor | = | I | (Same current) |
| Voltage drop across the resistance | = | $V_R = I R$ | (in - phase with current) |
| Voltage drop across the capacitor | = | $V_C = I X_C$ | (I leads the V by 90°) |
| Voltage V | = | Vector sum of V_R and V_C | |
| Phase angle difference between V & I | = | θ | |
| From phasor diagram, | V^2 | $= V_R^2 + V_C^2$ | |
| | V | $= \sqrt{V_R^2 + V_C^2} = \sqrt{(IR)^2 + (IX_C)^2}$ | |
| | | $= I \sqrt{R^2 + X_C^2}$ | |
| | $\frac{V}{I}$ | $= \sqrt{R^2 + X_C^2}$ | |
| | Z | $= \sqrt{R^2 + X_C^2}$ | |
| $\tan \theta$ | $=$ | $\frac{X_C}{R}$ | |
| θ | $=$ | $\tan^{-1}(\frac{X_C}{R})$ | |
| $\tan \theta$ | $=$ | $\frac{X_C}{R}$ | |

Average Power:

| | | | |
|--------------------------------|-----|--|--|
| Instantaneous current (v) | = | $V_m \sin \omega t$ | |
| Instantaneous voltage (i) | = | $I_m \sin(\omega t + \theta)$ | |
| Phase angle between v & i | = | θ | |
| Power factor ($\cos \theta$) | = | $\cos [\tan^{-1}(\frac{X_C}{R})]$ | |
| Relationship between v & i | = | Current leads the voltage by θ | |
| Instantaneous power: | p | $= v \times i$ | |
| Instantaneous power: | p | $= V_m \sin \omega t \times I_m \sin(\omega t + \theta)$ | |
| | p | $= V_m I_m [\sin \omega t \times \sin(\omega t + \theta)]$ | |
| | p | $= V_m I_m [\frac{\cos(-\theta) + \cos(2\omega t + \theta)}{2}]$ | |
| | p | $= \frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos(2\omega t + \theta)$ | |

$$\text{The average power over one complete cycle} = P_{av}$$

Average power :

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} p d\theta$$

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos(2\omega t + \theta) d\theta$$

$$P_{av} = \frac{1}{2\pi} \cdot \frac{V_m I_m}{2} \int_0^{2\pi} \cos \theta - \cos(2\omega t + \theta) d\theta$$

$$P_{av} = \frac{1}{2\pi} \cdot \frac{V_m I_m}{2} \left[\int_0^{2\pi} \cos \theta d\theta - \int_0^{2\pi} \cos(2\omega t + \theta) d\theta \right]$$

$$P_{av} = \frac{V_m I_m}{2} \cos \theta$$

$$P_{av} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \theta$$

$$P_{av} = V I \cos \theta$$

Where, V and I are rms values

3.34 SERIES RLC CIRCUIT:

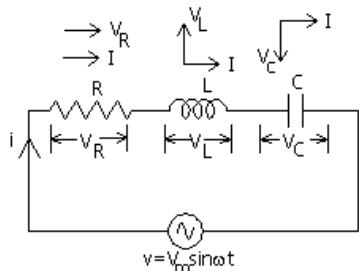


Fig. (i) RLC Series Circuit

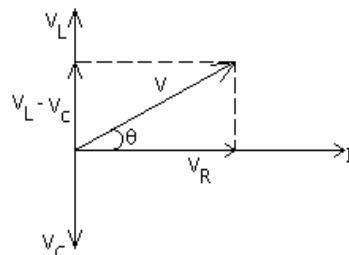


Fig. (ii) Phasor diagram ($X_L > X_C$)

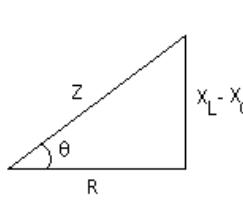


Fig. (iii) Impedance Triangle ($X_L > X_C$)

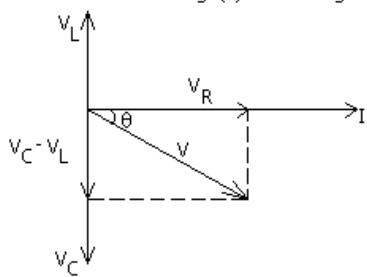


Fig. (iv) Phasor diagram ($X_C > X_L$)

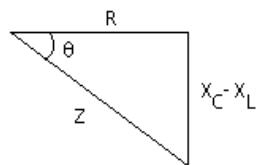


Fig. (v) Impedance Triangle ($X_C > X_L$)

Consider RLC series circuit is shown in the figure (i), a pure resistance R, a pure inductance L and a pure capacitance C are connected in series.

| | | |
|--------------------------------------|---|--------------------------------|
| r. m. s value of applied voltage | = V | |
| Current through R and L | = I | (Same current) |
| Reference phasor | = I | (Same current) |
| Voltage drop across the resistance | = $V_R = IR$ | (in – phase with current) |
| Voltage drop across the inductor | = $V_L = IX_L$ | (I lags the V by 90°) |
| Voltage drop across the capacitor | = $V_C = IX_C$ | (I leads the V by 90°) |
| Voltage V | = Vector sum of V_R , V_L and V_C | |
| Phase angle difference between V & I | = θ | |

Case – I: $X_L > X_C$

$$\text{The net reactnace } X = X_L - X_C$$

$$\begin{aligned} \text{From phasor diagram, } V^2 &= V_R^2 + (V_L - V_C)^2 \\ V &= \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(IR)^2 + (IX_L - IX_C)^2} \\ &= I\sqrt{R^2 + (X_L - X_C)^2} \\ \frac{V}{I} &= \sqrt{R^2 + (X_L - X_C)^2} \\ Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ \tan \theta &= \frac{(X_L - X_C)}{R} \\ \theta &= \tan^{-1}\left(\frac{X_L - X_C}{R}\right) \\ \tan \theta &= \frac{X_L - X_C}{R} \end{aligned}$$

| | |
|--------------------------------|--|
| Instantaneous voltage (v) | = $V_m \sin \omega t$ |
| Instantaneous current (i) | = $I_m \sin(\omega t - \theta)$ |
| Phase angle between v & i | = θ |
| Power factor ($\cos \theta$) | = $\cos [\tan^{-1}\left(\frac{X_L - X_C}{R}\right)]$ |
| Relationship between v & i | = Current lags the voltage by θ |

Case – II: $X_C > X_L$

$$\text{The net reactnace } X = X_C - X_L$$

$$\begin{aligned} \text{From phasor diagram, } V^2 &= V_R^2 + (V_C - V_L)^2 \\ V &= \sqrt{V_R^2 + (V_C - V_L)^2} = \sqrt{(IR)^2 + (IX_C - IX_L)^2} \end{aligned}$$

$$\begin{aligned}
 &= I\sqrt{R^2 + (X_C - X_L)^2} \\
 \frac{V}{I} &= \sqrt{R^2 + (X_C - X_L)^2} \\
 Z &= \sqrt{R^2 + (X_C - X_L)^2} \\
 \tan \theta &= \frac{(X_C - X_L)}{R} \\
 \theta &= \tan^{-1}\left(\frac{X_C - X_L}{R}\right) \\
 \tan \theta &= \frac{X_C - X_L}{R}
 \end{aligned}$$

$$\begin{aligned}
 \text{Instantaneous current (v)} &= V_m \sin \omega t \\
 \text{Instantaneous voltage (i)} &= I_m \sin(\omega t + \theta) \\
 \text{Phase angle between v & i} &= \theta \\
 \text{Power factor } (\cos \theta) &= \cos [\tan^{-1}\left(\frac{X_C - X_L}{R}\right)] \\
 \text{Relationship between v & i} &= \text{Current leads the voltage by } \theta
 \end{aligned}$$

Average Power:


$$\begin{aligned}
 \text{Instantaneous power: } p &= v \times i \\
 \text{Instantaneous power: } p &= V_m \sin \omega t \times I_m \sin(\omega t \pm \theta) \\
 \text{The average power over one complete cycle} &= P_{av} \\
 \text{Average power: } P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} p \, d\theta \\
 P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \times I_m \sin(\omega t \pm \theta) \, d\theta \\
 P_{av} &= \frac{V_m I_m}{2} \cos \theta \\
 P_{av} &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \theta \\
 P_{av} &= V I \cos \theta
 \end{aligned}$$

Where, V and I are rms values

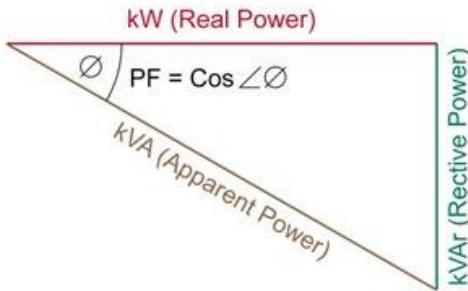3.35 Power triangle:

The relationship among active power, reactive power and apparent power is illustrated by a right angled triangle called the power triangle. Reactive power is the vertical axis of the triangle, active power is the horizontal axis and apparent power or total power is the hypotenuse.

$$\text{Power Factor (pf)} = \frac{\text{kW (Real Power)}}{\text{kVA (Total Power)}}$$



3.35.1 Active Power:

When an active component of current is multiplied with circuit voltage, it results in active or true power. This power produces torque in motors, heat in heaters, light in lamps etc., Further wattmeter indicates this power.

3.35.2 Reactive Power:

When a reactive component of current is multiplied with circuit voltage, it results in reactive power. This power flows back and forth without doing any work. This power determines the power factor of the circuit.

3.35.3 Apparent Power:

When the circuit current is multiplied with circuit voltage, it results in apparent power. i.e product of voltage and current. In a.c circuit, there is phase difference between voltage and current so that product of voltage and current does not give real power. To avoid confusion, it is measured in volt-ampere.

3.35.4 Power Factor:

From power triangle, the power factor may also be determined by taking the ratio of true power to apparent power.

$$\text{Power Factor} = \frac{\text{True Power or Active Power}}{\text{Apparent Power}}$$

Example: 9


Determine the impedance of a RL series circuit with $R=20 \Omega$ and $L=0.1H$ when connected to a 230V, 50Hz supply.

Given Data:

| | |
|----------------|---------------|
| Circuit | = R.L. Series |
| Resistance (R) | = 20Ω |
| Inductance (L) | = $0.1 H$ |
| Frequency (F) | = 50 Hz |
| Voltage (V) | = 230V |

To Find:

- i. Inductive reactance (X_L)
- ii. Impedance (Z)

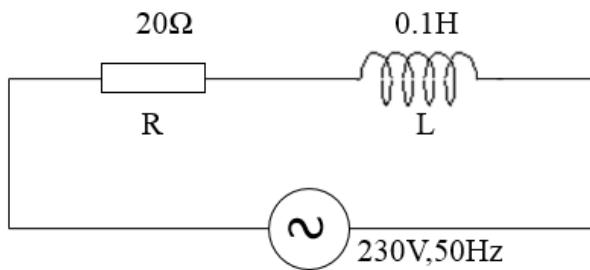Solution:

$$Z = R + j X_L$$

$$\begin{aligned} \text{Inductive Reactance } (X_L) &= 2\pi f L ; \Omega \\ &= 2 \times 3.14 \times 50 \times 0.1 ; \Omega \\ X_L &= 31.42 \Omega \end{aligned}$$

$$\begin{aligned} \text{Impedance } (Z) &= \sqrt{R^2 + (X_L)^2} \Omega \\ \text{Impedance } (Z) &= \sqrt{20^2 + (31.42)^2} \\ \text{Impedance } (Z) &= 37.24 \Omega \\ \text{Impedance } (Z) &= 20 + j37.24 ; \Omega \end{aligned}$$

Answer:

i) Inductive Reactance (X_L) = 31.42Ω ii) Impedance (Z) = 37.24Ω


Example: 10

Find the impedance, current and phase angle of the series circuit having a resistance of 10Ω and inductance of 10millihenry. The applied voltage is 200V, 50Hz.

Given Data:

| | | |
|----------------|-------------------------|-------------------------------|
| Circuit | = R.L. Series | To Find: |
| Resistance (R) | = 10Ω | i. Impedance (Z) |
| Inductance (L) | = 10 mH | ii. Current (I) |
| | = $10 \times 10^{-3} H$ | iii. Phase angle (θ) |
| Frequency (F) | = 50 Hz | |
| Voltage (V) | = 200V | |

Solution:

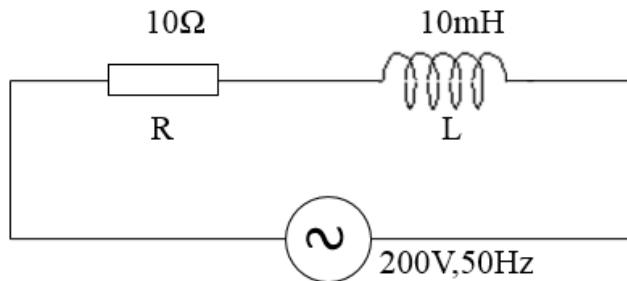

$$\begin{aligned}\text{Inductive Reactance } (X_L) &= 2\pi fL ; \Omega \\ &= 2 \times 3.14 \times 50 \times 10 \times 10^{-3} ; \Omega \\ X_L &= 3.14 \Omega\end{aligned}$$

$$\text{Impedance } (Z) = \sqrt{R^2 + (X_L)^2} \Omega$$

$$\text{Impedance } (Z) = \sqrt{10^2 + (3.14)^2}$$

Impedance (Z) = 10.48 Ω

$$\text{Current (I)} = \frac{V}{Z}$$

$$I = \frac{200}{1048}$$

$$I = 19.08 \text{ Amps}$$

$$\text{Power Factor } (\cos \theta) = \frac{R}{Z}$$

$$\cos \theta = \frac{10}{10.48} = 0.954 \text{ lag}$$

$$\text{Phase angle} \quad \theta = \cos^{-1} 0.954 = 17.44^\circ$$

Answer:

- i) Impedance (Z) = 10.48Ω
 - ii) Current (I) = $19.08Amps$
 - iii) Phase angle (θ) = 17.44°

Example: 11

A voltage of 125V at 60Hz is applied across a non-inductive resistor connected in series with an inductance. The current is 2.2A. The power loss in the resistor is 96.8W and that the inductor is negligible calculate the resistance and the inductance.

Given Data:

| | | | |
|----------------|---|-------------|--------------------|
| Circuit | = | R.L. Series | i. Resistance (R) |
| Voltage (V) | = | 125 V | ii. Inductance (L) |
| Frequency (F) | = | 60 Hz | |
| Current (I) | = | 2.2A | |
| Power loss (P) | = | 96.8W | |

To Find:

- i. Resistance (R)
 - ii. Inductance (L)

Solution:

$$\text{Power} = I^2 R$$

$$\text{Resistance } R = \frac{P}{I^2}$$

$$R = \frac{96.8}{2.2^2} = 20\Omega$$

$$\text{Power} = V I \cos \theta$$

$$\cos \theta = \frac{P}{V \cdot I}$$

$$= \frac{96.8}{125.2 \cdot 2} = 0.352$$

$$\theta = \cos^{-1} 0.325$$

$$\theta = 69.39^\circ \text{ lag}$$

$$\text{Impedance } (Z) = \frac{V}{I}$$

$$Z = \frac{125}{2.2} = 56.8\Omega$$

$$\sin \theta = \frac{X_L}{Z}$$

$$X_L = \sin \theta \times Z$$

$$= \sin 69.39 \times 56.8$$

$$X_L = 53.16\Omega$$

$$\text{Inductive Reactance } (X_L) = 2\pi f L ; \Omega$$

$$L = \frac{X_L}{2\pi f}$$

$$= \frac{53.16}{2 \times 3.14 \times 60}$$

$$L = 0.141 \text{ H}$$

Answer:

- i) Resistance (R) = 20 Ω ii) Inductance (L) = 0.141 H

Example: 12

A coil of power factor 0.8 is in series with a $100\mu\text{F}$ capacitor and the combination is put across a 50Hz supply. The potential across the coil is found equal to that across the capacitor. Find the resistance and inductance of the coil.

Given Data:

$$\text{Circuit} = \text{R.L.C Series}$$

$$\text{Power Factor } (\cos \theta) = 0.8$$

$$\text{Frequency } (F) = 50 \text{ Hz}$$

$$\text{Capacitor } (C) = 100\mu\text{F}$$

To Find:

i. Resistance (R)

ii. Inductance (L)

Solution:

$$\begin{aligned}
 \text{Voltage across coil} &= \text{Voltage across capacitor} \\
 \text{Also } Z_L &= Z_C \\
 \text{Capacitive Reactance } (X_C) &= \frac{1}{2\pi f C}; \Omega \\
 &= \frac{1}{2 \times \pi \times 50 \times 100 \times 10^{-6}} = 31.84 \Omega \\
 Z_C &= X_C = 31.84 \Omega \\
 Z_{Coil} &= Z_C = 31.84 \Omega \\
 \text{Resistance of the coil } (R) &= Z \cdot \cos \theta \\
 &= 31.48 \times 0.8 = 25.18 \Omega \\
 \text{Inductive Reactance } (X_L) &= Z \cdot \sin \theta \\
 &= 31.48 \times 0.6 = 18.89 \Omega \\
 \text{Inductive Reactance } (X_L) &= 2\pi f L; \Omega \\
 \text{Inductance } L &= \frac{X_L}{2\pi f} \\
 &= \frac{18.89}{2 \times 3.14 \times 50} \\
 L &= 0.06 \text{ H}
 \end{aligned}$$

Example: 13

A current of 10A flows in a circuit with a 45° angle of lag when the applied voltage is 100V.
Find the resistance, reactance and impedance of the circuit.

Given Data:

| | | |
|------------------------|---------------|------------------------------------|
| Circuit | = R.L. Series | To Find: |
| Current (A) | = 10A | i. resistance (R) |
| Phase Angle (ϕ) | = 45° | ii. Impedance (Z) |
| Voltage (V) | = 230V | iii. inductive reactance (X_L) |

Solution:

$$\begin{aligned}
 \text{Impedance } (Z) &= \frac{V}{I} \\
 &= \frac{100}{10} \\
 Z &= 10 \Omega \\
 \text{Power factor} &= \cos \theta \\
 &= \cos 45^\circ \\
 &= 0.707 \\
 \text{Also } \cos \theta &= \frac{R}{Z} \\
 R &= Z \cos \theta
 \end{aligned}$$

$$\begin{aligned}
 &= 10 \times 0.707 \\
 R &= 7.07 \Omega \\
 \text{Impedance } (Z) &= \sqrt{R^2 + (X_L)^2} \Omega \\
 X_L &= \sqrt{Z^2 - R^2} \Omega \\
 &= \sqrt{10^2 - 7.07^2} \Omega \\
 X_L &= 7.07 \Omega
 \end{aligned}$$

Answer:

- | | | | | |
|------|-----------------------------|----------|-----|----------------------|
| I. | Resistance (R) | = 7.07 Ω | II. | Impedance (Z) = 10 Ω |
| III. | Reactance (X _L) | = 7.07 Ω | | |


Example: 14

A resistor of 100Ω is connected in series with 50μF capacitor to supply of 200V, 50Hz. Find (i) impedance (ii) current (iii) power factor (iv) voltage across the resistor and (v) voltage across capacitor.

Given Data:

| | | |
|--------------------|---------------------------|-------------------------|
| Circuit | = R.C Series | To Find: |
| Resistance (R) | = 100 Ω | i) Impedance (Z) |
| Capacitance (C) | = 50 μF | ii) Current (I) |
| | = 50 × 10 ⁻⁶ F | iii) Power Factor (P.F) |
| Supply Voltage (V) | = 200 Volts | iv) P.D across R |
| Frequency (F) | = 50 Hz | v) P.D across C |

Solution:

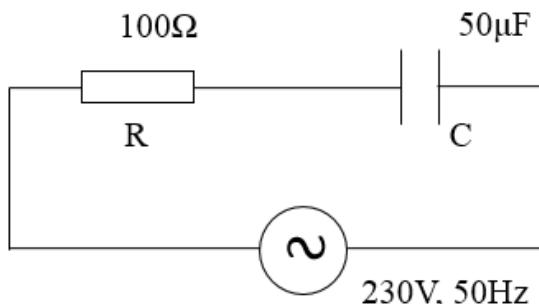

$$\begin{aligned}
 \text{Capacitive Reactance } (X_C) &= \frac{1}{2\pi f C}; \Omega \\
 &= \frac{1}{2 \times \pi \times 50 \times 50 \times 10^{-6}} \\
 X_C &= 63.66 \Omega \\
 \text{Impedance } (Z) &= \sqrt{R^2 + X_C^2} \Omega \\
 \text{Impedance } (Z) &= \sqrt{100^2 + (63.66)^2}
 \end{aligned}$$

$$\text{Impedance (Z)} = 118.6\Omega$$

$$\begin{aligned}\text{Current (I)} &= \frac{V}{Z} \\ &= \frac{200}{118.6} \\ I &= 1.69 \text{ Amps}\end{aligned}$$

$$\begin{aligned}\text{Power Factor } (\cos \theta) &= \frac{R}{Z} \\ &= \frac{100}{118.6} = 0.843 \text{ lead}\end{aligned}$$

$$\begin{aligned}\text{Voltage across coil } (V_R) &= I R \\ &= 1.69 \times 100 \\ &= 169 \text{ Volts}\end{aligned}$$

$$\begin{aligned}\text{Voltage across capacitor } (V_L) &= I X_C \\ &= 1.69 \times 63.66 \\ &= 107.6 \text{ Volts}\end{aligned}$$

Answer:

- | | |
|--|---|
| i) Capacitive Reactance (X_C) = 63.66 Ω | ii) Impedance (Z) = 118.6 Ω |
| iii) Current (I) = 1.69 Amps | iv) Power Factor = 0.843 |
| v) P.D across R (V_R) = 169 Volts | vi) P.D across coil (V_L) = 107.6 Volts |

Example: 15

A circuit consisting of a resistor in series with a capacitor takes 80 watts at a power factor of 0.4 from a 100V, 50Hz supply. Find the resistance and capacitance. Take the current as 2 Amps

Given Data:

| | | |
|---------------|---------------|---------------------|
| Circuit | = R.C. Series | To Find: |
| Frequency (F) | = 50 Hz | i. Resistance (R) |
| Voltage (V) | = 100 V | ii. Capacitance (C) |
| Current | = 2 A | |
| Power | = 80 W | |
| Power factor | = 0.4 | |

Solution:

$$\begin{aligned}P &= V I \cos \theta \\ I &= \frac{P}{V \cos \theta} = \frac{80}{100 \times 0.4} \\ &= 2A \\ \text{Also } P &= I^2 R \\ R &= \frac{P}{I^2} = \frac{80}{2^2} = 20 \text{ ohm}\end{aligned}$$

$$\begin{aligned}
 \text{Impedance } z &= \frac{v}{I} = \frac{100}{2} = 50 \text{ ohm} \\
 Z &= \sqrt{R^2 + X_c^2} \\
 X_c &= \sqrt{Z^2 - R^2} \\
 &= \sqrt{50^2 - 20^2} = 45.83 \text{ ohm} \\
 X_c &= \frac{1}{2\pi f C} \\
 C &= \frac{1}{2\pi f X_c} \\
 &= \frac{1}{45.83 \times 2\pi \times 50} \\
 &69.45 \times 10^{-6} \text{ farad} \\
 C &= 69.45 \text{ mfd}
 \end{aligned}$$

Answer:

- i) Resistance (R) = 20 ohm ii) Capacitance (C) = 69.45 mfd


Example: 16

A resistance of 10 ohms and a capacitance of 400mfd are connected in series to a 60V sinusoidal supply. If the current is 5A, find the frequency of the supply. Also determine the phase angle between the current and the applied voltage and the power factor of the circuit.

Given Data:

| | <u>To Find:</u> |
|-----------------|------------------|
| Circuit | i. Phase angle |
| Resistance (R) | ii. Power factor |
| Capacitance (C) | |
| Current (I) | |
| Voltage (V) | |

Solution:

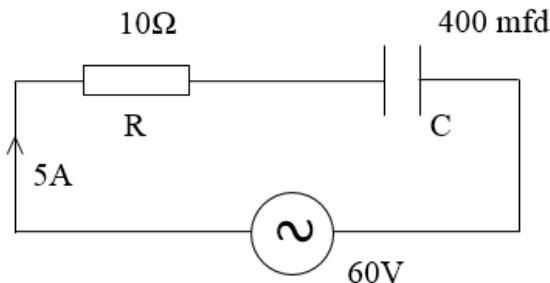

$$\text{Impedance } Z = \frac{v}{I} = \frac{60}{5} = 12\Omega$$

$$Z = \sqrt{R^2 + X_c^2}$$

$$X_c = \sqrt{Z^2 - R^2}$$

$$\begin{aligned}
 &= \sqrt{12^2 - 10^2} = 6.63\Omega \\
 X_c &= \frac{1}{2\pi f C} \\
 f &= \frac{1}{2\pi C X_c} \\
 &= \frac{1}{6.63 \times 2\pi \times 400 \times 10^{-6}} = 60\text{Hz}
 \end{aligned}$$

$$\begin{aligned}
 \text{Power factor} \quad \cos\theta &= \frac{R}{Z} = \frac{10}{12} = 0.833 \\
 \text{Phase angle} \quad \theta &= \cos^{-1} 0.833 = 33.56^\circ
 \end{aligned}$$

Answer:

i) Power factor = 0.833 ii) Phase angle = 33.56°

Example: 17

A coil of resistance 10Ω and inductance of 0.1H is connected in series with a 150μF capacitor across a 200V, 50Hz. Calculate (i) inductive reactance (ii) capacitive reactance (iii) impedance (iv) current (v) power factor (vi) power in the circuit.


Given Data:

| | |
|--------------------|--------------------------------------|
| Circuit | = R.L.C Series |
| Resistance (R) | = 10 Ω |
| Inductance (L) | = 0.1 H |
| Capacitance (C) | = 150 μF = 150×10^{-6} F |
| Supply Voltage (V) | = 200 Volts |
| Frequency (F) | = 50 Hz |

To Find:

- i) Inductive reactance (X_L)
- ii) Capacitive reactance (X_C)
- iii) Impedance (Z)
- iv) Line Current (I) = ?
- v) Power Factor (P.F) = ?
- vi) Power (P) = ?

Solution:

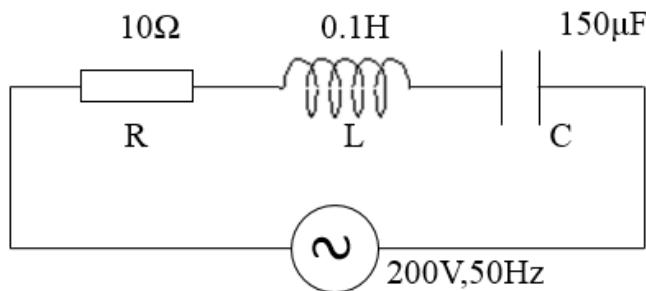

$$\begin{aligned}
 \text{Inductive Reactance } (X_L) &= 2\pi f L ; \Omega \\
 &= 2 \times 3.14 \times 50 \times 0.1 ; \Omega \\
 X_L &= 31.42 \Omega
 \end{aligned}$$

$$\begin{aligned}\text{Capacitive Reactance } (X_C) &= \frac{1}{2\pi f C} ; \Omega \\ &= \frac{1}{2 \times \pi \times 50 \times 150 \times 10^{-6}} \\ X_C &= 21.22 \Omega\end{aligned}$$

$$\begin{aligned}\text{Impedance } (Z) &= \sqrt{R^2 + (X_L - X_C)^2} \Omega \\ \text{Impedance } (Z) &= \sqrt{10^2 + (31.42 - 21.22)^2} \\ &= \sqrt{10^2 + (10.2)^2} = \sqrt{100 + 104.04} \\ &= \sqrt{204.04}\end{aligned}$$

$$Z = 14.28 \Omega$$

$$\begin{aligned}\text{Current } (I) &= \frac{V}{Z} \\ &= \frac{200}{14.28}\end{aligned}$$

$$I = 14 \text{ Amps}$$

$$\text{Power Factor } (\cos \theta) = \frac{R}{Z} = \frac{10}{14.28} = 0.7$$

$$\begin{aligned}\text{Power } (P) &= V I \cos \theta \\ &= 200 \times 14 \times 0.7 \\ &= 1960 \text{ Watts}\end{aligned}$$

Answer:

- | | | | |
|----------------------------------|------------------|------------------------------------|------------------|
| i) Inductive Reactance (X_L) | = 31.42 Ω | ii) Capacitive Reactance (X_C) | = 21.22 Ω |
| iii) Impedance (Z) | = 14.28 Ω | iv) Current (I) | = 14 A |
| v) Power Factor | = 0.7 | vi) Power (P) | = 1960 W |


Example: 18

A coil of resistance 8 Ω and an inductance of 0.1 H is connected in series with a capacitance of 75 μF with a voltage of 240V, 50Hz. Calculate (i) inductive reactance (ii) capacitive reactance (iii) impedance (iv) current (v) power factor (vi) power in the circuit.

Given Data:

| Circuit | = R.L.C Series | To Find: |
|------------------------|---|------------------------------------|
| Resistance (R) | = 8 Ω | i) Inductive reactance (X_L) |
| Inductance (L) | = 0.1 H | ii) Capacitive reactance (X_C) |
| Capacitance (C) | = $75\mu\text{F} = 75 \times 10^{-6} \text{ F}$ | iii) Impedance (Z) |
| Supply Voltage (V) | = 240 Volts | iv) Line Current (I) |
| Frequency (F) | = 50 Hz | v) Power (P) |

Solution:

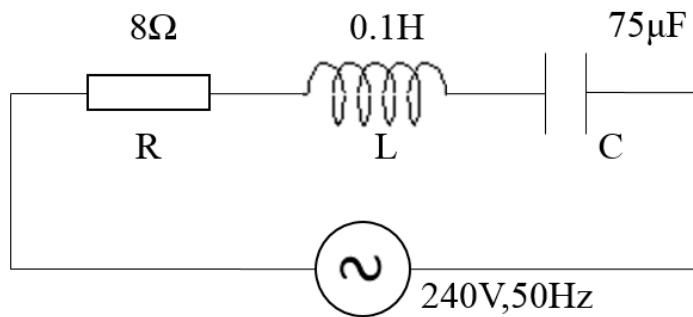

$$\begin{aligned}\text{Inductive Reactance } (X_L) &= 2\pi f L ; \Omega \\ &= 2 \times 3.14 \times 50 \times 0.1 ; \Omega \\ X_L &= 31.42 \Omega\end{aligned}$$

$$\begin{aligned}\text{Capacitive Reactance } (X_C) &= \frac{1}{2\pi f C} ; \Omega \\ &= \frac{1}{2 \times \pi \times 50 \times 75 \times 10^{-6}} \\ X_C &= 42.44 \Omega\end{aligned}$$

$$\begin{aligned}\text{Impedance } (Z) &= \sqrt{R^2 + (X_L - X_C)^2} \Omega \\ \text{Impedance } (Z) &= \sqrt{8^2 + (31.42 - 42.44)^2} \\ Z &= \sqrt{8^2 + (-11.02)^2} \\ &= \sqrt{64 + 121.44} \\ &= \sqrt{185.44} \\ \text{Impedance } (Z) &= 13.61 \Omega\end{aligned}$$

$$\begin{aligned}\text{Current } (I) &= \frac{V}{Z} \\ &= \frac{240}{13.61} \\ I &= 17.6 \text{ Amps}\end{aligned}$$

$$\text{Power Factor } (\cos \theta) = \frac{R}{Z} = \frac{8}{13.61} = 0.58$$

$$\begin{aligned}\text{Power } (P) &= VI \cos \theta \\ &= 240 \times 17.6 \times 0.58 \\ &= 2450 \text{ Watts}\end{aligned}$$

Answer:


- i) Inductive Reactance (X_L) = 31.42 Ω ii) Capacitive Reactance (X_C) = 42.44 Ω
- iii) Impedance (Z) = 13.61Ω iv) Current (I) = 17.6 Amps
- v) Power Factor = 0.58 vi) Power (P) = 2450 Watts

Example: 19

A coil of resistance 10Ω and an inductance of 0.1 H is connected in series with a capacitance of $150\mu\text{F}$ with a voltage of 200V , 50Hz supply. Calculate (i) inductive reactance (ii) capacitive reactance (iii) impedance (iv) current (v) power factor (vi) voltage across the coil and capacitor.

Given Data:

| | | |
|--------------------|----------------------------------|------------------------------------|
| Circuit | = R.L.C Series | To Find: |
| Resistance (R) | = 10Ω | i) Inductive reactance (X_L) |
| Inductance (L) | = 0.1 H | ii) Capacitive reactance (X_C) |
| Capacitance (C) | = $150 \mu\text{F}$ | iii) Impedance (Z) |
| | = $150 \times 10^{-6} \text{ F}$ | iv) Line Current (I) |
| Supply Voltage (V) | = 200 Volts | v) Power Factor (P.F) |
| Frequency (F) | = 50 Hz | vi) P.D across L and C |

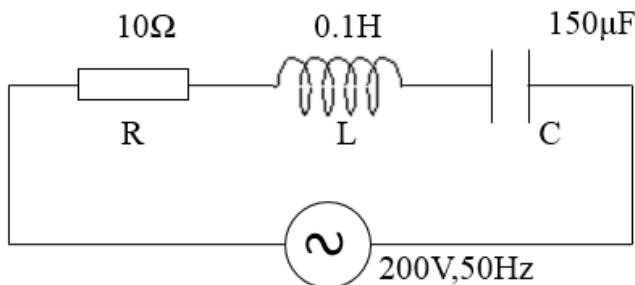Solution:

$$\begin{aligned}\text{Inductive Reactance } (X_L) &= 2\pi fL ; \Omega \\ &= 2 \times 3.14 \times 50 \times 0.1 ; \Omega \\ X_L &= 31.42 \Omega\end{aligned}$$

$$\begin{aligned}\text{Capacitive Reactance } (X_C) &= \frac{1}{2\pi fC} ; \Omega \\ &= \frac{1}{2 \times \pi \times 50 \times 150 \times 10^{-6}} \\ X_C &= 21.22 \Omega\end{aligned}$$

$$\begin{aligned}\text{Impedance } (Z) &= \sqrt{R^2 + (X_L - X_C)^2} \Omega \\ \text{Impedance } (Z) &= \sqrt{10^2 + (31.42 - 21.22)^2} \\ &= \sqrt{10^2 + (10.2)^2} \\ &= \sqrt{100 + 104.04} \\ &= \sqrt{221.44} \\ \text{Impedance } (Z) &= 14.28 \Omega\end{aligned}$$

$$\begin{aligned}\text{Current } (I) &= \frac{V}{Z} \\ &= \frac{200}{14.28}\end{aligned}$$

$$I = 14 \text{ Amps}$$

$$\begin{aligned}\text{Power Factor } (\cos \theta) &= \frac{R}{Z} \\ &= \frac{10}{14.28} = 0.7\end{aligned}$$

$$\begin{aligned}\text{Voltage across coil } (V_L) &= I X_L \\ &= 14 \times 31.42 \\ &= 439.88 \text{ Volts}\end{aligned}$$

$$\begin{aligned}\text{Voltage across capacitor } (V_C) &= I X_C \\ &= 14 \times 21.22 \\ &= 297.08 \text{ Volts}\end{aligned}$$

Answer:

- | | | | |
|----------------------------------|------------------|------------------------------------|------------------|
| i) Inductive Reactance (X_L) | = 31.42 Ω | ii) Capacitive Reactance (X_C) | = 21.22 Ω |
| iii) Impedance (Z) | = 14.28 Ω | iv) Current (I) | = 14 Amps |
| v) Power Factor | = 0.7 | vi) P.D across coil (V_L) | = 439.88 Volts |
| vii) P.D across coil (V_C) | = 297.08 Volts | | |


Example: 20

An inductor having an inductance of 0.4H and a resistance of 5 Ω is connected in series with a capacitor across 50Hz Supply. Calculate the capacitance required to give the circuit power factor 0.5 lagging. Assume supply voltage to be sinusoidal.

Given Data:

| Circuit | = R.L.C Series | To Find: |
|--------------------|----------------|----------------|
| Resistance (R) | = 5 Ω | I. Capacitance |
| Inductance (L) | = 0.4 H | |
| Frequency (F) | = 50 Hz | |
| Power factor | = 0.5 lagging | |

Solution:

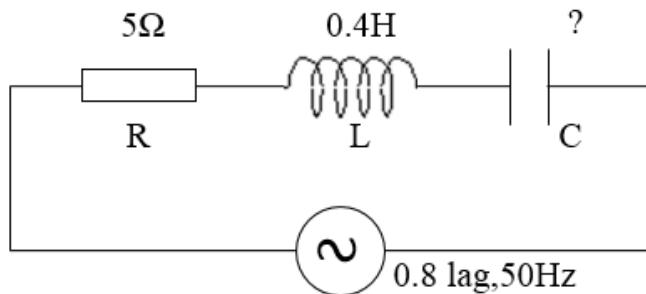

$$\begin{aligned}X_L &= 2\pi f L \\ &= 2\pi \times 50 \times 0.4 = 125.66 \Omega\end{aligned}$$

$$\text{Impedance, } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\begin{aligned}
 \text{Power Factor } (\cos \theta) &= \frac{R}{Z} \\
 0.5 &= \frac{5}{Z} \\
 Z &= \frac{5}{0.5} = 10 \Omega \\
 \text{i.e., } 10 &= \sqrt{R^2 + (X_L - X_C)^2} \\
 (X_L - X_C) &= \sqrt{10^2 - R^2} = \sqrt{10^2 - 5^2} \\
 125.66 - X_C &= 8.66 \text{ ohm} \\
 X_C &= 125.66 - 8.66 = 117 \text{ ohm} \\
 \text{But, } X_C &= \frac{1}{2\pi f C} \\
 C &= \frac{1}{2\pi f X_C} \\
 &= \frac{1}{117 \times 2\pi \times 50} = 27.2 \text{ mfd}
 \end{aligned}$$

Answer:

i) Capacitance = 27.2 mfd

Example: 21

A circuits takes a current of 3 amps at a p.f of 0.6 lag, When connected to a 120V, 50Hz source and another circuit takes a current of 5 amps at p.f of 0.707 lead when connected to the same source. If the two circuits are connected in series to a 240V, 50Hz supply. Calculate the current and power factor of the circuit?

Given Data:

| | <u>To Find:</u> |
|-------------------------------|------------------------------------|
| Circuit | i. resistance (R) |
| Current (A) | ii. Impedance (Z) |
| Power factor ($\cos\theta$) | iii. inductive reactance (X_L) |
| Voltage (V) | |
| Current (A) | |
| Power factor ($\cos\theta$) | |
| Voltage (V) | |
| Voltage (V) | |

Solution:

$$\begin{aligned}
 \text{Impedance } (Z_A) &= \frac{V}{I} & \text{Impedance } (Z_B) &= \frac{V}{I} \\
 &= \frac{120}{3} & &= \frac{120}{5} \\
 &= 40 \Omega & &= 24 \Omega \\
 R_A &= Z_A \cos \theta & R_B &= Z_B \cos \theta \\
 &= 40 \times 0.6 & &= 24 \times 0.707 \\
 &= 24 \Omega & &= 16.97 \Omega
 \end{aligned}$$

$$\begin{aligned} X_L &= Z_A \sin \theta \\ &= 40 \times 0.8 \\ &= 32 \Omega \end{aligned}$$

$$\begin{aligned} X_L &= Z_B \sin \theta \\ &= 24 \times 0.707 \\ &= 16.97 \Omega \end{aligned}$$

$$\begin{aligned} \text{Impedance (Z)} &= \sqrt{R^2 + (X_L - X_C)^2} \Omega \\ \text{Impedance (Z)} &= \sqrt{(24 + 16.97)^2 + (32 - 16.97)^2} \\ &= \sqrt{40.97^2 + (15.03)^2} \\ \text{Impedance (Z)} &= 43.64 \Omega \\ \text{Voltage (V)} &= 240 \text{ V} \\ I &= \frac{V}{Z} = \frac{240}{43.64} = 5.5 \text{ Amps} \\ \cos \theta &= \frac{R}{Z} = \frac{40.97}{43.64} = 0.94 \end{aligned}$$

Answer:

I. Current (I) = 5.5 Amps II. Cos = 0.94

Example: 22

A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250V, 50Hz. If the voltage across the resistance is 125V and across the coil is 200V, calculate (a) the impedance, reactance, and resistance of the coil, (b) the power observed by the coil and (c) the total power. Draw the vector diagram. Take the phase angle of the circuit as 52.4° lag.

Given Data:

| | |
|---------------------------------|-------------|
| Current (I) | = 5 A |
| Voltage (V) | = 250 V |
| Frequency (f) | = 50Hz |
| Voltage across resistance V_R | = 125 V |
| Voltage across coil V_{coil} | = 200 V |
| Phase angle | = 52.4° lag |

To Find:

- i). resistance (R)
- ii). reactance (X_L)
- iii). Impedance (Z)
- iv). power absorbed by the coil
- v). total power

Solution:

| | |
|----|--|
| AB | = V_R - voltage drop across the non-inductive resistor R |
| BC | = V_r - voltage drop across the resistance of the coil |
| CD | = V_L - voltage drop across the reactance of the coil |
| BD | = 200V - voltage across the choking coil |
| AD | = 250V - applied voltage to the series circuit |

$$\begin{aligned} V_R &= IR = 125 \text{ V} \\ \text{Impedance of the coil } Z_L &= \frac{\text{Voltage across the coil}}{I} \\ &= \frac{200}{5} \\ &= 40 \Omega \end{aligned}$$

Power factor of the circuit is:

$$\cos \theta = \cos 52.4^\circ = 0.61$$

$$\cos \theta = \frac{AC}{AD}$$

$$AC = AD \cos \theta$$

$$\text{But } AC = AB + BC$$

$$BC = AC - AB$$

$$= 152.54 - 125 = 27.54$$

$$BC = IX_r$$

$$X_r = \frac{BC}{I} = \frac{27.54}{5} = 5.51\Omega$$

$$\sin \theta = \frac{CD}{AD}$$

$$CD = AD \times \sin \theta$$

$$= 250 \times \sin 52.4^\circ = 198$$

$$\text{But } CD = IX_L$$

$$X_L = \frac{CD}{I} = \frac{198}{5} = 39.6\Omega$$

Power observed by the coil:


$$I^2 r = 5^2 \times 5.51 = 137.75 \text{ watts}$$

Power of resistor R:

$$= I^2 R$$

$$= 5^2 \times 25 = 625 \text{ watts}$$
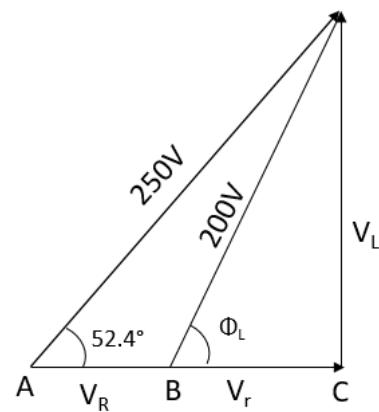
$$\text{Total power} = 137.75 + 625 = 762.75 \text{ watts}$$



Answer:

I. Resistance of the coil = 5.51Ω II. Reactance of the coil = 39.6Ω

III. Impedance of the coil $Z_L = 40 \Omega$ IV. Power observed by the coil = 137.75 watts

V. Total power = 762.75 watts

Example: 23

When a voltage of 100V at 50 Hz is applied to chocking coil 'A' the current is 8A and the power is 120 watts. When applied to a coil B the current is 10A and the power is 500W. What current and power will be taken when 100V at 50Hz is applied to the two coils connected in series.

Given Data:

| | |
|-----------|------------------|
| Circuit | = RL - RL Series |
| Voltage V | = 100 V |
| Frequency | = 50 Hz |
| Coil A | |
| Current | = 8 A |
| Power | = 120 W |

To Find:

- i. Current
- ii. Power

| | |
|---------|---------|
| Coil B | |
| Current | = 10 A |
| Power | = 500 W |

Solution:

Coil A
V = 100V, 50Hz

$$I_A = 8A$$

$$P_A = 120 \text{ watts}$$

$$\text{i.e., } I^2 R_A = 120$$

$$R_A = \frac{120}{I^2} = \frac{120}{8^2}$$

$$R_A = 1.875 \text{ ohm}$$

$$Z_A = \frac{V}{I_A} = \frac{100}{8} = 12.5 \Omega$$

$$X_{LA} = \sqrt{Z_A^2 - R_A^2}$$

$$X_{LA} = \sqrt{12.5^2 - 1.875^2}$$

$$X_{LA} = 12.36 \text{ ohm}$$

Coil B
V = 100V, 50Hz

$$I_B = 10A$$

$$P_B = 500 \text{ watts}$$

$$I_B^2 R_B = 500$$

$$R_B = \frac{500}{10^2}$$

$$R_R = 5 \text{ ohm}$$

$$Z_B = \frac{V}{I_B} = \frac{100}{10} = 10 \text{ ohm}$$

$$X_{LB} = \sqrt{Z_B^2 - R_B^2}$$

$$X_{LB} = \sqrt{10^2 - 5^2}$$

$$X_{LB} = 8.66 \text{ ohm}$$

When two coils are connected in series

$$\begin{aligned} \text{Total } R &= R_A + R_B \\ &= 1.875 + 5 = 6.875 \text{ ohm} \end{aligned}$$

$$\begin{aligned} X_L &= X_{LA} + X_{LB} \\ &= 12.36 + 8.66 = 21.02 \text{ ohm} \end{aligned}$$

$$\begin{aligned} Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{6.875^2 + 21.02^2} \\ &= 22.12 \text{ ohm} \end{aligned}$$

$$\text{Circuit current } I = \frac{V}{Z} = \frac{100}{22.12} = 4.52A$$

$$\text{Power} = I^2 R = 4.52^2 \times 6.875 = 140.46 \text{ watts}$$

Answer:

$$\text{i) Circuit current} = 4.52 \text{ A} \quad \text{ii) Power} = 140.46 \text{ W}$$

Example: 24


A two element series circuit of $R = 10\Omega$ and $X_L = 15\Omega$ has an effective voltage of 230Volts at 50Hz. Determine the active power, apparent power and reactive power.

Given Data:

| | |
|-------------------------------|---------------|
| Circuit | = R.L. Series |
| Resistance (R) | = 10Ω |
| Inductive Reactance (X_L) | = 15Ω |
| Frequency (F) | = 50 Hz |
| Voltage (V) | = 230V |

To Find:

- i. Active Power (P)
- ii. Apparent Power (S)
- iii. Reactive Power (Q)

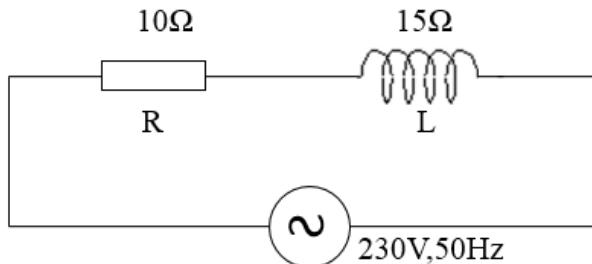Solution:

$$\text{Impedance } (Z) = \sqrt{R^2 + (X_L)^2} \Omega$$

$$\text{Impedance } (Z) = \sqrt{10^2 + 15^2}$$

$$\text{Impedance } (Z) = 18.03 \Omega$$

$$\begin{aligned}\text{Current } (I) &= \frac{V}{Z} \\ &= \frac{230}{18.03} = 12.76 \text{ Amps}\end{aligned}$$

$$\text{Phase angle } \theta = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{15}{10} = 56.3^\circ$$

$$\cos \theta = \cos 56.3 = 0.55$$

$$\begin{aligned}\text{Active Power } (P) &= VI \cos \theta \\ &= 230 \times 12.76 \times 0.55 \\ &= 1614 \text{ Watts}\end{aligned}$$

$$\begin{aligned}\text{Apparent Power } (S) &= VI \\ &= 230 \times 12.76 \\ &= 2935 \text{ VA}\end{aligned}$$

$$\begin{aligned}\text{Reactive Power } (Q) &= VI \sin \theta \\ &= 230 \times 12.76 \times 0.83 \\ &= 2436 \text{ VAR}\end{aligned}$$

Example: 25

What is the equation for a sinusoidal current of 25 Hz frequency having an RMS value of 40 Amps.

Given Data:

$$\begin{aligned}\text{RMS current } I_{\text{RMS}} &= 40 \text{ A} \\ \text{Frequency} &= 25 \text{ Hz}\end{aligned}$$

To Find:

Equation of sinusoidal current.

Solution:

Standard form of sinusoidal current is $i = i_m \sin \omega t$


$$\begin{aligned}i &= I_m \sin 2\pi ft \\ I_m &= I_{\text{rms}} \times \sqrt{2} \\ &= 40 \times \sqrt{2} \\ I_m &= 56.57 \text{ A} \\ i &= I_m \sin 2\pi ft \\ i &= 56.57 \sin 157t\end{aligned}$$

Answer:

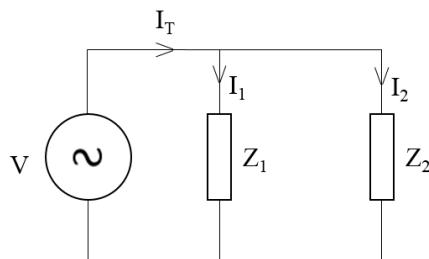i) $i = 56.57 \sin 157t$

PARALLEL AC CIRCUITS:

In an AC circuit, when the impedances are connected in parallel, it is said to be a parallel AC circuit. A parallel circuit can be solved by impedance method or Admittance method.



Impedance Method: A two branch parallel circuit is shown in fig. Let V be the applied voltage to the circuit and I is the total current supplied by the source. I_1 , and I_2 are the currents flowing through impedances Z_1 and Z_2 respectively.

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\frac{1}{Z_T} = \frac{Z_1 + Z_2}{Z_1 \cdot Z_2}$$

$$\text{Total Impedance: } Z_T = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$$

$$\text{Total Current : } I = \frac{V}{Z_T} = \frac{V}{R + jX_L} ; \text{Amps}$$

$$\text{Total Current : } I = \frac{V}{Z_T}$$

$$I = V \cdot \left[\frac{Z_1 + Z_2}{Z_1 \cdot Z_2} \right] ; \text{Amps}$$

$$\text{Current in Branch 1: } I_1 = \frac{V}{Z_1}$$

$$I_1 = I \cdot \left[\frac{Z_2}{Z_1 + Z_2} \right] ; \text{Amps}$$

$$\text{Current in Branch 2: } I_2 = \frac{V}{Z_2}$$

$$I_2 = I \cdot \left[\frac{Z_1}{Z_1 + Z_2} \right] ; \text{Amps}$$



$$\text{Also Total Current : } I = I_1 + I_2$$

Admittance Method:

$$\text{Conductance (G)} = \left(\frac{1}{R} \right) ; \text{Siemens}$$

$$\text{Susceptance (B)} = \left(\frac{1}{X} \right) ; \text{Siemens}$$
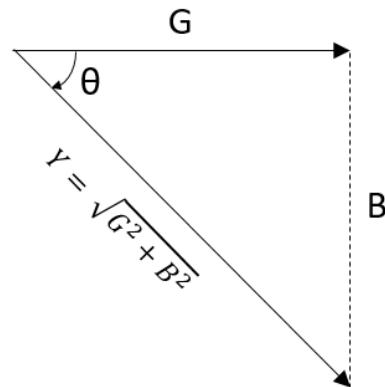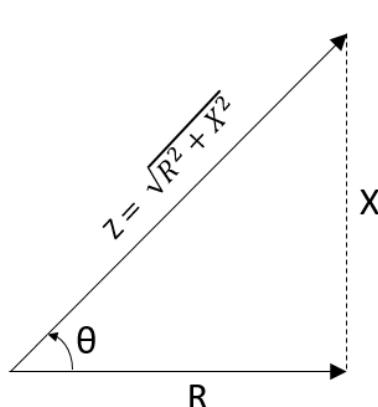
$$\text{Admittance (G)} = \left(\frac{1}{Z} \right) ; \text{Siemens}$$



Admittance has in-phase component as well as quadrature components. It can be represented by a right angled triangle called admittance triangle as shown in figure.

$$\begin{aligned}\text{Conductance (G)} &= Y \cdot \cos \theta \\ &= \left(\frac{1}{Z}\right) \cdot \left(\frac{R}{Z}\right) = \left(\frac{R}{Z^2}\right) \text{ siemens} \\ \text{Conductance (G)} &= \left(\frac{R}{Z^2}\right) \text{ siemens}\end{aligned}$$

If a parallel circuit consists of several branches, then the total conductance of the parallel circuit can be written as the sum of the individual conductances.

$$\begin{aligned}\text{Total Conductance (G)} &= G_1 + G_2 + G_3 + \dots + G_n \\ \text{Where } G_1, G_2, \dots, G_n &= \text{Conductance of the individual branches}\end{aligned}$$

$$\begin{aligned}\text{Susceptance (B)} &= Y \cdot \sin \theta \\ &= \left(\frac{1}{Z}\right) \cdot \left(\frac{X}{Z}\right) = \left(\frac{X}{Z^2}\right) \text{ siemens} \\ \text{Susceptance (B)} &= \left(\frac{X}{Z^2}\right) \text{ siemens}\end{aligned}$$

If a parallel circuit consists of several branches, then the total susceptance of the parallel circuit can be written as the sum of the individual susceptance.


$$\begin{aligned}\text{Total Susceptance (B)} &= B_1 + B_2 + B_3 + \dots + B_n \\ \text{Where } B_1, B_2, \dots, B_n &= \text{Susceptance of the individual branches}\end{aligned}$$

Note: In a parallel circuit the inductive susceptance is considered as negative ($-B_L$) and capacitive susceptance is consider as positive ($+B_C$).

$$\begin{aligned}\text{Admittance (Y)} &= \sqrt{\text{Conductance}^2 + \text{Susceptance}^2} \\ Y &= \sqrt{G^2 + B^2} \\ \text{Phase angle : } \theta &= \tan^{-1} \frac{B}{G}\end{aligned}$$

Power in AC Parallel Circuit:
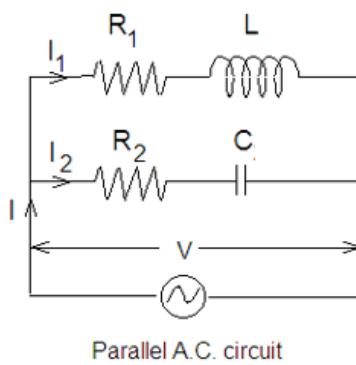
$$\begin{aligned}\text{Admittance : } Y &= \frac{1}{Z_1} = \frac{1}{V/I} = \frac{I}{V} \\ \text{Total Current : } I &= V \cdot Y \\ \text{Branch Current : } I_1 &= V \cdot Y_1 \\ \text{Branch Current : } I_2 &= V \cdot Y_2 \\ \text{Total Current : } I &= I_1 + I_2 \\ V \cdot Y &= V \cdot Y_1 + V \cdot Y_2 \\ Y &= Y_1 + Y_2\end{aligned}$$



In branch I:

$$\begin{aligned}
 \text{Admittance : } Y_1 &= \frac{1}{Z_1} = \frac{1}{R_1 + jX_L} \\
 &= \frac{1}{R_1 + jX_L} \cdot \frac{R_1 - jX_L}{R_1 - jX_L} \\
 &= \frac{R_1 - jX_L}{R_1^2 + X_L^2} \\
 &= \frac{R_1}{R_1^2 + X_L^2} - j \frac{X_L}{R_1^2 + X_L^2} \\
 &= \frac{R_1}{Z_1^2} - j \frac{X_L}{Z_1^2} \\
 Y_1 &= G_1 - jB_1
 \end{aligned}$$

In branch II:

$$\begin{aligned}
 \text{Admittance : } Y_2 &= \frac{1}{Z_2} = \frac{1}{R_2 - jX_C} \\
 &= \frac{1}{R_2 - jX_C} \cdot \frac{R_2 + jX_C}{R_2 + jX_C} \\
 &= \frac{R_2 + jX_C}{R_2^2 + X_C^2} \\
 &= \frac{R_2}{R_2^2 + X_C^2} + j \frac{X_C}{R_2^2 + X_C^2} \\
 &= \frac{R_2}{Z_2^2} + j \frac{X_C}{Z_2^2} \\
 Y_2 &= G_2 + jB_2
 \end{aligned}$$

$$\begin{aligned}
 \text{Total Admittance: } Y &= Y_1 + Y_2 \\
 &= (G_1 - jB_1) + (G_2 + jB_2) \\
 &= (G_1 + G_2) + j(-B_1 + B_2) \\
 &= \sqrt{(G_1 + G_2)^2 + (-B_1 + B_2)^2} \\
 Y &= \sqrt{G^2 + B^2}
 \end{aligned}$$

$$\text{Total Current: } I = V \cdot Y$$

$$\begin{aligned}
 \text{Phase angle: } \theta &= \tan^{-1} \frac{B}{G} \\
 \theta &= \tan^{-1} \frac{(-B_1 + B_2)}{(G_1 + G_2)}
 \end{aligned}$$

$$\text{Power: } P = V \cdot I \cdot \cos \theta$$

Example: 26


Two impedances $Z_1 = 8+j6$ ohm and $Z_2 = 5-j12$ ohm are connected in parallel across 200V, 50Hz supply. Find the total impedance.

Given Data:

| | | |
|---------------------|---|-----------|
| Impedance (Z_1) | = | $8+j6$ |
| Impedance (Z_2) | = | $5-j12$ |
| Supply Voltage (V) | = | 200 Volts |
| Frequency (F) | = | 50 Hz |

To Find:

- i) Total Impedance (Z) = ?

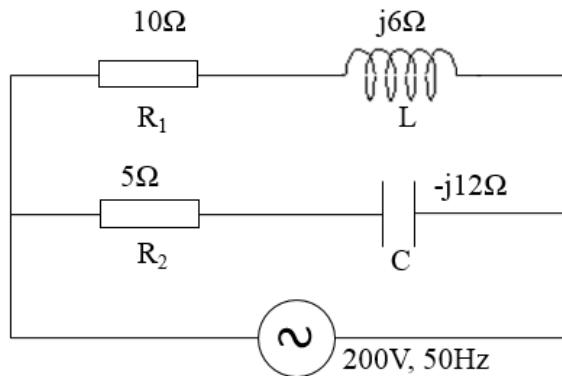Solution:

$$\begin{aligned}
 \text{Total Impedance } (Z) &= \frac{Z_1 Z_2}{Z_1 + Z_2} \\
 &= \frac{(8 + j6)(5 - j12)}{(8 + j6) + (5 - j12)} \\
 &= \frac{40 - j96 + j30 - j^2 72}{(13 - j6)} \\
 &= \frac{40 - j96 + j30 + 72}{13 - j6} \\
 &= \frac{112 - j66}{13 - j6} \\
 &= \frac{112 - j66}{13 - j6} \times \frac{13 + j6}{13 + j6} \\
 &= \frac{1456 + j672 - j858 - j^2 396}{13^2 - j^2 6^2} \\
 &= \frac{1852 - j186}{205} \\
 &= 9.034 - j0.907 \\
 &= 9.08 \angle -5.73^\circ
 \end{aligned}$$

Answer:

- i) Total Impedance (Z) = $9.08 \angle -5.73^\circ$ Ohm

Example: 27


In a coil of resistance 8 Ω and reactance of 6 Ω is connected in parallel with a resistance of 12 Ω and a capacitive reactance of 16 Ω across 200V mains. Calculate the current in each branch, total current, total power factor and total power.

Given Data:

| | |
|---------------------|--------------|
| Circuit | = Parallel |
| Impedance (Z_1) | = $8+j6$ |
| Impedance (Z_2) | = $12 - j16$ |
| Supply Voltage (V) | = 200 Volts |

To Find:

- i) Branch Current (I_1 & I_2)
- ii) Total Current (I)
- iii) Power Factor (P.F)
- iv) Power (P)

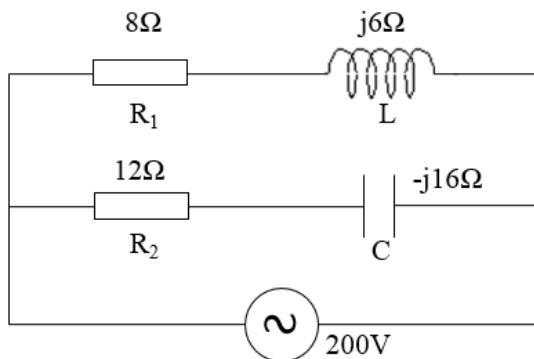Solution: Method-I

$$\text{Supply Voltage (V)} = 200+j0$$

$$Z_1 = 8 + j6$$

$$Z_2 = 12 - j16$$

$$\begin{aligned} \text{Current } (I_1) &= \frac{V}{Z_1} = \frac{200}{8 + j6} \\ &= \frac{200}{8 + j6} \times \frac{8 - j6}{8 - j6} \\ &= \frac{1600 - j1200}{8^2 + 6^2} \\ &= \frac{1600 - j1200}{100} \\ &= 16 - j12 \\ \text{Current } (I_1) &= 20\angle -36.87^\circ \end{aligned}$$

$$\begin{aligned} \text{Current } (I_2) &= \frac{V}{Z_2} = \frac{200}{12 - j16} \\ &= \frac{200}{12 - j16} \times \frac{12 + j16}{12 + j16} \\ &= \frac{2400 + j3200}{12^2 + 16^2} \\ &= \frac{2400 + j3200}{400} \end{aligned}$$

$$\begin{aligned}\text{Current } (I_2) &= 6 + j8 \\ \text{Current } (I_2) &= 10\angle 53.13^\circ\end{aligned}$$

$$\begin{aligned}\text{Total Current } (I) &= I_1 + I_2 \\ I &= (16 - j12) + (6 + j8) \\ I &= 22 - j4 \\ I &= 22.36 \angle -10.30^\circ \text{Amps}\end{aligned}$$

$$\begin{aligned}\text{Power Factor } (\cos \theta) &= \cos 10.3 \\ &= 0.98 \\ \text{Power } (P) &= VI \cos \theta \\ &= 200 \times 22.36 \times 0.98 \\ &= 4382.5 \text{ Watts}\end{aligned}$$

Answer:

- i) Current (I_1) = $10\angle 53.13^\circ$ Amps
- ii) Current (I_2) = $10\angle 53.13^\circ$ Amps
- iii) Total Current (I) = $22.36 \angle -10.30^\circ$ Amps
- iv) Power Factor (P.F) = 0.98
- v) Power (P) = 4382.5 Watts

Solution: Method-II

$$\begin{aligned}\text{Supply Voltage } (V) &= 200 + j0 = 200\angle 0^\circ \\ Z_1 &= 8 + j6 = 10\angle 36.8^\circ \\ Z_2 &= 12 - j16 = 20\angle -53.13^\circ \\ \text{Current } (I_1) &= \frac{V}{Z_1} = \frac{200\angle 0^\circ}{10\angle 36.8^\circ} = 20\angle -36.8^\circ \\ \text{Current } (I_1) &= 20\angle -36.87^\circ \\ \text{Current } (I_2) &= \frac{V}{Z_2} = \frac{200\angle 0^\circ}{20\angle -53.13^\circ} = 10\angle 53.13^\circ \\ \text{Current } (I_2) &= 10\angle 53.13^\circ\end{aligned}$$

$$\begin{aligned}\text{Total Current } (I) &= I_1 + I_2 \\ I &= 20\angle -36.8^\circ + 10\angle 53.13^\circ \\ I &= (16 - j12) + (6 + j8) \\ I &= 22 - j4 \\ I &= 22.36 \angle -10.30^\circ \text{Amps}\end{aligned}$$

$$\begin{aligned}\text{Power Factor } (\cos \theta) &= \cos 10.3 \\ &= 0.98 \\ \text{Power } (P) &= VI \cos \theta\end{aligned}$$

$$= 200 \times 22.36 \times 0.98 \\ = 4382.5 \text{ Watts}$$

Answer:

- i) Current (I_1) = $10 \angle 53.13^\circ$ Amps
- ii) Current (I_2) = $10 \angle -10.30^\circ$ Amps
- iii) Total Current (I) = $22.36 \angle -10.30^\circ$ Amps
- iv) Power Factor (P.F) = 0.98
- v) Power (P) = 4382.5 Watts

Example: 28

A capacitor of $80 \mu\text{F}$ is connected in parallel with a coil that has a resistance of 20Ω and inductance of 0.08H . If this combination is connected across 230V , 50Hz supply calculate current, P.F and power.


Given Data:

| | |
|--------------------|---|
| Circuit | = Parallel |
| Resistance (R) | = 20Ω |
| Inductance (L) | = 0.08 H |
| Capacitance (C) | = $80 \mu\text{F}$ = $80 \times 10^{-6}\text{F}$ |
| Supply Voltage (V) | = 230 Volts |
| Frequency (F) | = 50 Hz |

To Find:

- v) Total Current (I)
- vi) Power Factor (P.F)
- vii) Power (P)

Solution:

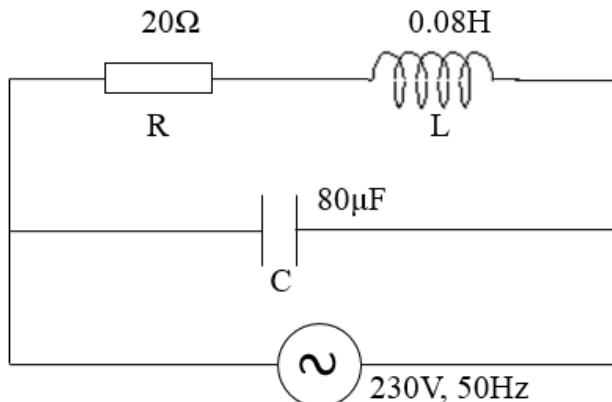

$$\begin{aligned} \text{Inductive Reactance } (X_L) &= 2\pi f L ; \Omega \\ &= 2 \times 3.14 \times 50 \times 0.08 ; \Omega \\ X_L &= 25.13 \Omega \end{aligned}$$

$$\begin{aligned} \text{Capacitive Reactance } (X_C) &= \frac{1}{2\pi f C} ; \Omega \\ &= \frac{1}{2 \times \pi \times 50 \times 80 \times 10^{-6}} \\ X_C &= 39.79 \Omega \end{aligned}$$

$$\text{Current } (I_1) = \frac{V}{Z_1} = \frac{230 \angle 0}{20 + j25.13} = \frac{230 \angle 0}{32.12 \angle 51.49^\circ}$$

$$I_1 = 7.16 \angle -51.49^\circ$$

$$\text{Current } (I_2) = \frac{V}{Z_2} = \frac{230 \angle 0}{0 - j39.79}$$

$$I_2 = 5.78 \angle 90^\circ \text{Amps}$$

$$I = I_1 + I_2$$

$$I = 7.16 \angle -51.49^\circ + 5.78 \angle 90^\circ$$

$$= 4.45 - j5.49 + 0 + j5.78$$

$$= 4.45 - j0.29$$

$$I = 4.46 \angle -3.72^\circ \text{Amps}$$

$$\text{Power Factor } (\cos \theta) = 0.9$$

$$\begin{aligned}\text{Power } (P) &= VI \cos \theta \\ &= 230 \times 4.46 \times 0.9 \\ &= 923.2 \text{ Watts}\end{aligned}$$

Answer:

- i) Current (I) = 4.46 Amps
- ii) Power Factor = 0.9
- iii) Power (P) = 923.2 Watts

Example: 29

Two impedances $Z_1 = 8+j6$ and $Z_2 = 3-j4$ are connected in parallel across 230V, 50Hz supply. Calculate (a) Current in each branch (b) the total current of the circuit (c) power factor (d) Power taken by the circuit.

Given Data:

$$\text{Impedance } (Z_1) = 8+j6$$

$$\text{Impedance } (Z_2) = 3-j4$$

$$\text{Supply Voltage } (V) = 230 \text{ Volts}$$

$$\text{Frequency } (F) = 50 \text{Hz}$$

To Find:


$$\text{i) Current in each branch=?}$$

$$\text{ii) Total current = ?}$$

$$\text{iii) Power factor (P.F) = ?}$$

$$\text{iv) Power (P) = ?}$$

Solution:

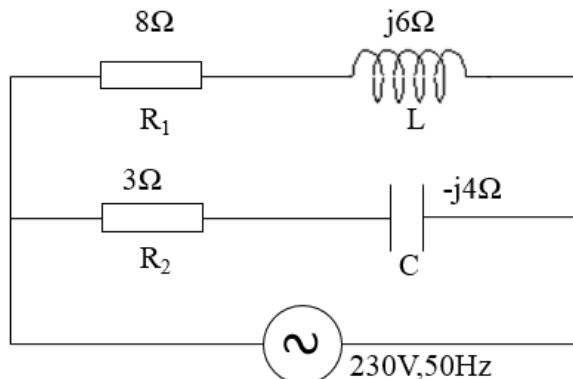

$$\begin{aligned}
Z_1 &= \sqrt{R_1^2 + X_L^2} \\
&= \sqrt{8^2 + 6^2} = 10\Omega \\
Z_2 &= \sqrt{R_2^2 + X_C^2} \\
&= \sqrt{3^2 + 4^2} = 5\Omega \\
\text{Conductance } (G_1) &= \frac{8}{Z_1^2} \\
&= \frac{8}{10^2} = 0.08\text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Conductance } (G_2) &= \frac{R_2}{Z_2^2} \\
&= \frac{3}{5^2} = 0.12\text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Susceptance } (B_1) &= \frac{-X_1}{Z_1^2} \\
&= \frac{-6}{10^2} = -0.06\text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Susceptance } (B_2) &= \frac{X_2}{Z_2^2} \\
&= \frac{4}{5^2} = 0.16\text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Admittance } (Y_1) &= \sqrt{G_1^2 + B_1^2} \\
&= \sqrt{0.08^2 + 0.06^2} = 0.1\text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Admittance } (Y_2) &= \sqrt{G_2^2 + B_2^2} \Omega \\
&= \sqrt{0.12^2 + 0.16^2} = 0.2\text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Current in branch 1 : } I_1 &= V \cdot Y_1 \\
&= 230 \times 0.1 = 23\text{Amps}
\end{aligned}$$

$$\begin{aligned}
\text{Current in branch 2 : } I_2 &= V \cdot Y_2 \\
&= 230 \times 0.2 = 46\text{Amps}
\end{aligned}$$

$$\begin{aligned}
\text{Total Conductance } (G) &= G_1 + G_2 \\
&= 0.08 + 0.12 = 0.2 \text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Total Susceptance } (B) &= B_1 + B_2 \\
&= -0.06 + 0.16 = 0.1\text{V}
\end{aligned}$$

$$\begin{aligned}
\text{Total Admittance } (Y) &= \sqrt{G^2 + B^2} \Omega \\
&= \sqrt{0.2^2 + 0.1^2} = 0.22 \text{V}
\end{aligned}$$

$$\begin{aligned}\text{Phase angle} &= \tan^{-1} \frac{B}{G} \\ &= \tan^{-1} \frac{0.1}{0.2} = 26.57\end{aligned}$$

$$\begin{aligned}\text{Power Factor : Cos } \theta &= \cos 26.57 \\ &= 0.89\end{aligned}$$

$$\begin{aligned}\text{Total Current (I)} &= V \cdot Y \\ &= 230 \times 0.22 = 66.7 \text{ Amps}\end{aligned}$$

$$\begin{aligned}\text{Power (P)} &= V I \cos \theta \\ &= 230 \times 66.7 \times 0.89 \\ &= 13653.5 \text{ Watts}\end{aligned}$$

Answer:

- | | |
|---|--|
| i) Current in branch 1 (I_1) = 23 A | ii) Current in branch 2 (I_2) = 46 A |
| iii) Total current (I) = 66.7 Amps | iv) Power factor = 0.89 |
| v) Power (P) = 13653.5 Watts | |

Example: 30

An impedance $(6+j8)$ is connected across 220V, 50Hz mains in parallel with another circuit having an impedance of $(8-j6)$ ohm. Calculate (a) the admittance, the conductance and the susceptance of the combined circuit (b) the total current taken from the mains (c) power factor (d) Total Power


Given Data:

| | |
|---------------------|-------------|
| Impedance (Z_1) | = $6+j8$ |
| Impedance (Z_2) | = $8-j6$ |
| Supply Voltage (V) | = 220 Volts |
| Frequency (F) | = 50Hz |

To Find:

- | |
|--|
| i) Admittance, Conductance & Susceptance = ? |
| ii) Total current = ? |
| iii) Power factor (P.F) = ? |
| iv) Power (P) = ? |

Solution:

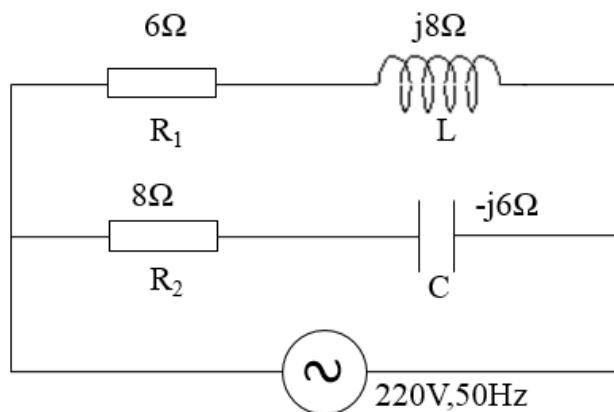

$$\begin{aligned}
 Z_1 &= \sqrt{R_1^2 + X_L^2} \\
 &= \sqrt{6^2 + 8^2} = 10\Omega \\
 Z_2 &= \sqrt{R_2^2 + X_C^2} \\
 &= \sqrt{8^2 + 6^2} = 10\Omega \\
 \text{Conductance } (G_1) &= \frac{R_1}{Z_1^2} = \frac{6}{10^2} = 0.06\text{U}
 \end{aligned}$$

$$\text{Conductance } (G_2) = \frac{R_2}{Z_2^2} = \frac{8}{10^2} = 0.08\text{U}$$

$$\text{Susceptance } (B_1) = \frac{-X_1}{Z_1^2} = \frac{-8}{10^2} = -0.08\text{U}$$

$$\text{Susceptance } (B_2) = \frac{X_2}{Z_2^2} = \frac{6}{10^2} = 0.06\text{U}$$

$$\begin{aligned}
 \text{Admittance } (Y_1) &= \sqrt{G_1^2 + B_1^2} \\
 &= \sqrt{0.06^2 + 0.08^2} = 0.1\text{U}
 \end{aligned}$$

$$\begin{aligned}
 \text{Admittance } (Y_2) &= \sqrt{G_2^2 + B_2^2} \\
 &= \sqrt{0.08^2 + 0.06^2} = 0.1\text{U}
 \end{aligned}$$

$$\begin{aligned}
 \text{Current in branch 1 : } I_1 &= V \cdot Y_1 \\
 &= 220 \times 0.1 = 22 \text{Amps}
 \end{aligned}$$

$$\begin{aligned}
 \text{Current in branch 2 : } I_2 &= V \cdot Y_2 \\
 &= 220 \times 0.1 = 22 \text{Amps}
 \end{aligned}$$

$$\begin{aligned}
 \text{Total Conductance } (G) &= G_1 + G_2 \\
 &= 0.06 + 0.08 = 0.14\text{U}
 \end{aligned}$$

$$\begin{aligned}
 \text{Total Susceptance } (B) &= B_1 + B_2 \\
 &= -0.08 + 0.06 = -0.02\text{U}
 \end{aligned}$$

$$\begin{aligned}
 \text{Total Admittance } (Y) &= \sqrt{G^2 + B^2} \Omega \\
 &= \sqrt{0.14^2 + 0.02^2} = 0.14 \text{ U}
 \end{aligned}$$

$$\begin{aligned}
 \text{Phase angle} &= \tan^{-1} \frac{B}{G} \\
 &= \tan^{-1} \frac{0.02}{0.14} = 8.13
 \end{aligned}$$

$$\begin{aligned}
 \text{Power Factor : } \cos \theta &= \cos 8.13 \\
 &= 0.98
 \end{aligned}$$

$$\text{Total Current } (I) = V \cdot Y$$

$$= 220 \times 0.14 = 30.8 \text{ Amps}$$

$$\text{Power (P)} = V I \cos \theta$$

$$= 220 \times 30.8 \times 0.98$$

$$= 6640 \text{ Watts}$$

Answer:

- | | |
|--|---------------------------------------|
| i) $G = 0.14 \Omega$, $B = 0.02 \Omega$ and $Y = 0.14 \Omega$ | ii) Total current (I) = 30.8 Amps |
| iii) Power factor = 0.98 | iv) Power (P) = 6640 Watts |

Example: 31

Two impedances $Z_1 = (10+j5) \Omega$ and $Z_2 = (8+j6) \Omega$ are connected in parallel across 200V. Find the total current taken and also the power factor of the circuit.

Given Data:

$$\text{Impedance } (Z_1) = 10+j5$$

$$\text{Impedance } (Z_2) = 8+j6$$


$$\text{Supply Voltage (V)} = 200 \text{ Volts}$$

To Find:

$$\text{i) Total current} = ?$$

$$\text{ii) Power factor (P.F)} = ?$$

Solution:

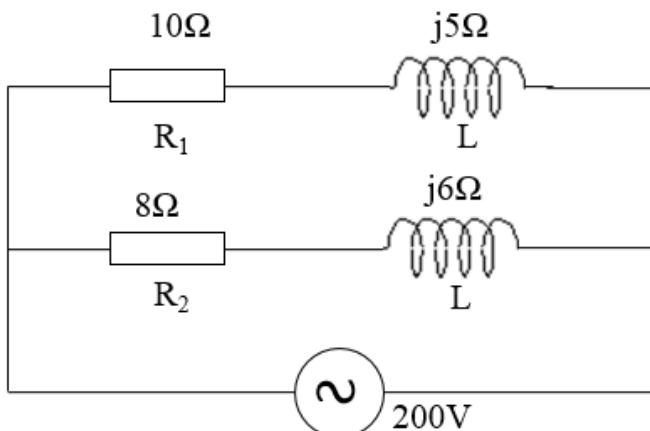

$$Z_1 = \sqrt{R_1^2 + X_L^2}$$

$$= \sqrt{10^2 + 5^2} = 11.18 \Omega$$

$$Z_2 = \sqrt{R_2^2 + X_C^2}$$

$$= \sqrt{8^2 + 6^2} = 10 \Omega$$

$$\text{Conductance } (G_1) = \frac{R_1}{Z_1^2} = \frac{10}{11.18^2} = 0.08 \Omega$$

$$\text{Conductance } (G_2) = \frac{R_2}{Z_2^2} = \frac{8}{10^2} = 0.08 \Omega$$

$$\text{Susceptance } (B_1) = \frac{-X_1}{Z_1^2} = \frac{-5}{11.18^2} = -0.04\text{U}$$

$$\text{Susceptance } (B_2) = \frac{-X_2}{Z_2^2} = \frac{-6}{10^2} = -0.06\text{U}$$

$$\begin{aligned}\text{Admittance } (Y_1) &= \sqrt{G_1^2 + B_1^2} \\ &= \sqrt{0.08^2 + 0.04^2} = 0.08\text{U}\end{aligned}$$

$$\begin{aligned}\text{Admittance } (Y_2) &= \sqrt{G_2^2 + B_2^2} \\ &= \sqrt{0.08^2 + 0.06^2} = 0.1\text{U}\end{aligned}$$

$$\begin{aligned}\text{Current in branch 1 : } I_1 &= V \cdot Y_1 \\ &= 200 \times 0.08 = 16 \text{Amps}\end{aligned}$$

$$\begin{aligned}\text{Current in branch 2 : } I_2 &= V \cdot Y_2 \\ &= 200 \times 0.1 = 20 \text{Amps}\end{aligned}$$

$$\begin{aligned}\text{Total Conductance } (G) &= G_1 + G_2 \\ &= 0.08 + 0.08 = 0.16\text{U}\end{aligned}$$

$$\begin{aligned}\text{Total Susceptance } (B) &= B_1 + B_2 \\ &= -0.04 - 0.06 = -0.1\text{U}\end{aligned}$$

$$\begin{aligned}\text{Total Admittance } (Y) &= \sqrt{G^2 + B^2} \Omega \\ &= \sqrt{0.16^2 + 0.1^2} = 0.18 \text{ U}\end{aligned}$$

$$\begin{aligned}\text{Phase angle} &= \tan^{-1} \frac{B}{G} \\ &= \tan^{-1} \frac{0.1}{0.16} = 32\end{aligned}$$

$$\begin{aligned}\text{Power Factor : Cos } \theta &= \cos 32 \\ &= 0.84\end{aligned}$$

$$\begin{aligned}\text{Total Current } (I) &= V \cdot Y \\ &= 200 \times 0.18 = 36 \text{ Amps}\end{aligned}$$

$$\begin{aligned}\text{Power } (P) &= V I \cos \theta \\ &= 200 \times 36 \times 0.84 \\ &= 6077 \text{ Watts}\end{aligned}$$

Answer:

$$\text{i) Total current } (I) = 36 \text{ Amps} \quad \text{ii) Power factor} = 0.84$$

Example: 32


A coil of resistance of 8 ohm and a reactance of 10 ohm are connected in parallel with a resistor of 10 ohm. If the voltage across the combination is 200 volts a.c. Find the total current taken from the mains. Also find the power factor of the circuit.

Given Data:

| | | |
|---------------------|---|-----------|
| Impedance (Z_1) | = | $8+j10$ |
| Impedance (Z_2) | = | $10+j0$ |
| Supply Voltage (V) | = | 200 Volts |

To Find:

- i) Total current = ?
- ii) Power factor (P.F) = ?

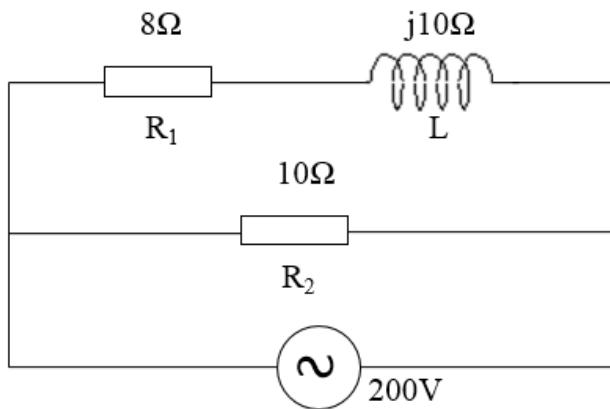Solution:

$$\begin{aligned} Z_1 &= \sqrt{R_1^2 + X_L^2} \\ &= \sqrt{8^2 + 10^2} = 12.8\Omega \end{aligned}$$

$$\begin{aligned} Z_2 &= \sqrt{R_2^2 + X_C^2} \\ &= \sqrt{10^2} = 10\Omega \end{aligned}$$

$$\text{Conductance } (G_1) = \frac{R_1}{Z_1^2} = \frac{8}{12.8^2} = 0.04\text{U}$$

$$\text{Conductance } (G_2) = \frac{R_2}{Z_2^2} = \frac{10}{10^2} = 0.1\text{U}$$

$$\text{Susceptance } (B_1) = \frac{-X_1}{Z_1^2} = \frac{-10}{12.8^2} = -0.06\text{U}$$

$$\text{Susceptance } (B_2) = 0$$

$$\begin{aligned} \text{Admittance } (Y_1) &= \sqrt{G_1^2 + B_1^2} \\ &= \sqrt{0.04^2 + 0.06^2} = 0.07\text{U} \end{aligned}$$

$$\begin{aligned} \text{Admittance } (Y_2) &= \sqrt{G_2^2 + B_2^2} \\ &= \sqrt{0.1^2 + 0^2} = 0.1\text{U} \end{aligned}$$

Current in branch 1 : $I_1 = V \cdot Y_1$
 $= 200 \times 0.07 = 14 \text{Amps}$

Current in branch 2 : $I_2 = V \cdot Y_2$
 $= 200 \times 0.1 = 20 \text{Amps}$

Total Conductance (G) $= G_1 + G_2$
 $= 0.04 + 0.1 = 0.14 \Omega$

Total Susceptance (B) $= B_1 + B_2$
 $= -0.06 \Omega$

Total Admittance (Y) $= \sqrt{G^2 + B^2} \Omega$
 $= \sqrt{0.14^2 + 0.06^2} = 0.15 \Omega$

Phase angle $= \tan^{-1} \frac{B}{G}$
 $= \tan^{-1} \frac{0.06}{0.14} = 23.19$

Power Factor : $\cos \theta = \cos 23.19$
 $= 0.91$


Total Current (I) $= V \cdot Y$
 $= 200 \times 0.15 = 30 \text{Amps}$

Power (P) $= V I \cos \theta$
 $= 200 \times 30 \times 0.91$
 $= 5460 \text{ Watts}$


- Answer:
- i) Total current (I) $= 30 \text{ Amps}$
 - ii) Power factor $= 0.91$

RESULT OF SIMULATION OF PROBLEMS IN UNIT III

Problem : 10

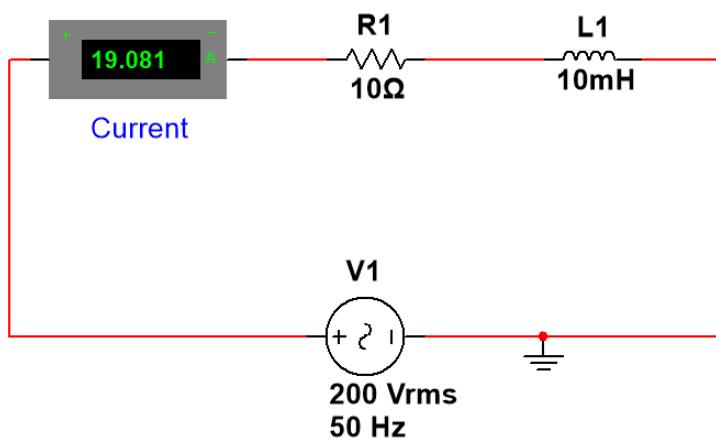


Problem : 11

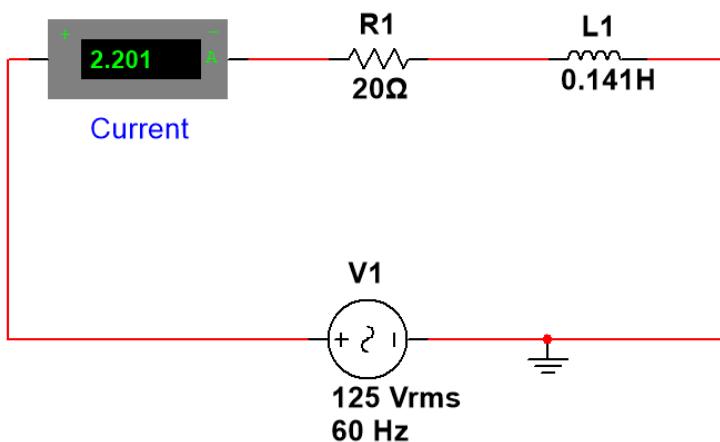


Problem: 14

Result of Simulation:

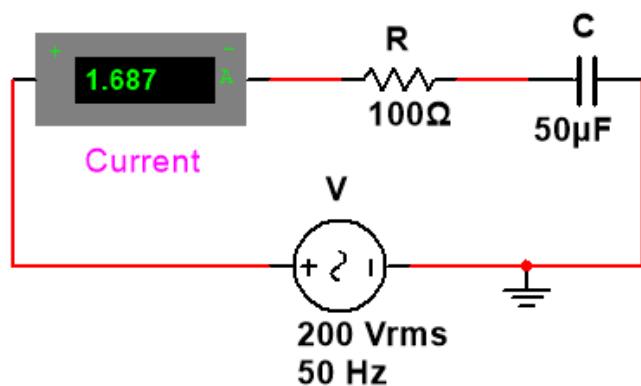


Problem: 15

Result of Simulation:

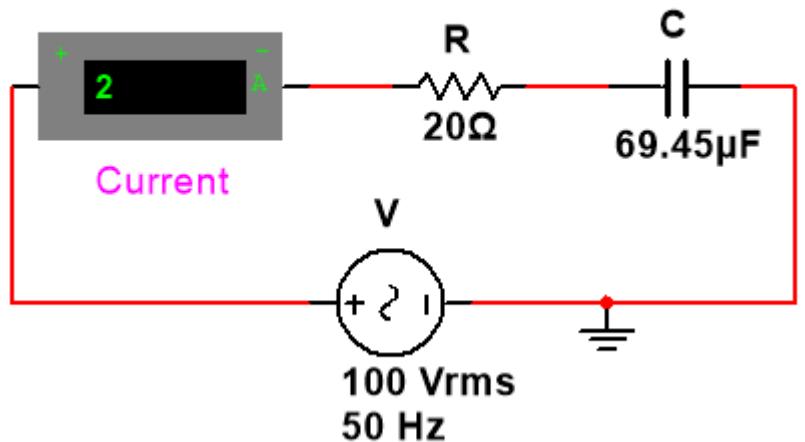


Problem: 18

Result of Simulation:

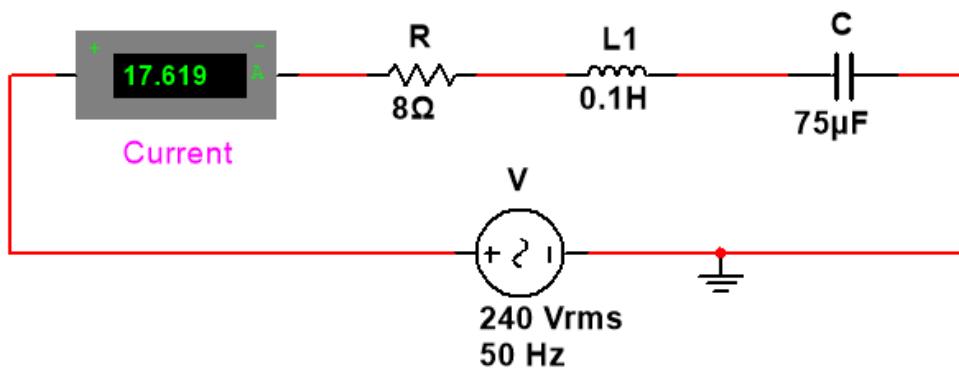


Problem: 19


Result of Simulation:

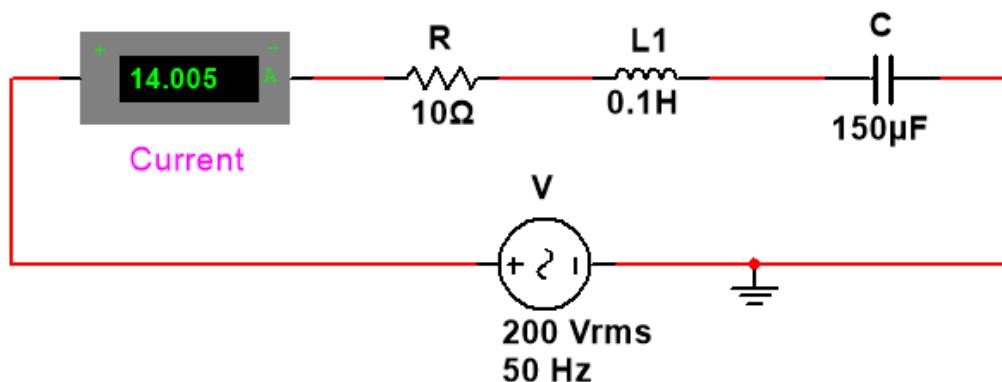


Problem: 28

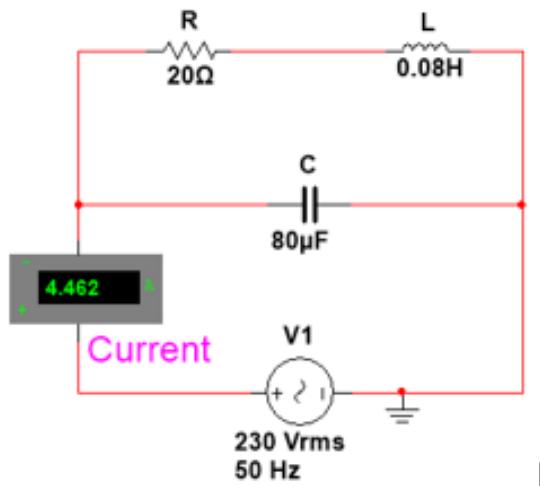

Problem 30:

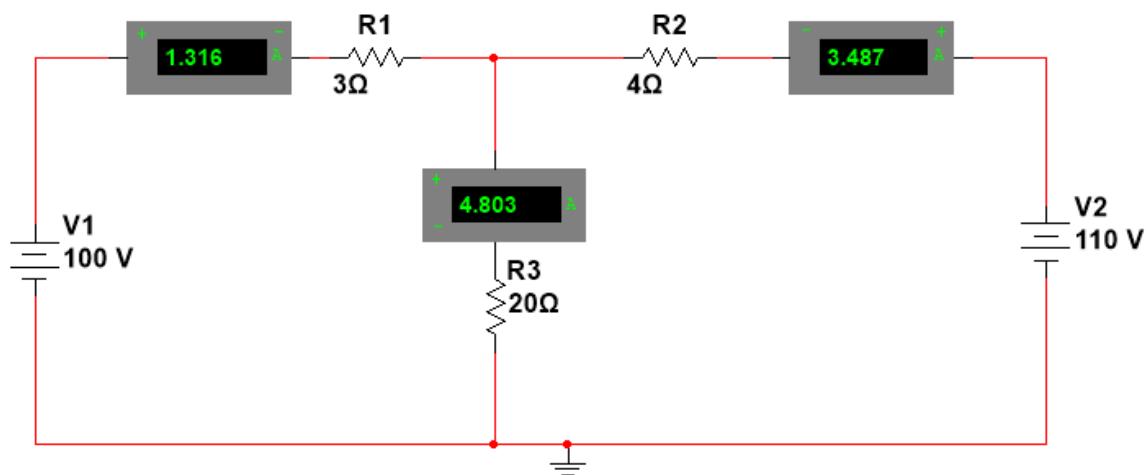

Problem 31:

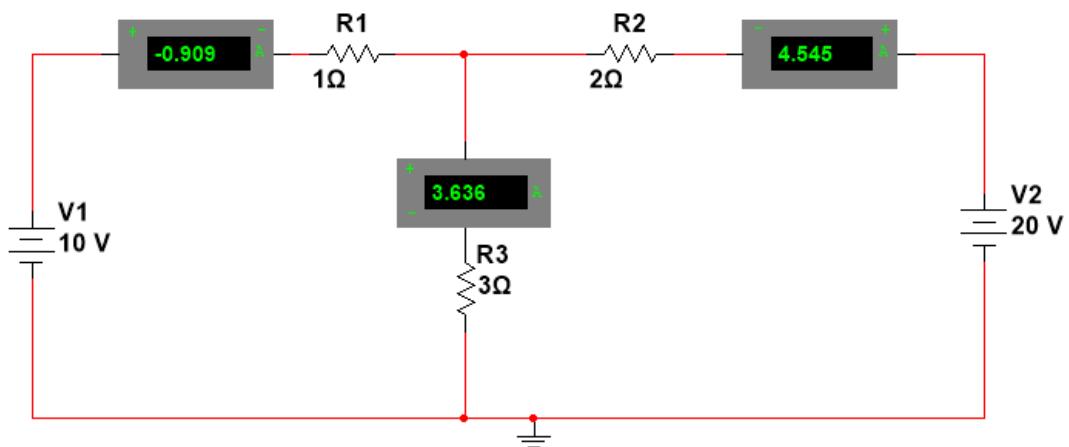

REVIEW QUESTIONS
UNIT : III SINGLE PHASE AC CIRCUITS

PART – A : 2 Mark Questions

1. Define A.C Voltage.
2. Define Cycle.
3. Define frequency and state its unit.
4. Define time period.
5. State the relationship between frequency and period.
6. Define instantaneous value of a.c voltage.
7. Define maximum or peak value or crest value?
8. Why average value for a symmetrical wave is computed for half cycle only?
9. Define form factor.
10. Define peak factor or Amplitude or crest factor.
11. Define power factor.
12. State the value of form factor and peak factor for sinusoidal a.c. quantity?
13. Define Phase difference?
14. What is meant by reference phasor?
15. Define in-phase quantities.
16. Define inductive reactance.
17. State the expression for inductance reactance.
18. What is the unit of inductive reactance?
19. Draw the phasor diagram for a pure inductor.
20. Define capacitive reactance.
21. State the expression for capacitive reactance and its unit.
22. Convert the following current in polar into rectangular form. $5 \angle 30^\circ$
23. Define admittance and state its unit.
24. What do you mean by conductance, admittance and susceptance.

PART – B : 3 Marks Questions

1. Define alternating quantity, amplitude and cycle.
2. Draw a sinusoidal voltage waveform and mark the cycle, time period and peak value.
3. Define: (i) Cycle (ii) Frequency (iii) Time period
4. Define : (i) Instantaneous value (ii) time period (iii) frequency
5. Define average value and RMS value of a.c quantity.
6. Derive an expression for average value of a.c quantity in terms of maximum value.
7. Define Instantaneous value of a.c current and write the equations in 3 different forms.

8. Explain the terms: (i) Form factor (ii) Peak factor
9. Prove that power drawn by a pure inductor connected across AC supply is zero.
10. Show that active power in pure capacitor connected across AC supply is zero
11. Draw impedance triangle and phasor diagram for RC series circuit.
12. Draw impedance triangle and phasor diagram for RL series circuit.
13. Draw the impedance triangle for a RLC series circuit and write the expression for impedance.
14. Define Power factor.
15. Explain what is meant by leading and lagging p.f?
16. Briefly explain about power triangle.
17. Explain the terms: (i) apparent power (ii) active power (iii) reactive power.
18. Draw admittance triangle and phasor diagram for RL Parallel circuit.
19. Draw admittance triangle and phasor diagram for RC Parallel circuit.

PART – C : 10 Mark Questions

1. Define and derive average value of alternating voltage.
2. Define and derive RMS value of alternating current.
3. Draw the vector diagram of a series R-L circuit and derive the impedance.
4. Draw the vector diagram of a series R-C circuit and derive the impedance.
5. Draw the vector diagram of a series R-L-C circuit and derive the impedance.
6. Show that the power in an R-L series circuit is $P= V.I.\cos\Phi$ watts.
7. Show that the power in an R-C series circuit is $P= V.I.\cos\Phi$ watts.
8. Show that the power in an R-L-C series circuit is $P= V.I.\cos\Phi$ watts.
9. An alternating voltage is given by $e = 100 \sin 314 t$. Find a) Max value b) Frequency c) Time period and d) value of current after $t=0.01$ sec.
10. The equation for a voltage is written as $E = 100 \sin 314 t$. find a) Frequency b) max value c) Average value d) RMS value and e) voltage at time $1/200$ sec after passing first zero.
11. An ac voltage of 50 Hz frequency has a peak value of 200 V. a) Write an equation to calculate the instantaneous value of the voltage b) write an equation for a current having a max value of 20 A and lagging the voltage by 45° and e) Find average effective values of voltage and current.
12. An alternating voltage $v = 200 \sin 314 t$ is applied to a device which offers an ohmic resistance of 25Ω to the flow of current in one direction while entirely preventing the flow of current in the opposite direction. Calculate the RMS value, average value.

13. A 50 Hz alternating voltage of 250 V sends a current of 2.5A through the pure inductive coil.
Find a) inductive reactance of the coil b) Inductance of the coil c) power absorbed and d) write down the equation for voltage and current.
14. An alternating current of maximum value 10A flows through a capacitor of 31.8 mfd.
Calculate a) capacitive reactance b) RMS value of applied voltage and c) RMS value of current.
15. A current 20A flows in a circuit with 45° angle of lag. When the applied voltage is 200V 50Hz.
Find a) Resistance b) Inductance and c) Impedance of the circuit.
16. A coil has a resistance of 20Ω and an inductance of 0.2 H, connected 230 V, 50 Hz supply.
Calculate a) the circuit current b) phase angle power factor & d) power consumed.
17. A coil of resistance of 8Ω , an inductance of 0.1 and a capacitance of 75 mfd across a 230 V 50 Hz supply. Find a) current in the circuit b) power factor c) power and d) voltage across coil and capacitor.
18. A resistance of 15Ω and a coil of inductance 30 mH and negligible resistance are connected in parallel across 240V 50Hz supply. Find a) the line current b) power factor and c) power consumed by the circuit.
19. A coil having a resistance of 5Ω and an inductance of 0.02H is connected in parallel with another coil having a resistance of 1Ω and an inductance 0.08H. Calculate the current through the combination and the power absorbed when a voltage of 100V 50 Hz is applied.
Draw the phasor diagram.
20. A circuit having a resistance of 6Ω and inductive reactance of 8Ω is connected across 230 V 50 Hz mains in parallel with another circuit having a resistance of 8Ω and a capacitive reactance of 6Ω . Find a) Total current b) phase angle between current supply voltage.
21. A voltage of $200 + j 100$ volts applied to a circuit causes a current of $10 + j2$ ampere to flow.
Find the impedance and power factor of the circuit.
22. A coil of resistance 15Ω and inductance 0.1 H is in parallel with a resistor of 2.5Ω . A voltage of 220 V at 50 Hz is applied to the parallel combination. Determine the total current and the power factor.

23. A $10\ \Omega$ resistor, 12.5 mH inductor and 150 mfd capacitor are connected in parallel to a 230 V 50 Hz source. Calculate the supply current and power factor.
24. A chocking coil of resistance $5\ \Omega$ and inductance 0.6 H is in series with a capacitor of 10 mfd . If a voltage of 200 V is applied and the frequency is adjusted to resonance, find the current and the voltage across inductance and capacitor.
25. A circuit having a resistance of $5\ \Omega$ an inductance of 0.5 H and a variable capacitor in series is connected across $200\text{V } 50\text{Hz}$ supply. Calculate a) the capacitance to give resonance b) voltage across inductance and capacitance c) 'Q' factor of the circuit.
26. A coil $10\ \Omega$ resistance and 0.2 H inductance is connected in parallel with a variable capacitor across a $230\text{V } 50\text{Hz}$ supply. Determine a) capacitance required for parallel resonance b) Effective impedance of the circuit and c) Power absorbed.

UNIT IV – RESONANT CIRCUITS

Syllabus:

Series resonance – parallel resonance (R,L &C; RL&C only) – quality factor – dynamic resistance – comparison of series and parallel resonance – Problems in the above topics - Applications of resonant circuits.

4.1 Introduction:


When introducing a.c. circuits in unit- III, a supply was defined by its voltage and frequency. For many applications, they are constant; for example, the source of supply to our homes. However, many communications systems involve circuits in which either the supply voltage or input signal operates with a varying frequency.

Circuits with both inductance and capacitance can exhibit the property of resonance, which is important in many types of applications. Resonance is the basis for frequency selectivity in communication systems. For example, the ability of a radio or television receiver to select a certain frequency that is transmitted by a particular station and, at the same time to eliminate frequencies from other stations is based on the principle of resonance. The conditions in RLC circuits that produce resonance and characteristics of resonance circuits are covered in this unit.

4.1 Resonance:

Inductive reactance increases as the frequency is increased, but capacitive reactance decreases with higher frequencies. Because of these opposite characteristics, for any LC combination there must be a frequency at which the X_L equals the X_C as one increases while other decreases. This case of equal and opposite reactance is called resonance and this circuit is called as resonance circuit.

4.2 R.L.C Series Resonance Circuit:

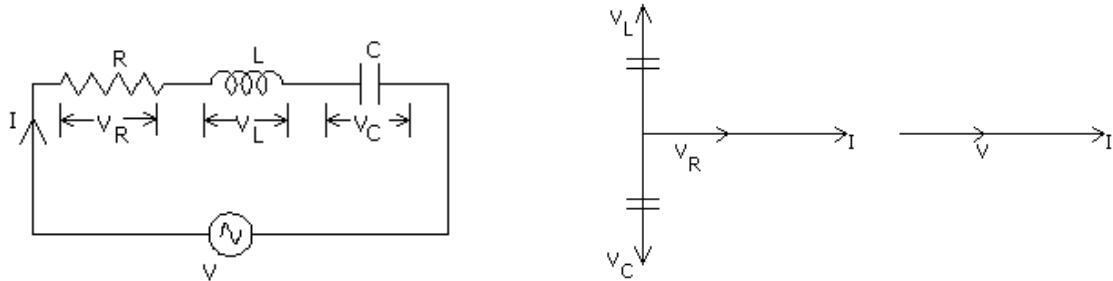

Resonance is a condition in a series RLC circuit in which the capacitive reactance and inductive reactance are equal in magnitude. When they are equal, they cancel each other and total reactance is zero and result is a purely resistive impedance. And also the p.f is unity.

$$\text{Impedance } (Z) = \sqrt{R^2 + (X_L - X_C)^2} \Omega$$

When, $X_L = X_C$

$$\text{Impedance } (Z) = \sqrt{R^2} = R$$

4.3 Resonance frequency:

The frequency at which the inductive reactance and capacitive reactance are equal is the resonant frequency.

At resonance:

Inductive Reactance = Capacitive Reactance

$$X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r^2 = \frac{1}{4\pi^2 L C}$$


$$f_r = \frac{1}{2\pi\sqrt{LC}} ; \text{Hz} \quad \text{Where, } f_r - \text{Resonance frequency}$$

Resonance Frequency:

$$f_r = \frac{1}{2\pi\sqrt{LC}} ; \text{Hz}$$

At the resonance frequency (f_r), the voltage across C and L are equal in magnitude but 180° out of phase and they cancel each other.

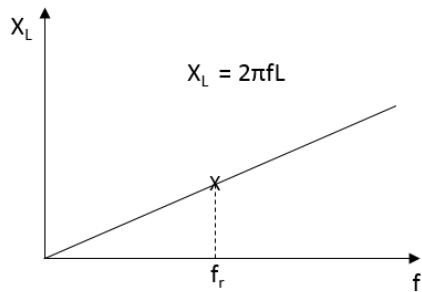4.4 Effect of varying frequency on Inductive reactance (X_L) :



$$\text{Inductive Reactance } (X_L) = 2\pi f L$$


When frequency = 0; $X_L = \infty$

When frequency increase = X_L also increases

When frequency = ∞ ; $X_L = 0$

Hence, X_L varies linearly with frequency and it is a straight line passing through origin.

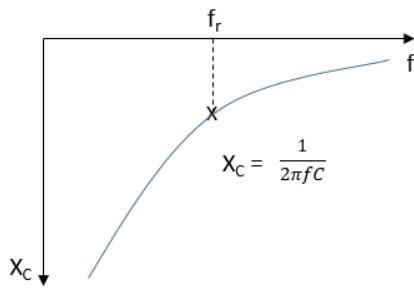4.5 Effect of varying frequency on Capacitive reactance (X_C) :



$$\text{Capacitive Reactance } X_C = \frac{1}{2\pi f C}$$


When frequency = 0; $X_C = 0$

When frequency increase = X_C decreases

When frequency = ∞ ; $X_C = \infty$

Hence, X_C varies indirectly with frequency and it is a rectangular hyperbola.

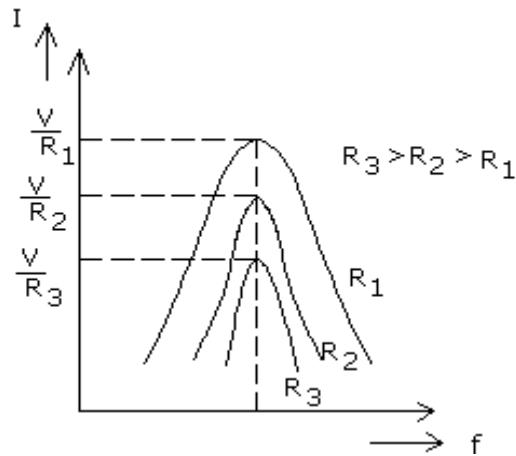
4.6 Effect of varying circuit resistance:



1. The impedance at resonance frequency is minimum, current is maximum.
2. Above f_r , $X_L > X_C$ and the circuit behaves as R_L circuit with lagging power factor.
3. At frequency less than f_r , $X_C < X_L$ and the circuit behaves as RC circuit drawing a leading current.

The resistance value does not affect the frequency at which resonance occurs, but the magnitude of current is decided by the resistance value. When R is increased, the current becomes less.


4.7 Characteristics of series resonance:

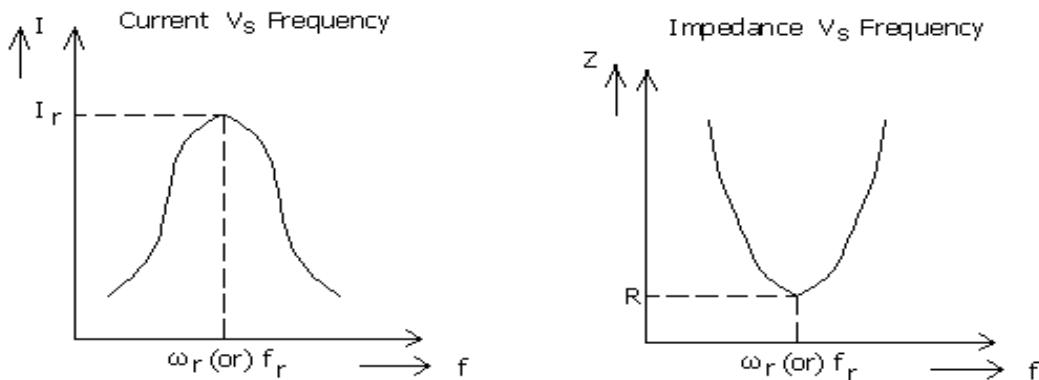

| Resonance frequency (f_r) | Effect on reactance | Effect on impedance | Behavior of circuit | Effect on current | Effect of power factor |
|-------------------------------|---------------------|---------------------|---------------------|-------------------|---------------------------|
| Below resonance frequency | $X_C > X_L$ | $Z > R$ | Capacitive | $I < I_{max}$ | Less than unity (leading) |
| At resonance frequency | $X_C = X_L$ | $Z = R$ | Resistive | $I = I_{max}$ | $p.f = 1$ (unity) |
| Above resonance frequency | $X_C < X_L$ | $Z > R$ | Inductive | $I < I_{max}$ | Less than unity (lagging) |

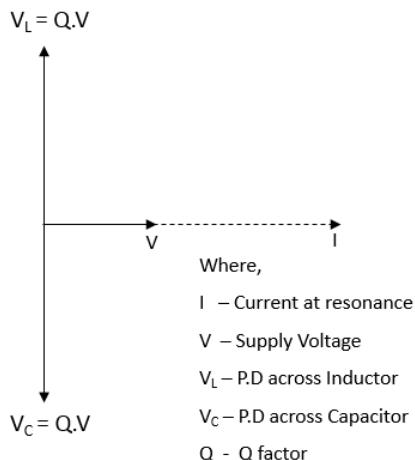4.8 Q-factor (or) Quality factor:

At series resonance, the p.d across L or C builds up to a value many times greater than the applied voltage. The voltage magnification produced by series resonance is termed as Q-factor of the series resonance circuit. It is also called as voltage magnification.



$$\text{Voltage magnification (or)} \quad \frac{\text{Q-factor}}{\text{Supply Voltage}} = \frac{\text{Voltage across L or C}}{\text{Supply Voltage}}$$

$$\text{At resonance,} \quad I = \frac{V}{R}$$

$$\text{P.D across L or C} = I \cdot X_L \quad (\text{or}) \quad I \cdot X_C$$

$$\text{Supply Voltage} \quad V = I \cdot R$$

$$\text{Q-factor} = \frac{I \cdot X_L}{I \cdot R} = \frac{X_L}{R}$$

$$\text{Q-factor} = \frac{2\pi f_r L}{R}$$

$$\text{Where,} \quad f_r = \frac{1}{2\pi\sqrt{LC}} ; \text{Hz}$$

$$\text{Q-factor} = \frac{2\pi L}{R \cdot 2\pi\sqrt{LC}}$$

$$\text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{(or)} \quad \text{Q-factor} = \frac{\text{Resonance Frequency}}{\text{Bandwidth}}$$

Q-factor is large only when the value of L is large.

The value of Q –factor depends upon the design of the coil because resistance arises in this rather in a capacitor. With a well-designed coil, the quality factor can be 200 or more.

4.8.1 Importance of Q-Factor:

The Q-factor of series a.c circuit indicates how many times the p.d across L or C is greater than the applied voltage at resonance. For example, consider an R.L.C series circuit connected to 240V a.c source. If Q-factor of the coil is 20, then voltage across L or C will be $20 \times 240 = 4800$ V at resonance

$$\text{i.e } V_C = V_L = Q \cdot V_R = 20 \times 240 = 4800 \text{ V.}$$


4.8.2 Q- Factor and Resonance curve:

At series resonance, the current is maximum and the current is limited by circuit resistance only. The smaller the circuit resistance, the greater is the circuit current and sharper will be resonance curve. Smaller circuit resistance means large value of Q-factor ($=X_L/R$). Therefore, the greater the Q-factor of resonance RLC circuit, the sharper is the resonance curve.

4.9 Bandwidth (BW):

The bandwidth is defined as the range of frequency at the limits of which the current is equal to or greater than 70.7% of maximum current. Thus

$$\text{Bandwidth} = f_2 - f_1$$

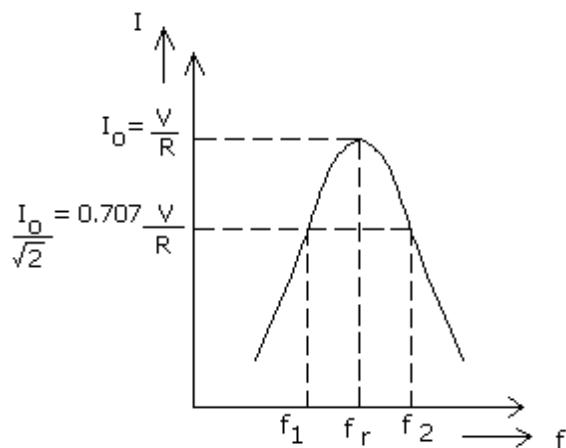

The frequency f_1 and f_2 are called as half power points or frequency. They are also referred to as cut-off frequencies. The bandwidth is an indication of sharpness or degree of tuning.

$$\begin{aligned}\text{Bandwidth} &= \frac{\text{Resonance Frequency}}{\text{Q factor}} \\ &= \frac{f_r}{Q}\end{aligned}$$

4.9.1 Derive Q factor from Bandwidth and Resonant frequency:

$$\text{Q-factor} = \frac{\text{Resonance Frequency}}{\text{Bandwidth}}$$

$$\text{Q-factor} = \frac{f_r}{\text{BW}}$$

$$\text{Q-factor} = \frac{f_r}{f_2 - f_1}$$

At smaller bandwidth, there is high Q-factor

4.10 Selectivity:

The ability of resonant circuit to reject the frequency other than the resonant frequency is known as *selectivity*. It is also defined as the ratio of bandwidth and resonant frequency.

$$\begin{aligned}\text{Selectivity} &= \frac{\text{Bandwidth}}{\text{Resonance Frequency}} \\ &= \frac{\text{BW}}{f_r} \\ \text{Selectivity} &= \frac{f_2 - f_1}{f_r}\end{aligned}$$

A circuit is said to be selective if the response has a sharp peak and narrow bandwidth and is achieved with a high Q factor. Q is therefore a measure of selectivity.

4.10.1 Importance of Selectivity:

1. Fine-tuning
2. To avoid the interference of adjacent channel
3. To reject the image frequency

4.11 Acceptor Circuit:

An RLC series circuit accepts maximum current from the source at resonance and for that reason is called an acceptor circuit.

4.12 Properties of Series Resonance:

1. Impedance $Z = R$
2. Voltage across L and C are equal (i.e.) $V_L = V_C$
3. Current in the resonance circuit is maximum.
4. It magnifies voltage.
5. It is also called as acceptor circuit.
6. Power factor is unity.(i.e.) $\cos \theta=1$

Example: 1

A coil having a resistance of 8Ω and an inductance of 20mH is connected in series with a 10 MFD capacitor. Calculate i) Resonance frequency ii) Q-factor of the coil iii) Bandwidth and iv) Half power frequencies.

Given Data:

| | | |
|---------------------|---|--|
| Connection | = Series | To Find: |
| Resistance (R) | = 8Ω | i) Resonance Frequency =? |
| Inductance (L) | = $20\text{mH} = 20 \times 10^{-3} \text{ H}$ | ii) Q-Factor =? |
| Capacitance (C) | = 10 MFD | iii) Bandwidth =? iv) Half power frequencies =? |

Solution:

$$\begin{aligned}\text{Resonance Frequency } (F_r) &= \frac{1}{2\pi\sqrt{LC}} \\&= \frac{1}{2 \times 3.14\sqrt{LC}} \\&= \frac{1}{2 \times 3.14\sqrt{20 \times 10^{-3} \times 10 \times 10^{-6}}} \\&= \frac{1}{2 \times 3.14 \times 4.47 \times 10^{-4}} \\&= 356.06 \text{ Hz}\end{aligned}$$

$$\begin{aligned}\text{Q- Factor} &= \frac{1}{R} \sqrt{\frac{L}{C}} \\&= \frac{1}{8} \sqrt{\frac{20 \times 10^{-3}}{10 \times 10^{-6}}} \\&= \frac{1}{8} \times 44.72 \\&= 5.59\end{aligned}$$

Half Power Frequencies:

$$\begin{aligned}\text{Lower cut-off frequencies } (F_1) &= F_r - \frac{R}{4\pi L} \\&= 356.06 - \frac{8}{4\pi \times 20 \times 10^{-3}} \\&= 356.06 - 31.84 \\&= 324.22 \text{ Hz}\end{aligned}$$

$$\begin{aligned}\text{Upper cut-off frequencies } (F_2) &= F_r + \frac{R}{4\pi L} \\&= 356.06 + \frac{8}{4\pi \times 20 \times 10^{-3}} \\&= 356.06 + 31.84 \\&= 387.9 \text{ Hz}\end{aligned}$$

$$\begin{aligned}\text{Bandwidth} &= F_2 - F_1 \\&= 387.9 - 324.22 \\&= 63.68 \text{ Hz}\end{aligned}$$

Answer:

- i) Resonance Frequency (F_r) = 356.06 Hz ii) Q- Factor = 5.59
- iii) Half power frequencies: iv) Bandwidth = 63.68 Hz
- $F_1 = 324.22 \text{ Hz}$ and $F_2 = 387.9 \text{ Hz}$

Example: 2

A series RLC circuit has resistance of 5 Ohm, inductance of 10mH and capacitance of 1mfd with an applied voltage of 100V, variable frequency. Calculate the resonant frequency, circuit current and voltage across inductor and capacitor. Also find the quality factor.

Given Data:

| | |
|-----------------|------------------------------|
| Connection | = Series |
| Resistance (R) | = 5 Ω |
| Inductance (L) | = 10mH = 10×10^{-3} |
| Capacitance (C) | = 1 MFD |
| Voltage (V) | = 100 V |

To Find:

- i) Resonance Frequency =?
- ii) Circuit Current (I) =?
- iii) P.D across L and C
- iv) Q-Factor =?

Solution:

$$\begin{aligned}\text{Resonance Frequency } (F_r) &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2 \times 3.14\sqrt{LC}} \\ &= \frac{1}{2 \times 3.14\sqrt{10 \times 10^{-3} \times 1 \times 10^{-6}}} \\ &= \frac{1}{2 \times 3.14 \times 1 \times 10^{-4}}\end{aligned}$$

$$\text{Resonance Frequency } (F_r) = 1592 \text{ Hz}$$

$$\begin{aligned}\text{Circuit Current } (I) &= \frac{V}{R} = \frac{100}{5} = 20 \text{ Amps} \\ I &= 20 \text{ Amps}\end{aligned}$$

$$\begin{aligned}\text{Q- Factor} &= \frac{1}{R} \sqrt{\frac{L}{C}} \\ &= \frac{1}{5} \sqrt{\frac{10 \times 10^{-3}}{1 \times 10^{-6}}} \\ &= \frac{1}{5} \times 100\end{aligned}$$

$$\text{Q- Factor} = 20$$

$$\begin{aligned}\text{P.D across inductor } (V_L) &= I \cdot X_L \\ &= I \times 2\pi f_r L \\ &= 20 \times 2 \times 3.14 \times 1592 \times 10 \times 10^{-3} \\ &= 2000 \text{ Volts}\end{aligned}$$

$$\begin{aligned}\text{P.D across Capacitor } (V_c) &= V_L \quad (\because V_L = V_c) \\ &= 2000 \text{ Volts}\end{aligned}$$

Example: 3

A series circuit contains a resistance of 4 Ohms and inductance of 0.5H and a variable capacitor across 100V, 50Hz supply. Find (i) the capacitance for getting resonance (b) the p.d across inductance and capacitance (iii) the Q-factor of the series circuit.

Given Data:

| | |
|----------------|----------|
| Connection | = Series |
| Resistance (R) | = 4 Ω |
| Inductance (L) | = 0.5H |
| Voltage (V) | = 100V |
| Frequency (F) | = 50Hz |

To Find:

- i) Capacitance (C) =?
- ii) P.D across L and C
- iii) Q-Factor =?

Solution:

At resonance:

$$\begin{aligned}
 X_L &= X_C \\
 2\pi fL &= \frac{1}{2\pi fC} \\
 2\pi fC &= \frac{1}{2\pi fL} \\
 C &= \frac{1}{4\pi^2 f^2 L} \\
 &= \frac{1}{4 \times 3.14^2 \times 50^2 \times 0.5} \\
 C &= 20.28\mu F
 \end{aligned}$$

$$\text{Circuit Current (I)} = \frac{V}{R} = \frac{100}{4} = 25 \text{ Amps}$$

$$\begin{aligned}
 \text{Q- Factor} &= \frac{1}{R} \sqrt{\frac{L}{C}} \\
 &= \frac{1}{4} \sqrt{\frac{0.5}{20.28 \times 10^{-6}}} \\
 &= \frac{1}{4} \times 157 \\
 \text{Q- Factor} &= 39.25
 \end{aligned}$$

$$\begin{aligned}
 \text{P.D across inductor (V}_L\text{)} &= I \cdot X_L \\
 &= I \times 2\pi f_r L \\
 &= 25 \times 2 \times 3.14 \times 50 \times 0.5 \\
 &= 3925 \text{ Volts}
 \end{aligned}$$

$$\begin{aligned}
 \text{P.D across Capacitor (V}_C\text{)} &= V_L \\
 &= 3925 \text{ Volts}
 \end{aligned}$$

Example: 4

In a RLC series resonance circuit a resistance of 10Ω and an inductance of 20mH is connected in series with a 0.5 MFD capacitor. Calculate i) Resonance frequency ii) Q-factor of the coil iii) Half power frequencies iv) Bandwidth and v) Power consumed at resonance if applied voltage to circuit is 200V a.c.

Given Data:

| | To Find: |
|-----------------|-------------------------------|
| Connection | i) Resonance Frequency =? |
| Resistance (R) | ii) Q-Factor =? |
| Inductance (L) | iii) Bandwidth =? |
| Capacitance (C) | iv) Half power frequencies =? |
| Voltage (V) | v) Power consumed =? |

Solution:

$$\begin{aligned}
 \text{Resonance Frequency } (F_r) &= \frac{1}{2\pi\sqrt{LC}} \\
 &= \frac{1}{2 \times 3.14\sqrt{LC}} \\
 &= \frac{1}{2 \times 3.14\sqrt{20 \times 10^{-3} \times 0.5 \times 10^{-6}}} \\
 &= \frac{1}{2 \times 3.14 \times 1 \times 10^{-4}} \\
 \text{Resonance Frequency } (F_r) &= 1592 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 \text{Q- Factor} &= \frac{1}{R} \sqrt{\frac{L}{C}} \\
 &= \frac{1}{10} \sqrt{\frac{20 \times 10^{-3}}{0.5 \times 10^{-6}}} \\
 &= \frac{1}{10} \times 200 \\
 \text{Q- Factor} &= 20
 \end{aligned}$$

Half Power Frequencies:

$$\begin{aligned}
 \text{Lower cut-off frequencies } (F_1) &= F_r - \frac{R}{4\pi L} \\
 &= 1592 - \frac{10}{4\pi \times 20 \times 10^{-3}} \\
 &= 1592 - 39.8 \\
 &= 1552 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 \text{Upper cut-off frequencies } (F_2) &= F_r + \frac{R}{4\pi L} \\
 &= 1592 + \frac{10}{4\pi \times 20 \times 10^{-3}}
 \end{aligned}$$

$$= 1592 + 39.8 \\ = 1632 \text{ Hz}$$

$$\begin{aligned} \text{Bandwidth} &= F_2 - F_1 \\ &= 1632 - 1552 \\ &= 80 \text{ Hz} \end{aligned}$$

$$\begin{aligned} \text{Power (P)} &= V \times I \times \cos\theta \\ &= 200 \times \frac{V}{R} \times 1 \\ &= 200 \times \frac{200}{10} \times 1 \\ &= 200 \times 20 \times 1 \\ P &= 4000 \text{ Watts} \end{aligned}$$

Answer:

- i) Resonance Frequency (F_r) = 1592 Hz
- ii) Q-Factor = 20
- iii) Half power frequencies:
- iv) Bandwidth = 80
- $F_1 = 1552 \text{ Hz}$ and $F_2 = 1632 \text{ Hz}$
- v) Power (P) = 4000 Watts

Example: 5

An R.L.C series circuit consists of a resistance of 10Ω an inductance of 100mH and a capacitance of $10\mu\text{F}$. If a voltage of 100V is applied across the combines find i) Resonance frequency ii) Q-factor of the circuit and iii) Bandwidth iv) Half power points v) Power.

Given Data:

| | | |
|-----------------|---------------------------------------|----------------------------|
| Connection | = Series | i) Resonance Frequency =? |
| Resistance (R) | = 10Ω | ii) Q-Factor =? |
| Inductance (L) | = $100\text{mH} = 100 \times 10^{-3}$ | iii) Bandwidth =? |
| Capacitance (C) | = $10\mu\text{F} = 10 \times 10^{-6}$ | iv) Half power frequencies |
| Voltage (V) | = 100V | v) Power consumed |

Solution:

$$\begin{aligned} \text{Resonance Frequency (F}_r\text{)} &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2 \times 3.14\sqrt{LC}} \\ &= \frac{1}{2 \times 3.14\sqrt{100 \times 10^{-3} \times 10 \times 10^{-6}}} \\ &= \frac{1}{2 \times 3.14 \times 1 \times 10^{-3}} \end{aligned}$$

$$\text{Resonance Frequency (F}_r\text{)} = 159 \text{ Hz}$$

$$\begin{aligned}
 \text{Q- Factor} &= \frac{1}{R} \sqrt{\frac{L}{C}} \\
 &= \frac{1}{10} \sqrt{\frac{100 \times 10^{-3}}{10 \times 10^{-6}}} \\
 &= \frac{1}{10} \times 100
 \end{aligned}$$

$$\text{Q- Factor} = 10$$

Half Power Frequencies:

$$\begin{aligned}
 \text{Lower cut-off frequencies } (F_1) &= F_r - \frac{R}{4\pi L} \\
 &= 159 - \frac{10}{4\pi \times 100 \times 10^{-3}} \\
 &= 159 - 7.96 \\
 &= 151 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 \text{Upper cut-off frequencies } (F_2) &= F_r + \frac{R}{4\pi L} \\
 &= 159 + \frac{10}{4\pi \times 100 \times 10^{-3}} \\
 &= 159 + 7.96 \\
 &= 167 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 \text{Bandwidth} &= F_2 - F_1 \\
 &= 167 - 151 \\
 &= 16 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 \text{Power } (P) &= V \times I \times \cos\theta \\
 &= 100 \times \frac{V}{R} \times 1 \\
 &= 100 \times \frac{100}{10} \times 1 \\
 &= 100 \times 10 \times 1
 \end{aligned}$$


$$P = 1000 \text{ Watts}$$

Answer:


- | | |
|---|--|
| i) Resonance Frequency (F_r) = 159 Hz | ii) Q- Factor = 10 |
| iii) Bandwidth = 16 Hz | iv) Half power frequencies: $F_1 = 151\text{Hz}$ and $F_2 = 167\text{Hz}$ |
| v) Power (P) = 1000 Watts | |

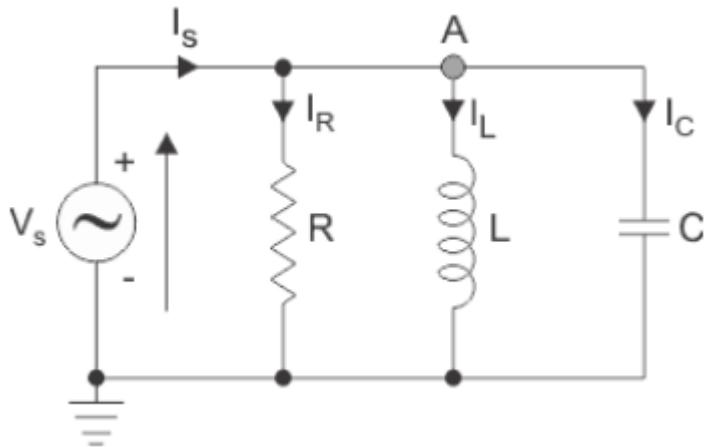4.13 PARALLEL RESONANCE:


Consider a RLC circuit in which resistor, inductor and capacitor are connected in parallel to each other. This parallel combination is supplied by voltage supply. In parallel resonance circuit, the voltage across each element remains the same and the current gets divided in each component depending upon the impedance of each component. The total current, I_s drawn from the supply is equal to the vector sum of the resistive, inductive and capacitive current.



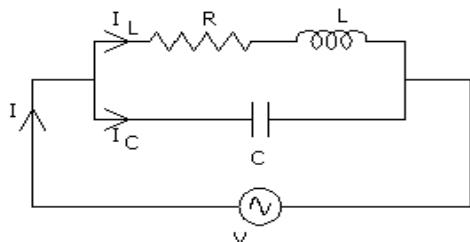Consider coil of inductance L and a low resistance R shunted across a pure capacitor C.



4.13.1 Vector diagram

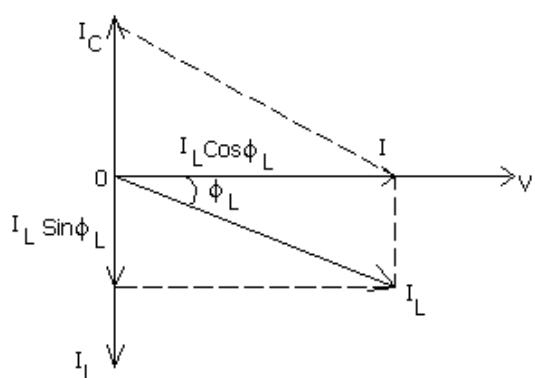

A variable frequency is applied across the circuit. At particular frequency, the reactive component of the line current becomes zero. This frequency is called *resonant frequency*.

When total current is in phase with supply voltage parallel resonance is said to occur. This is true, only if reactive component of inductive branch current is equal to capacitive branch current.

4.14 Q-factor:

At resonance, the current in the branches of the parallel circuit can be many times greater than the supply current. The factor of magnification in the parallel circuit, is called as Q factor. It is also called as the current magnification.

$$Q - \text{Factor or Current Magnification} = \frac{\text{Current in the inductive or Capacitive branch}}{\text{Current in supply at resonance}}$$

$$Q - \text{Factor} = \frac{I_C}{I}$$

$$I_C = \frac{V}{X_C} = \frac{1}{X_C} \cdot V = (2 \cdot \pi \cdot f \cdot c) \cdot V = \omega \cdot C \cdot V$$

$$I = \frac{V}{Z_0} = \frac{V}{\frac{L}{C \cdot R}} = \frac{V \cdot C \cdot R}{L}$$

$$Q - \text{Factor} = \frac{I_C}{I}$$

$$Q - \text{Factor} = \frac{\omega \cdot C \cdot V}{\frac{V \cdot C \cdot R}{L}} = \frac{\omega \cdot L}{R} = \frac{2 \cdot \pi \cdot f_o \cdot L}{R}$$

$$\text{Substitute, } f_o = \frac{1}{2 \cdot \pi \sqrt{LC}}$$

$$Q - \text{Factor} = \frac{2 \cdot \pi \cdot L}{2 \cdot \pi \sqrt{LC} \cdot R}$$

$$= \frac{1}{R} \frac{L}{\sqrt{LC}}$$

$$= \frac{1}{R} \frac{\sqrt{L} \sqrt{L}}{\sqrt{LC}}$$

$$Q - \text{Factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

4.15 Condition for Parallel Resonance:

Reactive component of inductive branch current is equal to capacitive branch current.

4.16 Resonance Frequency:

$$\text{At resonance, } I_C = I_L \sin \Phi_L$$

$$\text{We, Know that, } I_C = \frac{V}{X_C}$$

$$I_L = \frac{V}{Z_L}$$

$$\begin{aligned}
\sin \Phi_L &= \frac{X_L}{Z_L} \\
\frac{V}{X_C} &= \frac{V}{Z_L} \cdot \frac{X_L}{Z_L} \\
X_L X_C &= Z_L^2 \\
2 \cdot \pi \cdot f_r \cdot L \cdot \frac{1}{2 \cdot \pi f_r \cdot C} &= Z_L^2 \\
\frac{L}{C} &= Z_L^2 \\
Z_L^2 &= \frac{L}{C} \\
R^2 + X_L^2 &= \frac{L}{C} \\
R^2 + (2\pi f_r L)^2 &= \frac{L}{C} \\
(2\pi f_r L)^2 &= \frac{L}{C} - R^2 \\
(2\pi f_r)^2 &= \frac{1}{LC} - \frac{R^2}{L^2} \\
2\pi f_r &= \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \\
\text{Resonance Frequency: } f_r &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}
\end{aligned}$$

4.17 Impedance at Resonance:

The effective resistance of the RLC parallel circuit at resonance is called dynamic impedance or dynamic resistance.

$$\begin{aligned}
\text{At resonance, } I_r &= I_L \cos \Phi_L \\
\text{We, Know that, } I_r &= \frac{V}{Z_r} \\
I_L &= \frac{V}{Z_L} \\
\cos \Phi_L &= \frac{R}{Z_L} \\
\frac{V}{Z_r} &= \frac{V}{Z_L} \cdot \frac{R}{Z_L} \\
\frac{1}{Z_r} &= \frac{R}{Z_L^2}
\end{aligned}$$

$$\frac{1}{Z_r} = \frac{R}{L/C}$$


$$Z_r = \frac{L/C}{R}$$

$$Z_r = \frac{L}{CR}$$

The entire circuit behaves as a non-reactive resistor of L/CR ohms under resonance. The quantity L/CR ohm is often called dynamic impedance or dynamic resistance.

4.18 Graphical Representation:

Line current Vs Frequency curve

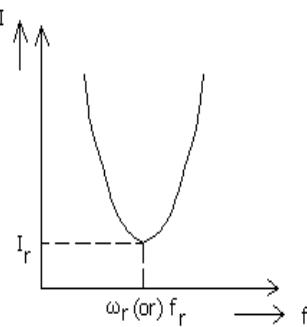



At parallel resonance, the line current I_r is minimum and is given by:

$$I_r = \frac{V}{Z_r}$$

$$\text{Where, } Z_r = \frac{L}{CR}$$

The small current is only the amount needed to supply the resistance losses in the circuit.

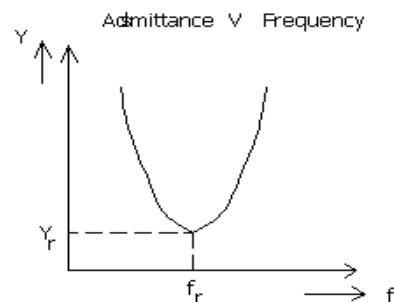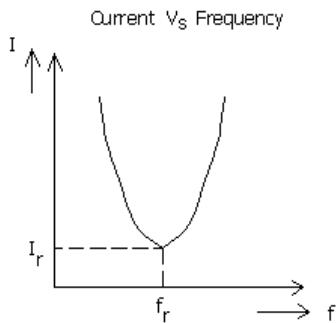4.18.1 Characteristics of Parallel Resonance:



Characteristic of Parallel Resonance

4.19 Rejector circuit:

The lowest current from the source occurs at the resonant frequency of a parallel circuit hence it is called a rejector circuit.

4.20 Properties of parallel resonance

1. At resonance the net reactance is zero.
2. At resonance the impedance is maximum
3. At resonance the current is minimum
4. At resonance the power factor of the circuit is unity
5. It magnifies current.
6. Line current is in phase with voltage

4.21 Comparison of Series and Parallel Resonant circuit:

| Criterion for comparison | Series circuit | Parallel circuit |
|----------------------------------|---------------------------|--|
| Impedance at resonance | Minimum | Maximum |
| Current at resonance | Maximum | Minimum |
| Effective impedance at resonance | R | $L/C R$ |
| Resonant frequency (f_r) | $\frac{1}{2\pi\sqrt{LC}}$ | $\frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$ |
| It magnifies | Voltage | Current |
| Power factor at resonance | 1 (unity) | 1 (unity) |
| Q-factor | $\omega L/R$ | $\omega L/R$ |
| Other name | Acceptor circuit | Rejector circuit |

4.22 Application of Resonance

1. Used in oscillator circuit to provide different frequencies.
2. Used in tuning circuit of Radio and TV to obtain the required station.

Example: 6

A coil of 10 Ohms resistance and 0.1H inductance is connected in parallel with a capacitor of 100mfd capacitance. Calculate the frequency at which the circuit will act as a non-inductive resistance of R ohm. Find also the dynamic resistance.

Given Data:

| | |
|-----------------|--|
| Connection | = Parallel Circuit |
| Resistance (R) | = 10Ω |
| Inductance (L) | = 0.1 H |
| Capacitance (C) | = $100\text{mfd} = 100 \times 10^{-6}$ |

To Find:

- i) Resonance Frequency =?
- ii) Dynamic Resistance =?

Solution:

$$\begin{aligned}
 \text{Resonance Frequency } (F_r) &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \\
 &= \frac{1}{2\pi} \sqrt{\frac{1}{0.1 \times 100 \times 10^{-6}} - \frac{10^2}{0.1^2}} \\
 &= \frac{1}{2\pi} \sqrt{100000 - 10000} \\
 &= \frac{1}{2\pi} \sqrt{90000} \\
 &= \frac{1}{2\pi} \times 300 \\
 &= 47.77 \text{ Hz}
 \end{aligned}$$

$$\text{Resonance Frequency } (F_r) = 47.77 \text{ Hz}$$

$$\begin{aligned}
 \text{Dynamic Resistance } (R_D) &= \frac{L}{CR} \\
 &= \frac{0.1}{100 \times 10^{-6} \times 10} \\
 \text{Dynamic Resistance } (R_D) &= 100 \Omega
 \end{aligned}$$

Answer:

- i) Resonance Frequency (F_r) = 47.77Hz
- ii) Dynamic Resistance (R_D) = 100Ω

Example: 7

A coil of 20 Ohms resistance and 0.2H inductance is connected in parallel with a capacitor of 100mfd capacitance. Calculate the frequency at which the circuit will act as a non-inductive resistance of R ohm. Also find the dynamic resistance.

Given Data:

| | |
|-----------------|--|
| Connection | = Parallel Circuit |
| Resistance (R) | = 20Ω |
| Inductance (L) | = 0.2 H |
| Capacitance (C) | = $100\text{mfd} = 100 \times 10^{-6}$ |

To Find:

- i) Resonance Frequency =?
- ii) Dynamic Resistance =?

Solution:

$$\begin{aligned}
 \text{Resonance Frequency } (F_r) &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \\
 &= \frac{1}{2\pi} \sqrt{\frac{1}{0.2 \times 100 \times 10^{-6}} - \frac{20^2}{0.2^2}} \\
 &= \frac{1}{2\pi} \sqrt{50000 - 10000} \\
 &= \frac{1}{2\pi} \sqrt{40000} \\
 &= \frac{1}{2\pi} \times 200
 \end{aligned}$$

$$\text{Resonance Frequency } (F_r) = 31.84 \text{ Hz}$$

$$\begin{aligned}
 \text{Dynamic Resistance } (R_D) &= \frac{L}{CR} \\
 &= \frac{0.2}{100 \times 10^{-6} \times 20}
 \end{aligned}$$

$$\text{Dynamic Resistance } (R_D) = 100 \Omega$$

Answer:

- i) Resonance Frequency (F_r) = 31.84Hz ii) Dynamic Resistance (R_D) = 100 Ω

Example: 8

A parallel circuit consists of a $2.5\mu\text{F}$ capacitor and a coil whose resistance and inductance are 15Ω and 260mH respectively. Determine (i) Resonant frequency (ii) Q-Factor of the circuit at resonance (iii) Dynamic resistance of the circuit.

Given Data:

| | |
|---------------------|--|
| Connection | = Parallel Circuit |
| Resistance (R) | = 15Ω |
| Inductance (L) | = $260\text{mH} = 260 \times 10^{-3} \text{ H}$ |
| Capacitance (C) | = $2.5 \mu\text{F} = 2.5 \times 10^{-6} \text{ F}$ |

To Find:

- i) Resonance Frequency =?
ii) Q-Factor =?
iii) Dynamic Resistance =?

Solution:

$$\begin{aligned}
 \text{Resonance Frequency } (F_r) &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \\
 &= \frac{1}{2\pi} \sqrt{\frac{1}{260 \times 10^{-3} \times 2.5 \times 10^{-6}} - \frac{15^2}{(260 \times 10^{-3})^2}} \\
 &= \frac{1}{2\pi} \sqrt{1538461.5 - 3328.4} \\
 &= \frac{1}{2\pi} \times 1239
 \end{aligned}$$

$$\text{Resonance Frequency } (F_r) = 197.3 \text{ Hz}$$

$$\begin{aligned} \text{Q- Factor} &= \frac{1}{R} \sqrt{\frac{L}{C}} \\ &= \frac{1}{15} \sqrt{\frac{260 \times 10^{-3}}{2.5 \times 10^{-6}}} \\ &= \frac{1}{15} \times 322.5 \\ \text{Q- Factor} &= 21.49 \end{aligned}$$

$$\begin{aligned} \text{Dynamic Resistance } (R_D) &= \frac{L}{CR} \\ &= \frac{260 \times 10^{-3}}{2.5 \times 10^{-6} \times 15} \end{aligned}$$

$$\text{Dynamic Resistance } (R_D) = 6933 \Omega$$

Answer:

- i) Resonance Frequency (F_r) = 197.3Hz
- ii) Q-Factor = 21.49
- iii) Dynamic Resistance (R_D) = 6933 Ω

Example: 9

A coil of resistance 12Ω and inductance 0.12 H is connected in parallel with a $60\mu\text{F}$ capacitor to a 100 Volt variable frequency supply. Calculate (i) the frequency at which the circuit will act as a non-inductive resistor (ii) the value of dynamic impedance at resonance.

Given Data:

| | |
|---------------------|--|
| Connection | = Parallel Circuit |
| Resistance (R) | = 12Ω |
| Inductance (L) | = 0.12 H |
| Capacitance (C) | = $60\text{mfd} = 60 \times 10^{-6}\text{F}$ |

To Find:

- i) Resonance Frequency =?
- ii) Dynamic Resistance =?

Solution:

$$\begin{aligned} \text{Resonance Frequency } (F_r) &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \\ &= \frac{1}{2\pi} \sqrt{\frac{1}{0.12 \times 60 \times 10^{-6}} - \frac{12^2}{0.12^2}} \\ &= \frac{1}{2\pi} \sqrt{138889 - 10000} \\ &= \frac{1}{2\pi} \times 359 \end{aligned}$$

$$\text{Resonance Frequency } (F_r) = 57.16 \text{ Hz}$$

$$\begin{aligned}\text{Dynamic Resistance } (R_D) &= \frac{L}{CR} \\ &= \frac{0.12}{60 \times 10^{-6} \times 12} \\ \text{Dynamic Resistance } (R_D) &= 167 \Omega\end{aligned}$$

Answer:

- i) Resonance Frequency (F_r) = 57.16Hz ii) Dynamic Resistance (R_D) = 167 Ω

Example: 10

An inductive circuit of resistance 2 Ohms and inductance of 0.01H is connected to a 250V, 50Hz supply. What capacitance placed in parallel will produce resonance? Find the total current taken from the supply and the current in each branch circuits.

Given Data:

| | |
|--------------------|--------------------|
| Connection | = Parallel Circuit |
| Resistance (R) | = 2 Ω |
| Inductance (L) | = 0.01 H |
| Voltage (V) | = 250V |
| Frequency (F) | = 50Hz |

To Find:

- i) Capacitance =?
ii) Total Current =?
iii) Branch Current = ?

Solution:

$$\begin{aligned}\text{Resonance Frequency } (F_r) &= \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \\ 50 &= \frac{1}{2\pi} \sqrt{\frac{1}{0.01 \times C} - \frac{2^2}{0.01^2}} \\ 50 &= \frac{1}{2\pi} \sqrt{\frac{1}{0.01 \times C} - 40000} \\ 50 \times 2\pi &= \sqrt{\frac{1}{0.01 \times C} - 40000} \\ (50 \times 2\pi)^2 &= \frac{1}{0.01 \times C} - 40000 \\ 98596 + 40000 &= \frac{1}{0.01 \times C} \\ 138596 &= \frac{1}{0.01 \times C} \\ C &= \frac{1}{0.01 \times 138596} \\ C &= 721 \mu F\end{aligned}$$

$$\begin{aligned}\text{Dynamic Resistance } (R_D) &= \frac{L}{CR} \\ &= \frac{0.01}{721 \times 10^{-6} \times 2} \\ \text{Dynamic Resistance } (R_D) &= 6.93 \Omega\end{aligned}$$

$$\text{Total Current } (I_T) = \frac{V}{R_D} = \frac{250}{6.93} = 36 \text{ Amps}$$

Branch Current:

$$\begin{aligned}\text{Inductive Reactance } (X_L) &= 2\pi FL \\ &= 2 \times 3.14 \times 50 \times 0.01 \\ X_L &= 3.14 \Omega \\ \text{Capacitive Reactance } (X_C) &= \frac{1}{2\pi fC} \\ &= \frac{1}{2 \times 3.14 \times 50 \times 721 \times 10^{-6}} \\ X_C &= 4.42 \Omega\end{aligned}$$

$$\begin{aligned}\text{Current through coil} &= \frac{V}{Z_L} \\ \text{Impedance } (Z_L) &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{2^2 + 3.14^2} \\ &= 3.72 \Omega\end{aligned}$$

$$\text{Current through coil} = \frac{V}{Z_L} = \frac{250}{3.72} = 67.2 \text{ Amps}$$

$$\begin{aligned}\text{Current through Capacitor} &= \frac{V}{X_C} \\ &= \frac{250}{4.42} \\ &= 56.56 \text{ Amps}\end{aligned}$$


Answer:

- | | |
|--|--|
| i) Capacitance (C) = 721 μF | ii) Total Current (I) = 36 Amps |
| iii) Current through coil = 67.2Amps | iv) Current through capacitor = 56.56A |

RESULT OF SIMULATION OF PROBLEMS IN UNIT IV


Problem : 2

Result of Simulation:

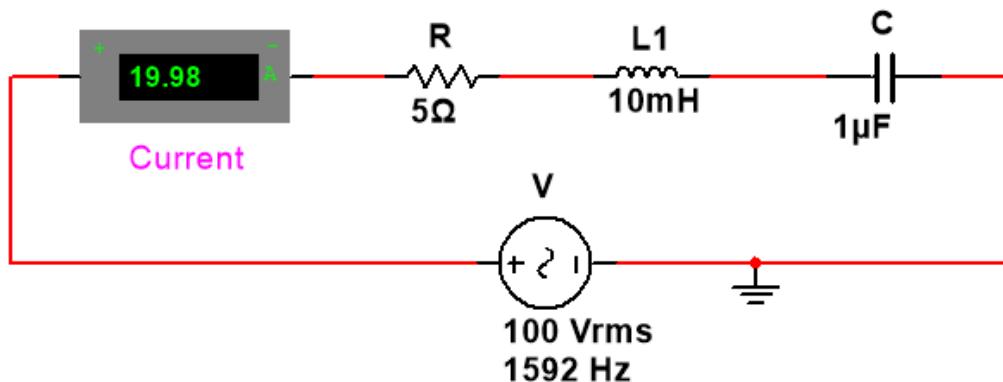


Problem : 3

Result of Simulation:

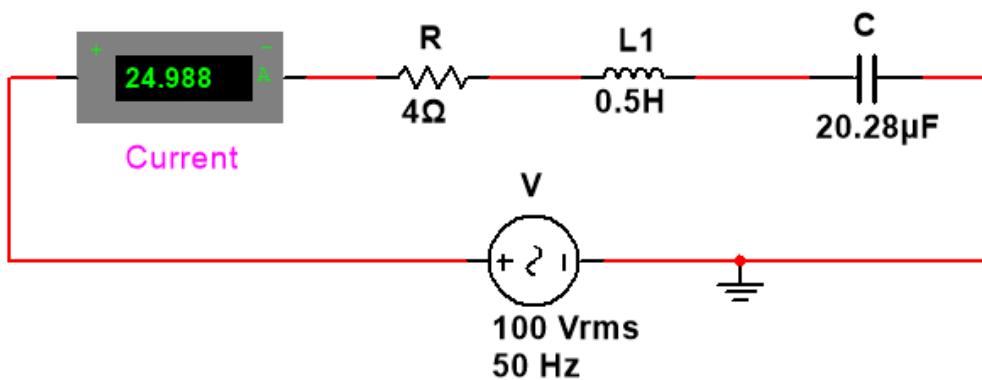


Problem : 4

Result of Simulation:

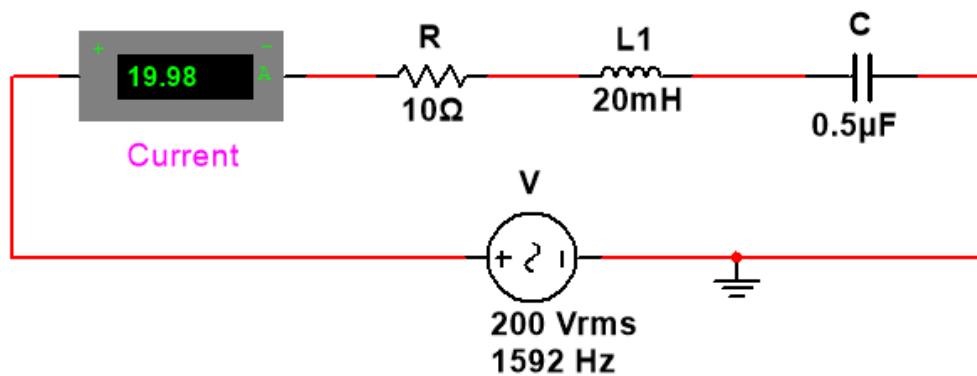

Problem : 5

Result of Simulation:

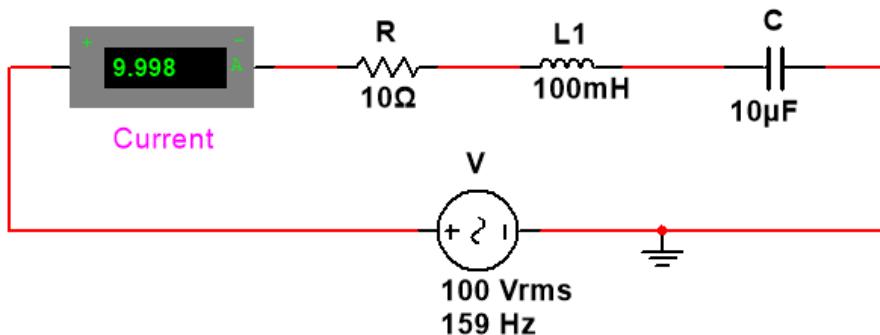

REVIEW QUESTIONS UNIT : IV RESONANT CIRCUITS

PART – A : 2 Mark Questions

1. What is resonance?
2. State the condition for resonance in R.L.C series circuit.
3. What is resonance frequency?
4. Write the expression for resonance frequency in R.L.C series circuit.
5. What is the power factor of the R.L.C series circuit at resonance?
6. What is meant by voltage magnification in R.L.C series resonance circuit?
7. Define voltage magnification factor in R.L.C series resonance circuit.
8. Why the series resonance circuit is called as acceptor circuit?
9. Define Q - factor in series resonance.
10. Write the expression for quality factor of a series RLC circuit.
11. Define half power frequency.
12. Define band width of an RLC series circuit.
13. Write the expression for band width of an RLC series circuit.
14. Define Selectivity.
15. What are half power frequencies?
16. Write the expression for lower cut off frequency.
17. Write the expression for upper cut off frequency.
18. Write the expression for resonance frequency in the circuit R.L parallel with C.
19. Draw the frequency response of an RLC parallel circuit.
20. Define Q factor in parallel resonance circuit.
21. Write the expression for quality factor of a parallel RLC circuit.
22. What is dynamic resistance? Write the expression for dynamic resistance of an RL circuit parallel with C.
23. Draw a curve showing the relationship between current and frequency in a parallel resonance circuit.
24. Draw the curve for impedance versus frequency in parallel resonance circuit.

PART – B : 3 Mark Questions

1. Draw the phasor diagram and state the condition for series resonance.
2. Derive an expression for resonance frequency in RLC series circuit.
3. Draw the frequency response of RLC series circuit.
4. Sketch the response of RLC series circuit and mark (i) Bandwidth (ii) Both cut off frequencies (iii) resonance frequency.
5. Define Selectivity and state its importance
6. Define “Q” factor in series resonant circuit and derive its expression.
7. Define half power frequencies and band width.
8. Write the expression for half power frequencies of an RLC series circuit.
9. Write the properties of series resonance.
10. Draw the frequency response of RLC parallel circuit.
11. Draw the phasor diagram and state the condition for parallel resonance.
12. Define “Q” factor in parallel resonant circuit and derive its expression.
13. Define dynamic impedance and derive its expression for parallel resonance.
14. Write the properties of parallel resonance.
15. A circuit has the resonant frequency of 60Hz and lower half power frequency of 40 Hz. What is the band width?
16. A coil having an inductance of 0.5mH and resistance 10Ω is connected in series with $10\mu F$ capacitor across a 200V AC supply. Calculate the resonance frequency of the circuit.
17. A coil having an inductance of 50mH and resistance 10Ω is connected in series with $25\mu F$ capacitor across a 200V AC supply. Calculate the resonance frequency of the circuit.
18. A coil having an inductance of 5H and resistance 90Ω is connected in series with $100\mu F$ capacitor across a 10V AC supply. Calculate the Q factor.
19. An RLC series circuit consists of Resistance of 16Ω , an inductance of 5mH and capacitance of $2 \mu F$. Calculate the quality factor.
20. Parallel circuit consists of a coil of 50mH and $0.01\mu F$ capacitor are connected across a 100V AC supply. Calculate the resonance frequency of the circuit.

PART – C : 10 Mark Questions

1. What is resonance frequency. Derive the expression to find the resonance frequency in series RLC circuit.
2. Compare series and parallel resonance.
3. Define the following terms:
 - (i) Q – factor (ii) selectivity (iii) half power frequency (iv) band width.
4. Derive the expression to find the resonance frequency in parallel RLC circuit.
5. Define quality factor. Derive the expression to find the quality factor in parallel resonance circuit.
6. A series RLC circuit consists of $R=5\Omega$, $L=40mH$ and $C = 1\mu F$. Calculate the Resonance frequency, Q factor, Bandwidth and half power frequencies.

7. A series RLC circuit consists of $R=100\Omega$, $L=10mH$ and $C = 1\mu F$ is connected to a 20V a.c supply. Find the the Resonance frequency, Q factor, Bandwidth and half power frequencies.
8. An inductive coil having a resistance of 20Ω and an inductance of $0.02H$ is connected in series with $0.01\mu F$ capacitor. Calculate (q) Q –Factor (b) Resonant frequency and (c) Bandwidth.
9. A series RLC circuit has an impedance of 40Ω at a frequency of 200rad/sec . When the circuit is made to resonate by connecting a 10V source of variable frequency the current at resonance is $0.5A$ and the quality factor at resonance is 10. Determine the circuit parameters.
10. A series circuit consists of a 10Ω resistor, a 30 mH inductor and a $1 \mu F$ capacitor, and is supplied from a 10V variable-frequency source. Find the frequency for which the voltage developed across the capacitor is a maximum and calculate the magnitude of this voltage.
11. A coil of 5Ω resistance and $15mH$ inductance is connected in parallel with a capacitor of $160 \mu F$. Calculate the frequency at which resonance occurs. Also calculate the dynamic impedance of the circuit.
12. A coil of $1 k\Omega$ resistance and $0.15 H$ inductance is connected in parallel with a variable capacitor across a $2.0V$, 10 kHz a.c. supply. Calculate:(a) the capacitance of the capacitor when the supply current is minimum; (b) the effective impedance Z_r of the network at resonance; (c) the supply current.
13. A coil of resistance 1Ω and inductance $0.12 H$ is connected in parallel with a $60\mu F$ capacitor to a $100V$ variable-frequency supply. Calculate the frequency at which the circuit will behave as a non-reactive resistor, and also the value of the dynamic impedance.

UNIT V – THREE PHASE CIRCUITS

Syllabus:

Three phase systems-phase sequence – necessity of three phase system – concept of balanced and unbalanced load - balanced star & delta connected loads – relation between line and phase voltages and currents – phasor diagram – three phase power and power factor measurement by single wattmeter and two wattmeter methods – Problems in all above topics.

5.1 Three Phase Systems:

In general, generation, transmission and distribution of electrical energy are in three phase. Three phase system can be viewed as the combination of three single phase systems with a phase difference of 120° between each winding. Hence, a three phase generating system is formed by three separate windings with 120° phase difference between them. As the windings are made to rotate in a common magnetic field in a three phase generator, three voltages of the same magnitude and frequency but 120° phase difference between each other are produced. The convention adopted to identify each of the phase voltages is: R-red, Y-yellow, and B-blue.

Consider three coils RR_1 , YY_1 and BB_1 placed in a magnetic field of maximum value of flux Φ_m Weber is shown in figure (i). Let all the coils rotate in the anticlockwise direction at an angular velocity ω .

Fig. (i) Generation of three phase emf


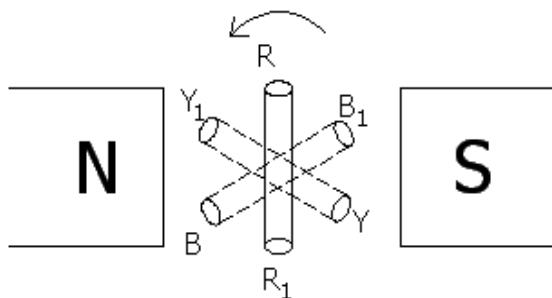


Fig. (ii) waveform of induced emf

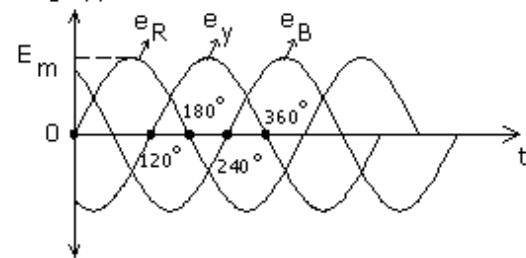

According to Faradays law of electromagnetic induction, emfs are induced in the coils RR_1 , YY_1 and BB_1 . The induced emf in coil YY_1 lags behind the induced emf in coil RR_1 by 120° and the induced emf in coil BB_1 lags behind that in coil by 240° .

All the three induced emfs have the same amplitude, same period and frequency. Thus, the above sets of voltages are called three phase-balanced system of voltages. The waveforms of the induced voltages are shown in figure.

5.1.1 Expressions for Voltage and Current in a three phase system:

$$E_R = E_m \sin \omega t$$

$$E_Y = E_m \sin(\omega t - 120^\circ)$$

$$E_B = E_m \sin(\omega t - 240^\circ)$$

5.1.1 Expressions for Voltage and Current in a three phase system:

$$I_R = I_m \sin \omega t$$

$$I_Y = I_m \sin(\omega t - 120^\circ)$$

$$I_B = I_m \sin(\omega t - 240^\circ)$$

5.2 Necessity of Three Phase system:

For resistive loads (Lamps and Heater etc.,) single phase supply works satisfactorily. However, when a.c motors were developed, it was found that the single phase a.c supply did not work properly as it was not able to produce the starting torque. Hence three phase system is necessary to power large motors and other heavy loads. A three-phase system is usually more economical than an equivalent single-phase at the same line to ground voltage because it uses less conductor material to transmit three phase electrical power.


5.2.1 Advantages of three phase system:

The three phase system has the following advantages compared to a single phase system:

- i) The amount of copper or aluminium wires required to transfer the given amount of power is minimum in a three phase system than that is required in a single phase system.
- ii) A 3 phase machine gives more output compared to a single phase machine of the same size.
- iii) Three phase motors have uniform torque whereas most of the single phase motors have pulsating torque.
- iv) A three phase motor produces more torque as compared to a single phase motor.
- v) Domestic power and industrial or commercial power can be supplied from the same source.
- vi) Three phase motors are self-starting whereas single phase induction motors are not.
- vii) In three phase system has better voltage regulation.
- viii) Three phase machines have better power factor and efficiency.
- ix) Generation, transmission and utilisation of power is more economical in three phase systems compared to single phase system.
- x) In a three phase system power never falls to zero.

5.3 Terms and Definition:

5.3.1 Phasor Representation:

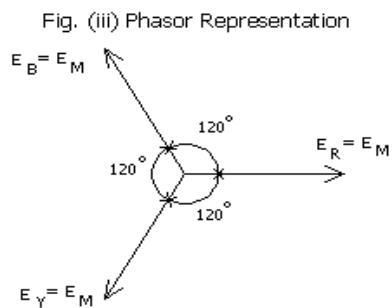


Let the emf induced in R phase, E_R be taken as reference. E_Y lags E_R by 120° and E_B lags E_R by 240° . The three phasors are represented in figure (iii).

5.3.2 Phase sequence:

In three phase system the order in which the three phase emfs or currents attain their maximum value is called Phase Sequence. The three phases are generally represented as R (Red), Y (Yellow) and B (Blue).

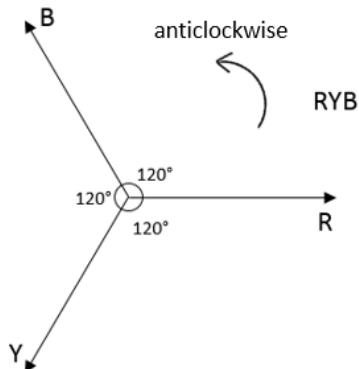
5.3.3 Positive sequence:

If the phase sequence is given as RYB then the convention is R phase reaches its maximum value first, Y phase follows 'R' and 'B' phase follows Y in reaching the maximum value. The RYB sequence in the anticlockwise direction defines the positive sequence.



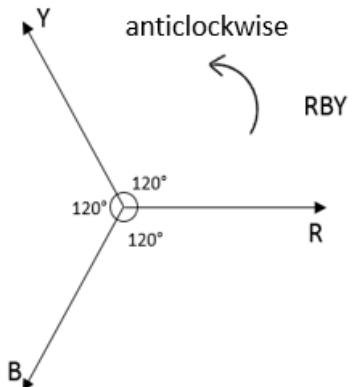
5.3.4 Negative sequence:

A three-phase system in which the voltages and currents in each of the three phases reach their maximum values in the reverse order to conventional phase sequence, ie R, B, Y as opposed to R, Y, B is called as negative sequence.



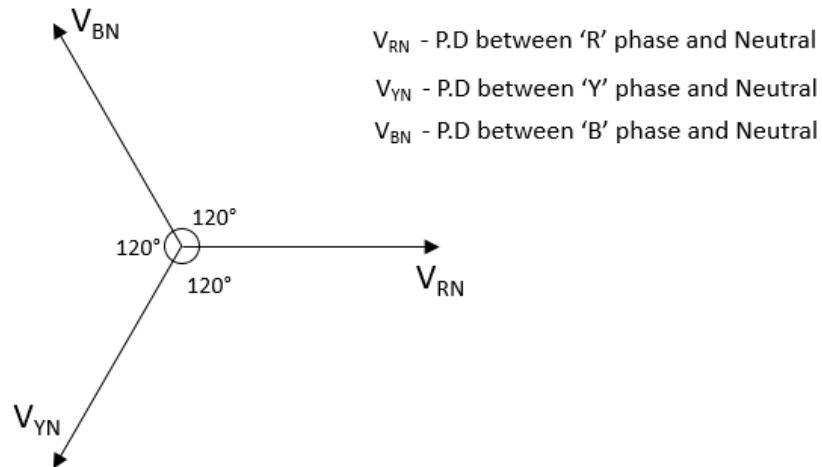5.3.5 Phase voltage:

The voltage between one of the phase terminal and the neutral terminal is known as phase voltage and is represented by V_{ph} .




V_{RN} , V_{YN} and V_{BN} are the phase voltages.

5.3.6 Line voltage:

A line voltage is the phasor difference between the appropriate pair of phase voltage. Thus V_{RY} is the phasor difference between V_{RN} and V_{YN} .

(or)

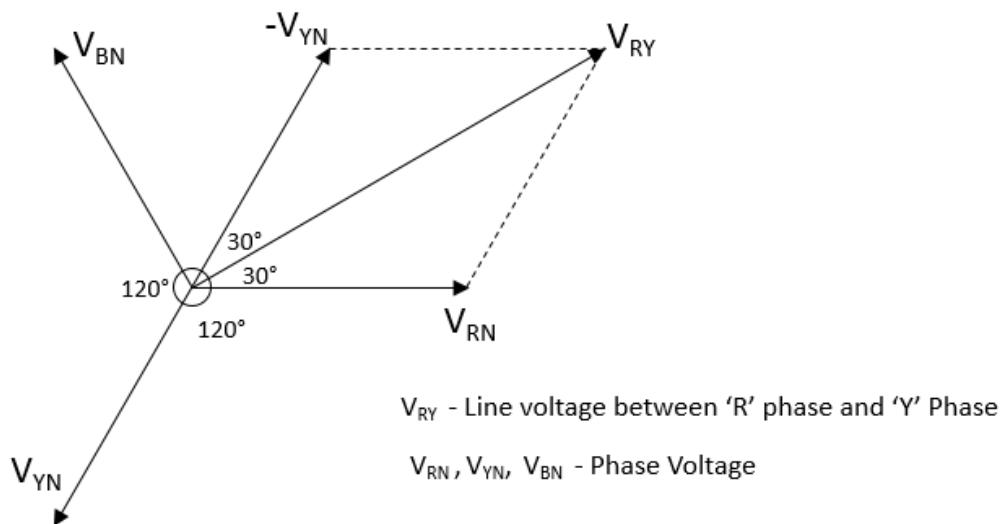The voltage between any two phase terminals of a three phase system is known as line voltage and is represented by V_L .



V_{RY} - Line voltage between 'R' phase and 'Y' Phase

V_{RN} , V_{YN} , V_{BN} - Phase Voltage

5.3.7 Phase current:

The current flowing through any one of the phase windings of the system is called phase current and is denoted by I_{ph}

5.3.8 Line current:

Line current means the current flowing through the AC supply lines and it is denoted by I_L

5.4 Concept of balanced and unbalanced load:

5.4.1 Balanced load:

The balanced load is a load in which each phase have identical impedances. i.e each impedance has the same magnitude and phase angle. Hence each impedances draws equal current and power factor.


5.4.2 Unbalanced load:

The unbalanced load is a load in which each phase have unequal impedances. i.e each impedance has the different magnitude and phase angle. Hence each impedances draws unequal current and power factor.

5.5 Methods of three phase connection:


In a three phase alternator, there are three independent phase windings or coils. Each phase or coil has two terminals, viz start and finish. The coil ends are interconnected to form a star (Y) or delta (Δ) connected three phase system.

5.5.1 Star or Why (Y) connection:

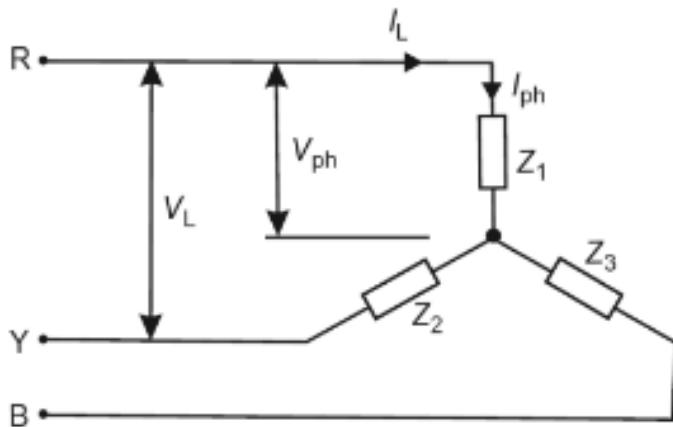

In star connection, similar ends of the three phase windings are jointed together within the alternator and three lines are run from the other free ends as shown in fig. The common terminal so formed is referred as Neutral point (N) or Neutral terminal. The terminals R, Y and B are called the line terminals. The voltage between any line and neutral point is called the phase voltage (V_{RN} , V_{YN} and V_{BN}), while the voltage between any two lines is called line voltage (V_{RY} , V_{YB} and V_{BR}). The current flowing through the phases are called the phase currents, while those flowing in the lines are called the line currents.


5.5.2 Delta (Δ) connection:

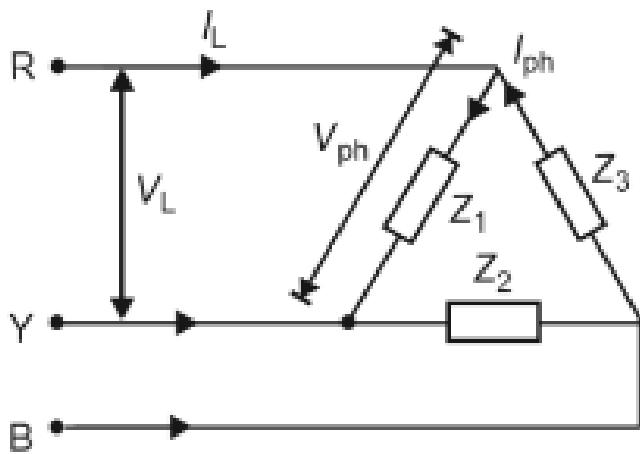

If the start end of one winding is connected to the finish end of the next, and so on until all three windings are interconnected, the result is the delta or mesh connection. Hence in delta connection, dissimilar ends of the phases are jointed to each other to form a closed mesh. Here there is no common terminal. Hence only three line voltages (V_{RY} , V_{YB} and V_{BR}) are available.

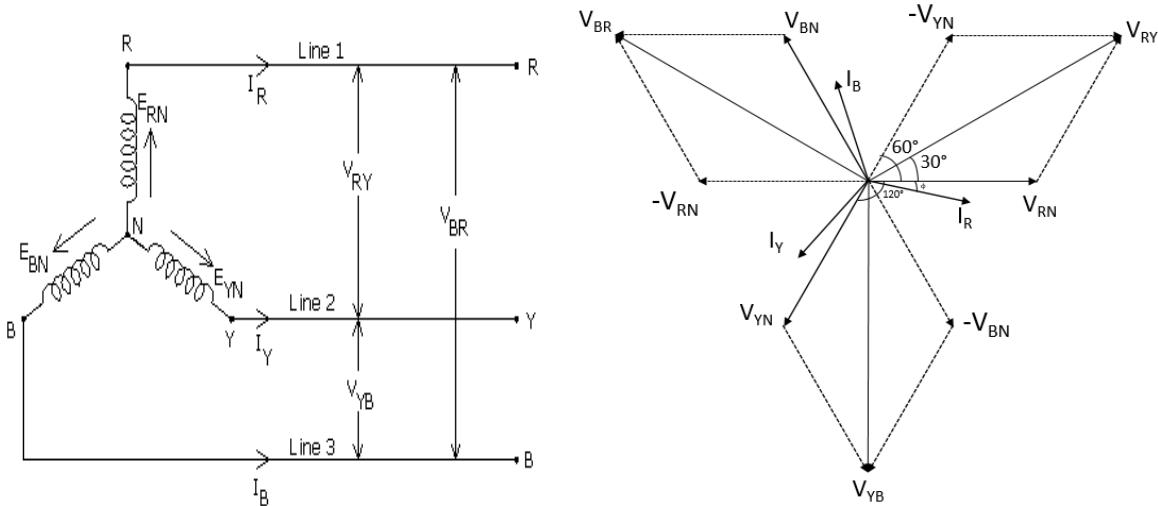5.6 Relationship between line current and phase current, line voltage and phase voltage in a star connected system.

In star connection, the three phases are joined together to form a common junction N. N is the star point or neutral point. When three phases supply feeds a balanced load, the current in three phase conductors will be equal in magnitude and displaced 120° from each other.



Phasor Diagram

Line Voltage and Phase Voltage:

The potential difference between any two line terminals is the phasor difference between the potentials of these terminals w.r.t neutral point.

$$V_{RN} = V_{YN} = V_{BN} = V_{Ph} \quad ; \text{Phase Voltage}$$

$$V_{RY} = V_{YB} = V_{BR} = V_L \quad ; \text{Line Voltage}$$

$$\text{P.D between lines R and Y: } V_{RY} = V_{RN} + V_{NY} = V_{RN} - V_{YN}$$

$$\text{P.D between lines Y and B: } V_{YB} = V_{YN} + V_{NB} = V_{YN} - V_{BN}$$

$$\text{P.D between lines B and R: } V_{BR} = V_{BN} + V_{NR} = V_{BN} - V_{RN}$$

$$\text{From Phasor Diagram: } V_{RY} = V_{RN} - V_{YN}$$

$$V_{RY} = 2 \times V_{ph} \times \cos 30^\circ$$

$$V_{RY} = 2 \times V_{ph} \times \frac{\sqrt{3}}{2}$$

$$V_{RY} = \sqrt{3} \times V_{ph}$$

Similarly

$$V_{YB} = V_{YN} - V_{BN} = \sqrt{3} \times V_{ph}$$

$$V_{BR} = V_{BN} - V_{RN} = \sqrt{3} \times V_{ph}$$

$$V_{RY} = V_{YB} = V_{BR} = V_L \quad ; \text{Line Voltage}$$

Hence in star connection, $V_L = \sqrt{3} \times V_{ph}$

Line Current Vs Phase Current:

It is seen from Fig. the line current in each line is the same as the current in the phase winding to which the line is connected.

Current in line 1 = I_R

Current in line 2 = I_Y

Current in line 3 = I_B

Since $I_R = I_Y = I_B = I_{ph}$; Phase Current

Line Current = Phase Current

$$I_L = I_{ph}$$

Power:

Total Power = Sum of three phase powers

Total power = 3 x Phase Power

$$P = 3 \times V_{ph} I_{ph} \cos \varphi$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} \quad \text{and} \quad V_L = \sqrt{3} \times V_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} \quad \text{and} \quad I_L = I_{ph}$$

$$\text{Total Power} = P = 3 \times \frac{V_L}{\sqrt{3}} \times I_L \times \cos \varphi$$

$$P = \sqrt{3} \times V_L \times I_L \times \cos \varphi$$

5.7 Relationship between line current and phase current, line voltage and phase voltage in a delta connected system.

In delta connection, the three windings are joined in series to form a closed mesh as shown in fig. If the system is balanced then sum of the three voltages around the closed mesh is zero. It has no common point.

Line Voltage and Phase Voltage:



In delta connection, Line voltage is equal to phase voltage.

$V_{RY} = V_{YB} = V_{BR} = V_L = \text{Line Voltage}$

$V_{RN} = V_{YN} = V_{BN} = V_{ph} = \text{Phase Voltage}$

Line Voltage = Phase Voltage

$$V_L = V_{ph}$$

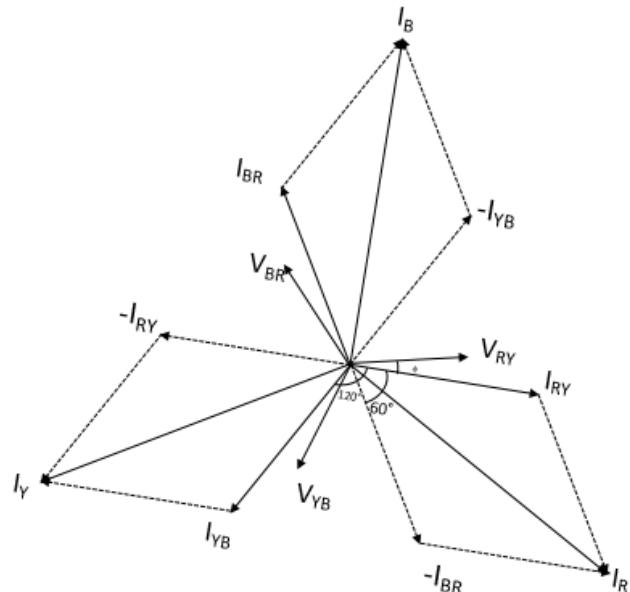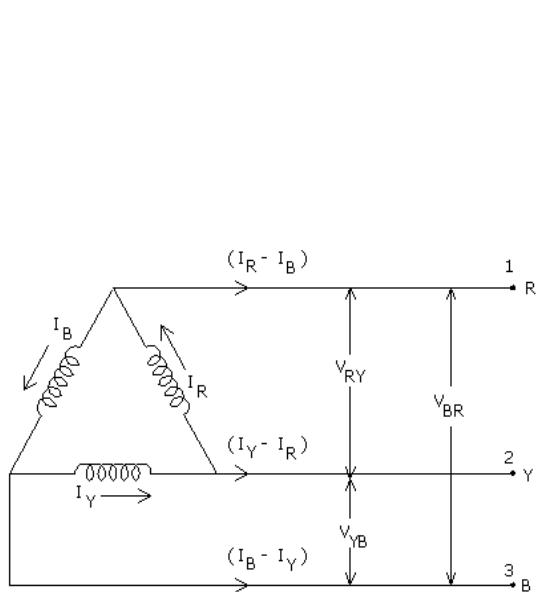

Line Current and Phase Current:

The current in any line is equal to the phasor difference between the potentials of currents in the two phases attached to that lines.

$$\text{Current in line 1: } I_R = I_{RY} - I_{BR}$$

$$\text{Current in line 2: } I_Y = I_{YB} - I_{RY}$$

$$\text{Current in line 3: } I_B = I_{BR} - I_{YR}$$

From Phasor Diagram:

$$I_R = I_{RY} - I_{BR}$$

$$I_R = 2 \times I_{ph} \times \cos 30^\circ$$

$$I_R = 2 \times I_{ph} \times \frac{\sqrt{3}}{2}$$

$$I_R = \sqrt{3} \times I_{ph}$$

Similarly

$$I_Y = I_{YB} - I_{RY} = \sqrt{3} \times I_{ph}$$

$$I_B = I_{BR} - I_{YR} = \sqrt{3} \times I_{ph}$$

$$I_R = I_Y = I_B = I_L ; \text{Line Current}$$

$$\text{Hence in delta connection, } I_L = \sqrt{3} \times I_{ph}$$

Power:

Total Power = Sum of three phase powers

Total power = 3 x Phase Power

$$P = 3 \times V_{ph} I_{ph} \cos \varphi$$

$$\text{Substitute } I_{ph} = \frac{I_L}{\sqrt{3}} \quad \text{and } V_{ph} = V_L$$

$$\text{Total Power} = P = 3 \times V_L \times \frac{I_L}{\sqrt{3}} \times \cos \varphi$$

$$P = \sqrt{3} \times V_L \times I_L \times \cos \varphi$$

5.71 Advantages of star connection:

- i) In star connection, phase voltage $V_{ph}=V_l/\sqrt{3}$. Hence a star connected alternator will require less number of turns than a Δ - connected alternator for the same line voltage.
- ii) For the same line voltage, a star connected alternator requires less insulation than a delta connected alternator
- iii) In star connection, we can get 3-phase 4-wire system. This permits to use two voltages viz., phase voltages as well as line voltages.
- iv) Single phase loads can be connected between any one line and neutral wire while the 3-phase loads can be put across the three lines. Such flexibility is not available in Δ - connection.
- v) In star connection, the neutral point can be earthed.

5.72 Advantages of delta connection:

1. Most of 3- phase induction motors are delta connected.
2. Delta connection is most suitable for rotary convertors.
3. High Reliability

5.73 Floating neutral point:

The isolated neutral (star) point of a load is called floating neutral point.

5.8 Power Measurement by single wattmeter method:

This method can be only used for balanced three phase load. Wattmeter must be connected in such a way that its current coil must carry I_{ph} and its voltage coil must be V_{ph} . When the load is balanced, total power can be calculated as :


$$P = 3 V_{ph} I_{ph} \cos \phi$$

$$P = 3 \times \text{Wattmeter reading}$$

Hence one wattmeter is to be used to measure single phase power and then reading is to be multiplied by 3.

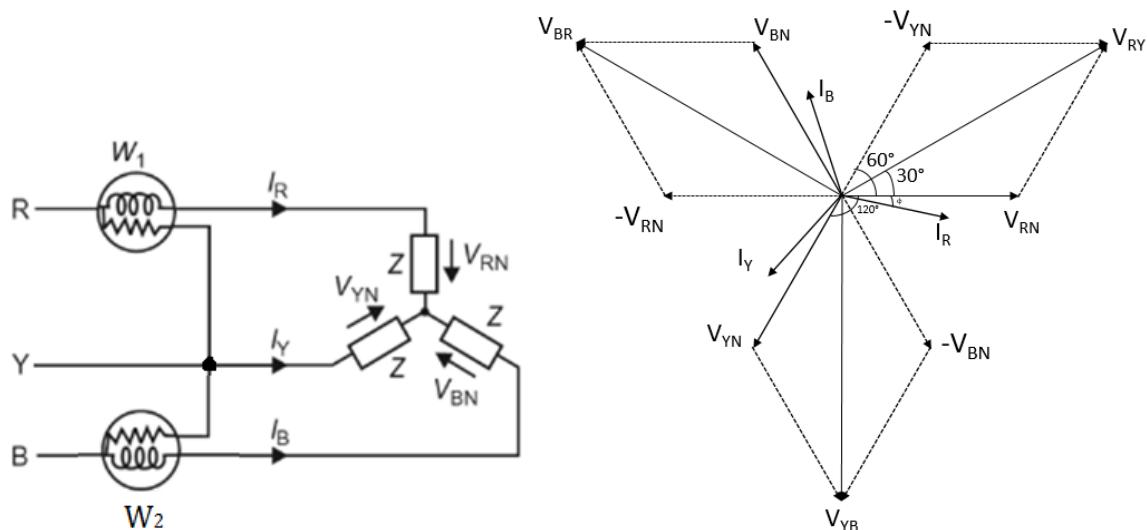5.9 Power Measurement by two wattmeter method:

The connection diagram (a) and phasor diagram (b) for a three phase balanced load is shown in figure. The three phase voltages V_{RN} , V_{YN} and V_{BN} displaced by an angle of 120° are shown in phasor diagram. The phase currents lags behind their respective phase voltage by an angle Φ .



Reading of Wattmeter W_1 :

Current through current coil of W_1 = I_R

$$\text{P.D across potential coil of } W_1 = V_{RY}$$

$$V_{RY} = V_{RN} - V_{YN}$$

From phasor diagram, phase angle between V_{RY} and I_R is $(30^\circ + \Phi)$

$$W_1 = V_{RY} \cdot I_R \cdot \cos(30^\circ + \Phi) \dots\dots (1)$$

Reading of Wattmeter W_2 :

$$\text{Current through current coil of } W_2 = I_B$$

$$\text{P.D across potential coil of } W_2 = V_{BY}$$

$$V_{BY} = V_{BN} - V_{YN}$$

From phasor diagram, phase angle between V_{BY} and I_B is $(30^\circ - \Phi)$

$$W_2 = V_{BY} \cdot I_B \cdot \cos(30^\circ - \Phi) \dots\dots (2)$$

Since the load is balanced

$$V_{RY} = V_{BY} = \text{Line Voltage } (V_L) \quad \text{and}$$

$$I_R = I_B = \text{Line Current } (I_L)$$

From equ. (1) and (2)

$$W_1 = V_L \cdot I_L \cdot \cos(30^\circ + \Phi)$$

$$W_2 = V_L \cdot I_L \cdot \cos(30^\circ - \Phi)$$

$$W_1 + W_2 = V_L \cdot I_L \cdot \cos(30^\circ + \Phi) + V_L \cdot I_L \cdot \cos(30^\circ - \Phi)$$

$$W_1 + W_2 = V_L \cdot I_L \cdot (2 \cos 30^\circ + \cos \Phi)$$

$$W_1 + W_2 = V_L \cdot I_L \cdot \left(2 \times \frac{\sqrt{3}}{2} \times \cos \Phi\right)$$

$$W_1 + W_2 = \sqrt{3} V_L \cdot I_L \cdot \cos \Phi$$

$W_1 + W_2 = \text{Total Power in the 3 phase load.}$

Now

$$W_2 - W_1 = [V_L \cdot I_L \cos(30^\circ - \Phi) - V_L \cdot I_L \cos(30^\circ + \Phi)]$$

$$W_2 - W_1 = V_L \cdot I_L [\cos 30^\circ \cos \Phi + \sin 30^\circ \sin \Phi] -$$

$$(\cos 30^\circ \cos \Phi - \sin 30^\circ \sin \Phi)]$$

$$W_2 - W_1 = V_L \cdot I_L \cdot (2 \cdot \sin 30^\circ \sin \Phi)$$

$$W_2 - W_1 = V_L \cdot I_L \cdot \sin \Phi$$

Power Factor:

$$W_2 + W_1 = \sqrt{3} V_L \cdot I_L \cdot \cos \Phi$$

$$W_2 - W_1 = V_L \cdot I_L \cdot \sin \Phi$$

$$\frac{W_2 - W_1}{W_2 + W_1} = \frac{V_L I_L \sin \Phi}{\sqrt{3} V_L I_L \cos \Phi}$$

$$\frac{W_2 - W_1}{W_2 + W_1} = \frac{\tan \Phi}{\sqrt{3}}$$

$$\tan \Phi = \sqrt{3} \left\{ \frac{W_2 - W_1}{W_2 + W_1} \right\}$$

$$\Phi = \tan^{-1} \sqrt{3} \left\{ \frac{W_2 - W_1}{W_2 + W_1} \right\}$$


Advantages of two wattmeter method:

- i) Access to the star point is not necessary
- ii) The power dissipated in both balanced and unbalanced load is obtained, without any modification to the connections.
- iii) For balanced loads, the power factor can be determined.

5.10 Effects of Load P.F on Wattmeter Readings:

| Φ | 0° | 60° | More than 60° | 90° |
|-------------|---|-------------------------------------|---|--------------------------------------|
| $\cos \Phi$ | 1 | 0.5 | < 0.5 | 0 |
| W_2 | Positive | Positive | Positive | Positive |
| W_1 | Positive | 0 | Negative | Negative |
| Conclusion | $W_1 = W_2$ Total Power $= W_1 + W_2$ | $W_1 = 0$ Total Power $= W_2$ | $W_2 > W_1$ Total Power $= W_2 - W_1$ | $W_2 = -W_1$ Total Power $= 0$ |

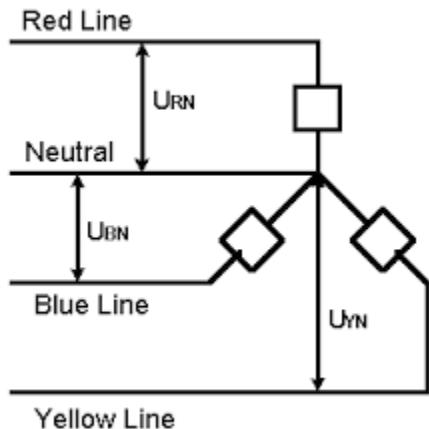5.11 3 phase, 4 wire star connected system:



The three phase loads are directly connected across the three lines while single phase loads are connected between one of the lines and the neutral wire. Three phase loads are mostly balanced and the single phase loads introduces the imbalance or unbalance.

If the load is unbalanced, then the three lines currents will be unequal. Consequently the line currents I_R , I_Y and I_B will be different in magnitude and displaced from one another by unequal angles. In this case the neutral has to carry the resulting out-of-balance current. This current is simply obtained by calculating the phasor sum of the line currents.

$$\text{Current in neutral wire, } I_N = I_R + I_Y + I_B$$

Example: 1

A balanced delta connected load of $(8+j6)$ ohms per phase is connected to a 3 phase 230V supply. Find the line current, power factor, power and total volt ampere.

Given Data:

| | | |
|-----------------------------------|---|------------|
| Connection | = | DELTA |
| Resistance (R_{ph}) | = | 8Ω |
| Inductive Reactance (X_{Lph}) | = | 6Ω |
| Line Voltage | = | 230 Volts |

To Find:

| |
|------------------------------------|
| Line Current (I_L) = ? |
| Power Factor ($\cos \theta$) = ? |
| Power (P) = ? |
| Volt-Ampere (VA) = ? |

Solution:

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned}\text{Impedance } (Z_{ph}) &= \sqrt{8^2 + 6^2} \\ &= \sqrt{64 + 36} \\ &= \sqrt{100}\end{aligned}$$

$$\text{Impedance } (Z_{ph}) = 10\Omega$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}}$$

$$\text{Phase Voltage } (V_{ph}) = V_L = 230V \quad [\because \text{Delta Connection}]$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}} = \frac{230}{10} = 23A$$

$$I_{ph} = 23A$$

$$\begin{aligned}\text{Line Current } (I_L) &= \sqrt{3} I_{ph} \\ &= \sqrt{3} \times 23 = 39.84 A\end{aligned}$$

$$I_L = 39.84 A$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{8}{10} = 0.8$$

$$\begin{aligned}\text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 230 \times 39.84 \times 0.8 \\ &= 12696.5 \text{ Watts}\end{aligned}$$

$$\begin{aligned}\text{Volt -Ampere (VA)} &= \sqrt{3} V_L I_L \\ &= \sqrt{3} \times 230 \times 39.84 \\ &= 15870.6 \text{ VA}\end{aligned}$$

Example: 2

Each branch of a delta connected load has an impedance of $(16+j12) \Omega$. Calculate the line current and total power when connected to a 400V, 3 phase 50Hz mains.

Given Data:

| | | |
|-----------------------------------|---|-------------|
| Connection | = | DELTA |
| Resistance (R_{ph}) | = | 16Ω |
| Inductive Reactance (X_{Lph}) | = | 12Ω |
| Line Voltage (V_L) | = | 400 Volts |
| Frequency (F) | = | 50Hz |

To Find:

| |
|----------------------------|
| Line Current (I_L) = ? |
| Power (P) = ? |

Solution:

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned}\text{Impedance } (Z_{ph}) &= \sqrt{16^2 + 12^2} \\ &= \sqrt{256 + 144} \\ &= \sqrt{400}\end{aligned}$$

$$\text{Impedance } (Z_{ph}) = 20\Omega$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}}$$

$$\text{Phase Voltage } (V_{ph}) = V_L = 400V \quad [\because \text{Delta Connection}]$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}} = \frac{400}{20} = 20A$$

$$I_{ph} = 20A$$

$$\begin{aligned}\text{Line Current } (I_L) &= \sqrt{3} I_{ph} \\ &= \sqrt{3} \times 20 = 34.64 A\end{aligned}$$

$$I_L = 34.64 A$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{16}{20} = 0.8$$

$$\begin{aligned}\text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 400 \times 34.64 \times 0.8 \\ &= 19198.8 \text{ Watts}\end{aligned}$$

Answer:

$$\text{i) Line Current } (I_L) = 34.64 A \quad \text{ii) Power} = 19198.8 \text{ Watts}$$

Example: 3

A balanced three phase load consists of three coils each of resistance 6Ω and an inductive reactance of 8Ω . Determine the line current and power absorbed when the coils are delta connected across a 400V 3 phase supply.

Given Data:

| | To Find: |
|-----------------------------------|-------------------------------|
| Connection | i) Line Current (I_L) = ? |
| Resistance (R_{ph}) | ii) Power (P) = ? |
| Inductive Reactance (X_{Lph}) | |
| Line Voltage (V_L) | |

Solution:

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned} \text{Impedance } (Z_{ph}) &= \sqrt{6^2 + 8^2} \\ &= \sqrt{36 + 64} \\ &= \sqrt{100} \end{aligned}$$

$$\text{Impedance } (Z_{ph}) = 10\Omega$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}}$$

$$\text{Phase Voltage } (V_{ph}) = V_L = 400V \quad [\because \text{Delta Connection}]$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}} = \frac{400}{10} = 40A$$

$$I_{ph} = 40A$$

$$\begin{aligned} \text{Line Current } (I_L) &= \sqrt{3} I_{ph} \\ &= \sqrt{3} \times 40 = 69.28 A \end{aligned}$$

$$I_L = 69.28 A$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{6}{10} = 0.6$$

$$\begin{aligned} \text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 400 \times 69.28 \times 0.6 \\ &= 28798.3 \text{ Watts} \end{aligned}$$

Answer:

$$\text{i) Line Current } (I_L) = 69.28 A \quad \text{ii) Power} = 28798.3 \text{ Watts}$$

Example: 4

A load in each branch of delta connected balanced 3 phase circuit consists of an inductance of 0.0318H in series with a resistance of 10 Ohms. The line voltage is 400V at 50Hz. Calculate (i) the line current and (ii) the total power in the circuit

Given Data:

| | | <u>To Find:</u> |
|-------------------------|---------------|-------------------------------|
| Connection | = DELTA | i) Line Current (I_L) = ? |
| Resistance (R_{ph}) | = 10Ω | ii) Power (P) = ? |
| Inductance (L_{ph}) | = 0.0318 H | |
| Line Voltage (V_L) | = 400 Volts | |
| Frequency (F) | = 50 Hz | |

Solution:

$$\begin{aligned} \text{Inductive Reactance } (X_{Lph}) &= 2\pi f L ; \Omega \\ &= 2 \times 3.14 \times 50 \times 0.0318 ; \Omega \\ X_{Lph} &= 9.98 \Omega = 10 \Omega \end{aligned}$$

$$\begin{aligned} \text{Impedance } (Z_{ph}) &= \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega \\ \text{Impedance } (Z_{ph}) &= \sqrt{10^2 + 10^2} \\ &= \sqrt{100 + 100} = \sqrt{200} \\ \text{Impedance } (Z_{ph}) &= 14.14 \Omega \end{aligned}$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}}$$

$$\text{Phase Voltage } (V_{ph}) = V_L = 400V \quad [\because \text{Delta Connection}]$$

$$\begin{aligned} \text{Phase Current } (I_{ph}) &= \frac{V_{ph}}{Z_{ph}} = \frac{400}{14.14} = 28.28A \\ I_{ph} &= 28.28A \end{aligned}$$

$$\begin{aligned} \text{Line Current } (I_L) &= \sqrt{3} I_{ph} \\ &= \sqrt{3} \times 28.28 = 48.98 A \\ I_L &= 48.98 A \end{aligned}$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{10}{14.14} = 0.7$$

$$\begin{aligned} \text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 400 \times 48.98 \times 0.7 \\ &= 23753.3 \text{ Watts} \end{aligned}$$

Answer: i) Line Current (I_L) = 48.98 A ii) Power = 23753.3 Watts

Example: 5

Three similar coils each having a resistance of 15Ω and inductance of 0.5 H are connected in delta to a three phase $415V$, 50Hz supply. Find the i) Line Current ii) P.F and iii) Power.

Given Data:

| | | |
|-----------------------------------|---|---------------------|
| Connection | = | DELTA |
| Resistance (R_{ph}) | = | 15Ω |
| Inductive Reactance (X_{Lph}) | = | 0.5 H |
| Line Voltage (V_L) | = | 415 Volts |
| Frequency (F) | = | 50 Hz |

To Find:

- i) Line Current (I_L) = ?
- ii) Power Factor ($\cos \theta$) = ?
- iii) Power (P) = ?

Solution:

$$\begin{aligned}\text{Inductive Reactance } (X_{Lph}) &= 2\pi f L ; \Omega \\ &= 2 \times 3.14 \times 50 \times 0.5 ; \Omega \\ X_{Lph} &= 157 \Omega\end{aligned}$$

$$\begin{aligned}\text{Impedance } (Z_{ph}) &= \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega \\ Z_{ph} &= \sqrt{15^2 + 157^2} \\ &= \sqrt{225 + 24649} = \sqrt{24874} \\ Z_{ph} &= 157.7 \Omega\end{aligned}$$

$$\begin{aligned}\text{Phase Current } (I_{ph}) &= \frac{V_{ph}}{Z_{ph}} \\ V_{ph} &= V_L = 415V \quad [\because \text{Delta Connection}]\end{aligned}$$

$$\begin{aligned}\text{Phase Current } (I_{ph}) &= \frac{V_{ph}}{Z_{ph}} = \frac{415}{157.7} = 2.63 \text{ A} \\ I_{ph} &= 2.63 \text{ A}\end{aligned}$$

$$\begin{aligned}\text{Line Current } (I_L) &= \sqrt{3} I_{ph} \\ &= \sqrt{3} \times 2.63 = 4.56 \text{ A} \\ I_L &= 4.56 \text{ A}\end{aligned}$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{15}{157.7} = 0.09$$

$$\begin{aligned}\text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 415 \times 4.56 \times 0.09 \\ &= 295 \text{ Watts}\end{aligned}$$

Answer:

- i) Line Current (I_L) = 4.56 A ii) P.F = 0.09 iii) Power = 295 Watts

Example: 6

A balanced star connected load of $(8+j6)$ ohms per phase is connected to a 3 phase 230V supply. Find the line current, power factor, power and total volt ampere.

Given Data:

| | |
|-----------------------------------|--------------|
| Connection | = STAR |
| Resistance (R_{ph}) | = 8Ω |
| Inductive Reactance (X_{Lph}) | = 6Ω |
| Line Voltage | = 230 Volts |

To Find:

| |
|------------------------------------|
| Line Current (I_L) = ? |
| Power Factor ($\cos \theta$) = ? |
| Power (P) = ? |
| Volt-Ampere (VA) = ? |

Solution:

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned}\text{Impedance } (Z_{ph}) &= \sqrt{8^2 + 6^2} \\ &= \sqrt{64 + 36} \\ &= \sqrt{100}\end{aligned}$$

$$\text{Impedance } (Z_{ph}) = 10\Omega$$

$$\text{Phase Voltage } (V_{ph}) = \frac{V_L}{\sqrt{3}} \quad [\because \text{Star Connection}]$$

$$\text{Phase Voltage } (V_{ph}) = \frac{230}{\sqrt{3}} = 132.8 \text{ V}$$

$$\begin{aligned}\text{Phase Current } (I_{ph}) &= \frac{V_{ph}}{Z_{ph}} = \frac{132.8}{10} = 13.28 \text{ A} \\ I_{ph} &= 13.28 \text{ A}\end{aligned}$$

$$\begin{aligned}\text{Line Current } (I_L) &= I_{ph} = 13.28 \text{ A} \quad [\because \text{Star Connection}] \\ I_L &= 13.28 \text{ A}\end{aligned}$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{8}{10} = 0.8 \text{ Lag}$$

$$\begin{aligned}\text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 230 \times 13.28 \times 0.8 \\ &= 4232 \text{ Watts}\end{aligned}$$

$$\begin{aligned}\text{Volt -Ampere (VA)} &= \sqrt{3} V_L I_L \\ &= \sqrt{3} \times 230 \times 39.84 \\ &= 5290 \text{ VA}\end{aligned}$$

Answer:

- | | | | |
|---------------------------|--------------|------------------|-----------|
| i) Line Current (I_L) | = 13.28 A | ii) Power Factor | = 0.8 |
| iii) Power | = 4232 Watts | iv) Volt Ampere | = 5290 VA |

Example: 7

Each phase of a 3 phase wye connected load has an impedance of $(100 - j120)\Omega$. It is connected to 440V, 3 phase, 50Hz supply. Calculate the line current and power factor.

Given Data:

| | |
|-----------------------------------|-----------------|
| Connection | = STAR (Y) |
| Resistance (R_{ph}) | = $100\ \Omega$ |
| Inductive Reactance (X_{Lph}) | = $120\ \Omega$ |
| Line Voltage (V_L) | = 440 Volts |
| Frequency (F) | = 50Hz |

To Find:

| |
|------------------------------------|
| Line Current (I_L) = ? |
| Power factor ($\cos \theta$) = ? |

Solution:

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned}\text{Impedance } (Z_{ph}) &= \sqrt{100^2 + 120^2} \\ &= \sqrt{10000 + 14400} \\ &= \sqrt{24400}\end{aligned}$$

$$\text{Impedance } (Z_{ph}) = 156.2\Omega$$

$$\text{Phase Voltage } (V_{ph}) = \frac{V_L}{\sqrt{3}} \quad [\because \text{Star Connection}]$$

$$\text{Phase Voltage } (V_{ph}) = \frac{440}{\sqrt{3}} = 254\ \text{V}$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}} = \frac{254}{156.2} = 1.63\ \text{A}$$

$$I_{ph} = 1.63\ \text{A}$$

$$\text{Line Current } (I_L) = I_{ph} = 1.63\ \text{A} \quad [\because \text{Star Connection}]$$

$$I_L = 1.63\ \text{A}$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{100}{156.2} = 0.64 \text{ Lead}$$

$$\begin{aligned}\text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 440 \times 1.63 \times 0.64 \\ &= 795 \text{ Watts}\end{aligned}$$

Answer:

- i) Line Current (I_L) = 1.63 A
- ii) Power Factor = 0.64
- iii) Power = 795 Watts

Example: 8

Three similar coils each having a resistance of 20Ω and reactance of 15Ω are connected in star to a three phase $400V$, $50Hz$ supply. Determine the i) Phase current ii) Line Current c) Power factor and d) Total power.

Given Data:

| | |
|-----------------------------------|---------------|
| Connection | = STAR |
| Resistance (R_{ph}) | = 20Ω |
| Inductive Reactance (X_{Lph}) | = 15Ω |
| Line Voltage (V_L) | = 400 Volts |
| Frequency (F) | = 50 Hz |

To Find:

| |
|------------------------------------|
| Phase Current (I_{ph}) = ? |
| Line Current (I_L) = ? |
| Power Factor ($\cos \theta$) = ? |
| Power (P) = ? |

Solution:

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned}\text{Impedance } (Z_{ph}) &= \sqrt{20^2 + 15^2} \\ &= \sqrt{400 + 225} \\ &= \sqrt{625}\end{aligned}$$

$$\text{Impedance } (Z_{ph}) = 25\Omega$$

$$\text{Phase Voltage } (V_{ph}) = \frac{V_L}{\sqrt{3}} \quad [\because \text{Star Connection}]$$

$$\text{Phase Voltage } (V_{ph}) = \frac{400}{\sqrt{3}} = 231 \text{ V}$$

$$\text{Phase Current } (I_{ph}) = \frac{V_{ph}}{Z_{ph}} = \frac{231}{25} = 9.24 \text{ A}$$

$$I_{ph} = 9.24 \text{ A}$$

$$\text{Line Current } (I_L) = I_{ph} = 9.24 \text{ A} \quad [\because \text{Star Connection}]$$

$$I_L = 9.24 \text{ A}$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{ph}}{Z_{ph}} = \frac{20}{25} = 0.8 \text{ Lag}$$

$$\begin{aligned}\text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 400 \times 9.24 \times 0.8 \\ &= 5121 \text{ Watts}\end{aligned}$$

Answer:

- | | | | | | |
|------|------------------------|------------------------|-----|--------------|---------|
| i) | Line Current (I_L) | = 9.24 A | ii) | Power Factor | = 0.8 |
| iii) | Power | = 5121 Watts | | | |

Example: 9

Three identical impedances are connected in delta to a 3 phase 400V supply. The line current is 34.65A and the total power taken from the supply is 14.4KW. Calculate the resistance and reactance values of each impedance.

Given Data:

| | | |
|------------------------|---|-----------|
| Connection | = | DELTA |
| Line Current (I_L) | = | 34.65 A |
| Total Power (P) | = | 14.4 KW |
| Line Voltage (V_L) | = | 400 Volts |

To Find:

$$\begin{aligned} \text{Resistance } (R_{ph}) &= ? \\ \text{Reactance } (X_{ph}) &= ? \end{aligned}$$

Solution:

$$\begin{aligned} \text{Phase Current } (I_{ph}) &= \frac{I_L}{\sqrt{3}} && [\because \text{Delta Connection}] \\ &= \frac{34.65}{\sqrt{3}} && [\because \text{Delta Connection}] \\ &= 20 \text{ A} \end{aligned}$$

$$\text{Phase Voltage } (V_{ph}) = V_L = 400 \text{ V} \quad [\because \text{Delta Connection}]$$

$$\begin{aligned} \text{Impedance } (Z_{ph}) &= \frac{V_{ph}}{I_{ph}} \\ Z_{ph} &= \frac{400}{20} = 20\Omega \end{aligned}$$

$$\text{Power } (P) = \sqrt{3} V_L I_L \cos \theta$$

$$\begin{aligned} \cos \theta &= \frac{P}{\sqrt{3} V_L I_L} \\ &= \frac{14.4 \times 10^3}{\sqrt{3} \times 400 \times 34.65} \\ &= \frac{14400}{24005.5} \end{aligned}$$

$$\cos \theta = 0.6$$

$$\cos \theta = \frac{R_{ph}}{Z_{ph}}$$

$$\begin{aligned} R_{ph} &= Z_{ph} \times \cos \theta \\ &= 20 \times 0.6 \end{aligned}$$

$$\text{Resistance } (R_{ph}) = 12\Omega$$

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned}\text{Reactance } (X_{ph}) &= \sqrt{Z_{ph}^2 - R_{ph}^2} \\ &= \sqrt{20^2 - 12^2} \\ &= \sqrt{400 - 144}\end{aligned}$$

$$X_{ph} = 16 \Omega$$

Answer:

i) Resistance (R_{ph}) = 12 Ω ii) Reactance (X_{ph}) = 16 Ω

Example: 10

Three similar coils are connected in star taken at a total power of 1.5KW at a P.F of 0.2 lagging from a 3 phase 400V, 50Hz supply. Calculate the resistance and inductance of each phase.

Given Data:

| | | | |
|--------------------------------|-------------|----------|-----------------------------|
| Connection | = STAR | To Find: | Resistance (R_{ph}) = ? |
| Total Power (P) | = 1.5 KW | | Inductance (L_{ph}) = ? |
| Power Factor ($\cos \theta$) | = 0.2 | | |
| Line Voltage (V_L) | = 400 Volts | | |
| Frequency (F) | = 50 Hz | | |

Solution:

$$\text{Power } (P) = \frac{\sqrt{3} V_L I_L \cos \theta}{P}$$

$$\begin{aligned}\text{Line Current } (I_L) &= \frac{\sqrt{3} V_L \cos \theta}{\sqrt{3} \times 400 \times 0.2} \\ &= \frac{1500}{138.56} \\ &= 10.8 \text{ A}\end{aligned}$$

$$\text{Phase Voltage } (V_{ph}) = \frac{V_L}{\sqrt{3}} \quad [\because \text{Star Connection}]$$

$$\begin{aligned}&= \frac{400}{\sqrt{3}} = 231 \text{ Volts} \quad [\because \text{Star Connection}] \\ &= 231 \text{ Volts}\end{aligned}$$

$$\text{Impedance } (Z_{ph}) = \frac{V_{ph}}{I_{ph}}$$

$$= \frac{231}{10.8} = 21.3 \Omega$$

$$\text{Impedance } (Z_{ph}) = 21.3 \Omega$$

$$\cos \theta = \frac{R_{ph}}{Z_{ph}}$$

$$R_{ph} = Z_{ph} \times \cos \theta$$

$$= 21.3 \times 0.2$$

$$\text{Resistance } (R_{ph}) = 4.26 \Omega$$

$$\text{Impedance } (Z_{ph}) = \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega$$

$$\begin{aligned}\text{Reactance } (X_{ph}) &= \sqrt{Z_{ph}^2 - R_{ph}^2} \\ &= \sqrt{21.3^2 - 4.26^2} \\ &= \sqrt{453.7 - 18.15} \\ &= 20.87 \Omega\end{aligned}$$

$$\text{Inductive Reactance } (X_{Lph}) = 2\pi f L ; \Omega$$

$$\begin{aligned}\text{Inductance } (L_{ph}) &= \frac{X_L}{2\pi f} \\ &= \frac{20.87}{2 \times \pi \times 50} \\ L_{ph} &= 0.06 \text{ H}\end{aligned}$$

Answer:

i) Resistance (R_{ph}) = 4.26 Ω ii) Inductance (L_{ph}) = 0.06 Ω

Example: 11

Three similar resistors are connected in star across 400V, 3 phase supply. The line current is 5A. Calculate the value of each resistor. To what value should the line voltage be changed to obtain the same line current with the resistors are in delta connected?

Given Data:

| | | |
|------------------------|-----------------|----------------------------|
| Connection | = STAR To DELTA | To Find: |
| Line Voltage (V_L) | = 400 Volts | Line Voltage (V_L) = ? |
| Line Current (I_L) | = 5 Amps | |

Solution:

$$\text{Phase Current } (I_{ph}) = I_L = 5 \text{ A} \quad [\because \text{Star Connection}]$$

$$\text{Phase Voltage } (V_{ph}) = \frac{V_L}{\sqrt{3}} \quad [\because \text{Star Connection}]$$

$$= \frac{400}{\sqrt{3}} = 231 \text{ Volts} \quad [\because \text{Star Connection}]$$

$$V_{ph} = 231 \text{ Volts}$$

$$\text{Impedance } (Z_{ph}) = \text{Resistance } (R_{ph})$$

$$\text{Impedance } (Z_{ph}) = \frac{V_{ph}}{I_{ph}}$$

$$Z_{ph} = \frac{231}{5} = 46.2 \Omega$$

$$= 46.2 \Omega$$

$$\text{Impedance } (Z_{ph}) = 46.2 \Omega$$

$$\text{Impedance } (Z_{ph}) = \text{Resistance } (R_{ph})$$

If same resistors are connected in delta

$$\text{Phase Voltage } (V_{ph}) = V_L = 400 \text{ V} \quad [\because \text{Delta Connection}]$$

$$V_{ph} = I_{ph} \times Z_{ph}$$

$$= \frac{I_L}{\sqrt{3}} \times 46.2$$

$$= \frac{5}{\sqrt{3}} \times 46.2$$

$$= 133.34 \text{ V}$$

$$\text{Phase Voltage } (V_{ph}) = 133.34 \text{ V}$$

$$\text{Line Voltage } (V_L) = 133.34 \text{ V}$$

Answer:

- i) Resistance (R_{ph}) = 4.26Ω
- ii) Inductance (L_{ph}) = 0.06Ω
- iii) Line Voltage (V_L) = 133.34 V

Example: 12

A balanced three phase star connected load of 150KW takes a leading current of 100A with a line voltage of 1100V, 50Hz. Find the circuit constants of the load per phase.

Given Data:

| | |
|------------------------|--------------|
| Connection | = STAR |
| Line Current (I_L) | = 100 A |
| Total Power (P) | = 150 KW |
| Line Voltage (V_L) | = 1100 Volts |

To Find:

$$\begin{aligned} \text{Resistance } (R_{ph}) &= ? \\ \text{Reactance } (X_{ph}) &= ? \end{aligned}$$

Solution:

$$\begin{aligned} \text{Phase Current } (I_{ph}) &= I_L = 100 \text{ A} & [\because \text{Star Connection}] \\ I_{ph} &= 100 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Phase Voltage } (V_{ph}) &= \frac{V_L}{\sqrt{3}} & [\because \text{Star Connection}] \\ &= \frac{1100}{\sqrt{3}} = 635 \text{ Volts} & [\because \text{Star Connection}] \\ &= 635 \text{ Volts} \end{aligned}$$

$$\begin{aligned} \text{Impedance } (Z_{ph}) &= \frac{V_{ph}}{I_{ph}} \\ Z_{ph} &= \frac{635}{100} = 6.35\Omega \end{aligned}$$

$$\begin{aligned} \text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ \cos \theta &= \frac{\sqrt{3} V_L I_L}{P} \\ &= \frac{150 \times 10^3}{\sqrt{3} \times 1100 \times 100} \\ &= \frac{150 \times 10^3}{190520} \\ \cos \theta &= 0.79 \end{aligned}$$

$$\begin{aligned} \cos \theta &= \frac{R_{ph}}{Z_{ph}} \\ R_{ph} &= Z_{ph} \times \cos \theta \\ &= 6.35 \times 0.79 \end{aligned}$$

$$\text{Resistance } (R_{ph}) = 5\Omega$$

$$\begin{aligned}
 \text{Impedance } (Z_{ph}) &= \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega \\
 \text{Reactance } (X_{ph}) &= \sqrt{Z_{ph}^2 - R_{ph}^2} \\
 &= \sqrt{6.35^2 - 5^2} \\
 &= \sqrt{40.3 - 25} = \sqrt{15.3} \\
 X_{ph} &= 3.9 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \text{Capacitive Reactance } (X_{Cph}) &= \frac{1}{2\pi f C}; \Omega \\
 \text{Capacitance } (C_{ph}) &= \frac{1}{2\pi f X_C} \\
 &= \frac{1}{2 \times \pi \times 50 \times 3.9} \\
 C_{ph} &= 812 \text{ MFD}
 \end{aligned}$$

Answer:

$$\text{i) Resistance } (R_{ph}) = 5 \Omega \quad \text{ii) Capacitance } (C) = 812 \text{ MFD}$$

Example: 13

A balanced connected to a three phase supply comprises three identical coils in star. The line current is 25 Amps. KVA input is 20 and KW input is 11. Find KVAR input, phase voltage, line voltage, resistance and reactance of each coil of the load.

Given Data:

$$\begin{aligned}
 \text{Connection} &= \text{STAR} \\
 \text{Line Current } (I_L) &= 25 \text{ A} \\
 \text{KW} &= 11 \\
 \text{KVA} &= 20
 \end{aligned}$$

To Find:

$$\begin{aligned}
 \text{Resistance } (R_{ph}) &=? \\
 \text{Reactance } (X_{ph}) &= ?
 \end{aligned}$$

Solution:

$$\begin{aligned}
 \text{KVA} &= \sqrt{\text{KW}^2 + \text{KVAR}^2} \\
 \text{KVAR} &= \sqrt{\text{KVA}^2 - \text{KW}^2} \\
 \text{Reactance } (X_{ph}) &= \sqrt{20^2 - 11^2} \\
 &= \sqrt{400 - 121} \\
 &= \sqrt{279} = 16.7 \\
 \text{KVAR} &= 16.7
 \end{aligned}$$

$$\text{KVA} = \frac{\sqrt{3} V_L I_L}{1000}$$

$$\begin{aligned}
 \text{Line Voltage } (V_L) &= \frac{\text{KVA} \times 1000}{\sqrt{3} V_L} \\
 &= \frac{20 \times 1000}{\sqrt{3} I_L} \\
 &= \frac{20 \times 1000}{\sqrt{3} \times 25} \\
 &= 461.89 \text{ Volts}
 \end{aligned}$$

$$\begin{aligned}
 \text{Phase Voltage } (V_{ph}) &= \frac{V_L}{\sqrt{3}} \quad [\because \text{Star Connection}] \\
 &= \frac{461.89}{\sqrt{3}} = 266.6 \text{ Volts} \quad [\because \text{Star Connection}] \\
 V_{ph} &= 266.6 \text{ Volts}
 \end{aligned}$$

$$\begin{aligned}
 \text{Phase Current } (I_{ph}) &= I_L = 25 \text{ A} \quad [\because \text{Star Connection}] \\
 I_{ph} &= 25 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 \text{Impedance } (Z_{ph}) &= \frac{V_{ph}}{I_{ph}} \\
 Z_{ph} &= \frac{266.6}{25} = 10.67 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \cos \theta &= \frac{\text{KW}}{\text{KVA}} \\
 &= \frac{11}{20} \\
 \cos \theta &= 0.55
 \end{aligned}$$

$$\begin{aligned}
 \cos \theta &= \frac{R_{ph}}{Z_{ph}} \\
 R_{ph} &= Z_{ph} \times \cos \theta \\
 &= 10.67 \times 0.55
 \end{aligned}$$

$$\text{Resistance } (R_{ph}) = 5.86 \Omega$$

$$\begin{aligned}
 \text{Reactance } (X_{ph}) &= \sqrt{Z_{ph}^2 - R_{ph}^2} \\
 &= \sqrt{10.67^2 - 5.86^2} \\
 &= \sqrt{113.8 - 34.3} = \sqrt{79.5} \\
 X_{ph} &= 8.9 \Omega
 \end{aligned}$$

Answer:

$$\text{i) Resistance } (R_{ph}) = 5.86 \Omega \quad \text{ii) Reactance } (X_{ph}) = 8.9 \Omega$$

Example: 14

A 440V, three phase delta connected induction motor has an output of 14.92KW at p.f of 0.82 and efficiency 85%. Calculate the readings on each of the two wattmeters connected to measure the input

Given Data:

| | <u>To Find:</u> |
|--------------------------------|--------------------|
| Connection | W ₁ = ? |
| Line Voltage (V _L) | W ₂ = ? |
| Output Power | 14.92 KW |
| Power factor (Cos θ) | 0.82 |
| Efficiency (η) | 85% = 0.85 |

Solution:

$$\begin{aligned} W_2 + W_1 &= \frac{\text{Output Power}}{\text{Efficiency}} \\ W_2 + W_1 &= \frac{14.92 \times 10^3}{0.85} \\ W_2 + W_1 &= 17553 \text{ Watts} \quad \text{----- (1)} \end{aligned}$$

$$\begin{aligned} \text{Power Factor (Cos } \varphi) &= 0.82 \\ \varphi &= \cos^{-1} 0.82 \\ &= 35.92^\circ \\ \tan \varphi &= \tan 35.92^\circ \\ &= 0.698 \end{aligned}$$

$$\begin{aligned} \tan \varphi &= \frac{\sqrt{3} (W_2 - W_1)}{(W_1 + W_2)} \\ 0.698 &= \frac{\sqrt{3} (W_2 - W_1)}{17553} \\ 0.698 \times 17553 &= \sqrt{3} (W_2 - W_1) \\ \frac{0.698 \times 17553}{\sqrt{3}} &= (W_2 - W_1) \\ W_2 - W_1 &= \frac{0.698 \times 17553}{\sqrt{3}} \\ W_2 - W_1 &= \frac{12252}{\sqrt{3}} \\ W_2 - W_1 &= 7074 \text{ W} \quad \text{----- (2)} \end{aligned}$$

$$\begin{aligned} W_2 + W_1 &= 17553 \quad \text{----- (1)} \\ W_2 - W_1 &= 7074 \quad \text{----- (2)} \end{aligned}$$

By adding equ (1) and (2)

$$\begin{aligned}2W_2 &= 24627 \\W_2 &= \frac{24627}{2} \\W_2 &= 12313.5 \text{ Watts}\end{aligned}$$

Substitute the value of W_2 in equ (1)

$$\begin{aligned}12313.5 + W_1 &= 17553 \quad \dots\dots (1) \\W_1 &= 17553 - 12313.5 = 5239.5 \text{ W} \\W_1 &= 5239.5 \text{ Watts}\end{aligned}$$

Answer:

i) $W_1 = 5239.5 \text{ Watts}$ ii) $W_2 = 12313.5 \text{ Watts}$

Example: 15

A 500 volts, 3 phase motor has an output of 3.73KW and operates at a power factor of 0.85 with an efficiency of 90%. Calculate the reading on each of the two wattmeter connected to measure the input.

Given Data:

| | | |
|--------------------------------|-------------|-----------------|
| Line Voltage (V_L) | = 500 Volts | <u>To Find:</u> |
| Output Power | = 3.73 KW | $W_1 = ?$ |
| Power factor ($\cos \theta$) | = 0.85 | $W_2 = ?$ |
| Efficiency (η) | = 90% = 0.9 | |

Solution:

$$\begin{aligned}W_2 + W_1 &= \frac{\text{Output Power}}{\text{Efficiency}} \\W_2 + W_1 &= \frac{3.73 \times 10^3}{0.9} \\W_2 + W_1 &= 4144 \text{ Watts} \quad \dots\dots (1)\end{aligned}$$

$$\begin{aligned}\text{Power Factor} (\cos \varphi) &= 0.85 \\ \varphi &= \cos^{-1} 0.85 \\ &= 31.79^\circ \\ \tan \varphi &= \tan 31.79^\circ \\ &= 0.619\end{aligned}$$

$$\tan \varphi = \frac{\sqrt{3} (W_2 - W_1)}{(W_1 + W_2)}$$

$$\begin{aligned}
 0.619 &= \frac{\sqrt{3} (W_2 - W_1)}{17553} \\
 0.619 \times 4144.4 &= \sqrt{3} (W_2 - W_1) \\
 \frac{0.619 \times 4144.4}{\sqrt{3}} &= (W_2 - W_1) \\
 W_2 - W_1 &= \frac{0.619 \times 4144}{\sqrt{3}} \\
 W_2 - W_1 &= \frac{2565}{\sqrt{3}} \\
 W_2 - W_1 &= 1481 \text{ W} \quad \text{----- (2)}
 \end{aligned}$$

$$W_2 + W_1 = 4144 \quad \text{----- (1)}$$

$$W_2 - W_1 = 1481 \quad \text{----- (2)}$$

By adding equ (1) and (2)

$$\begin{aligned}
 2W_2 &= 5625 \\
 W_2 &= \frac{5625}{2} \\
 W_2 &= 2813 \text{ Watts}
 \end{aligned}$$

Substitute the value of W_2 in equ (1)

$$2813 + W_1 = 4144 \quad \text{----- (1)}$$

$$W_1 = 4144 - 2813 = 5239.5 \text{ W}$$

$$W_1 = 1331 \text{ Watts}$$

Answer:

$$\text{i) } W_1 = 1331 \text{ Watts} \qquad \text{ii) } W_2 = 2813 \text{ Watts}$$

Example: 16

A 3 phase motor delivers an output of 46KW and operated within efficiency of 90% at 0.85 lagging power factor. Calculate the line current and total power drawn if the supply voltage is 400V.

Given Data:

| | | |
|--------------------------------|---|-----------|
| Line Voltage (V_L) | = | 400 Volts |
| Output Power | = | 46 KW |
| Power factor ($\cos \theta$) | = | 0.85 |
| Efficiency (η) | = | 90% = 0.9 |

To Find:

$$\begin{aligned}
 W_1 &= ? \\
 W_2 &= ?
 \end{aligned}$$

Solution:

$$W_2 + W_1 = \frac{\text{Output Power}}{\text{Efficiency}}$$

$$W_2 + W_1 = \frac{46 \times 10^3}{0.9}$$

$$W_2 + W_1 = 51111 \text{ Watts} \quad \dots\dots (1)$$

$$\begin{aligned}\text{Power Factor (Cos } \varphi) &= 0.85 \\ \varphi &= \cos^{-1} 0.85 \\ &= 31.79^\circ \\ \tan \varphi &= \tan 31.79^\circ \\ &= 0.619\end{aligned}$$

$$\begin{aligned}\tan \varphi &= \frac{\sqrt{3} (W_2 - W_1)}{(W_1 + W_2)} \\ 0.619 &= \frac{\sqrt{3} (W_2 - W_1)}{51111} \\ 0.619 \times 51111 &= \sqrt{3} (W_2 - W_1) \\ \frac{0.619 \times 51111}{\sqrt{3}} &= (W_2 - W_1) \\ W_2 - W_1 &= \frac{0.619 \times 51111}{\sqrt{3}} \\ W_2 - W_1 &= \frac{31637.7}{\sqrt{3}} \\ W_2 - W_1 &= 18267 \text{ W} \quad \dots\dots (2)\end{aligned}$$

$$\begin{aligned}W_2 + W_1 &= 51111 \quad \dots\dots (1) \\ W_2 - W_1 &= 18267 \quad \dots\dots (2)\end{aligned}$$

By adding equ (1) and (2)

$$\begin{aligned}2W_2 &= 69378 \\ W_2 &= \frac{69378}{2} \\ W_2 &= 34689 \text{ Watts}\end{aligned}$$

Substitute the value of W_2 in equ (1)

$$\begin{aligned}34689 + W_1 &= 51111 \quad \dots\dots (1) \\ W_1 &= 51111 - 34689 = 16422 \text{ W} \\ W_1 &= 16422 \text{ Watts}\end{aligned}$$

Answer:

$$\text{i) } W_1 = 16422 \text{ Watts} \qquad \text{ii) } W_2 = 34689 \text{ Watts}$$

Example: 17

A three phase 440 volts motor operates with a power factor of 0.4. Two wattmeters are connected to measure the input power, and the total power taken from the mains is 30KW. Find the readings of each wattmeter.

Given Data:

| | To Find: |
|--------------------------------|-------------|
| Line Voltage (V_L) | $W_1 = ?$ |
| Output Power | $W_2 = ?$ |
| Power factor ($\cos \theta$) | = 0.4 |
| Efficiency (η) | = 90% = 0.9 |

Solution:

$$W_2 + W_1 = \frac{\text{Output Power}}{\text{Efficiency}}$$

$$W_2 + W_1 = \frac{30 \times 10^3}{0.9}$$

$$W_2 + W_1 = 33333 \text{ Watts} \quad \dots\dots (1)$$

$$\text{Power Factor} (\cos \varphi) = 0.4$$

$$\varphi = \cos^{-1} 0.4$$

$$= 66.42^\circ$$

$$\tan \varphi = \tan 66.42^\circ$$

$$= 2.29$$

$$\tan \varphi = \frac{\sqrt{3} (W_2 - W_1)}{(W_1 + W_2)}$$

$$2.29 = \frac{\sqrt{3} (W_2 - W_1)}{33333}$$

$$2.29 \times 33333 = \sqrt{3} (W_2 - W_1)$$

$$\frac{2.29 \times 33333}{\sqrt{3}} = (W_2 - W_1)$$

$$W_2 - W_1 = \frac{2.29 \times 33333}{\sqrt{3}}$$

$$W_2 - W_1 = \frac{76332}{\sqrt{3}}$$

$$W_2 - W_1 = 44072 \text{ W} \quad \dots\dots (2)$$

$$W_2 + W_1 = 33333 \quad \dots\dots (1)$$

$$W_2 - W_1 = 44072 \quad \dots\dots (2)$$

By adding equ (1) and (2)

$$\begin{aligned}2W_2 &= 77405 \\W_2 &= \frac{77405}{2} \\W_2 &= 38702.5 \text{ Watts}\end{aligned}$$

Substitute the value of W_2 in equ (1)

$$\begin{aligned}38702.5 + W_1 &= 33333 \quad \dots\dots (1) \\W_1 &= 33333 - 38702.5 = -5369.5 \text{ W} \\W_1 &= -5369.5 \text{ Watts}\end{aligned}$$

Answer:

i) $W_1 = -5369.5 \text{ Watts}$ ii) $W_2 = 38702.5 \text{ Watts}$

Example: 18

The power input to a 400 volts, 50Hz, 3 phase motor is measured by two wattmeters which indicate 300KW and 100KW respectively. Calculate (a) the input power (b) power factor and (c) the line current.

Given Data:

$$\begin{array}{lcl}\text{Wattmeter } (W_2) & = & 300\text{KW} \\ \text{Wattmeter } (W_1) & = & 100\text{KW} \\ \text{Line Voltage } (V_L) & = & 400 \text{ Volts} \\ \text{Frequency } (F) & = & 50 \text{ Hz}\end{array}$$

To Find:

- i) The input Power (P) = ?
- ii) Power factor ($\cos \phi$) = ?
- iii) Line Current (I_L) = ?

Solution:

$$\begin{aligned}\text{Input Power } (P) &= W_2 + W_1 \\&= 300 + 100 \\W_2 + W_1 &= 400 \text{ KW}\end{aligned}$$

Power Factor ($\cos \phi$):

$$\begin{aligned}\varphi &= \tan^{-1} \left[\frac{\sqrt{3} (W_2 - W_1)}{(W_2 + W_1)} \right] \\&= \tan^{-1} \left[\frac{\sqrt{3} (300 - 100)}{300 + 100} \right] \\&= \tan^{-1} \left[\frac{\sqrt{3} \times 200}{400} \right] \\&= \tan^{-1} \left[\frac{346.4}{400} \right] \\&= \tan^{-1}[0.866] \\&= 40.89\end{aligned}$$

$$\cos \varphi = \cos 40.89$$

$$\cos \varphi = 0.76$$

$$\text{Power (P)} = \sqrt{3} V_L I_L \cos \theta$$

$$\begin{aligned}\text{Line Current (I}_L\text{)} &= \frac{P}{\sqrt{3} V_L \cos \theta} \\ &= \frac{400 \times 10^3}{\sqrt{3} \times 400 \times 0.76} \\ &= \frac{400 \times 10^3}{526.5} \\ I_L &= 759.7 \text{ A}\end{aligned}$$

Answer:

- i) Input Power = 400 KW
- ii) Power Factor ($\cos \phi$) = 0.76
- iii) Line Current (I_L) = 759.7 A

Example: 19

Two wattmeters are connected to measure the power of a 3 phase circuit indicated 2500W and 500 W respectively. Find the power factor of the circuit when (a) both the readings are positive and (b) the later reading is obtained after reversing the connection of the current coil of the wattmeter.

Given Data:

$$\begin{aligned}\text{Wattmeter (W}_2\text{)} &= 2500 \text{ W} \\ \text{Wattmeter (W}_1\text{)} &= 500 \text{ W}\end{aligned}$$

To Find:

- Power factor ($\cos \phi$) when
- i) Both the readings are positive
- ii) Later reading is negative

Solution:

Power Factor ($\cos \varphi$): When both the readings are positive

$$\text{Wattmeter (W}_2\text{)} = 2500 \text{ W}$$

$$\text{Wattmeter (W}_1\text{)} = 500 \text{ W}$$

$$\begin{aligned}\varphi &= \tan^{-1} \left[\frac{\sqrt{3} (W_2 - W_1)}{(W_2 + W_1)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3} (2500 - 500)}{(2500 + 500)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3} (2000)}{(3000)} \right] \\ &= \tan^{-1}[1.154] \\ \varphi &= 49.08\end{aligned}$$

$$\cos \varphi = \cos 49.09$$

$$\cos \varphi = 0.66$$

Power Factor ($\cos \varphi$): Later wattmeter reading is negative

$$\text{Wattmeter } (W_2) = 2500 \text{ W}$$

$$\text{Wattmeter } (W_1) = -500 \text{ W}$$

$$\begin{aligned}\varphi &= \tan^{-1} \left[\frac{\sqrt{3}(W_2 - W_1)}{(W_2 + W_1)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3}(2500 - (-500))}{(2500 + 500)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3}(2500 + 500)}{(3000)} \right] \\ \varphi &= \tan^{-1} \left[\frac{\sqrt{3} \times 3000}{3000} \right] \\ &= \tan^{-1}[2.59]\end{aligned}$$

$$\varphi = 68.88$$

$$\cos \varphi = \cos 68.88$$

$$\cos \varphi = 0.36$$

Answer:

i) Power factor when both readings are positive = 0.66

ii) Power factor when later reading is negative = 0.36

Example: 20

Two wattmeter are connected to measure the power in a 3 phase balanced load. Determine the total power and power factor if the two wattmeters read 1000Watts each (i) both positive and (ii) Second reading is negative.

Given Data:

$$\text{Wattmeter } (W_2) = 1000 \text{ W}$$

$$\text{Wattmeter } (W_1) = 1000 \text{ W}$$

To Find:

Power factor ($\cos \phi$) when

i) Both the readings are positive

ii) Second reading is negative

Solution:

Power Factor ($\cos \varphi$): When both the readings are positive

$$\text{Wattmeter } (W_2) = 1000 \text{ W}$$

$$\text{Wattmeter } (W_1) = 1000 \text{ W}$$

$$\begin{aligned}\varphi &= \tan^{-1} \left[\frac{\sqrt{3} (W_2 - W_1)}{(W_2 + W_1)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3} (1000 - 1000)}{(1000 + 1000)} \right] \\ \varphi &= \tan^{-1} \left[\frac{\sqrt{3} \times 0}{2000} \right] \\ &= \tan^{-1}[0] \\ \varphi &= 0 \\ \cos \varphi &= \cos 0 \\ \cos \varphi &= 1\end{aligned}$$

Power Factor ($\cos \varphi$): **Later wattmeter reading is negative**

$$\text{Wattmeter } (W_2) = 1000 \text{ W}$$

$$\text{Wattmeter } (W_1) = -1000 \text{ W}$$

$$\begin{aligned}\varphi &= \tan^{-1} \left[\frac{\sqrt{3} (W_2 - W_1)}{(W_2 + W_1)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3} (1000 - (-1000))}{(1000 - 1000)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3} \times 2000}{0} \right] \\ \varphi &= \tan^{-1}[\sqrt{3} \times 2000] \\ &= \tan^{-1}[3464] \\ \varphi &= 89.98 \\ \cos \varphi &= \cos 89.98 \\ \cos \varphi &= 0.00035\end{aligned}$$

Answer:

- iii) Power factor when both readings are positive = 1
- iv) Power factor when later reading is negative = 0.00035

Example: 21

The power input to a 3 phase induction motor is read by two wattmeters. The readings are 860W and 240W. What is the input power and power factor of the motor?

Given Data:

$$\begin{aligned}\text{Wattmeter } (W_2) &= 860 \text{ W} \\ \text{Wattmeter } (W_1) &= 240 \text{ W}\end{aligned}$$

To Find:

- i) The input Power (P) = ?
- ii) Power factor ($\cos \phi$) = ?

Solution:

$$\begin{aligned}\text{Input Power (P)} &= W_2 + W_1 \\ &= 860 + 240 \\ W_2 + W_1 &= 1100 \text{ W}\end{aligned}$$

Power Factor ($\cos \varphi$):

$$\begin{aligned}\varphi &= \tan^{-1} \left[\frac{\sqrt{3} (W_2 - W_1)}{(W_2 + W_1)} \right] \\ &= \tan^{-1} \left[\frac{\sqrt{3} (860 - 240)}{(860 + 240)} \right] \\ \varphi &= \tan^{-1} \left[\frac{\sqrt{3} \times 620}{1100} \right] \\ &= \tan^{-1} \left[\frac{1074}{1100} \right] \\ &= \tan^{-1}[0.976] \\ \varphi &= 44.3 \\ \cos \varphi &= \cos 44.3 \\ \cos \varphi &= 0.72\end{aligned}$$

Answer:

i) Input Power = 1100 W ii) Power Factor ($\cos \varphi$) = 0.72

Example: 22

Three identical coils each having a resistance of 10 ohms and reactance of 10 ohms are connected in delta across 400 volts, 3 phase supply. Find the line current and the readings on each of the two wattmeters connected to measure the power.

Given Data:

| | | |
|-----------------------------------|---|-------------|
| Connection | = | DELTA |
| Resistance (R_{ph}) | = | 10Ω |
| Inductive Reactance (X_{Lph}) | = | 10Ω |
| Line Voltage | = | 400 Volts |

To Find:

| |
|----------------------------|
| Line Current (I_L) = ? |
| $W_1 = ?$ |
| $W_2 = ?$ |

Solution:

$$\begin{aligned}\text{Impedance } (Z_{ph}) &= \sqrt{R_{ph}^2 + X_{Lph}^2} \Omega \\ &= \sqrt{10^2 + 10^2} \\ &= \sqrt{100 + 100} \\ &= \sqrt{200}\end{aligned}$$

$$\text{Impedance } (Z_{\text{ph}}) = 14.14\Omega$$

$$\text{Phase Current } (I_{\text{ph}}) = \frac{V_{\text{ph}}}{Z_{\text{ph}}}$$

$$\text{Phase Voltage } (V_{\text{ph}}) = V_L = 400 \text{ V} \quad [\because \text{Delta Connection}]$$

$$\begin{aligned}\text{Phase Current } (I_{\text{ph}}) &= \frac{V_{\text{ph}}}{Z_{\text{ph}}} = \frac{400}{14.14} = 28.28\text{A} \\ I_{\text{ph}} &= 28.28\text{A}\end{aligned}$$

$$\begin{aligned}\text{Line Current } (I_L) &= \sqrt{3} I_{\text{ph}} \\ &= \sqrt{3} \times 28.28 = 48.9 \text{ A} \\ I_L &= 48.9 \text{ A}\end{aligned}$$

$$\text{Power Factor } (\cos \theta) = \frac{R_{\text{ph}}}{Z_{\text{ph}}} = \frac{10}{14.14} = 0.707$$

$$\begin{aligned}\text{Power } (P) &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} \times 400 \times 48.9 \times 0.707 \\ &= 23952 \text{ Watts}\end{aligned}$$

$$W_2 + W_1 = 23952 \text{ Watts} \quad \text{----- (1)}$$

$$\begin{aligned}\text{Power Factor } (\cos \varphi) &= 0.707 \\ \varphi &= \cos^{-1} 0.707 \\ &= 45^0 \\ \tan \varphi &= \tan 45^0 \\ &= 1\end{aligned}$$

$$\begin{aligned}\tan \varphi &= \frac{\sqrt{3} (W_2 - W_1)}{(W_1 + W_2)} \\ 1 &= \frac{\sqrt{3} (W_2 - W_1)}{30 \times 10^3} \\ 1 \times 23952 &= \sqrt{3} (W_2 - W_1) \\ \frac{23952}{\sqrt{3}} &= (W_2 - W_1) \\ W_2 - W_1 &= \frac{23952}{\sqrt{3}}\end{aligned}$$

$$W_2 + W_1 = 23952 \text{ ----- (1)}$$

$$W_2 - W_1 = 13829 \text{ (2)}$$

By adding equ (1) and (2)

$$W_2 = \frac{37781}{2}$$

Substitute the value of W_2 in equ (1)

$$34832.5 + W_1 = 23952 \quad \dots\dots (1)$$

$$W_1 = 23952 - 18891 = 5061 \text{ W}$$

$$W_1 = 5061 \text{ Watts}$$

Answer:

i) $W_1 = 5061 \text{ Watts}$

$$\text{ii) } W_2 = 18891 \text{ Watts}$$

REVIEW QUESTIONS
UNIT : V THREE PHASE CIRCUITS

PART – A : 2 Mark Questions

1. What is phase sequence?
2. Define phase voltage.
3. Define Line voltage.
4. Define phase current.
5. Define Line current.
6. Define balanced load.
7. Define unbalanced load.
8. What is a star connection?
9. What is a Delta connection?
10. Write the expression for 3 phase power in Star connection.
11. State the relationship between line current and phase current in a balanced star connected load.
12. State the relationship between line voltage and phase voltage in a balanced star connected load
13. State the relationship between line current and phase current in a balanced delta connected load.
14. State the relationship between line voltage and phase voltage in a balanced delta connected load.
15. Write the expression for calculating real power in a three phase circuit.
16. Write the expression for calculating apparent power in a three phase circuit.
17. Write the expression for calculating reactive power in a three phase circuit.
18. Write down the expression of power factor in two wattmeter method of power measurement.
19. What is the p.f of 3 phase load if $W_1=W_2$.
20. What is the p.f of 3 phase load if $W_1 = -W_2$

PART – B : 3 Mark Questions

1. List the advantages of 3-phase system.
2. Write the voltage expressions of a three phase sinusoidal voltage.
3. Define positive sequence.
4. Define negative sequence.
5. Show that in a balanced 3 phase star connected system, the neutral current is zero.
6. What is meant by balanced and unbalanced load?
7. Show that the line voltage in a balanced star connected system is 3 times of phase voltage.
8. Derive an expression for line current in terms of phase current in a three phase delta connected system.
9. How can you determine the phase angle from two wattmeter readings?
10. Prove that 3 phase power is given by $\sqrt{3} VI \cos\Phi$ in delta connection.
11. Discuss the effect of unbalanced loads in star connected system.
12. Write the relation between the power factor and wattmeter readings in two wattmeter method of power measurement.

13. A star connected load has $6+j8\Omega$ impedance per phase. Determine the line current if it is connected to 400V, 3 phase , 50Hz supply.
14. A delta connected load has $30-j40\Omega$ impedance per phase. Determine the line current if it is connected to 415V, 3 phase , 50Hz supply.
15. A star connected balanced load draw a current of 35A per phase when connected to a 440V supply. Determine the apparent power.

PART – C : 10 Mark Questions

1. Establish the relationship between line current and phase current, line voltage and phase voltage in a star connected system.
2. Establish the relationship between line current and phase current, line voltage and phase voltage in a delta connected system.
3. Prove that the sum of the readings on two single-phase wattmeter's connected in 3-phase circuit give 3-phase power.
4. Explain the two wattmeter method of 3-phase power measurement in a 3 phase star or delta connected load.
5. A balanced star connected load of $(4+j3)\Omega$ per phase is connected to a balanced 3 phase 400V, AC supply. The phase current is 12A. Find (1) the total active power (2) reactive power and (3) apparent power.
6. A three phase, balanced delta connected load of $(4+j8)\Omega$ per phase is connected across a 400V, AC supply. Determine the phase current, line current and power consumed by the load.
7. A three phase, balanced star connected load of $(15+j20)\Omega$ per phase is connected across a 400V, 50Hz, AC supply. Determine the line current and power consumed by the load.
8. Each phase of a delta connected load consists of a resistance 10Ω and a capacitance $100 \mu F$. A supply of 440V, 50Hz is applied to the load. Find (i) line current, (ii) Power factor (iii) Power consumed by the load.
9. The power consumed in a three phase balanced star connected load is 2KW at a power factor of 0.8 lagging. The supply voltage is 400V, 50Hz.Calculate the resistance and reactance of each phase.
10. A delta connected balanced 3 phase load is supplied from a 3 phase, 400V supply. The line current is 20A and the power taken by the load is 10,000W. Find (i) impedance in each branch, (ii) line current, power factor and power consumed if the same load is connected in star.

11. The input power to a three phase load is 10KW at 0.8 p.f. Two wattmeters are connected to measure the power. Find the individual readings of the wattmeters.
12. The readings of the two wattmeters used to measure power in a capacitive load are 3000W and 8000W respectively. Calculate (i) the input power and (ii) the power factor at the load.
13. The power input to a 2000V, 50Hz, three phase motor is measured by two wattmeters which indicate 300KW and 100KW respectively. Calculate the input power, power factor and line current.
14. A 500V, 3 phase induction motor has an output of 3.73KW and operates at a power factor of 0.85, with an efficiency of 90%. Calculate the reading on each wattmeter connected to measure the input power.
15. The input power to a three phase motor was measured by two wattmeter method. The readings are 5.2KW and 1.7KW. The later reading has been obtained after reversing the current coil connections. The line voltage was 400V. Calculate a) The total power b) Power factor and c) Line current.
16. Two wattmeters are used to measure power in a three phase load. The wattmeter readings are 400W and -35W. Calculate a) Total active power b) Power factor c) Reactive Power and d) Volt-ampere.
17. Calculate the total power input and reading of the two wattmeters connected to measure power in a three phase balanced load, if the reactive power input is 15KVAR and the load power factor is 0.8.
18. A 3v phase star connected load draws a line current of 25A. The load KVA and KW are 20 and 16 respectively. Find the readings on each of the two wattmeters used to measure the three phase power.
